
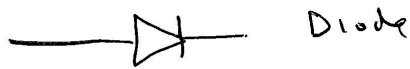



Input/output Characteristic

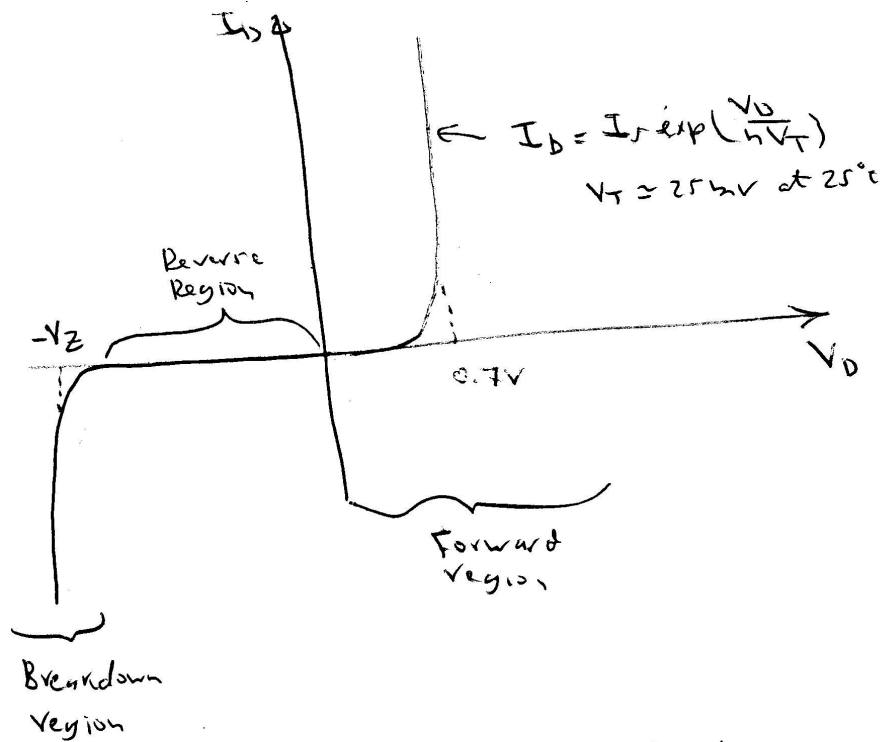

Diode



Zener Diode

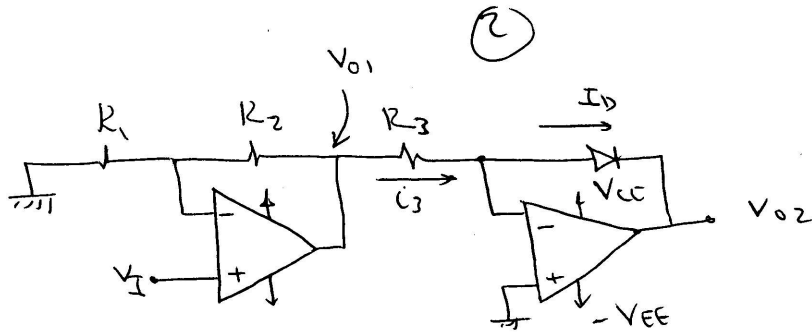

$$V_{01} = V_I \left(1 + \frac{R_2}{R_1}\right)$$

IF $V_I > 0 \Rightarrow V_{01} > 0 \Rightarrow i_3 > 0 \Rightarrow$ Diode is forward Biased

* Here, there is a feedback so $V_- = V_+ = 0$


$$i_3 = \frac{V_{01}}{R_3} = \frac{V_I}{R_3} \left(1 + \frac{R_2}{R_1}\right) = I_D$$

$$V_{02} = -V_D$$

* By changing V_I , we are changing I_D
and we measure $V_{02} = -V_D$

* Note if $V_I < 0$, $V_{01} < 0$, Diode is reverse biased $\Rightarrow I_D = 0 = i_3 \Rightarrow V^- = V_{01}$ and $V_{02} = -V_{EE}$

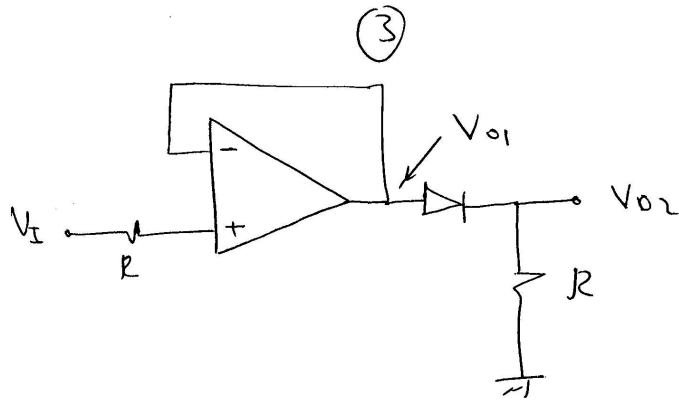
* The Diode may reach breakdown for large negative V_I




* If $V_I > 0$, $V_{O1} = V_I$, Diode is forward-biased,
 $V_{O2} \approx V_{O1}$ (neglecting the small diode drop)

If $V_I < 0$, $V_{O1} = V_I$, Diode is reverse-biased

$$V_{O2} = 0$$

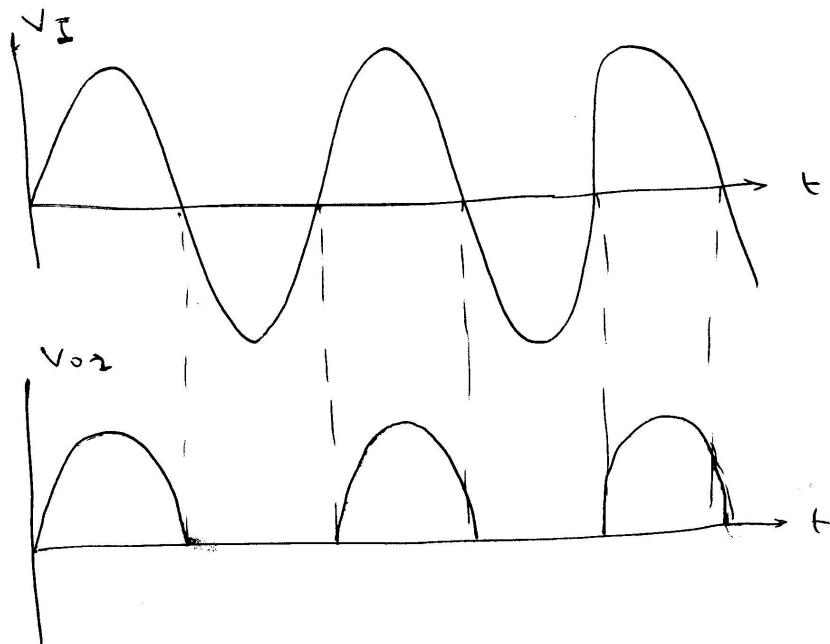

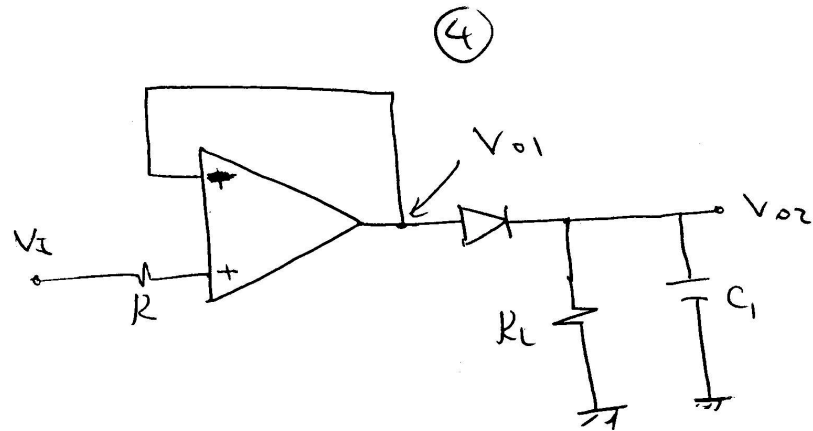

At $t=0$, $V_C = 0$

* If $V_I > 0$, $V_{o1} = V_I > 0$, Diode conducts,


$$V_{o2} = V_{o1} = V_I.$$

* This continues until V_I starts to drop. Here


$V_{o1} < V_C \Rightarrow$ Diode is reverse biased \Rightarrow

Capacitor is discharging slowly through R_L

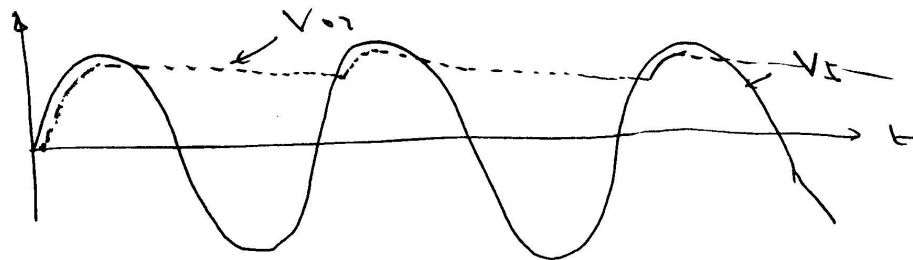* If $V_I < 0$, $V_{o1} = V_I$. Diode is off



(5)

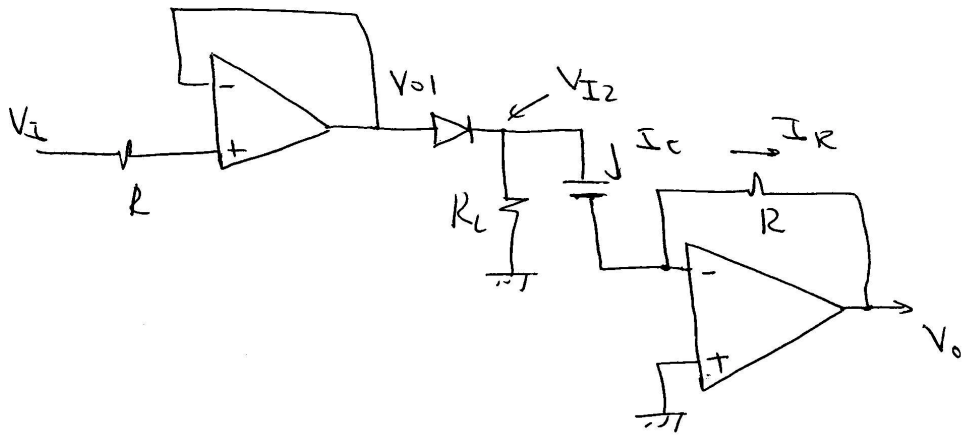

This circuit is identical to the previous one except that capacitor is now connected to virtual ground

$$V_{o1} = V_i$$

$$V_{i2} = V_{iC}, \quad I_C = C \frac{dV_{i2}}{dt}$$

$$I_R = -I_C \Rightarrow V_o = -I_R R = -C \frac{dV_{i2}}{dt} R$$

