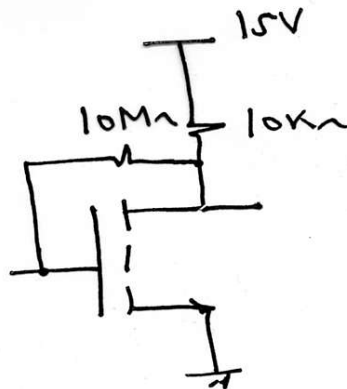


Determine the gain of this circuit.
Ignore λ for DC Analysis

DC Circuit



$$15 = 10 I_{DS} + V_{DS} = 10 I_{DS} + V_{GS} \quad (V_{GS} \approx V_D)$$

$$I_{DS} = \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

$$\frac{15 - V_{GS}}{10} = \frac{0.5}{2} (V_{GS} - 1.5)^2$$

$$15 - V_{GS} = 2.5 (V_{GS}^2 - 3V_{GS} + 2.25)$$

$$2.5 V_{GS}^2 - 6.5 V_{GS} - 9.375 = 0$$




$$V_{GS}^2 - 2.6 V_{GS} - 3.75 = 0$$


$$V_{GS} = \frac{2.6 \pm \sqrt{6.76 + 15}}{2} = 3.632 \text{ V}$$

$$\therefore I_{DS} = 1.05 \text{ mA}$$

$$\text{Q-point } (I_{DS}, V_{DS}) = (1.05 \text{ mA}, 3.632 \text{ V})$$

SS Analysis

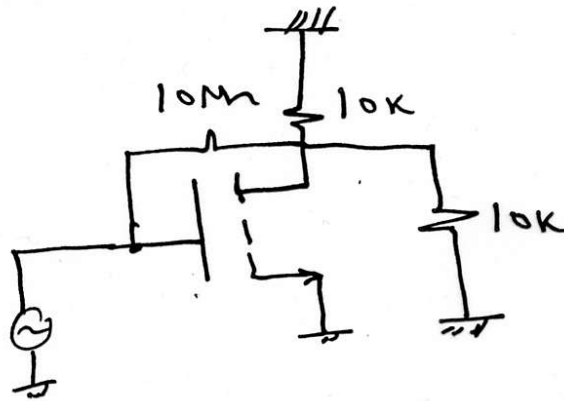

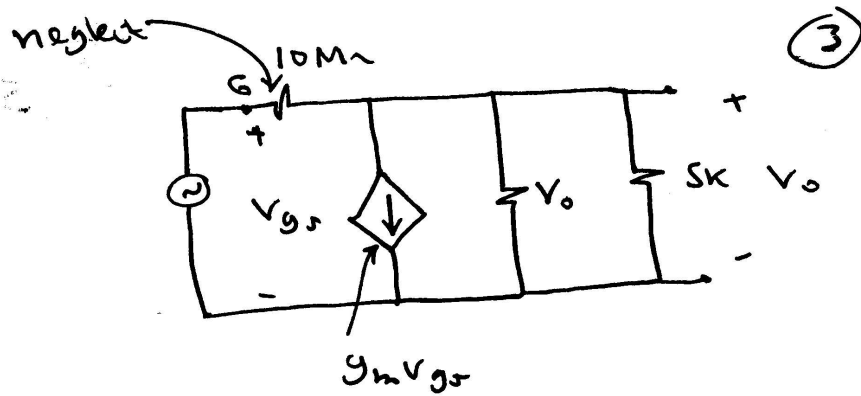

$$g_m = \sqrt{2 K_n I_{D_r} (1 + \lambda V_{D_r})}$$


$$g_m = \sqrt{2 \times 0.5 \times 1.06 \times (1.07264)} = 1.0622 \text{ mA/V}$$

$$Y_0 = \frac{1 + \lambda V_{D_r}}{\lambda I_{D_r}} = \frac{1.0726}{0.02 \times 1.06} = 50.5 \text{ k}\Omega$$

$$V_o \approx -g_m v_{g_s} (Y_0 \parallel 5k)$$

$$V_o = -1.0622 \times 4.525 v_{g_s} = -4.8 v_{g_s}$$

(4)

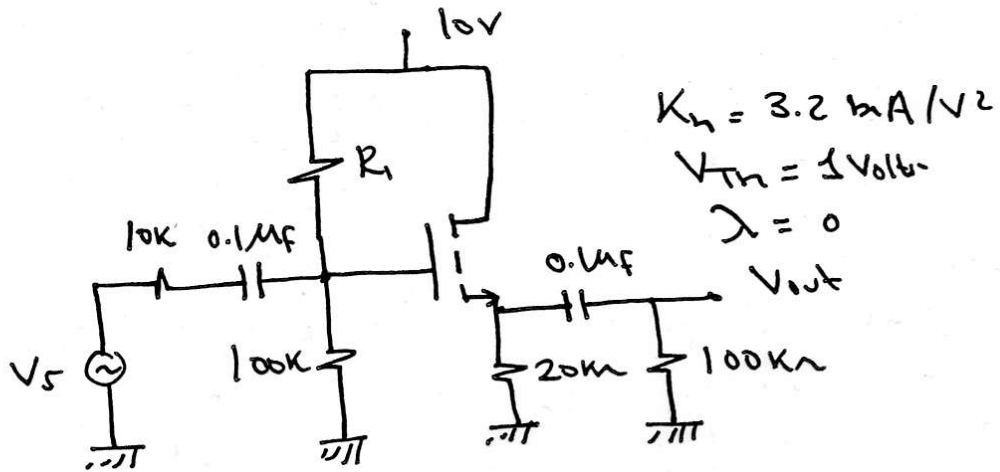

* Determine R_1 to set $V_{DS} = 6 \text{ Volts}$

* Determine the gain V_{out}/V_s

Solution: \downarrow $V_{DS} = 6 \text{ V} \Rightarrow V_s = 4 \text{ V}$

$$\therefore I_{DS} = \frac{4}{20\text{k}} = 200 \mu\text{A}$$

Assuming Saturation

$$I_{DS} = \frac{K_n}{2} (V_{GS} - V_{th})^2$$

$$0.2 \times 10^{-3} = 1.6 \times 10^{-3} (V_{GS} - 1)^2$$




$$0.125 = (V_{GS} - 1)^2 \Rightarrow V_{GS} = 1.35 \text{ V}$$

$$\therefore V_G = 5.35 \text{ V} = \frac{10 \times 100\text{k}}{100\text{k} + R_1}$$

$$5.35 R_1 = 465 \Rightarrow R_1 = 87\text{k}$$

SS Analysis

(5)

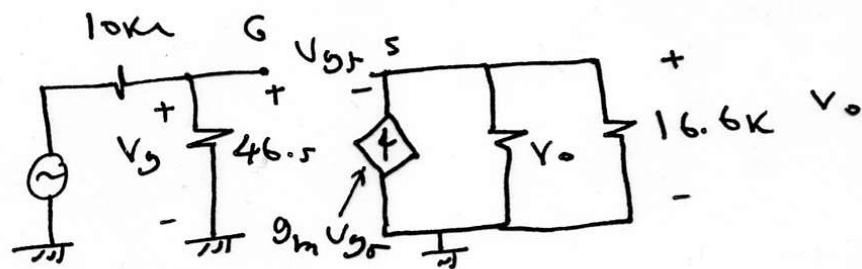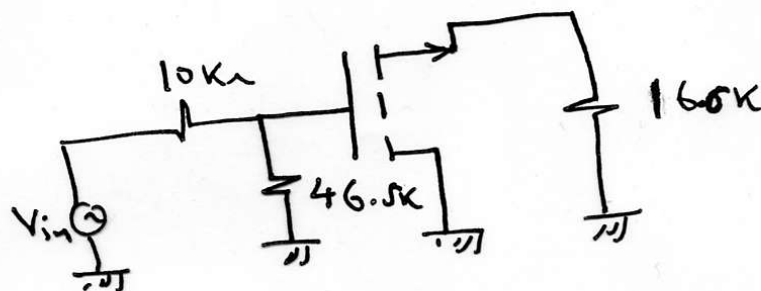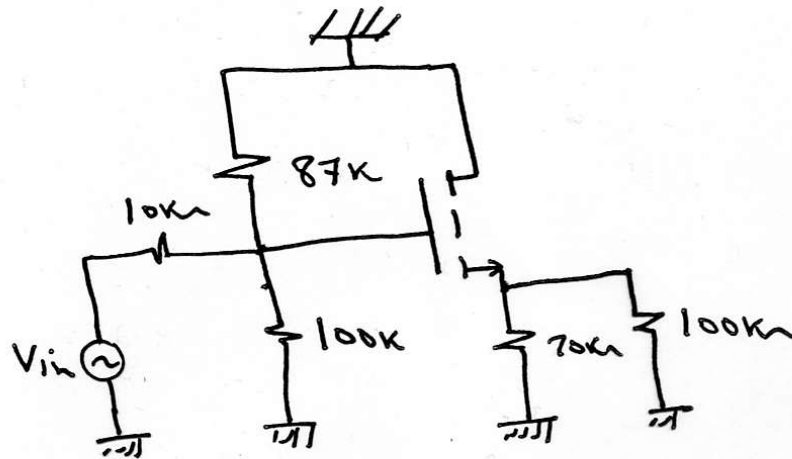

$$\lambda = 0 \Rightarrow V_o = \infty$$

$$g_m = \sqrt{2K_n I_{DQ}} = \sqrt{2 \times 3.2 \times 10^{-3} \times 200 \times 10^{-6}}$$

$$g_m = 1.1313 \text{ mA/V}$$

$$V_o = g_m V_{gs} \times 16.6k$$

(6)

$$V_o = g_m (V_{gs} - V_o) \times 16.6k$$

$$(1 + g_m \times 16.6k) V_o = g_m \times 16.6k \times V_{gs}$$

$$188.807 V_o = 187.807 V_{gs}$$

$$\therefore \frac{V_o}{V_{gs}} = 0.9947 \quad \text{But } V_{gs} = \frac{V_{in} \times 46.5}{46.5 + 10}$$


$$V_{gs} = 0.823 V_{in}$$

$$\therefore \frac{V_o}{V_{in}} = 0.9947 \times 0.823 = 0.8186$$

$$K_n = 1.0 \text{ mA/V}^2$$

$$V_{TN} = 1.0 \text{ V}$$

$$\lambda = 0 \text{ V}^{-1}$$

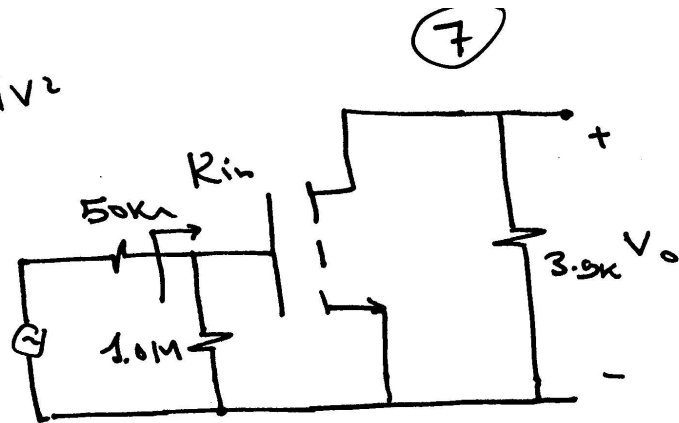

The figure shows the AC equivalent circuit. The operating point is $(I_{DS}, V_{DS}) = (2.0 \text{ mA}, 7.5 \text{ V})$. Determine the voltage gain & input resistance


Solution: $V_o = \infty$ ($\lambda = 0$)

$$g_m = \sqrt{2K_n I_{DS}}$$

$$g_m = \sqrt{2 \times 10^{-3} \times 2 \times 10^{-3}}$$

$$g_m = 2 \text{ mA/V}$$

SS Analysis

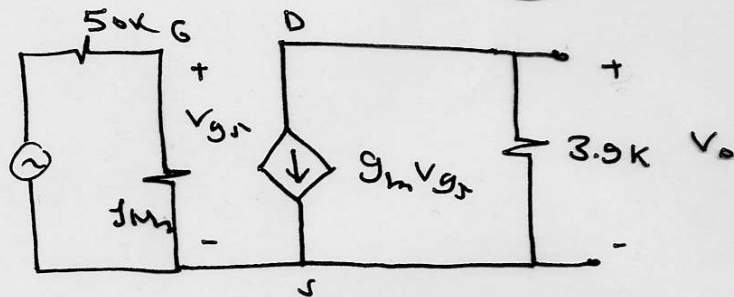

$$V_o = -g_m V_{gs} = -7.8 V_{gs}$$

$$\text{but } V_{gs} = V_{in} \frac{1000}{1050} = 0.95 V_{in}$$

$$\therefore \frac{V_o}{V_{in}} = -7.8 * 0.95 = -7.4$$

$$R_{in} = 1 M\Omega$$