

## Chapter 10 (extra)

10.13 At  $V_B = 0.5V$ ,  $\frac{dV_o}{dV_i}$  is different for positive & negative values of  $V_A \sin 1000t$ . So the gain is different on both sides & the output signal will always be distorted. Thus, it's not a good choice of a bias point for the amplifier.

10.16  $V_{in} = 10 \times 10^{-3} \sin(2\pi \times 1000t) = 10 \sin(2000\pi t) \text{ mV}$   
 $V_o = 5 \sin(2000\pi t) + 0.25 \sin(6000\pi t) + 0.10 \sin(10000\pi t) \text{ V}$   
 $A_v = \frac{5V}{10 \text{ mV}} = 500$


The harmonics generated by the amplifier are 3 kHz & 5 kHz which are the 3rd & 5th harmonics.

$$THD\% = 100\% \times \frac{\sqrt{(0.25^2 + 0.10^2)}}{5} = 5.4\%$$

10.22

$$y_{11} = \frac{i_1}{V_1} \Big|_{V_2=0} = \frac{i_1}{10k i_1} = \frac{1}{10k} = 10^{-5} \text{ S}$$


$$y_{21} = \frac{i_2}{V_1} \Big|_{V_2=0} = \frac{-10i_1}{10k i_1} = -1.0 \times 10^{-2} \text{ S}$$

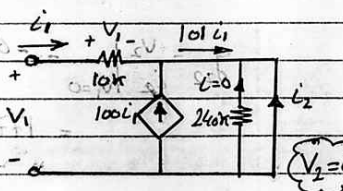

$$y_{12} = \frac{i_1}{V_2} \Big|_{V_1=0} = \frac{-V_2/10k}{V_2} = -10^{-4} \text{ S}$$


$$y_{22} = \frac{i_2}{V_2} \Big|_{V_1=0} = \frac{-10i_1 + V_2/240k}{V_2}$$
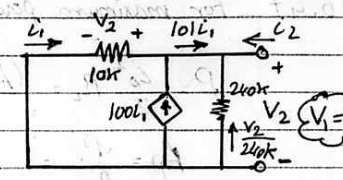
$$= -\frac{(-10i_1/V_2 + V_2/240k)}{V_2} = 0.01 \text{ S}$$



*Hebrew*


$$10.23 \quad Z_{11} = \frac{V_1}{i_1} \Big|_{i_2=0} = \frac{10k \cdot i_1 + 100k \cdot 240k \cdot i_1}{i_1} = 2.43 \times 10^7 \Omega$$

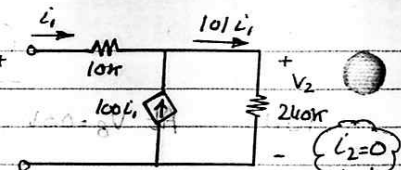

$$Z_{21} = \frac{V_2}{i_1} \Big|_{i_2=0} = \frac{100k \cdot 240k \cdot i_1}{i_1} = 2.42 \times 10^7 \Omega$$


$$Z_{12} = \frac{V_1}{i_2} \Big|_{i_1=0} = \frac{240k \cdot i_2}{i_2} = 240k$$

$$Z_{22} = \frac{V_2}{i_2} \Big|_{i_1=0} = \frac{240k \cdot i_2}{i_2} = 240k$$

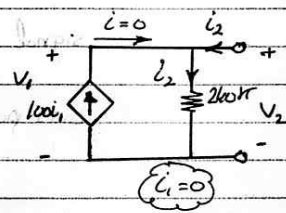


$$10.25 \quad g_{11} = \frac{i_1}{V_1} \Big|_{i_2=0} = \frac{i_1}{2.5k i_1 + 1k \cdot 100i_1} = 9.66 \times 10^{-6} S$$

$$g_{21} = \frac{i_2}{V_1} \Big|_{i_2=0} = \frac{-60k \cdot 100i_1 + 1k \cdot 100i_1}{2.5k i_1 + 1k \cdot 100i_1} = -5.7$$

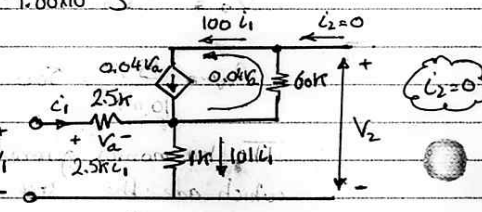

$$g_{12} = \frac{i_1}{i_2} \Big|_{V_1=0} = \frac{i_1}{-3.5i_2} = -0.286$$

$$g_{22} = \frac{i_2}{V_2} \Big|_{V_1=0} = \frac{60k \cdot 103.5i_1 - 1k \cdot 2.5i_1}{-3.5i_2} = 1775 \mu S$$

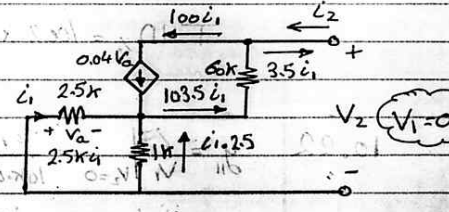

10.47 For maximum power  $R_{in} = 0 \Omega$ ,  $R_{out} = \infty$

$$P = \frac{V_o^2}{2 R_L} = \frac{(B E_s)^2}{2} R_L = \frac{(5000 \times 10^{-4})^2}{2} 10 \times 10^3 = 125 \text{ mW}$$

$$A_p = \frac{P}{P_{in}} = \frac{125 \text{ mW}}{\frac{V_s^2}{2} \cdot R_{in}} = \frac{125 \text{ mW}}{0} = \infty$$

10.53

$$A_{mid} = \frac{R_2}{R_1 + R_2} = \frac{20k}{10k + 20k} = 0.667$$

$$\omega_L = \frac{1}{(R_1 + R_2)C} = \frac{1}{(10k + 20k)0.01\mu F} = 3333.33 \text{ rad/s}$$

$$f_L = \frac{\omega_L}{2\pi} = 530.52 \text{ Hz}$$

10.60

$$A_v(s) = -\frac{10^7 s}{s^2 + 10^5 s + 10^{14}} = -10^2 \frac{10^5 s}{s^2 + 10^5 s + 10^{14}} = A_{mid} \frac{s \frac{\omega_0}{Q}}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

So it's a bandpass amplifier with

$$A_{mid} = 100 = 40 \text{ dB}$$

$$f_0 = \frac{10^7}{2\pi} = 1.592 \text{ MHz}, \quad Q = \frac{\omega_0}{10^5} = 100$$

$$BW = \frac{1.592 \text{ MHz}}{100} = 15.92 \text{ kHz}$$

$$f_L \approx f_0 - \frac{BW}{2} = 1.584 \text{ MHz}, \quad f_H \approx f_0 + \frac{BW}{2} = 1.6 \text{ MHz}$$

10.61

$$A_v(s) = -20 \frac{s^2 + 10^{12}}{s^2 + 10^4 s + 10^{12}} = A_{mid} \frac{s^2 + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

This is a notch filter

$$A_{mid} = -20 = 26 \text{ dB}, \text{ but } A_v = 0 \text{ at } f_0$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{10^6}{2\pi} = 159.2 \text{ kHz}, \quad Q = \frac{\omega_0}{10^4} = 100$$

$$BW = \frac{159.2 \text{ kHz}}{100} = 1.592 \text{ kHz}$$

$$f_L \approx f_0 - \frac{BW}{2} = 158.4 \text{ kHz}, \quad f_H \approx f_0 + \frac{BW}{2} = 160.4 \text{ kHz}$$