

Homework From Chapter 11

11.7

This is an inverting amplifier, so we can use the known formulas directly.

$$A_v = -\frac{R_2}{R_1}, \quad R_{in} = R_1, \quad R_{out} = 0$$

a. $A_v = -46.8 \Rightarrow |A_v| = 33.4 \text{ dB}$
 $R_{in} = 4.7 \text{ k}\Omega, \quad R_o = 0 \text{ }\Omega$


b. $A_v = -46.8 \Rightarrow |A_v| = 33.4 \text{ dB}$
 $R_{in} = 4.7 \text{ k}\Omega, \quad R_o = 0 \text{ }\Omega$

11.13

For an ideal op-amp
 $V^- = V^+ = 0 \text{ V}$

We've $i_1 + i_2 + i_3 = 0$

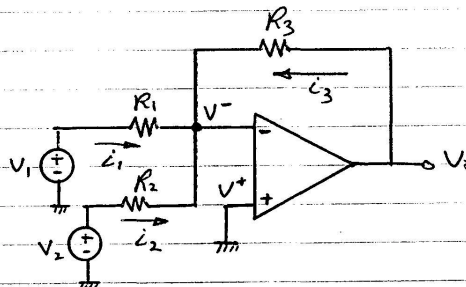but $i_1 = V_1/R_1, \quad i_2 = V_2/R_2, \quad i_3 = V_o/R_3$



$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_o}{R_3} = 0 \Rightarrow V_o = -\frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2$$

$$\therefore V_o(t) = -51(0.01 \sin 3770t) - 25.5(0.04 \sin 10000t)$$

$$\Rightarrow V_o(t) = 0.51 \sin 3770t - 1.02 \sin 10000t \text{ V}$$

$$\& V^-(t) = 0 \text{ (virtual ground)}$$

11.15

For the ideal opamp $V^- = V^+$

but $V^+ = \frac{10R}{10R+R} V_2 = \frac{10V_2}{11}$

& $V^- = V_1 - i_1 R$, $i_1 = \frac{V_1 - V_0}{R + 10R}$

$\therefore V^- = V_1 - \frac{V_1 - V_0}{11} = \frac{10V_1}{11} + \frac{V_0}{11}$

a. $V^- = V^+ \Rightarrow \frac{10V_2}{11} = \frac{10V_1}{11} + \frac{V_0}{11} \Rightarrow V_0 = -10(V_1 - V_2)$


$\Rightarrow A_V = \frac{V_0}{V_1 - V_2} = -10$

b. $R_{i2} = \frac{V_2}{i_2} \Big|_{V_1=0} = 11R = 110k\Omega$

$R_{i1} = \frac{V_1}{i_1} \Big|_{V_2=0}$

when $V_2=0$, $i_2=0$ & $V^+=0 \Rightarrow V^-=0$

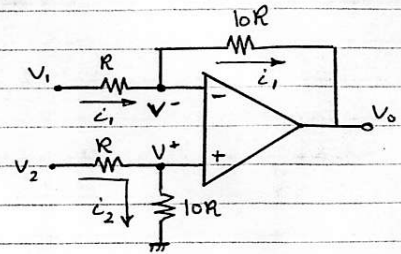$\therefore i_1 = V_1/R \Rightarrow R_{i1} = R = 10k\Omega$




11.41

For stage 1: $A_V = -\frac{240k}{24k} = -10$, $R_{in} = 24k$

For stage 2: $A_V = -\frac{50k}{10k} = -5$, $R_{in} = 10k$

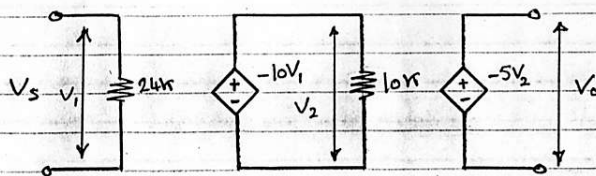a. So now we can draw the two-port representation for each stage



Hilroy

$$b. \frac{V_o}{V_s} = \frac{V_o}{V_2} \cdot \frac{V_2}{V_s} = -5 \cdot -10 = 50$$

$$R_{in} = 24 \text{ k} \quad \& \quad R_o = 0 \text{ } \Omega$$

11.58

Check section 11.4 before solving this problem.

$$V_{th} = V_s \left(-\frac{R_2}{R_1} \right) \left(\frac{AB}{1+AB} \right)$$

where $A = 5 \times 10^4$ is the open loop gain

$$\& \quad \beta = \frac{R_1}{R_1+R_2} \text{ is the feedback factor}$$

$$\Rightarrow V_{th} = -16.2 V_s$$

$$R_{th} = R_{out} = \frac{R_o}{1+AB} = 85.9 \text{ m} \Omega$$

For $AB \gg 1$, we can use the following apx.

$$V_{th} \approx V_s \left(-\frac{R_2}{R_1} \right) \quad \& \quad R_{th} \approx \frac{R_o}{AB}$$

11.78

This is an inverting amplifier with ~~open loop~~ gain $-\frac{6.2 \text{ k}}{1 \text{ k}} = -6.2$ as

long as $|V_o| \ll 10 \text{ V}$, which is the limit of the opamp supply voltages.

$$a. U_i = 1 \text{ V} \Rightarrow V_o = -6.2 \text{ V}, \quad V^- = 0 \text{ V (due to feedback)}$$

$$b. U_i = -3 \text{ V} \Rightarrow V_o = 18.6 \text{ V} \text{ which can't be, so } V_o \text{ remains at } 10 \text{ V}$$

$\&$ the feedback loop is broken, so V^- is calculated using superposition

$$V^- = -3 \frac{6.2 \text{ k}}{1 \text{ k} + 6.2 \text{ k}} + 10 \frac{1 \text{ k}}{1 \text{ k} + 6.2 \text{ k}} = -1.19 \text{ V}$$

Hibroy


11.87

The circuit can be redrawn as shown.

where $Z_1 = R_1$ & $Z_2 = R_2 \parallel C$

$$Z_2 = \frac{R_2 \cdot (1/sC)}{R_2 + 1/sC} = \frac{R_2}{1 + sCR_2}$$

we've $V^+ = V^- = V_s$

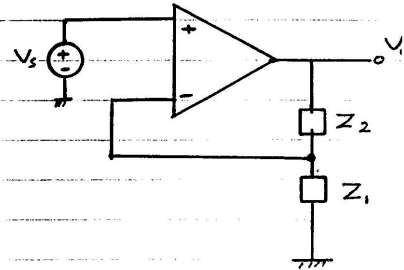

Using voltage division: $V_s = V_o \frac{Z_1}{Z_1 + Z_2}$

$$A_v = \frac{V_o}{V_s} = \frac{Z_1 + Z_2}{Z_1} = \left(R_1 + \frac{R_2}{1 + sCR_2} \right) / R_1$$

$$= \frac{R_1 + sCR_1R_2 + R_2}{R_1 + sCR_1R_2} = \frac{(R_1 + R_2)(1 + sC \frac{R_1R_2}{R_1 + R_2})}{R_1(1 + sCR_2)}$$

$$\Rightarrow A_v = \left(1 + \frac{R_2}{R_1} \right) \frac{1 + sC (R_1 \parallel R_2)}{1 + sCR_2}$$