

## Chapter 1 (extra)

1.13  $V_{LSB} = 2^{-n} V_{FS} = 3.052 \times 10^{-4} \text{ V}$

$$\frac{6.83}{V_{LSB}} = (22380.544)_{10}$$

This input will be approximated with  $(22381)_{10}$  to get a digital output of

$$\begin{aligned} (22381)_{10} &= 2^{14} + 5997 = 2^{14} + 2^{12} + 1901 = 2^{14} + 2^{12} + 2^{10} + 877 \\ &= 2^{14} + 2^{12} + 2^{10} + 2^9 + 2^8 + 2^6 + 2^5 + 2^3 + 2^2 + 2^0 \\ &= (101011101101101)_2 \end{aligned}$$

1.28

$$R_{in} = \frac{V_s}{i_s}$$

$$i_s = -i - \beta i = -(\beta + 1)i$$

but  $i = -\frac{V_s}{R_1}$

$$\therefore i_s = \frac{(\beta + 1)V_s}{R_1}$$

$$\therefore R_{in} = \left(\frac{\beta + 1}{R_1}\right)^{-1} = \frac{R_1}{\beta + 1} = 662 \Omega$$

