

## ELEC ENG 2E15 ELECTRONIC DEVICES and CIRCUITS I

Term II, January – April 2005


# PSPICE Demonstrations and Exercises (SET: 14)

Instructor: Dr. M. Bakr

Prepared by: Dr. M. Bakr and Anthony Bilinski

**Objective:** To learn and use the PSpice model and its parameters for Bipolar Junction Transistors(BJT). To understand and explain the output and transfer characteristics of the BJT.

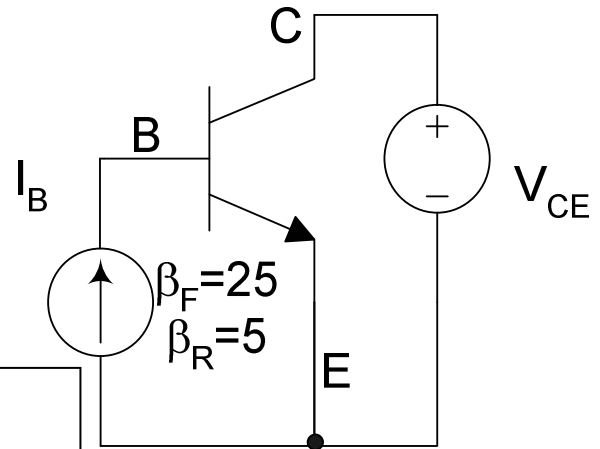**Example 1)** Sketch the common-emitter output characteristic for the npn Bipolar Junction transistor in the shown circuit for  $I_B=10\mu\text{A}$ . Verify your result using a simulation in PSpice. Vary the collector-emitter voltage  $V_{CE}$  between -5V and 10V with a step size of 10mV. Perform this sweep for base currents  $I_B=\{10\mu\text{A}, 30\mu\text{A}, 50\mu\text{A}\}$ . Plot the resulting collector current waveforms. For the BJT the saturation current is  $I_S=0.1\text{fA}$



**Analysis:**

To determine the shape of the output characteristic calculate the collector current as a function of the collector-emitter voltage  $V_{CE}$ . For  $V_{CE}<0.2$  (an assumed small voltage). The transistor is operating in the reverse-active region.  $I_E=-\beta_R I_B=-50\mu\text{A}$ .


$$I_C=I_E/\alpha_R=-60\mu\text{A}.$$

For  $-0.2<V_{CE}<0.2\text{V}$  the transistor is operating in the saturation region and appears as a closed switch with varying currents maintaining  $I_B+I_C-I_E=0$ . For  $V_{CE}>0.2$  the transistor is operating in the forward active region.  $I_C=\beta_F I_B$  and

$$I_E=I_C/\alpha_F=260\mu\text{A}.$$

The  $\pm 0.2\text{V}$  value is an assumed small voltage range around 0V.


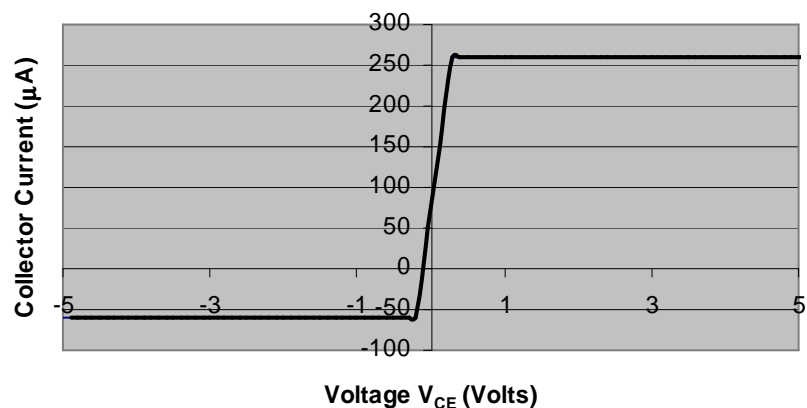
**Common-emitter Output  
Characteristic of the NPN transistor**




PSPICE Demonstrations and Exercises (SET: 14)

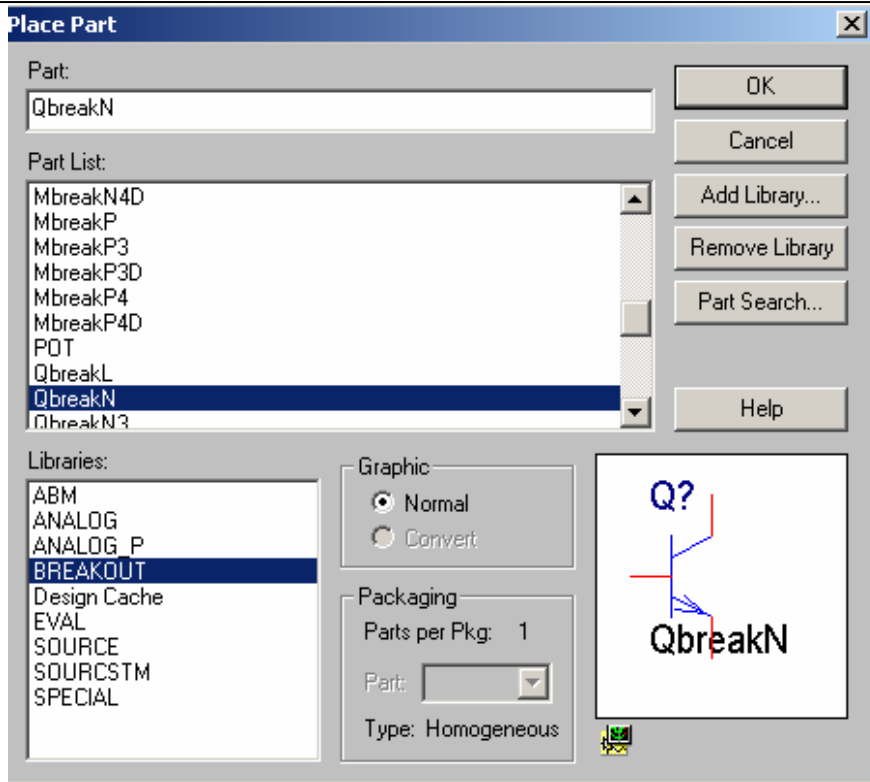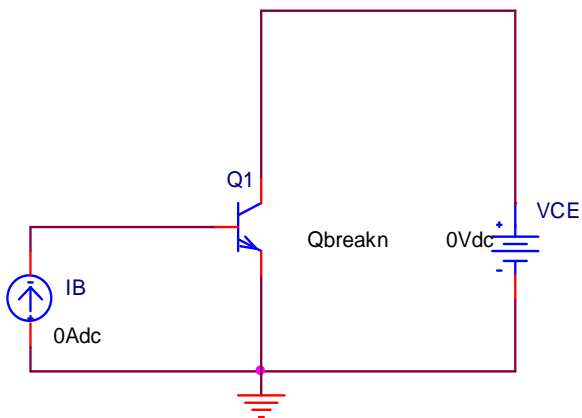**Building the Circuit:**

The circuit consists of 3 components: A current source, voltage source and an npn BJT. The name of the generic model for the npn BJT is QBreakN. Similarly the pnp transistor is referred to as QBreakP. These devices can be found in the BREAKOUT library. Construct the circuit as shown.




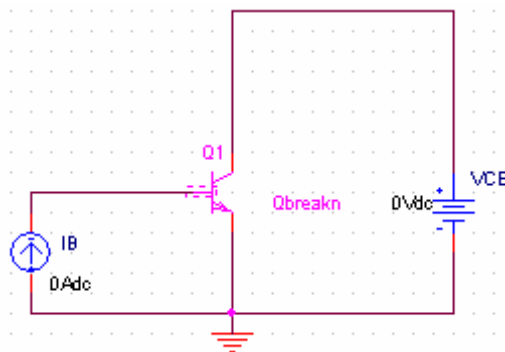Rename the ground node to be "0". Now edit the PSpice model parameters for the npn transistor: Select the npn transistor by clicking on it and then from the edit menu click PSpice Model to load the model editor. The QBreak model for the BJT has many parameters. Some of them are summarized in the shown table.



Symbol	Spice Name	Model Parameter	Default Value
$I_S$	Is	Saturation Current	0.1fA
$\beta_F$	Bf	Forward current gain	100
$V_{AF}$	VAf	Forward Early Voltage	$\infty$
$r_B$	Rb	Base ohmic resistance	$0\Omega$
$\beta_R$	Br	Reverse current gain	1

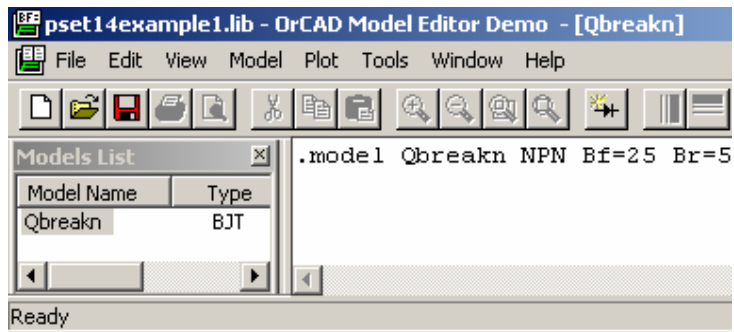In the PSpice Model Editor change the forward and reverse Beta parameters to 25 and 5 respectively as given in the problem statement. Save the changes and return to the schematic editor.



PSPICE Demonstrations and Exercises (SET: 14)

View the netlist to see how PSpice represents the BJT in this format.

**Netlist:**



```
* source PSET14EXAMPLE1
Q_Q1      N00065  N00118      0 Qbreakn
V_VCE     N00065  0              0Vdc
I_IB      0        N00118      DC 0Adc
```

The model for the operation of the BJT transistor used in Jaeger is actually a simplified version of a more complex model called the Gummel-Poon Model. It is this complex model that forms the heart of the model used by PSpice for simulation. Calculations using the simplified model should not exhibit very much deviation from the more complex and accurate model used by Spice however the results may differ slightly.

The BJT statement begins with Q followed by a unique name. The nodes to which the element is connected are then listed in the order of those connected to the collector, base, and emitter. Take note that the collector current  $I_C$  is the negative(-) of the current through the source  $V_{CE}$ .

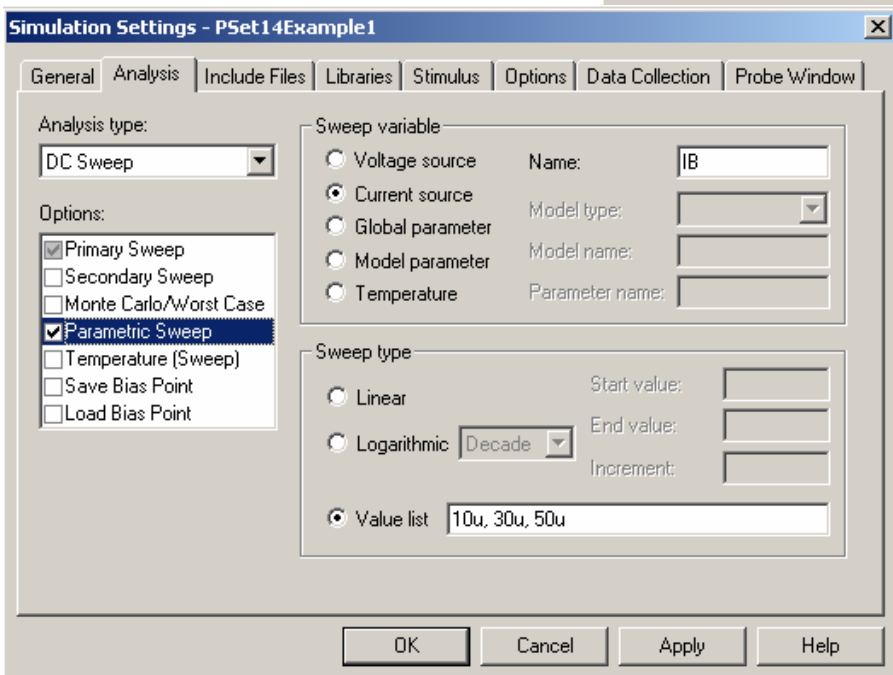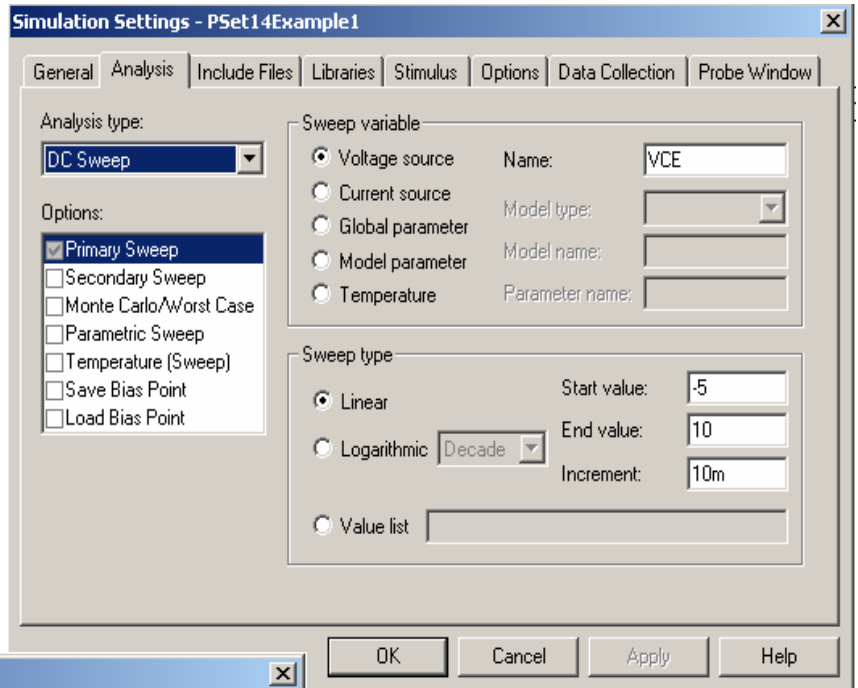**Simulating the Circuit:**

To construct the common-emitter output characteristics for the npn transistor a DC Sweep simulation must be performed on  $V_{CE}$  for each of the requested values of  $I_B$ . Create a new simulation profile and for the analysis type select DC Sweep. Set up the primary sweep of VCE as shown.





Select a Parametric Sweep as shown and set it up to sweep the current source  $I_B$  for the values specified in the problem statement. Ensure the box beside the Parametric Sweep option contains a checkmark and click OK to complete the set-up and return to the schematic. Run the simulation.



PSPICE Demonstrations and Exercises (SET: 14)

The probe window appears. Click the Add traces Button and add a trace for the collector current  $I_C$  which is given by the negative of the output variable  $I(V_{CE})$ . The resulting graph is shown.

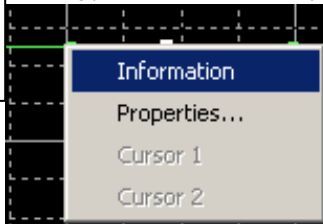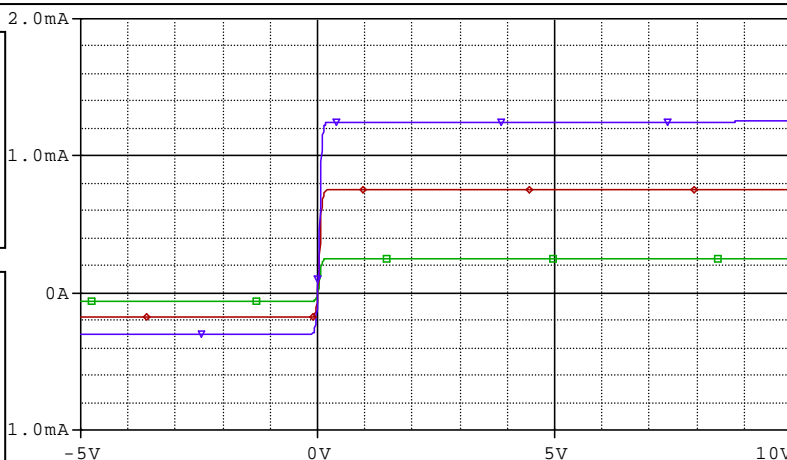
To determine which curves corresponds to which value of the current  $I_B$  click on a curve with the right mouse button and select information. A dialog will appear containing information about the state of the circuit when the simulation was performed. Thus the green curves corresponds to  $I_B=10\mu A$ .



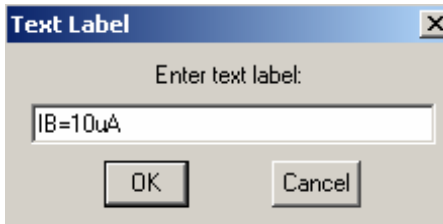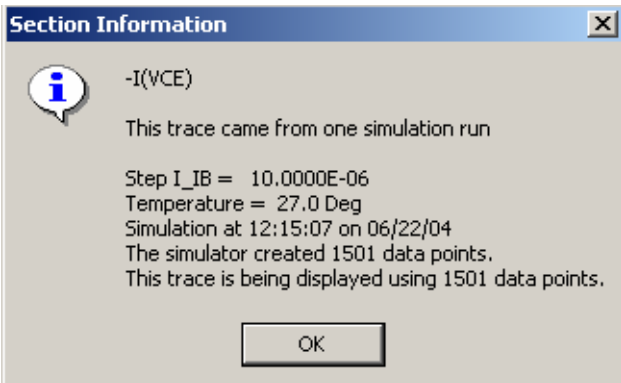Labels can be added to each curve using the Text Label Button. Click the text label button and type  $I_B=10\mu A$ .



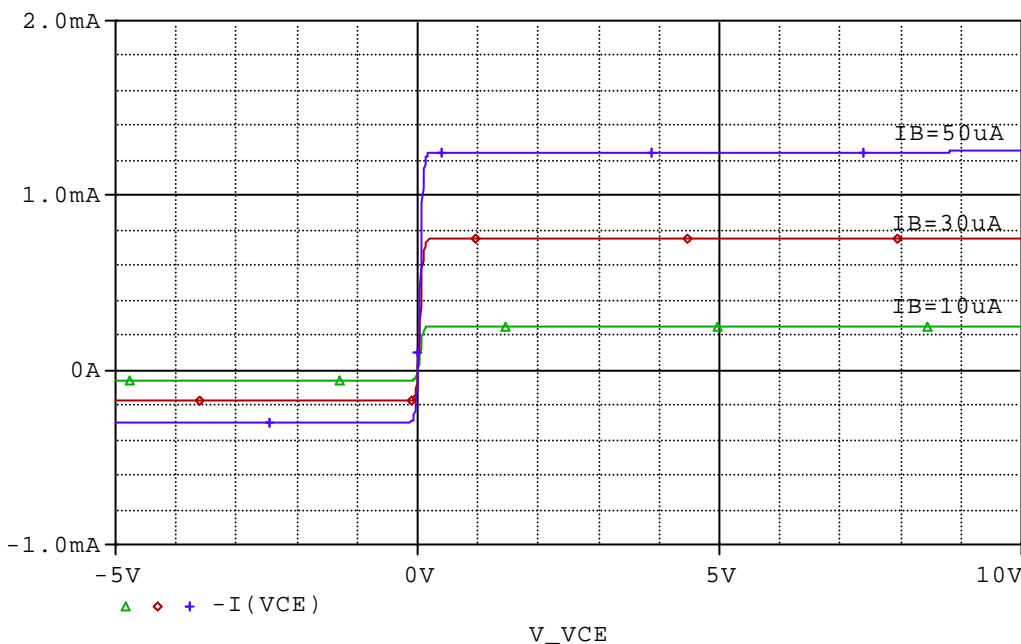Click OK and stamp the label beside the green curve to which it corresponds. Repeat for the other two plots which correspond to  $30\mu A$  and  $50\mu A$ .






Notice that the collector current is higher when  $I_B$  is higher. Note that in the reverse and forward active regions the collector current is virtually constant and does not depend on  $V_{CE}$  but in the saturation region the current varies quite dramatically with small changes in  $V_{CE}$ .

Using the cursor measure the collector current in the reverse and forward active regions to determine if our calculations were correct. Click the Toggle Cursor button to activate the cursor.

Use cursor A1 and its controlling left mouse button to move the cursor to any point in the reverse active region on the curve corresponding to  $I_B=10\mu A$ . the value is read from the second column as  $-60\mu A$ . This is exactly the value previously calculated.

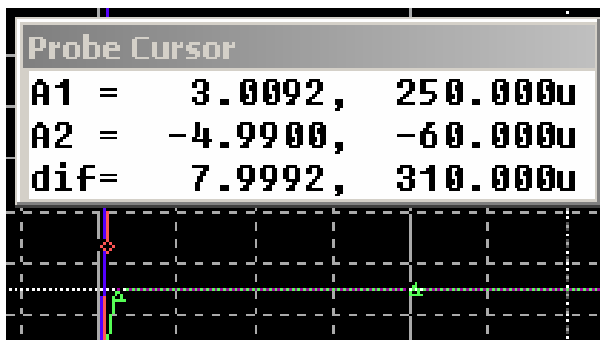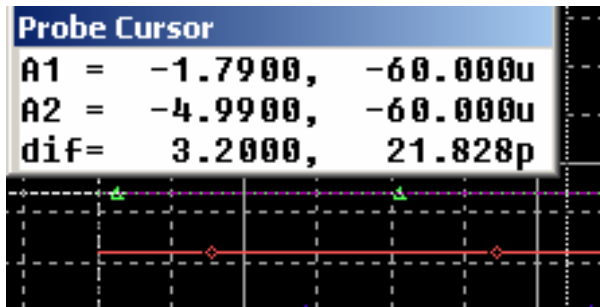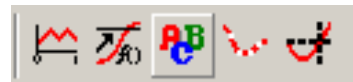
Now move the cursor to any point on the same plot in the forward active region. The value is again read from the second column as  $250\mu A$ . The value calculated was  $260\mu A$  and thus there is a minor and negligible difference between the two results.




**Example 2)** Sketch the common-emitter transfer characteristic for the npn Bipolar Junction transistor for the case when  $V_{BC}=0$ . The CE transfer characteristic shows the relationship between the collector current  $I_C$  and the Base-emitter voltage  $V_{BE}$ . Verify your result using a simulation in PSpice. Discuss the similarities between this characteristic and that of a pn junction diode. For the BJT the saturation current is  $I_S=0.1fA$

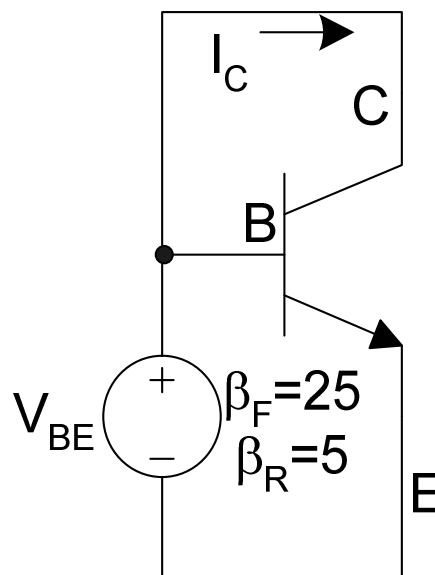**Analysis:**

Since  $V_{BC}=0$  the equation for the collector current reduces to  $I_C = I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$ . This is exactly the formula for the diode current.



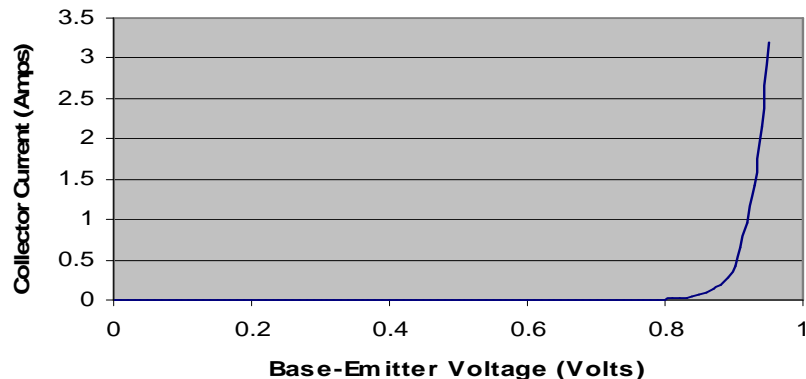
**Common-Emitter Transfer Characteristic for the npn BJT**



PSPICE Demonstrations and Exercises (SET: 14)

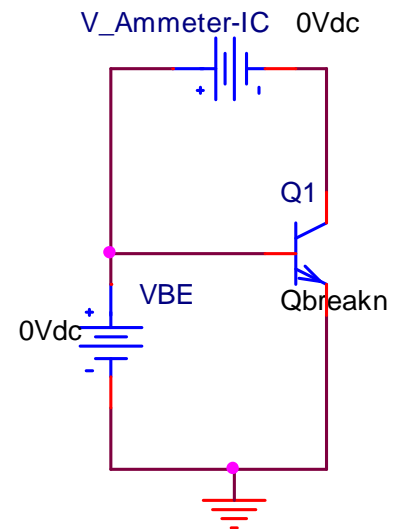**Building the Circuit:**

The circuit is basically the same as that used in Example 1 above. Again a 0Vdc voltage source is used to function as an ammeter to monitor the collector current  $I_C$ . The Circuit is shown to the right.





**Netlist:**

```
*source PSET14EXAMPLE2
Q_Q1          N00087      N00007 0 Qbreakn
V_VBE         N00007      0 0Vdc
V_V_Ammeter-IC N00007      N00087 0Vdc
```

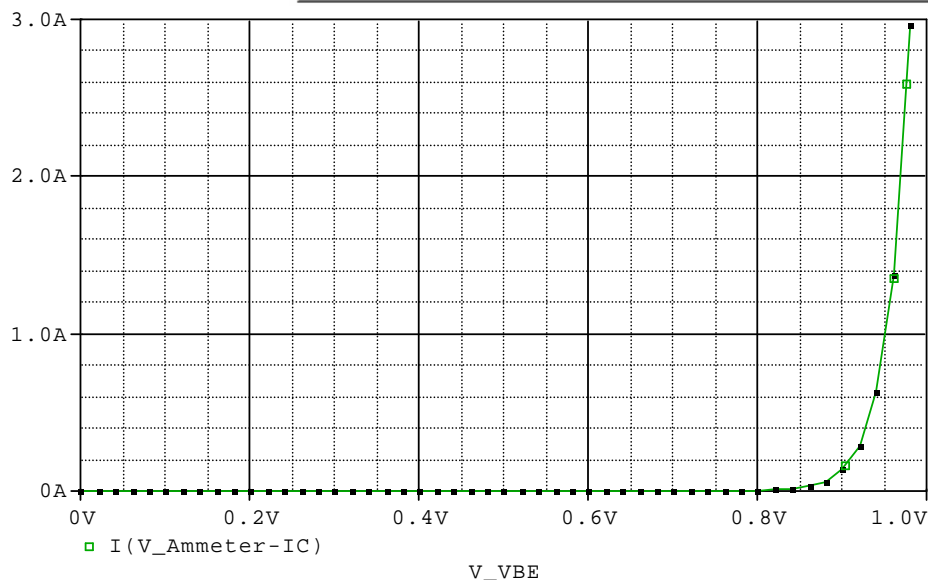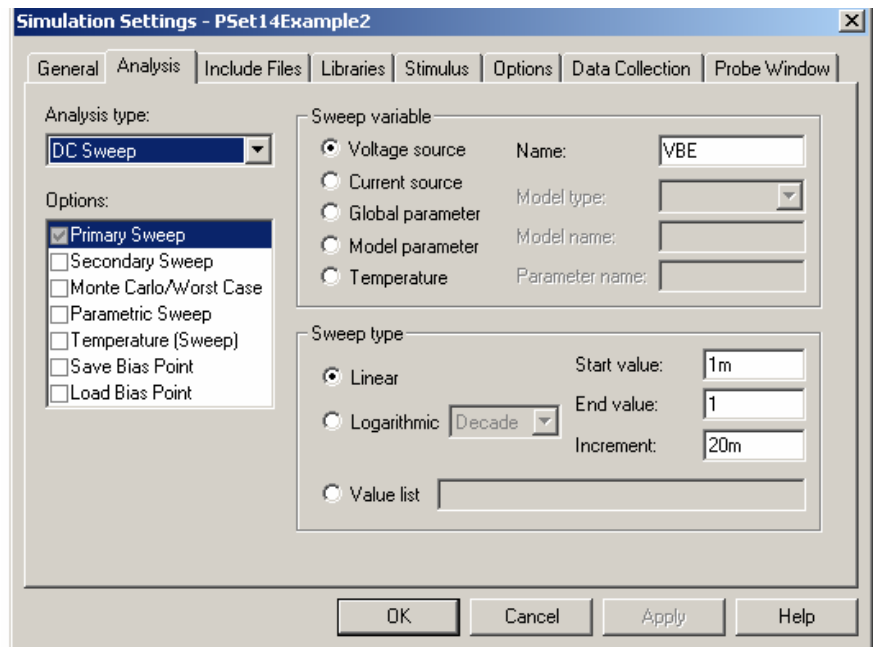**Simulating the Circuit:**


Create a new simulation profile and set-up a DC Sweep for the voltage  $V_{BE}$  as shown. Run the simulation and add a trace for the collector current which corresponds to the current through the 0Vdc ammeter voltage source. The resulting plot is shown below.



View the semi log plot of the transfer characteristic by clicking the Log Y Axis button. The plot appears as a straight line. To find the slop of this line we use the cursor. Applying cursor 1 at approximately 100pA and cursor 2 at approximately 10μA account for 5 decades. Thus the voltage difference between these two points divided by 5 gives the voltage difference per decade.


$$\frac{\text{Voltage}}{\text{decade}} = \frac{297.727\text{mV}}{5 \text{ decades}} = 59.5\text{mV/decade} \cong 60\text{mV/decade}$$

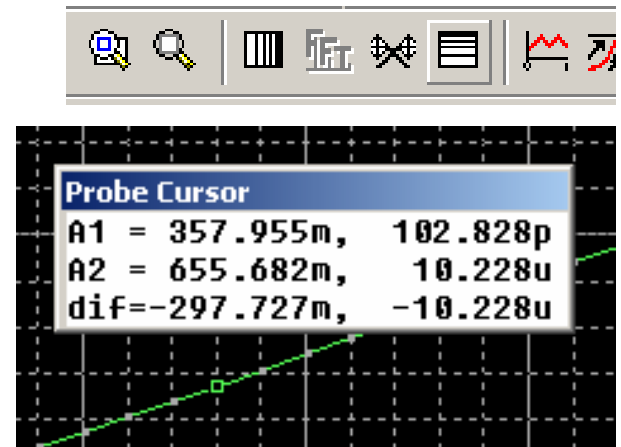An increase of only 60mV in the base-emitter voltage will increase the collector current by a factor of 10.



**Similar Circuits and Exercises:**

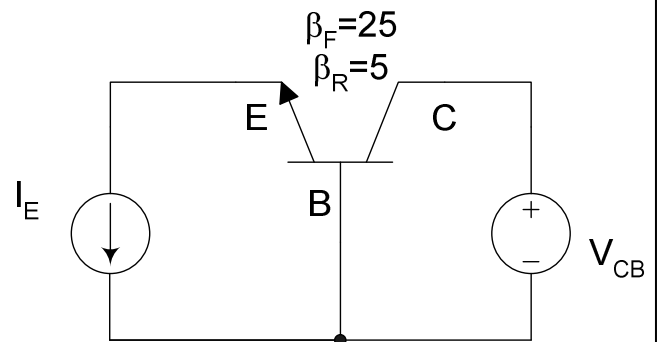**Problem 1)** Sketch the common-base output characteristic for the npn Bipolar Junction transistor in the shown circuit for  $I_E=0.2\text{mA}$ . Verify your result using a simulation in PSpice. Vary the collector-base voltage  $V_{CB}$  between  $-0.85\text{V}$  and  $5\text{V}$  with a step size of  $10\text{mV}$ . Perform this sweep for emitter currents  $I_E = \{0.2\text{mA}, 0.6\text{mA}, 1\text{mA}\}$ . Plot the resulting collector current waveforms.



**Problem 2)** Sketch the common-emitter output characteristic for the pnp Bipolar Junction transistor in the shown circuit for  $I_B=10\mu\text{A}$ . Verify your result using a simulation in PSpice. Vary the emitter-collector voltage  $V_{CE}$  between  $-5\text{V}$  and  $10\text{V}$  with a step size of  $10\text{mV}$ . Perform this sweep for base currents  $I_B = \{10\mu\text{A}, 30\mu\text{A}, 50\mu\text{A}\}$ . Plot the resulting collector current waveforms.

