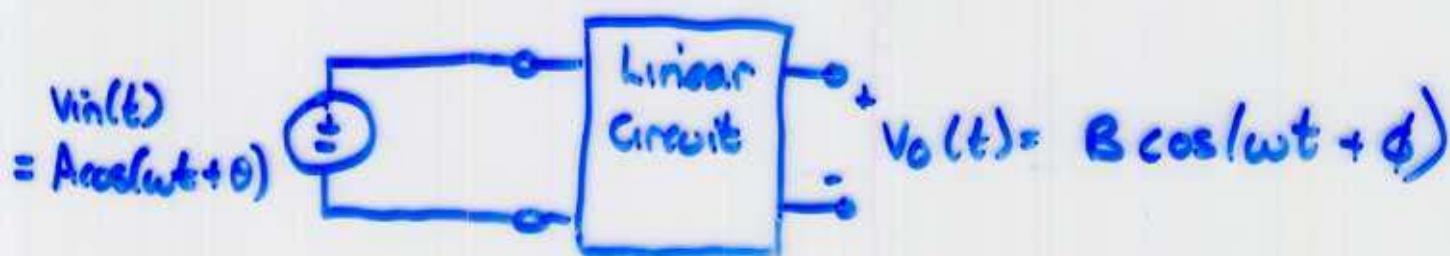


## FREQUENCY RESPONSE

- \* We have already observed that capacitors and inductors have different impedances for sinusoids of different frequencies.
- \* We now provide a framework for analyzing this effect for more general signals



- \* A linear (time-invariant) circuit changes the amplitude + phase of a sinusoid
- \* Moreover the amount of change varies with frequency
- \* Controlling these variations is the key to building filters for stereo equipment, radio reception, cell phones, biomedical equipment, etc.
- \* Note "Frequency response" refers to steady-state behaviour

## Basic Definitions

If  $v_{in}(t) = A \cos(\omega t)$

$$v_{out}(t) = B \cos(\omega t + \phi)$$

then.

$$\text{gain} = B/A.$$

$$\text{phase shift} = \phi - 0 = \phi$$

\* The gain and phase can be combined to form a

single complex number  $\underline{H} = \frac{B}{A} e^{j\phi}$

\* This is actually the ratio of the phasors for  $v_{in}(t)$  and  $v_{out}(t)$ , ie  $\underline{H} = \frac{\underline{V}_{out}}{\underline{V}_{in}}$


\* The value of  $\underline{H}$  is different for different frequencies.

Make this explicit by  $\underline{H}(\omega)$

Gain =  $|H(\omega)|$

phase shift =  $\angle H(\omega)$

EXAMPLE

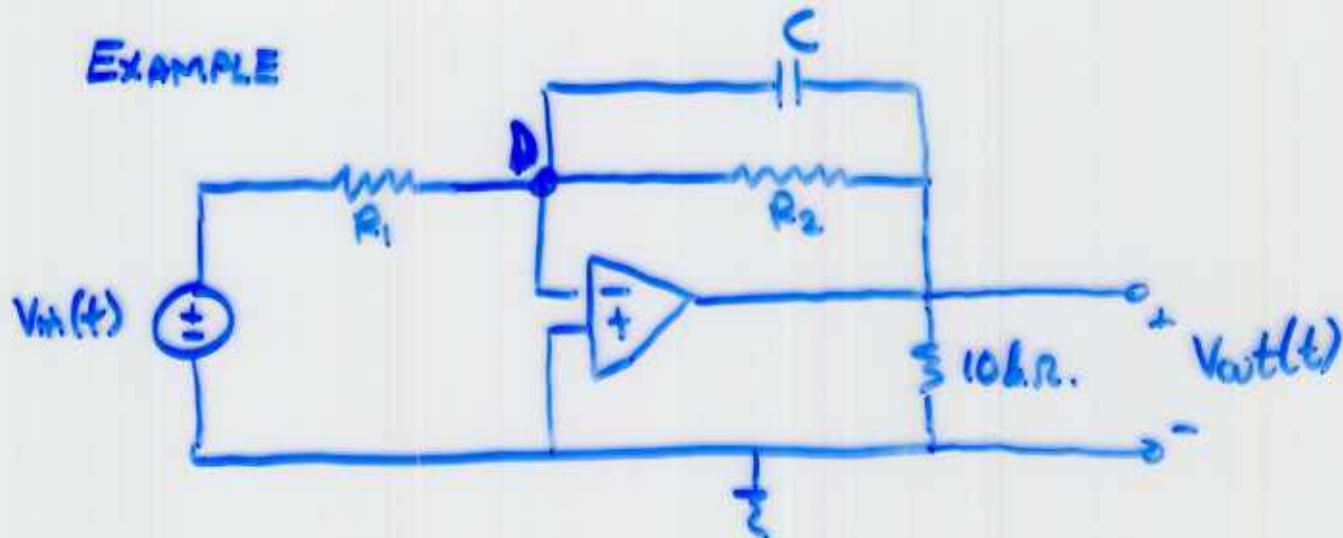

Let  $V_{in}(t) = A \square \omega t$

then its phasor is  $V_{in} = Ae^{j\theta} \approx A$ .

Using KCL at node D, and phasor analysis



(sum currents going in, ideal opamp  $\Rightarrow V_D = 0$ )

$$\Rightarrow \underline{H}(\omega) = \frac{V_{out}}{V_{in}} = \frac{-R_2/R_1}{1 + j\omega CR_2}$$

$$\text{gain} = \frac{R_2/R_1}{\sqrt{1 + \omega^2 C^2 R_2^2}}$$

$$\text{phase shift} = \pi - \tan^{-1}(\omega CR_2)$$


- \* This analysis is useful because it applies to all frequencies, not just one.

What we have just seen is an example of a first order low-pass filter

$$H(\omega) = \frac{H_0}{1 + j\omega/\omega_0}$$

Here  $H_0 = -R_2/R_1$ ,  $\omega_0 = \frac{1}{R_2 C}$

Plot gain. (sketch).

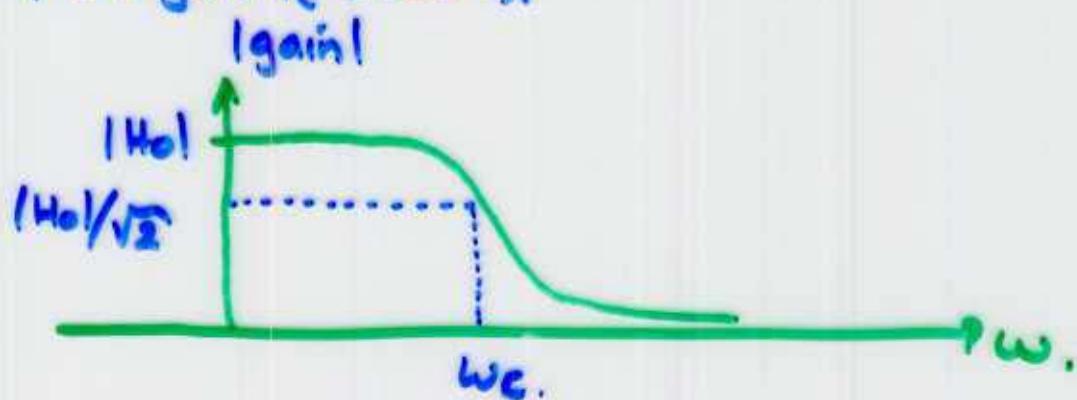

At low frequencies, gain is large

At high frequencies, gain is small

$\omega_c$  is one way to measure the "bandwidth" of the filter; it tells us which frequencies are small + which ones are large

What is the significance of  $\omega_c$ ?

Consider case where  $H_0 = 1$

If  $v_{in}(t) = A \sin \omega_c t$

then  $v_{out}(t) = \frac{A}{\sqrt{2}} \sin(\omega_c t + \Theta)$

The average power of  $v_{in}(t)$  is energy per unit time

$$= \int_0^T v_{in}^2(t) dt, \text{ where } T = \frac{2\pi}{\omega_c}$$

$$= \frac{A^2}{T} \int_0^T \sin^2(\omega_c t) dt$$

$$= \frac{A^2}{2T} \int_0^T 1 - \cos(2\omega_c t) dt.$$

$$= \frac{A^2}{2} - \underbrace{\frac{A^2}{2T} \int_0^T \cos(2\omega_c t) dt}_{\text{Integral of 2 periods of a cosine}}$$

$\approx 0$


$$\Rightarrow P_{in} = \frac{A^2}{2}$$

The average power of the output,  $P_{out} = \frac{A^2}{4} = \frac{P_{in}}{2}$

$\Rightarrow \omega_c$  is the point at which half the power of the sinusoid is attenuated
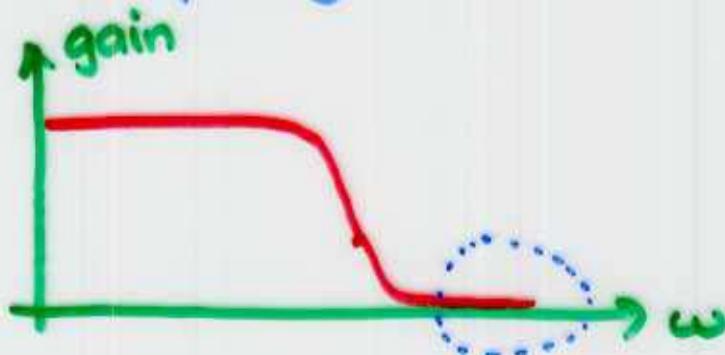
## BODE Plots

- \* These are simply special plots of gain + phase versus frequency
- \* The plots are constructed in such a way that they
  - illustrate how the circuit operates
  - can be approximated quite quickly for "back of the envelope" type computation
- \* One way to see what is happening is to simply plot gain vs frequency



- \* However this is of limited use, because the dashed area is important, but hard to see.
- \* The dashed area may also be important for a broad range of frequencies.
- \* How can we plot all of these things on one graph?  
Take logarithms

\* Define logarithmic gain

$$\text{log. gain} = 20 \log_{10} (|H(\omega)|)$$

\* Unit is "decibel", abbrev. dB.

log.gain often called "gain in dB"

\* where does the name come from?

\* Power ratios.

Given two powers,  $P_1, P_2$

both  $P_1/P_2$  and  $\log_{10}(P_1/P_2)$  measure relative size

The units of  $\log_{10}(P_1/P_2)$  are "bel's", after  
Alexander Graham Bell.

\* The log gain is in decibels because.

$$10 \log_{10} \left( \frac{P_{\text{out}}}{P_{\text{in}}} \right) = 10 \log_{10} (|H(\omega)|^2)$$

=

A Bode Plot consists of two graphs

a) gain in dB vs  $\log_{10}(\omega)$

b) phase shift in degrees vs  $\log_{10}(\omega)$

\* Choice of logarithmic measures allows us to capture all relevant information on one graph.

\* it also allows us to approximate the plots "by hand"

### Drawing Bode Plots by Hand

Let us try this for the simple first-order low-pass filter

$$H(\omega) = \frac{1}{1 + j(\omega/\omega_0)}$$

The gain is

$$\text{gain} = |H(\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$

The log. gain is

$$\text{log. gain} = -20 \log_{10} \left( \sqrt{1 + (\omega/\omega_0)^2} \right)$$

To get an idea of what this looks like, observe that  
for  $\omega \ll \omega_0$ ,

$$1 + (\omega/\omega_0)^2 \approx 1$$

$$\Rightarrow \text{gain in dB} \approx 0 \text{dB}$$

This corresponds to a horizontal line

For large  $\omega$ , i.e.  $\omega \gg \omega_0$ .

$$1 + (\omega/\omega_0)^2 \approx (\omega/\omega_0)^2.$$

$$\Rightarrow \text{gain in dB} \approx -20 \log_{10} \left( \frac{\omega}{\omega_0} \right)$$

$$= +20 \log_{10} \omega_0$$


$$-20 \log_{10} \omega.$$

This is a straight line with slope  
-20 as a function of  $\log_{10} \omega$ .

This slope is often said to be  
-20dB per decade,

where 'decade' is a factor of 10 in frequency

So what do we know?

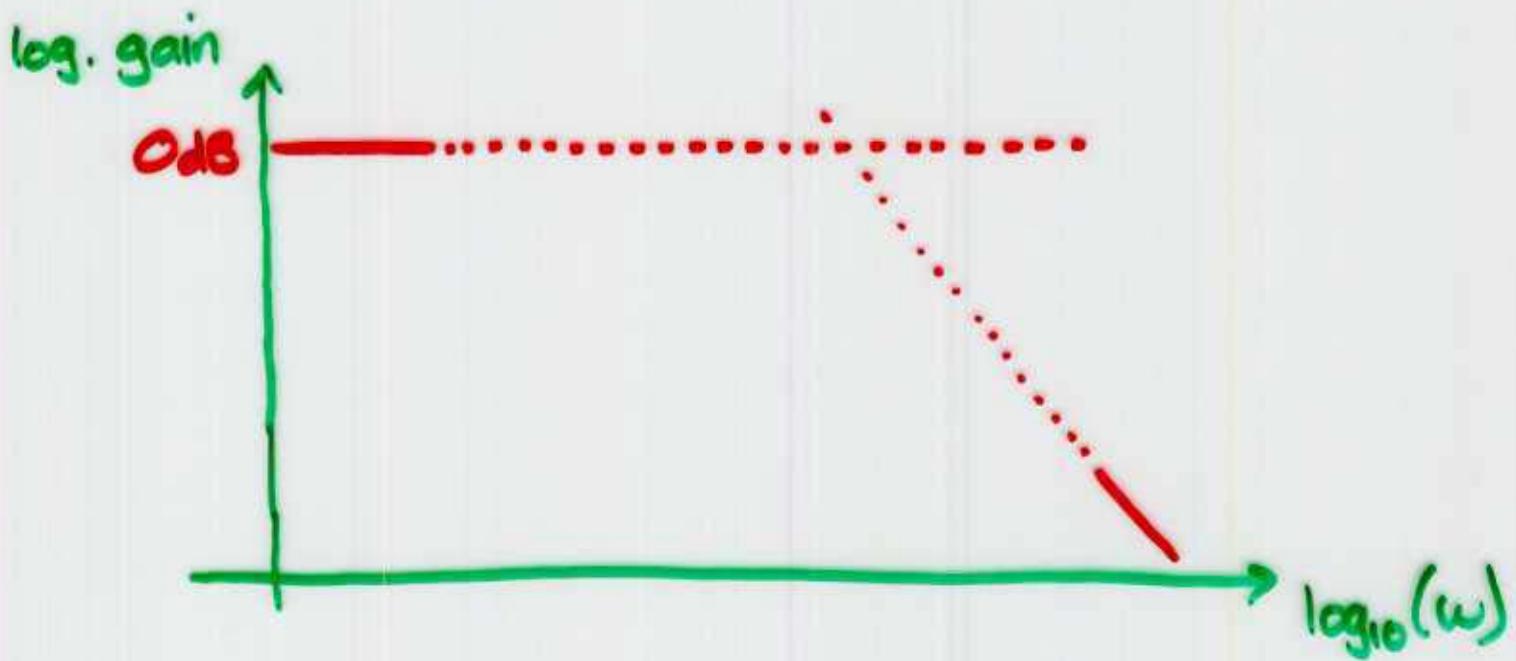

where do these asymptotic approximations intersect?

$$0 = 20 \log_{10}(w_0) - 20 \log_{10}(w)$$

$$\Rightarrow w = w_0.$$

What is the value of the gain at  $w_0$ ?

$$\text{gain} = \frac{1}{\sqrt{1 + (\frac{w_0}{w_0})^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \text{log. gain} = 20 \log_{10}(\frac{1}{\sqrt{2}}) \approx -3 \text{dB}$$

Now what about the phase?


$$H(\omega) = \frac{1}{1+j\omega/\omega_0}$$

$$\Rightarrow \angle H(\omega) = -\tan(\omega/\omega_0)$$

for  $\omega \ll \omega_0$ ,  $\angle H(\omega) \approx -\tan(0) = 0^\circ$


for  $\omega \gg \omega_0$ ,  $\angle H(\omega) \approx -\tan(\infty) = -90^\circ$

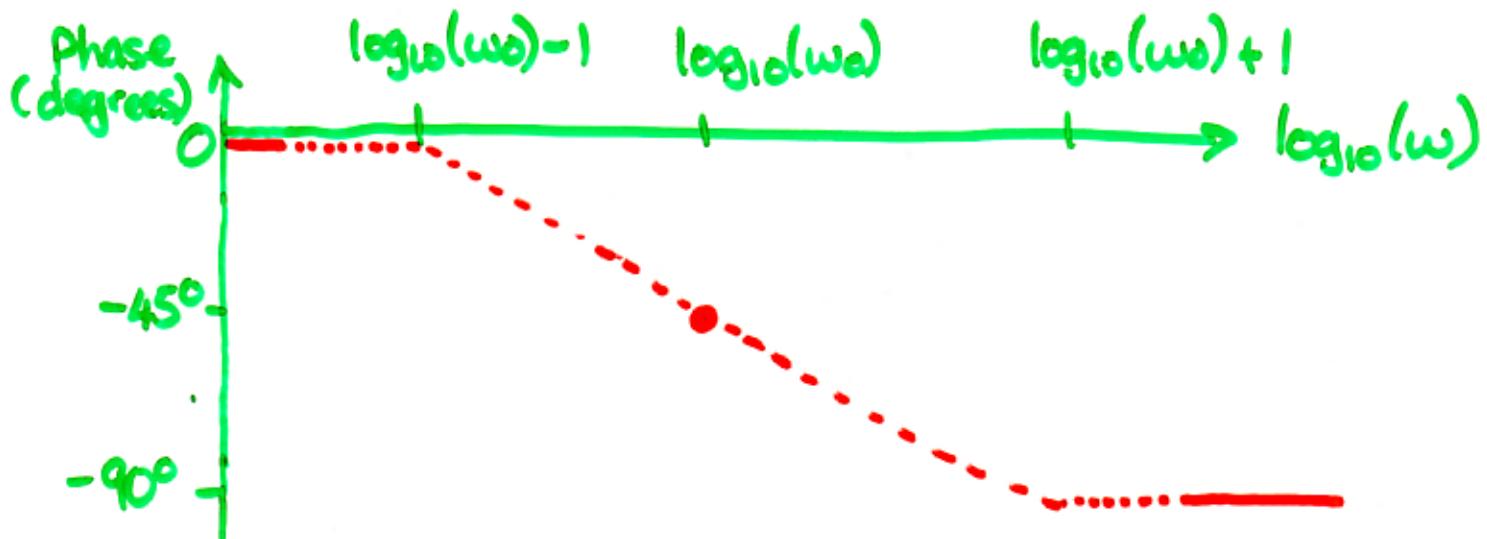for  $\omega = \omega_0$   $\angle H(\omega) = -\tan(1) = -45^\circ$



Accurate to within  $6^\circ$  !

Why is phase important?

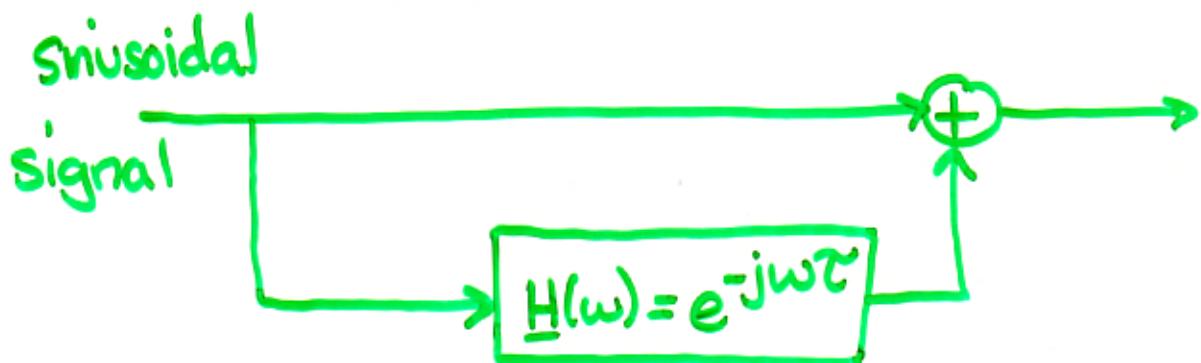

Note that  $|H(j\omega)| = 1$

At what frequencies is the output zero?