
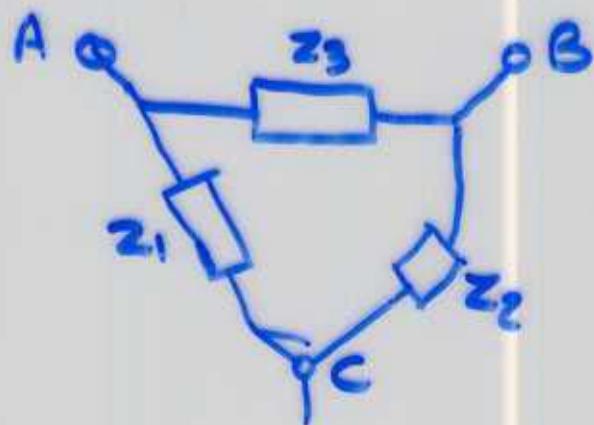

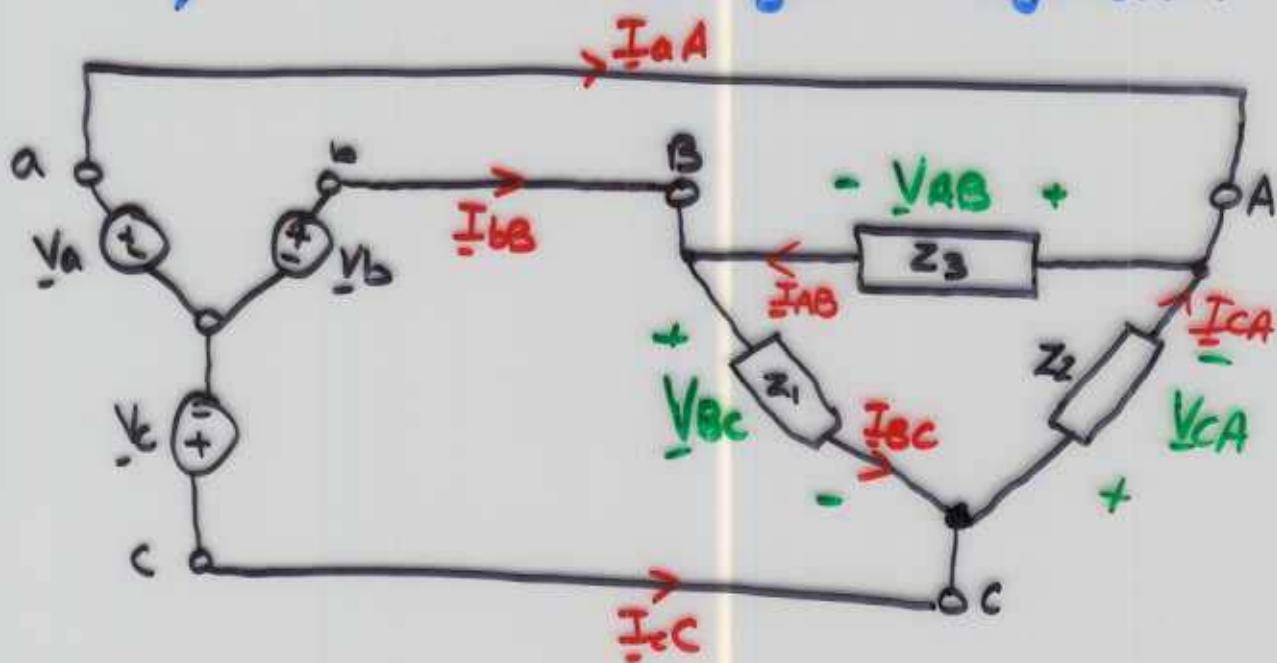
## The Y-Δ Circuit.

In some applications, the load is more naturally configured as a  $\Delta$  connection rather than a  $Y$  connection.



We can build a "Y-equivalent model" for this circuit, but first we analyze it in general.



KCL at nodes A,B,C.

$$\boxed{\quad}$$

$$I_{bB} = I_{Bc} - I_{AB}$$

$$I_{cC} = I_{ca} - I_{Bc}$$

Now  $I_{AB} = \frac{V_{AB}}{Z_3}$

Also  $V_{AB} = V_a - V_b$

If  $V_a = V_p \angle 0^\circ$ ,  $V_b = V_p \angle -120^\circ$

$$\begin{aligned} V_{AB} &= V_p - V_p \cos(-120^\circ) - j V_p \sin(-120^\circ) \\ &= \sqrt{3} V_p \angle 30^\circ \end{aligned}$$


Now if the load is "balanced", ie  $Z_1 = Z_2 = Z_3 = Z \angle 0^\circ$

Then.  $I_{AB} = \frac{\sqrt{3} V_p}{Z} \angle 30^\circ$


Similarly,  $I_{ca} = \frac{\sqrt{3} V_p}{Z} \angle 150^\circ$

$$I_{Bc} = \frac{\sqrt{3} V_p}{Z} \angle -90^\circ$$

- \* We can now find the line currents  $I_{aA}$ , etc using the KCL equations at nodes A, B and C
- \* However, even when the  $\Delta$ -load is balanced, this is much more difficult than dealing with a Y-Y circuit
- \* Wouldn't it be nice if we could calculate the line currents by first transforming the  $\Delta$ -load to an equivalent Y-load, and then using Y-Y analysis.
- \* This can be done for both balanced and unbalanced loads. We will only look at the balanced case.
- \* The question is, given

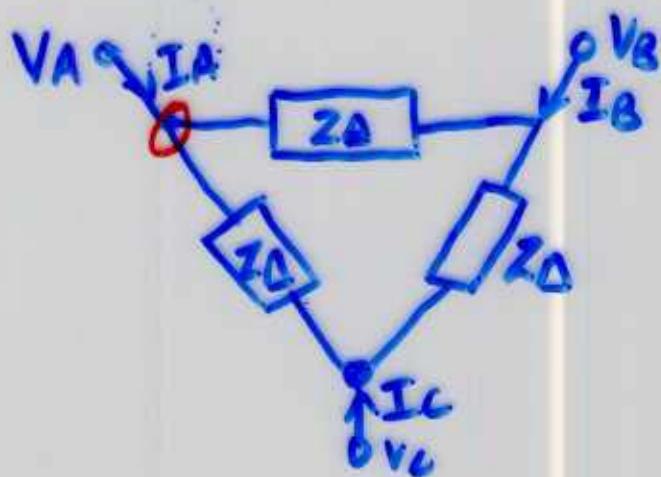

Can we find a  $Z_Y$

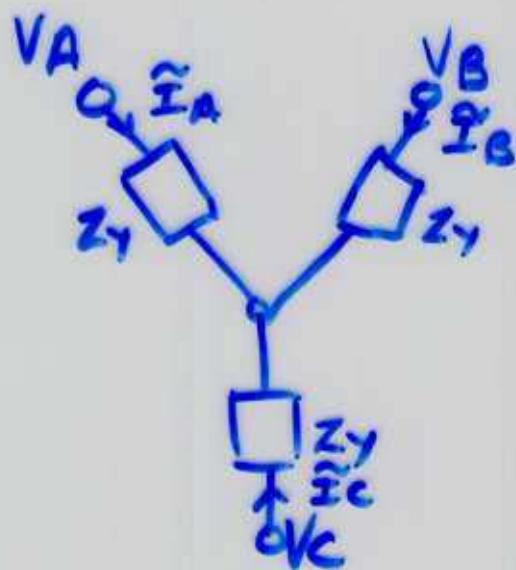

such that

$$\tilde{I}_A = I_A$$

$$\tilde{I}_B = I_B$$

$$\tilde{I}_C = I_C.$$

The answer is Yes!

In fact its enough just to consider  $\tilde{I}_A$  and  $I_A$ .

From Y circuit,  $\tilde{I}_A = \frac{V_A}{Z_Y}$  ①

From  $\Delta$  circuit,  $I_A = I_{AB} - I_{CA}$  ②

If the voltages are balanced,

i.e  $V_A = V_p \angle 0^\circ$ ,  $V_B = V_p \angle -120^\circ$ ,  $V_C = V_p \angle -240^\circ$

Then for ① = ② we require

$$\frac{V_A}{Z_Y} = \frac{V_A - V_B}{Z_\Delta} - \left( \frac{V_C - V_A}{Z_\Delta} \right)$$

$$\Rightarrow \frac{V_A}{Z_Y} = \frac{\sqrt{3} V_p L_{30} - \sqrt{3} V_p L_{-210}}{Z_\Delta}$$

$$\Rightarrow Z_Y = \frac{V_A Z_\Delta}{\sqrt{3} V_p (L_{30} - L_{-210})}$$

$$= \frac{V_p L_0 Z_\Delta}{\sqrt{3} V_p (\cos 30 + j \sin 30 - (\cos(-210) + j \sin(-210)))}$$

$$= \frac{Z_\Delta}{\sqrt{3} \cdot 2 \cdot \cos(30^\circ)}$$

$$= \frac{Z_\Delta}{3}$$


This is the  $\Delta \rightarrow Y$  transformation for balanced loads

This makes it easy to calculate the line currents.

$I_{aA}, I_{bB}, I_{cC}$

To calculate  $I_{AB}, I_{BC}, I_{CA}$ , we must then return to the  $\Delta$  model

## EXAMPLE

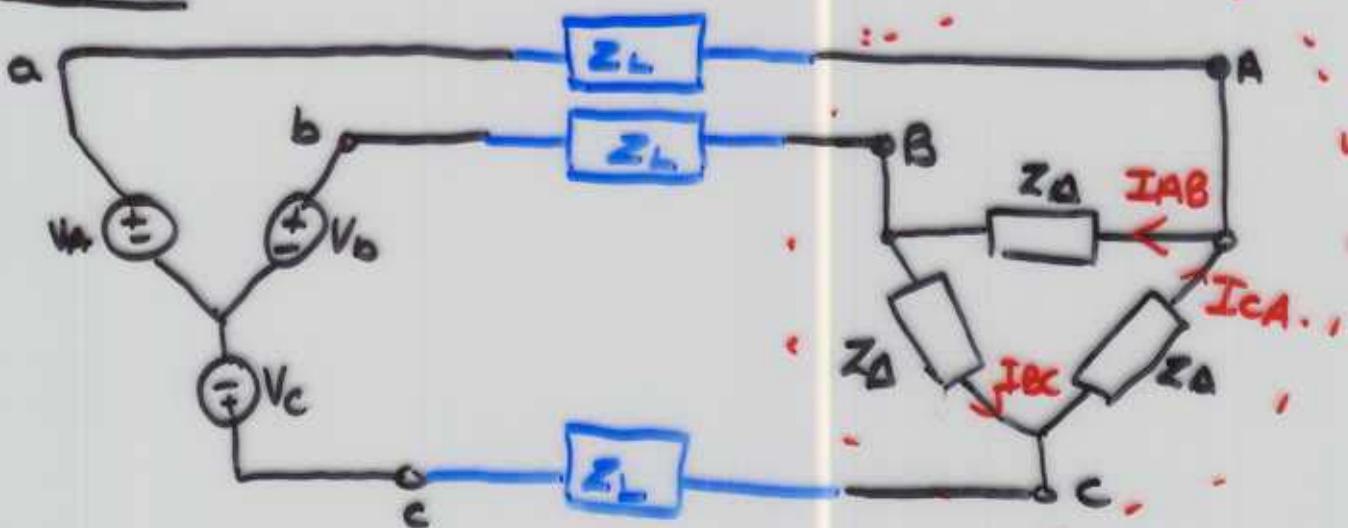

The RMS values of the source voltages

$V_a, V_b, V_c$  are  $110\angle 0^\circ$ ,  $110\angle -120^\circ$  and  $110\angle -240^\circ$  respectively

$$\text{If } Z_L = 10 + j5 \Omega$$

$$\text{and } Z_D = 75 + j225 \Omega$$


Find  $I_{AB}$ ,  $I_{BC}$  and  $I_{CA}$

## SOLUTION

STEP 1 Do A  $\Delta$ - $\gamma$  transformation

The equivalent  $Z_\gamma = 25 + j75 \Omega$

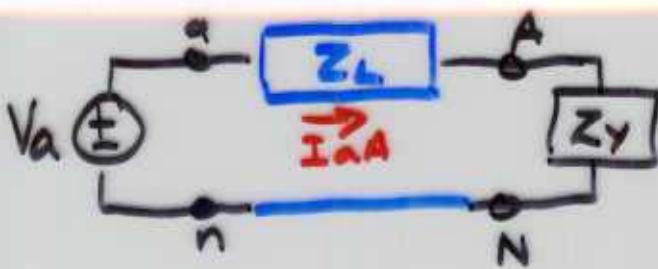STEP 2 PER Phase equivalent circuit for phase A



$$I_{AA} = \boxed{\quad} = \frac{110 \angle 0^\circ}{10 + j5 + 25 + j75} \approx 1.26 \angle -66^\circ \text{ Arms}$$

The other line currents have the same magnitude but phase differences of  $120^\circ$  and  $240^\circ$

$$\Rightarrow I_{BB} = 1.26 \angle -186^\circ \text{ Arms}$$

$$I_{CC} = 1.26 \angle 54^\circ \text{ Arms}$$

Hence the load voltage

$$V_{AN} = I_{AA} Z_Y = 99.6 \angle 50^\circ \text{ Vrms}$$

Similarly  $V_{BN} = 99.6 \angle -115^\circ$

$$V_{CN} = 99.6 \angle 125^\circ$$

Hence the line-to-line voltages are

$$V_{AB} = V_{AN} - V_{BN} = 172 \angle 35^\circ \text{ Vrms}$$

$$V_{BC} = V_{BN} - V_{CN} = 172 \angle -85^\circ \text{ Vrms}$$

$$V_{CA} = V_{CN} - V_{AN} = 172 \angle 155^\circ \text{ Vrms}$$

Therefore the currents in the  $\Delta$  load are

$$I_{AB} = \frac{V_{AB}}{Z_0} = 0.727 \angle -36^\circ \text{ Arms}$$

$$I_{BC} = 0.727 \angle -156^\circ \text{ Arms}$$

$$I_{CA} = 0.727 \angle 84^\circ \text{ Arms.}$$

Now that we have voltages + currents,  
powers are easy to calculate.

~~Graph~~

## Suggested Problems

12-3: 3

12-4: 1-4, 6

12-6: 1, 2

12-7: 1, 2

12-8: 1, 3, 5, 7