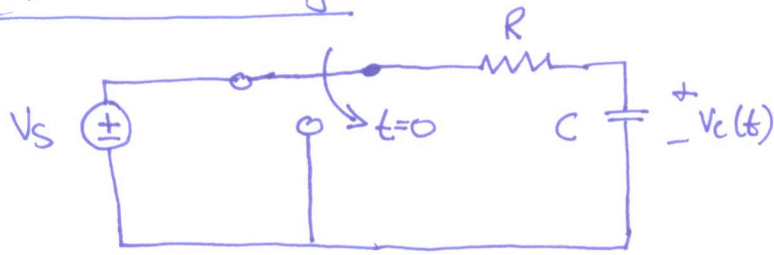


Capacitor Discharge



Assume that the switch has been connected for a long time before $t=0$,

for example, assume that the source was connected before $t = -5RC$


In that case we can assume the circuit is in the steady state.

That means that the capacitor acts as an open circuit to the DC source

Hence $V_c(t)|_{t=0^-} = V_s$

Since the capacitor voltage is ~~continuous~~ ^{continuous}, that implies $V_c(t)|_{t=0^+} = V_s$

For $t \geq 0$

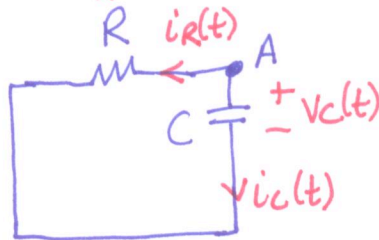

KVL: $-v_R(t) + V_c(t) = 0$

Capacitor: $i_C(t) = C \frac{dV_c(t)}{dt}$

Resistor: $i_R(t) = \frac{V_R(t)}{R}$

KCL at Node A: $i_R(t) + i_C(t) = 0$


By substitution: $\frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = 0$

Solving differential equation: $V_c(t) = K e^{-t/RC}, t \geq 0$

Using initial condition $V_c(0^+) = V_s$

$\Rightarrow V_c(t) = V_s e^{-t/RC}, t \geq 0$

Sketch of $V_C(t)$

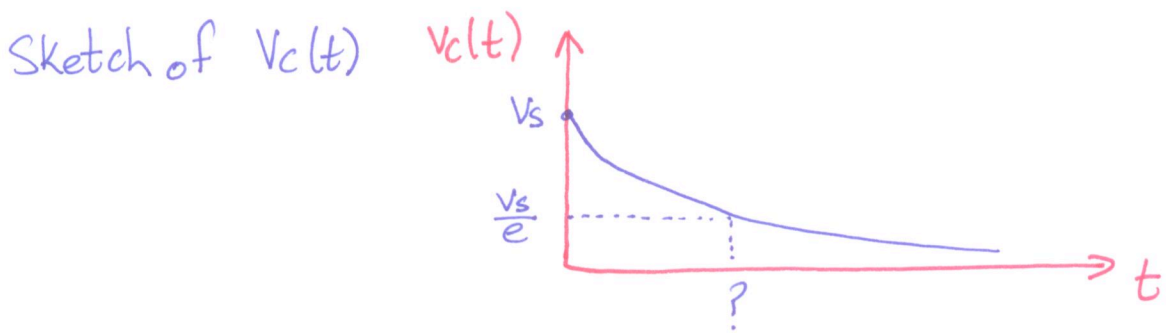

How long does it take for the voltage to drop to $\frac{V_s}{e}$?

One time constant, $\tau = RC$

How long does it take for the voltage to drop below 1% of V_s ?


Find t such that $V_s e^{-t/RC} \leq V_s/100$

$$\Rightarrow \frac{t}{RC} \geq \ln(100)$$

$$\Rightarrow t \gtrsim 4.6 RC = 4.6 \tau$$

How can this analysis be modified to model a (low-frequency) square wave input?

INDUCTOR

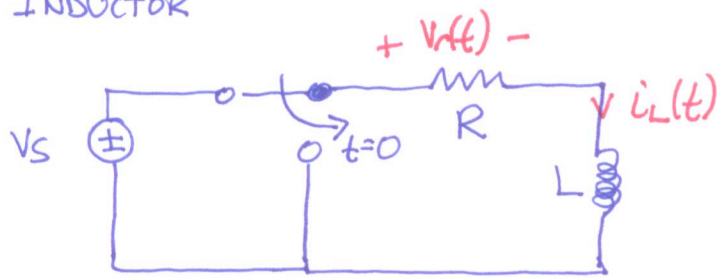


Assume that the source was connected a long time before $t=0$
say before $t = -5L/R$

Then the circuit can be assumed to be in the steady state
That means the inductor acts as a short circuit for the DC input

$$\text{Hence } i_L(t) \Big|_{t=0^-} = \frac{V_s}{R}$$

Since the inductor ~~current~~ current is continuous, $i_L(t) \Big|_{t=0^+} = \frac{V_s}{R}$

For $t \geq 0$

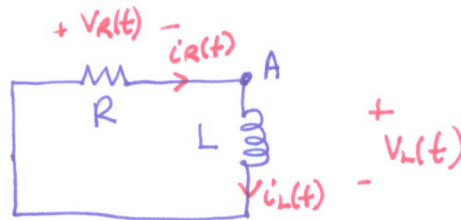

$$\text{KVL: } V_R(t) + V_L(t) = 0$$

$$\text{Inductor: } V_L(t) = L \frac{di_L(t)}{dt}$$

$$\text{Resistor: } V_R(t) = R i_R(t)$$

$$\text{KCL at Node A: } i_R(t) = i_L(t)$$

$$\text{Substitute: } \frac{di_L(t)}{dt} + \frac{R}{L} i_L(t) = 0$$

$$\text{Generic solution: } i_L(t) = K e^{-t/(L/R)}, \quad t \geq 0.$$

$$\text{Initial condition: } i_L(0^+) = \frac{V_s}{R} \Rightarrow i_L(t) = \frac{V_s}{R} e^{-t/(L/R)}, \quad t \geq 0$$

$$\Rightarrow \text{time constant: } \tau = L/R$$