

MESH CURRENT ANALYSIS WITH CURRENT SOURCES

When there are only independent voltage sources, mesh current analysis boils down to

- * identifying the meshes

- * writing the KVL equation for each mesh

if there are N_m meshes $\Rightarrow N_m$ equations in N_m unknowns

The presence of current sources

- sometimes makes things easier


- sometimes makes things ~~harder~~ a bit more complicated

This depends on where the current source is located

CURRENT SOURCES ON AN "EDGE" OF THE CIRCUIT

- ~~Make~~ Make things easier
- Current source affects only one mesh
- Hence we immediately know the current in the mesh
- We do not need to do KVL for that mesh
- Solve the KVLs for the other meshes

EXAMPLE

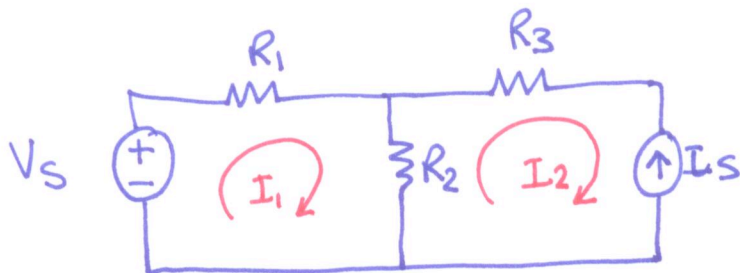


$$I_2 = -I_s$$

$$\text{KVL Loop 1: } -V_s + R_1 I_1 + R_2 (I_1 - I_2) = 0$$

$$\Rightarrow I_1 = \frac{V_s - R_2 I_s}{R_1 + R_2}$$

CURRENT SOURCE IN A BRANCH THAT IS SHARED BY TWO MESHES

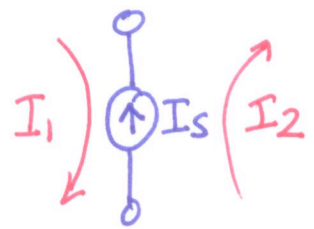- Makes things a little more complicated
- Just writing KVLs around each mesh yields an undetermined linear system
- We need an additional equation




$$I_1 - I_2 = I_s$$

- Can become cumbersome
- Can we streamline the procedure?

SUPER MESH

- Construct a supermesh by fusing the meshes that share the current source
- write KVL around the supermesh
- Use the source to relate mesh currents

EXAMPLE

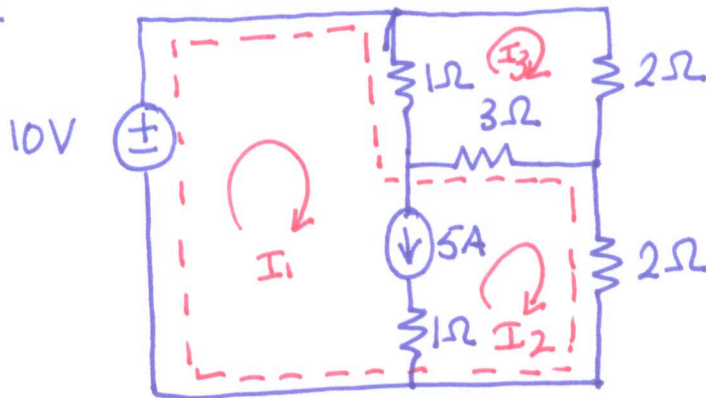

KVL around supermesh $-10 + 1(I_1 - I_3) + 3(I_2 - I_3) + 2I_2 = 0$

Use source $I_1 - I_2 = 5$

KVL for other mesh $1(I_3 - I_1) + 2I_3 + 3(I_3 - I_2) = 0$

3 equations, 3 unknowns

↕
Rewrite



$$I_1 + 5I_2 - 4I_3 = 10$$

$$-I_1 - 3I_2 + 6I_3 = 0$$

$$I_1 - I_2 = 5$$

SOLVE

$$I_1 = 7.5A$$

$$I_2 = 2.5A$$

$$I_3 = 2.5A$$

NODE OR MESH?

- Depends on circuit and question

- Question:

- if required answer is current, tempting to use mesh
- if required answer is voltage, tempting to use node

- However, the circuit is the key factor

① Count number of nodes, N_n

② Count number of meshes, N_m

③ Count number of voltage sources connected to reference node, N_{vr}


Remember you can choose the reference node.
Try to make N_{vr} large

④ Count number of current sources that affect only one mesh current, N_{ie}

⑤ NODE requires $N_n - N_{vr} - 1$ equations

MESH requires $N_m - N_{ie}$ equations

EXAMPLE

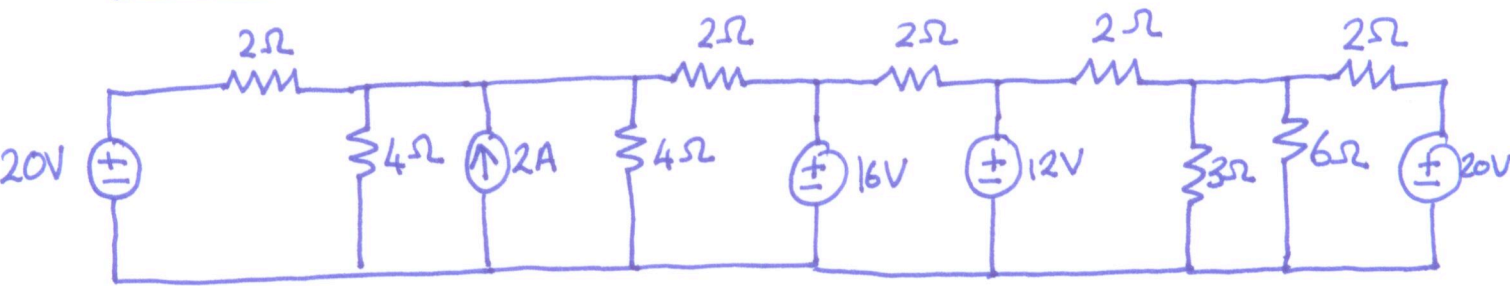

~~Number of nodes~~

Number of nodes $N_n = 7$

Number of meshes $N_m = 8$

~~Choose~~ Choose ref node to be the bottom node

Number of indep. voltage sources connected to ref. node $N_{Vr} = 4$

Number of indep current sources on an edge $N_{Ie} = 0$

Number^{of} equations for mesh analysis: $N_m - N_{Ie} = 8$

Number of equations for node analysis: $N_n - N_{Vr} - 1 = 2$