

## NODE VOLTAGE ANALYSIS WITH VOLTAGE SOURCES.

When the only sources are independent current sources, node voltage analysis boils down to

- \* picking a reference node

- \* writing the KCL equation at all other nodes

if there are  $N$  nodes  $\Rightarrow$   $N-1$  equations in  $N-1$  unknowns

- \* solve the linear system

The presence of voltage sources

- sometimes makes things easier


- sometimes makes things a little more complicated

This depends on how the sources are connected.

# VOLTAGE SOURCES CONNECTED TO THE REFERENCE NODE

- Make things easier
- Immediately know the voltage at the other node to which the source is connected
- We do not need the KCL equation at that node
- Solve the set of KCL equations for the other nodes

## EXAMPLE

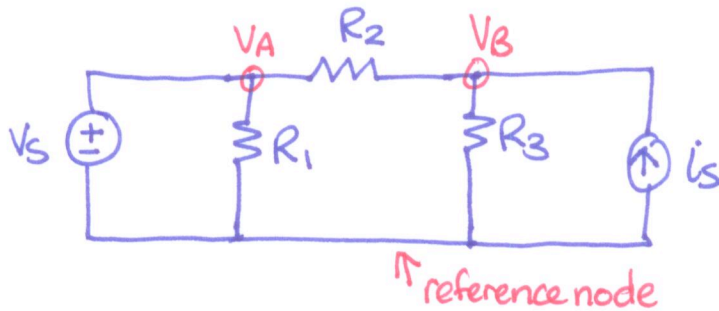

Using the voltage source,  $V_A = V_s$

KCL at node B 
$$\frac{V_A - V_B}{R_2} + i_s = \frac{V_B}{R_3}$$

Two equations, two unknowns

Solution:

$$V_B = \frac{R_2 R_3 i_s + R_3 V_s}{R_2 + R_3}$$

# VOLTAGE SOURCE CONNECTED BETWEEN NON-REFERENCE NODES

- Make things a little more complicated
- Writing KChs at non-reference nodes yields an undetermined linear system
- Reason: there is no Ohm's Law for the branch with the voltage source
- Therefore we need to add an equation that equates the voltage difference between the nodes to the value of the source. e.g.,




$$V_A - V_B = V_S$$

- Can become cumbersome
- Can we streamline the procedure?

# SUPERNODE

- (A) Place the voltage source of interest inside a "supernode"
- (B) Write the KCL equation for the supernode
- (C) Use the source to relate voltages of nodes.

## EXAMPLE

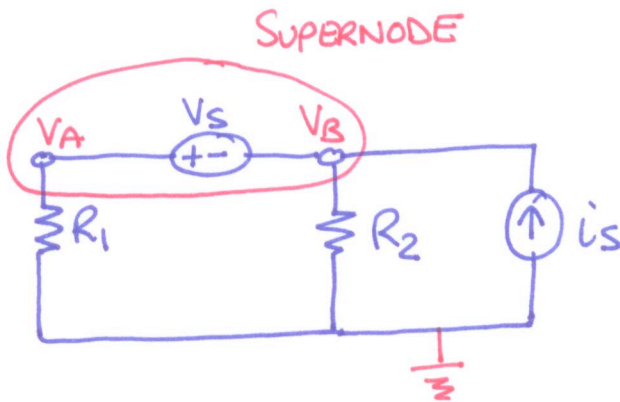

KCL @ supernode

$$i_s = \frac{V_A}{R_1} + \frac{V_B}{R_2}$$

Use source

$$V_A - V_B = V_s$$


Solve :

$$V_B = \frac{R_1 R_2 i_s - R_2 V_s}{R_1 + R_2}$$

What is  $V_A$  ?



# AN EXAMPLE WITH TWO VOLTAGE SOURCES.

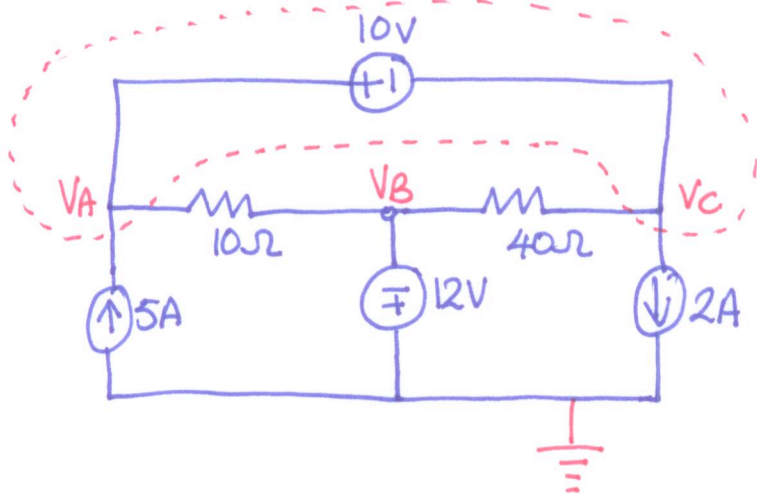

## STEPS

1. Choose reference node
2. Observe that  $V_B = -12V$
3. Place 10V source in a supernode
4. KCL @ supernode :

$$5 = \frac{V_A - V_B}{10} + \frac{V_C - V_B}{40} + 2$$

5. Relate node voltages in supernode.

$$V_A - V_C = 10$$

6. 3 equations, 3 unknowns

7. Solve:

$$V_B = -12V$$

$$V_C = 4V$$


$$V_A = 14V$$

# NODE ANALYSIS WITH DEPENDENT SOURCES.

STEP 1 - Express controlling voltage or current in terms of node voltages

STEP 2 - Proceed as before

## EXAMPLE

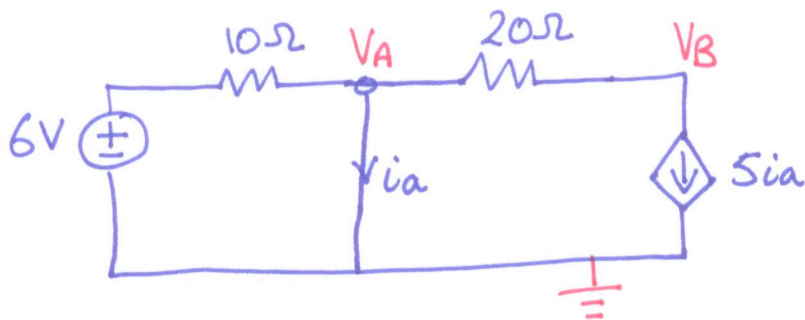

KCL at node A yields :  $\frac{6 - V_A}{10} = i_a + \frac{V_A - V_B}{20}$

Short to reference node :  $V_A = 0$

KCL at node B :  $\frac{V_A - V_B}{20} = 5i_a$

3 equations, 3 unknowns

$$V_B = -10V$$