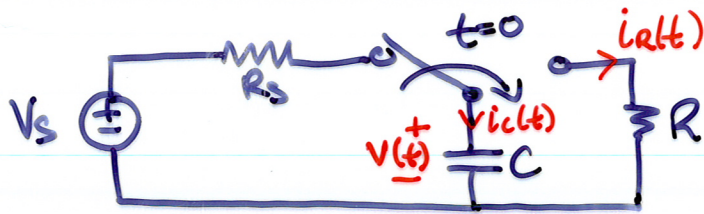


# REVIEW OF FLASH EXAMPLE



For  $t \geq 0$



$$v(0^-) = V_s \\ \Rightarrow v(0^+) = V_s$$

$$\frac{dv(t)}{dt} + \frac{1}{RC} v(t) = 0$$

$$\Rightarrow v(t) = V_s e^{-t/RC}$$


what about current?
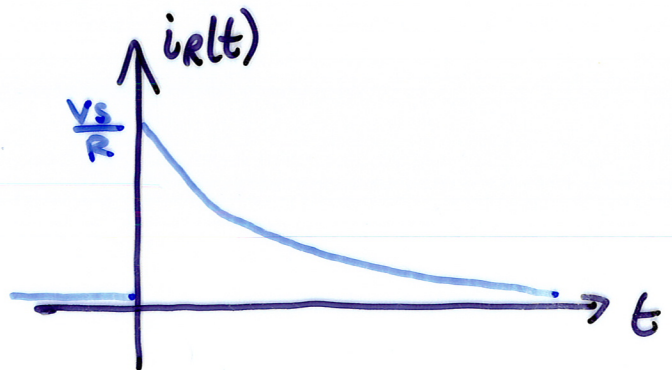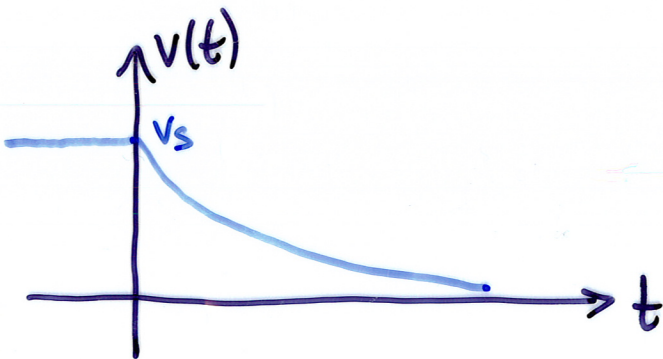
$$i_R(t) = -i_C(t) = -C \frac{dv(t)}{dt} \\ = \frac{V_s}{R} e^{-t/RC}$$



WHAT HAPPENS IF WE CHANGE THE CIRCUIT SLIGHTLY?

Now discharge through an inductor

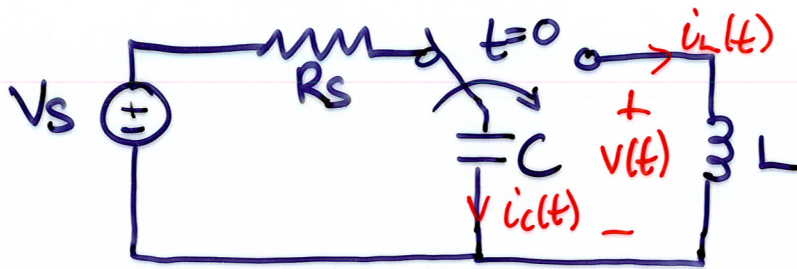

As in previous case,

$$v(0^-) = V_s \Rightarrow v(0^+) = V_s.$$


What about the differences ?

- $i_L(t)$  must be continuous


$$i_L(0^-) = 0 \Rightarrow i_L(0^+) = 0$$

- there are only energy storage elements for  $t > 0$   
No dissipative elements.

LET'S ANALYZE THE CIRCUIT

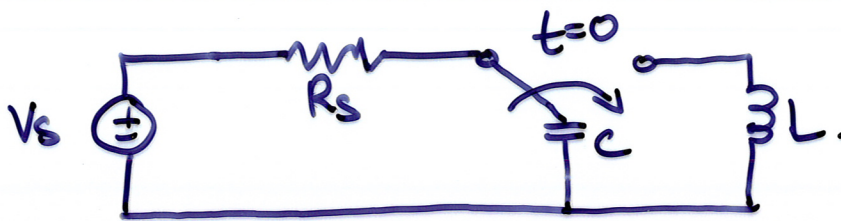

~~After~~ For  $t > 0$  we have.

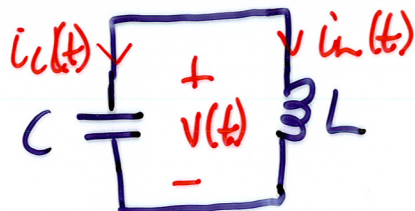

KCL:  $i_C(t) + i_L(t) = 0$

$$\Rightarrow C \frac{dv(t)}{dt} + i_L(t) + \frac{1}{L} \int_0^t v(x) dx = 0$$

Differentiate + divide by C

$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC} v(t) = 0$$

Alternatively

$$\frac{d^2v(t)}{dt^2} = -\frac{1}{LC} v(t)$$

Do you know any functions with this property?

How about  $f(t) = K \cos(\omega t + \theta)$  ?

$$\frac{df(t)}{dt} = -K \omega \sin(\omega t + \theta)$$

$$\frac{d^2f(t)}{dt^2} = -K \omega^2 \cos(\omega t + \theta)$$

Recall that  $\sin(\omega t + \phi) = \cos(\omega t + \phi - \pi/2)$

This suggests that the solution of the equation takes the form.

$$v(t) = K \cos(\omega t + \theta)$$

and indeed we will make this rigorous soon.

First, let's try to determine  $\omega$ ,  $K$  and  $\theta$ .

Aside: Since  $\cos(A+B) = \cos(A)\cos(B) - \sin(A)\sin(B)$

$$K \cos(\omega t + \theta) = [K \cos(\theta)] \cos \omega t - [K \sin(\theta)] \sin \omega t$$

## ● FINDING THE FREQUENCY

$$\frac{d^2 v(t)}{dt^2} = -\frac{1}{LC} v(t)$$

Let's put in our postulated solution  $v(t) = k \cos(\omega t + \theta)$

$$\Rightarrow -k\omega^2 \cos(\omega t + \theta) = -\frac{1}{LC} k \cos(\omega t + \theta)$$

This must hold for all values of  $t$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$

Let's take the positive root:  $\omega = \frac{1}{\sqrt{LC}}$

## ● FINDING $k$ and $\theta$

• Capacitor voltage is continuous  $\Rightarrow v(0^+) = V_s$

$$\Rightarrow k \cos(\theta) = V_s$$

• Inductor current is continuous  $\Rightarrow i_L(0^+) = 0$

by KCL  $i_L(t) = -C \frac{dv(t)}{dt}$

$$\Rightarrow -C k \omega \sin(\theta) = 0$$

## FINAL SOLUTION



$$Q = 0$$

$$K = V_s$$

$$\Rightarrow V(t) = V_s \cos\left(\frac{1}{\sqrt{LC}} t\right)$$

$$\Rightarrow i_L(t) = V_0 \sqrt{\frac{C}{L}} \sin\left(\frac{1}{\sqrt{LC}} t\right)$$

Sketch. ~~these sketches~~

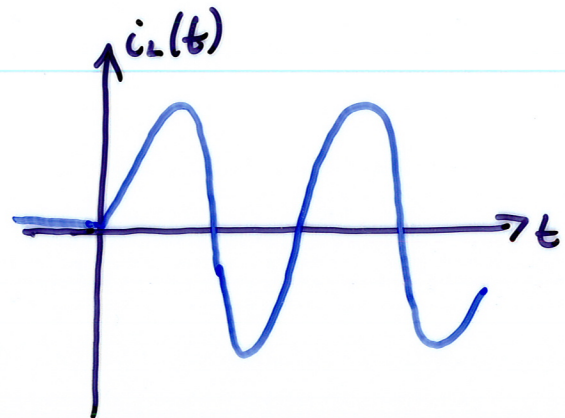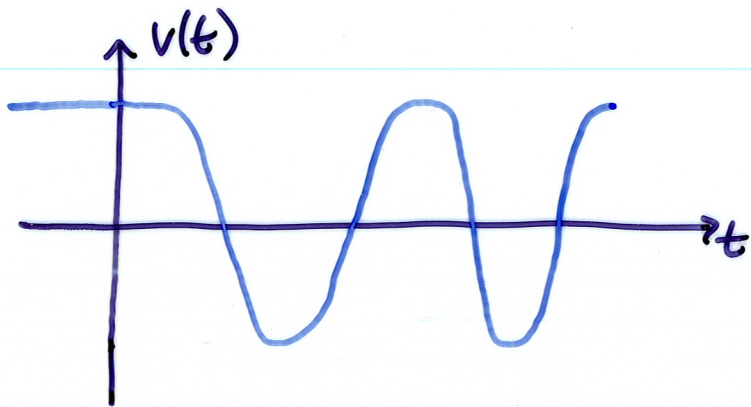

Do these solutions make sense?

What might this circuit be used for?

Notes: frequency only dependent on LC  
Amplitude dependent on  $V_s$