
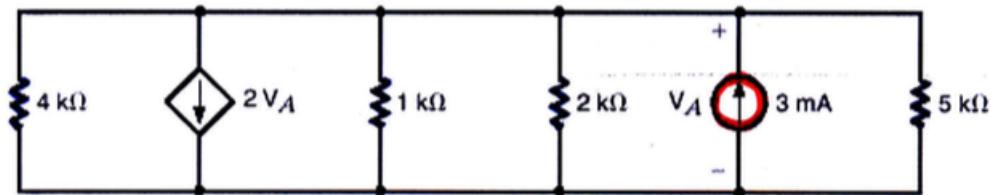


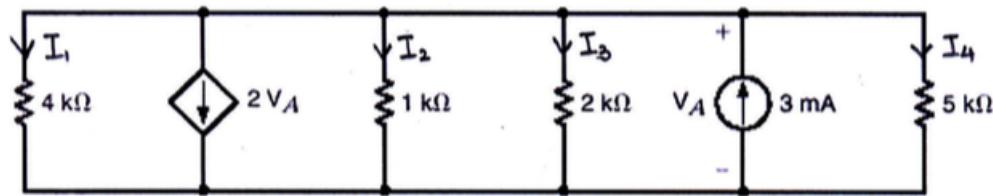Question 1

Find the power absorbed by the dependent source in the network below.



Solution:



$$\text{KCL: } 3m = I_1 + 2V_A + I_2 + I_3 + I_4$$

$$I_1 = \frac{V_A}{4K}, I_2 = \frac{V_A}{1K}, I_3 = \frac{V_A}{2K} \text{ and } I_4 = \frac{V_A}{5K}$$

$$3m = \frac{V_A}{4K} + 2V_A + \frac{V_A}{1K} + \frac{V_A}{2K} + \frac{V_A}{5K}$$

$$60 = 5V_A + 40KV_A + 20V_A + 10V_A + 4V_A$$

$$V_A = 1.5mV$$


$$P_{2V_A} = V_A I = V_A (2V_A)$$

$$P_{2V_A} = (1.5m)(2)(1.5m)$$


$$P_{2V_A} = 4.5\mu W$$

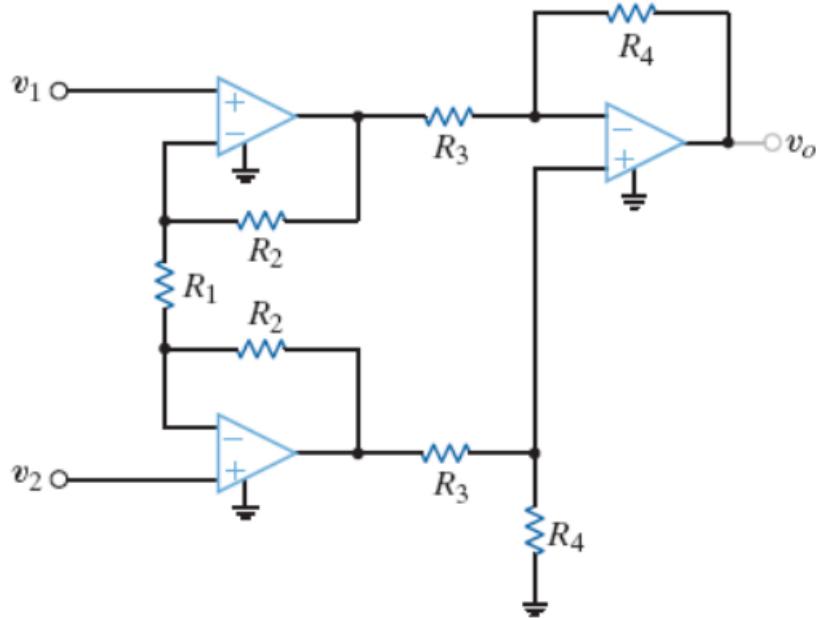Question 2

Find the output voltage, V_O , in the circuit below.



Solution:

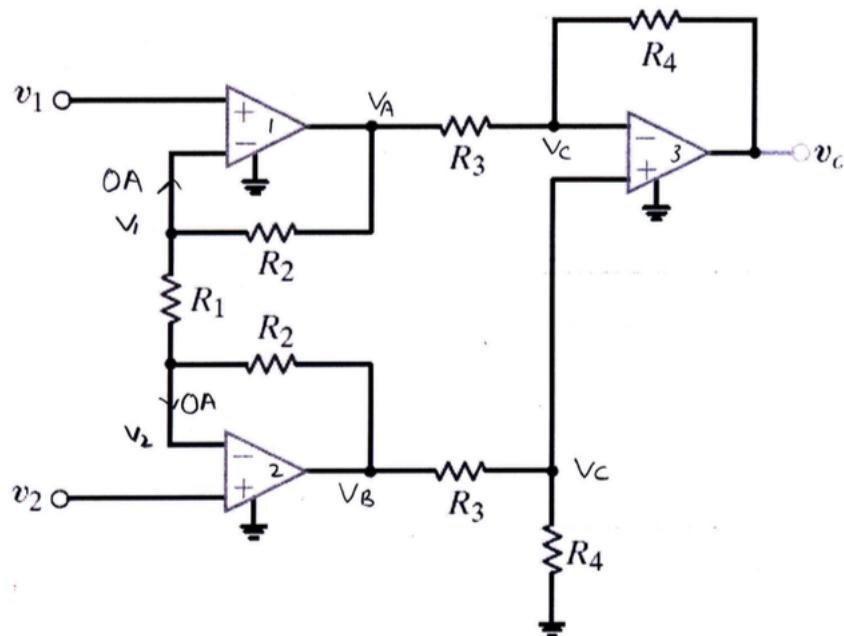

KCL at V_- of op-amp 1:

$$\frac{V_A - V_1}{R_2} = \frac{V_1 - V_2}{R_1}$$

$$V_A = \frac{V_1 - V_2}{R_1} R_2 + V_1$$

$$V_A = (1 + \frac{R_2}{R_1})V_1 - \frac{R_2}{R_1}V_2$$

KCL at V_- of op-amp 2:

$$\frac{V_B - V_2}{R_2} = \frac{V_2 - V_1}{R_1}$$

$$V_B = -\frac{V_1}{R_1}R_2 + \frac{V_2}{R_1}R_2 + V_2$$

$$V_B = (1 + \frac{R_2}{R_1})V_2 - \frac{R_2}{R_1}V_1$$

KCL at V_+ of op-amp 3:

$$\frac{V_B - V_C}{R_3} = \frac{V_C}{R_4}$$

$$V_C(\frac{1}{R_4} + \frac{1}{R_3}) = \frac{V_B}{R_3}$$

$$V_C = (\frac{R_4}{R_3 + R_4})V_B$$

KCL at V_- of op-amp 3:

$$\frac{V_A - V_C}{R_3} + \frac{V_O - V_C}{R_4} = 0$$

$$V_O = -\frac{V_A}{R_3}R_4 + \frac{V_C}{R_3}R_4 + V_C$$


$$V_O = -\frac{V_A}{R_3}R_4 + (1 + \frac{R_4}{R_3})V_C$$

$$V_O = -\frac{R_4}{R_3} \left[(1 + \frac{R_2}{R_1})V_1 - \frac{R_2}{R_1}V_2 \right] + (1 + \frac{R_4}{R_3})(\frac{R_4}{R_3 + R_4}) \left[(1 + \frac{R_2}{R_1})V_2 - \frac{R_2}{R_1}V_1 \right]$$


$$V_O = \frac{R_4}{R_3}(1 + 2\frac{R_2}{R_1})(V_2 - V_1)$$

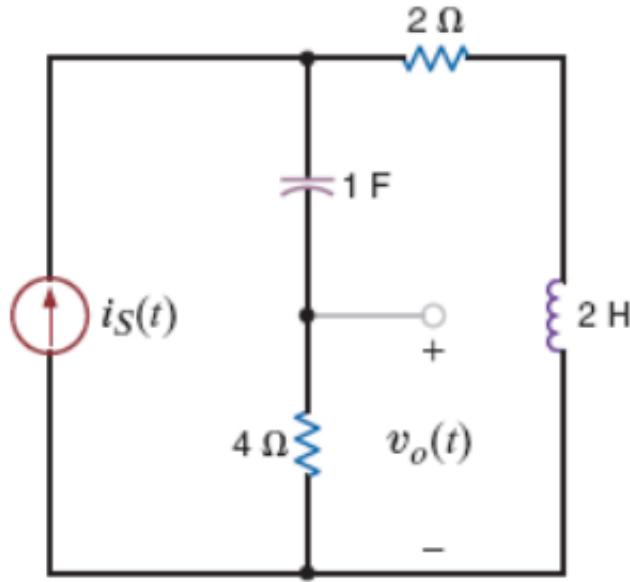Question 3

Find the transfer impedance $V_o(s)/I_s(s)$ for the network.



Solution:

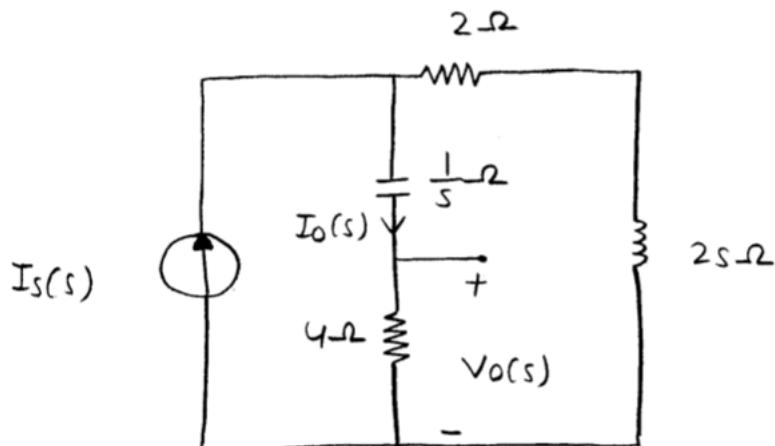

$$I_o = I_s \left(\frac{2+2s}{2+2s+\frac{1}{s}+4} \right)$$

$$I_o = I_s \left[\frac{s(2+2s)}{2s+2s^2+1+4s} \right]$$

$$I_o = I_s \left(\frac{2+2s}{2s^2+6s+1} \right)$$


$$\frac{I_o}{I_s} = \frac{2+2s}{2s^2+6s+1}$$

$$\frac{V_o}{I_s} = \frac{4I_o}{I_s} = 4 \left[\frac{2s(s+1)}{2s^2+6s+1} \right]$$

$$\frac{V_o}{I_s} = \frac{8s(s+1)}{2s^2+6s+1}$$

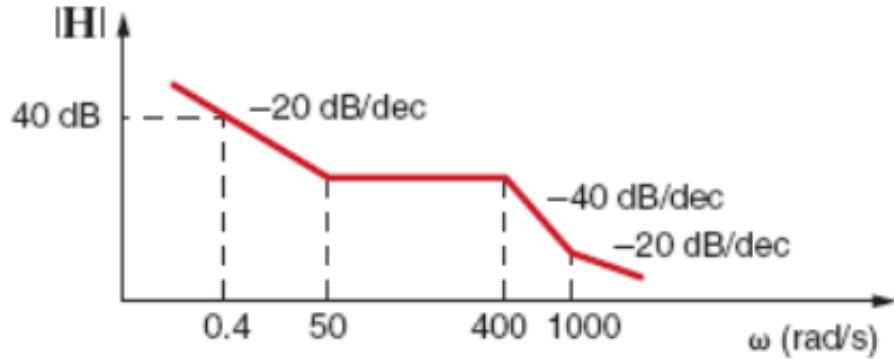Question 4

Find $H(j\omega)$ if its magnitude characteristic is shown below.



Solution:

Poles exist at:

double pole at 400 rad/s

zeroes exist at: 50 rad/s and 1000 rad/s .

$$H(j\omega) = \frac{K(j\omega+50)(j\omega+1000)}{j\omega(j\omega+400)^2}$$

at $\omega = 0.4 \text{ rad/s}$

$$|H(j\omega)| = 40 \text{ dB} = 100$$

$$100 = \frac{K(50)(1000)}{0.4(400)^2}$$

$$K = 128$$

$$H(j\omega) = \frac{128(j\omega+50)(j\omega+1000)}{j\omega(j\omega+400)^2}$$