

Student Name: \_\_\_\_\_  
Student Number: \_\_\_\_\_

**ELEC ENG 2CJ4**

**INSTRUCTOR NAME  
JUN CHEN**

# **McMaster University Final Examination**

**DAY CLASS**

**DURATION OF EXAMINATION: 2 Hours**

**McMASTER UNIVERSITY FINAL EXAMINATION**

**This examination paper includes 4 pages and 7 questions. You are responsible for ensuring that your copy of the paper is complete. Bring any discrepancy to the attention of your invigilator.**

- 1. Use of Casio FX-991 calculator only is allowed.**
- 2. There are seven questions. Please answer all of them.**

1. Find  $\mathbf{H}(j\omega)$  if its magnitude characteristic is shown in Fig. 1.

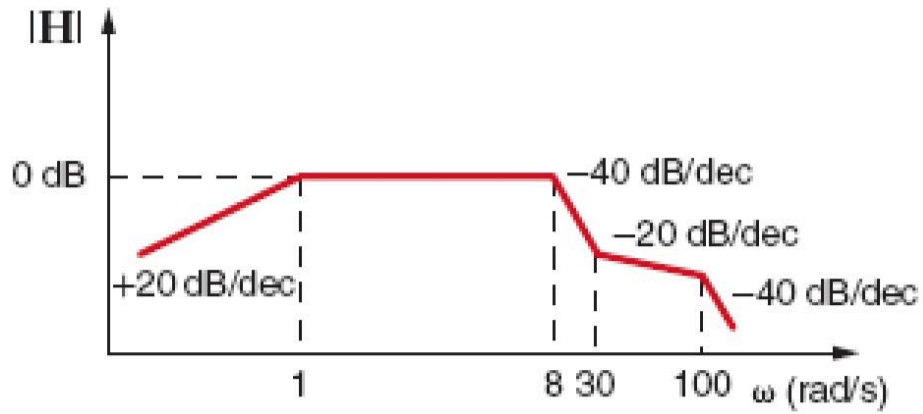


Figure 1

(10%)

2. Given the following functions  $\mathbf{F}(s)$ , find the inverse Laplace transform of each function.

(a)  $\mathbf{F}(s) = \frac{10(s+1)}{s^2+2s+2}$

(b)  $\mathbf{F}(s) = \frac{s+1}{s(s^2+4s+5)}$

(15%)

3. Find  $v_0(t), t > 0$ , in the circuit in Fig. 2

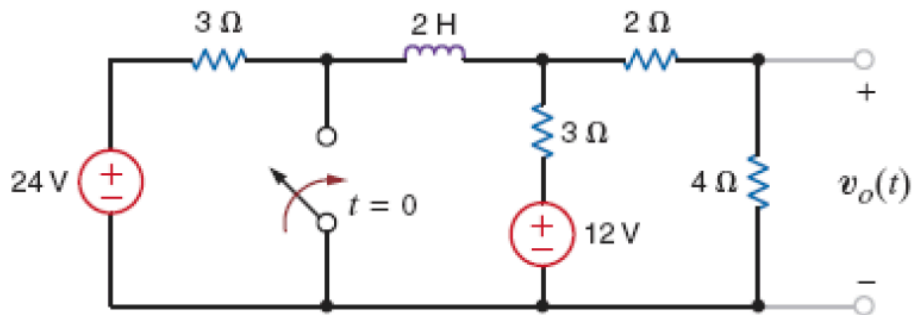


Figure 2

(15%)

4. Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. 3

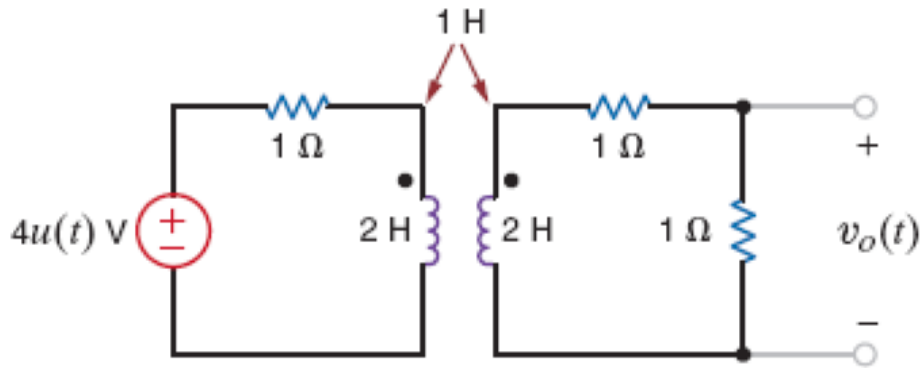


Figure 3

(15%)

5. Find the transfer function for the network in Fig. 4.

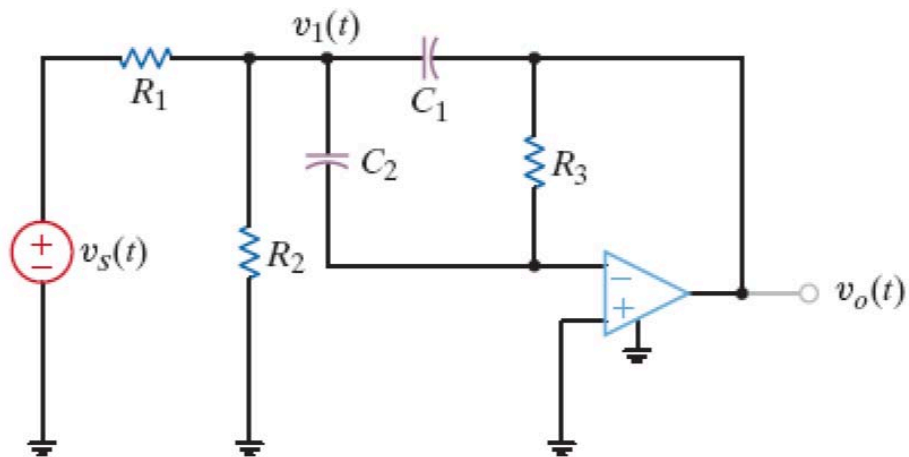


Figure 4

(15%)

6. Find the steady-state response  $v_o(t)$  for the network in Fig.5.

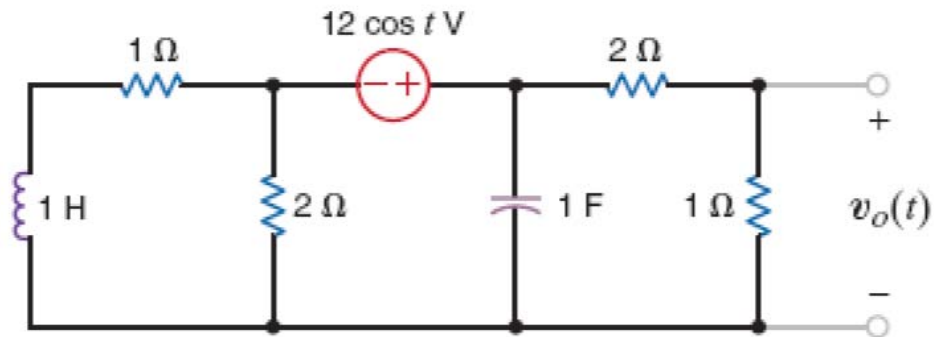


Figure 5

(15%)

7. Find the Z parameters for the two-port network in Fig.6 and then determine  $I_o$  for the specified terminal conditions.

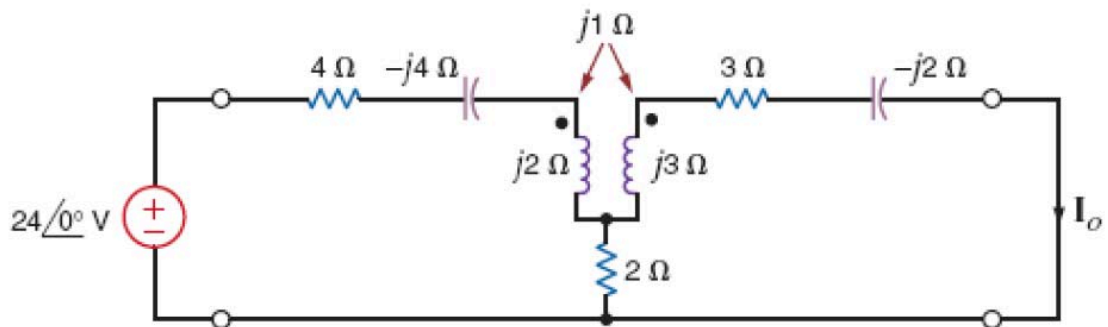


Figure 6

(15%)

THE END

Page 4 of 4