

WAVE REFLECTION

~~GENERAL SOLUTION~~

FOR A FORWARD PROPAGATING WAVE,

$$\left. \begin{aligned} V_S(z) &= V_0^+ e^{-\gamma z} \\ I_S(z) &= \frac{V_0^+}{Z_0} e^{-\gamma z} \end{aligned} \right\} \rightarrow (1)$$

$\gamma = \alpha + j\beta$; $Z_0 = \text{CHARACTERISTIC IMPEDANCE}$

FOR A BACKWARD PROP. WAVE


$$\left. \begin{aligned} V_S(z) &= V_0^- e^{\gamma z} \\ I_S(z) &= -\frac{V_0^-}{Z_0} e^{\gamma z} \end{aligned} \right\} \rightarrow (2)$$

THE GENERAL SOLUTION IS (ADD (1) & (2))

$$\left. \begin{aligned} V_S(z) &= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ I_S(z) &= \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \end{aligned} \right\} \rightarrow (3)$$

HERE V_0^+ & V_0^- ARE UNKNOWN TO BE DETERMINED FROM THE BOUNDARY CONDITIONS. AS AN EXAMPLE, CONSIDER THE WAVE REFLECTION AT THE ~~END~~ END OF TRANSMISSION LINES.

(2)

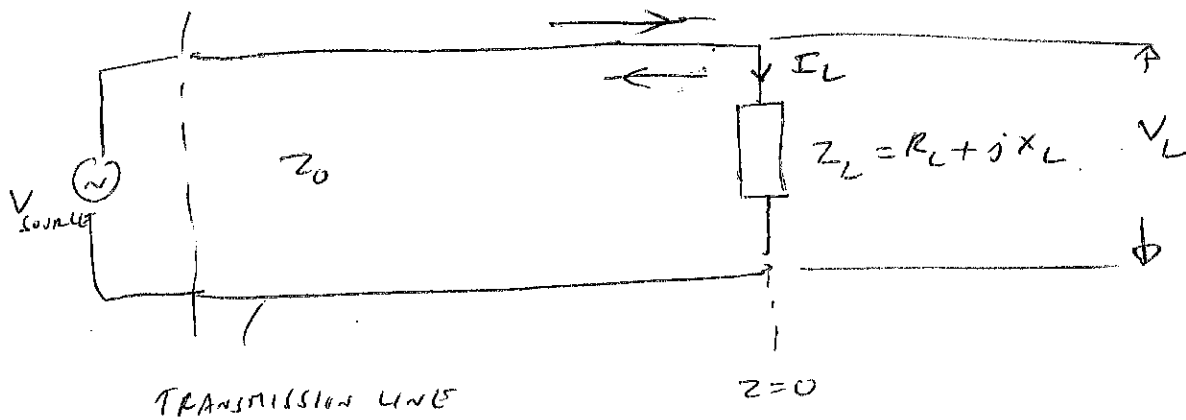

TRANSMISSION LINE

$Z=0$

FIG. 1

IF THE TRANSMISSION LINE IS INFINITELY LONG, IT CAN BE SHOWN THAT THERE IS ONLY FORWARD PROPAGATING WAVE IF THE VOLTAGE SOURCE IS ON THE LEFT. HOWEVER,

IF THE TRANSMISSION LINE OF FINITE LENGTH IS TERMINATED WITH A LOAD IMPEDANCE, THE REFLECTED WAVE (BACKWARD PROPAGATING WAVE) COULD EMERGE.

~~DETERMINED BY THE~~ THE MAGNITUDE OF THE REFLECTED WAVE DEPENDS ON THE DIFFERENCE BETWEEN THE

CHARACTERISTIC IMPEDANCE, Z_0 , OF THE TRANSMISSION LINE

& THE LOAD IMPEDANCE, Z_L , THE REFLECTIONS COULD ALSO

OCCUR AT LOCATIONS AT WHICH TWO DISSIMILAR TR. LINES

ARE CONNECTED TO EACH OTHER, AS SHOWN IN FIG. 2.

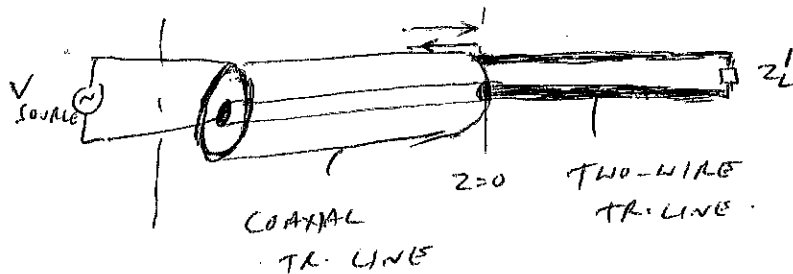


FIG. 2.

(3)

IN FIG. 2, REFLECTION OCCURS AT THE ~~INTERFERENCE~~ OF THE POINTS WHERE COAXIAL & TWO-WIRE LINES ARE CONNECTED TO EACH OTHER. IN THIS CASE, THE EFFECTIVE LOAD TO COAXIAL TR. LINE IS

$$Z_L = \text{IMPEDANCE OF TWO-WIRE LINE} + \text{ACTUAL LOAD, } Z_L'$$

FOR CONVENIENCE, WE CHOOSE THE LOCATION OF LOAD (FIG. 1) OR THE LOCATION AT WHICH TWO (FIG. 2) DISSIMILAR TR. LINES ARE CONNECTED AS $z=0$.

FROM (3), (a) $z=0$,

$$V_L(0) = V_L = V_0^+ + V_0^- \quad \rightarrow (4)$$

$$I_L(0) = I_L = (V_0^+ - V_0^-) / Z_0 \quad \rightarrow (5)$$

~~NOTE THAT~~ V_0^+ = AMPLITUDE OF THE FORWARD WAVE
 V_0^- = " " BACKWARD OR REFLECTED WAVE.

THE RATIO OF THE ~~REFLECTED~~ AMPLITUDE OF THE REFLECTED WAVE TO THE FORWARD (INCIDENT) WAVE AMPLITUDE IS CALLED THE REFLECTION COEFFICIENT, Γ

$$\Gamma = \frac{V_0^-}{V_0^+} \quad \rightarrow (6)$$

FROM (4) & (5),

(4)

$$Z_L = \frac{V_L}{I_L} = \frac{V_0^+ + V_0^-}{(V_0^+ - V_0^-)/Z_0} = \frac{V_0^+ (1 + V_0^-/V_0^+) \cdot Z_0}{V_0^+ (1 - V_0^-/V_0^+)}$$

~~$$Z_L = \frac{V_0^+ + V_0^-}{(V_0^+ - V_0^-)/Z_0}$$~~

$$\frac{Z_L}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma}$$

$$Z_L (1 - \Gamma) = Z_0 (1 + \Gamma)$$

$$Z_L - Z_0 = \Gamma (Z_L + Z_0)$$

or

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

→ (7)

IN GENERAL, Γ IS COMPLEX

$$\Gamma = |\Gamma| e^{j\phi_r}$$

WHEN, $Z_L = Z_0$, $\Gamma = 0 \Rightarrow V_0^- = 0$ (FROM (6))

\therefore NO REFLECTED WAVE WHEN $Z_L = Z_0$. THIS IS

KNOWN AS IMPEDANCE MATCHING. NOW, THE LOAD IS

MATCHED TO THE ~~LINE~~ LINE.

From (4),

(5)

$$\begin{aligned}V_L &= V_0^+ + V_0^- \\ &= V_0^+ \left(1 + \frac{V_0^-}{V_0^+}\right) = V_0^+ (1 + \Gamma)\end{aligned}$$

$$\tau \equiv \frac{V_L}{V_0^+} = 1 + \Gamma \quad \rightarrow (8)$$

τ IS KNOWN AS TRANSMISSION COEFFICIENT.

From (7),

$$\tau = 1 + \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_L + Z_0 + Z_L - Z_0}{Z_L + Z_0}$$

$$\tau = \frac{2Z_L}{Z_L + Z_0} = | \tau | e^{j\phi_L}$$