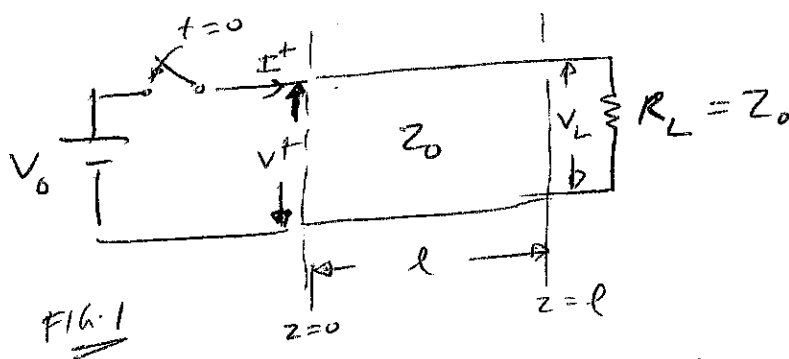


TRANSIENT ANALYSIS

SO FAR WE ~~NEW~~ CONSIDERED THE OPERATION OF TRANSMISSION LINES UNDER STEADY-STATE CONDITIONS WITH AC INPUT. IN THIS SECTION, WE CONSIDER THE TRANSIENTS IN A TRANSMISSION LINE EXCITED WITH DC INPUT. LET US FIRST ANALYZE THE CASE IN WHICH THE LINE IS TERMINATED BY A MATCHED LOAD, $R_L = Z_0$. NOTE THAT FOR A ~~LOSSLESS~~ LOSSLESS LINE, $R=0$ & $G=0$ & HENCE,

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{L}{C}} \text{ IS REAL.}$$



AT $t=0$, THE SWITCH IS CLOSED & THE LINE VOLTAGE AT THE INPUT (~~at $t=0$~~), ~~BECOMES~~ V^+ BECOMES EQUAL TO THE BATTERY VOLTAGE, V_0 . AT $t=0$, THE LOAD VOLTAGE V_L IS ZERO BECAUSE IT TAKES A CERTAIN TIME FOR THE VOLTAGE WAVE TO APPEAR ~~at~~ AT THE LOAD.

(a) $z = 0$

(2)

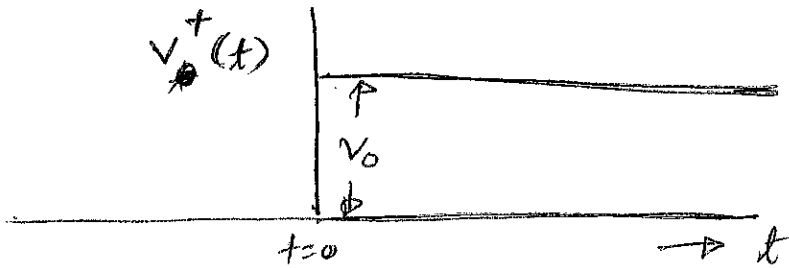


Fig. 2

AS CAN BE SEEN THE LINE VOLTAGE AT THE INPUT IS A STEP FUNCTION. THE VOLTAGE WAVE PROPAGATES AT SPEED v , THE VOLTAGE AT ~~A POINT~~ z_1 IN THE LINE IS SHOWN BELOW.

(a) $z = z_1$

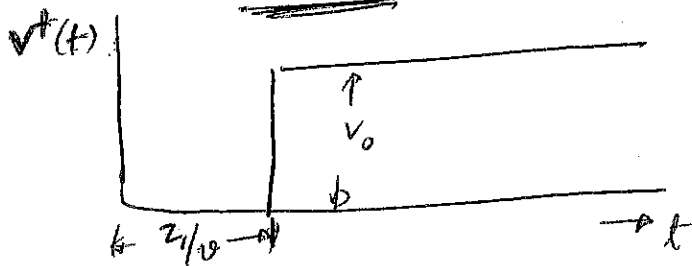


Fig. 3

THE TIME TAKEN BY THE VOLTAGE WAVE TO TRAVERSE THE LINE IS l/v & HENCE ^{THE} LOAD VOLTAGE ~~IS A FUNCTION OF~~

~~THIS~~ IS DELAYED BY l/v AS SHOWN BELOW

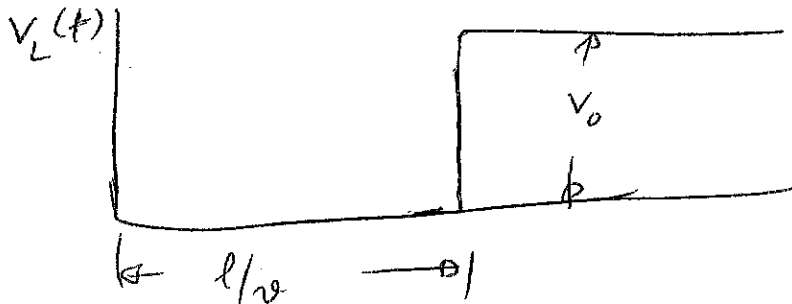


Fig. 4

(3)

THE CURRENT IN THE LINE IS

$$I^+ = \frac{V^+}{Z_0}$$

THE TIME-DEPENDENCE OF I^+ IS THE SAME AS THAT OF

V^+ SHOWN IN FIGS. 2 & 3 (WITH V_0 REPLACED BY ~~V_0~~

$V_0/2_0$ IN FIGS. 2 & 3). THE LOAD CURRENT AT $t = l/v$

IS $I_L = \cancel{V_0/2_0} = V_0/R_L$. TO SUMMARIZE,

$$V_L = \begin{cases} V_0 & \text{FOR } t > l/v \\ 0 & \text{OTHERWISE} \end{cases} \rightarrow \textcircled{1}$$

$$I_L = \begin{cases} V_0/R_L & \text{FOR } t > l/v \\ 0 & \text{OTHERWISE} \end{cases} \rightarrow \textcircled{2}$$

NEXT, LET US CONSIDER A MORE GENERAL CASE IN WHICH THE LOAD IS NOT MATCHED TO THE LINE ($R_L \neq Z_0$). LET US ALSO INTRODUCE A SOURCE RESISTANCE R_g :

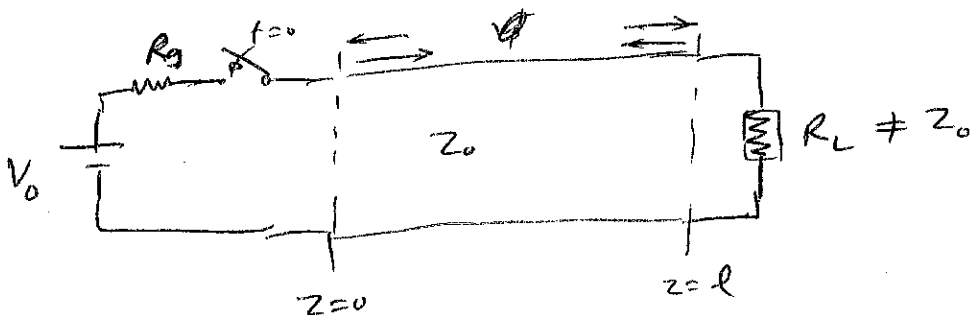


Fig. 5

(4)

At $t = 0$, THE SWITCH IS CLOSED & A VOLTAGE WAVE V_1^+ PROPAGATES TO THE RIGHT. AFTER REACHING THE LOAD, THE VOLTAGE WAVE WILL REFLECT, PRODUCING A BACK-PROPAGATING WAVE V_1^- .

$$\frac{V_1^-}{V_1^+} = \Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} \rightarrow (3)$$

HERE, Γ_L IS THE REFLECTION COEFFICIENT AT THE LOAD. (NOTE: THE SUBSCRIPT L IS ADDED BECAUSE WE HAVE REFLECTIONS AT THE SOURCE, TOO).

THE VOLTAGE IN THE LINE AFTER THE (FIRST) REFLECTION IS $V_1^+ + V_1^-$. ~~AT THE SOURCE~~ THE REFLECTED VOLTAGE V_1^- HEADS TOWARDS THE SOURCE. AT THE

SOURCE, LET US SUPPOSE $R_S \neq Z_0$. BECAUSE OF THE IMPEDANCE MISMATCH, THE V_1^- WAVE IS REFLECTED AT THE SOURCE TO PRODUCE A NEW FORWARD WAVE

V_2^+

$$\frac{\text{REFLECTED } V_2^+}{\text{INCIDENT } V_1^-} = \Gamma_S = \frac{R_S - Z_0}{R_S + Z_0} \rightarrow (4)$$

(\therefore "AS SEEN" BY V_1^- , THE LOAD IS R_S)

(5)

THE NEW FORWARD WAVE V_2^+ PROPAGATES TOWARDS THE LOAD. AT THIS TIME, THE VOLTAGE IN THE LINE IS

$$\begin{aligned}
 V_1^+ + V_1^- + V_2^+ &= V_1^+ + \Gamma_L V_1^+ + \Gamma_g V_1^- \\
 &= V_1^+ + \Gamma_L V_1^+ + \Gamma_L \Gamma_g V_1^+ \quad \rightarrow \textcircled{5}
 \end{aligned}$$

V_2^+ IS REFLECTED AT THE LOAD TO PRODUCE A NEW BACKWARD WAVE V_2^- .


$$\frac{V_2^-}{V_2^+} = \Gamma_L$$

AFTER MANY ROUNDTrips, THE ^{LINE/} LOAD VOLTAGE IS (i.e. STEAD STATE)


$$\begin{aligned}
 V_L &= V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ + V_3^- + \dots \\
 &= V_1^+ \left(1 + \frac{\Gamma_L}{x} + \frac{\Gamma_L \Gamma_g}{x} + \frac{\Gamma_L^2 \Gamma_g}{x} + \frac{\Gamma_L^2 \Gamma_g^2}{x} + \dots \right) \\
 &= V_1^+ \left(1 + \Gamma_g \Gamma_L + \Gamma_g^2 \Gamma_L^2 + \dots \right) + \Gamma_L \left(1 + \Gamma_L \Gamma_g + \Gamma_g^2 \Gamma_L^2 + \dots \right) \\
 &= V_1^+ (1 + \Gamma_L) \left(1 + \Gamma_g \Gamma_L + \Gamma_g^2 \Gamma_L^2 + \dots \right) \rightarrow \textcircled{6} \\
 &= \frac{V_1^+ (1 + \Gamma_L)}{(1 - \Gamma_g \Gamma_L)} \rightarrow \textcircled{7}
 \end{aligned}$$

(6)

(∴ FOR A GEOMETRIC SERIES, $1 + a + a^2 + \dots$
 $= \frac{1}{1-a}$ if $|a| < 1$)

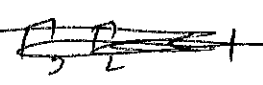~~IT CAN BE SHOWN THAT~~ )

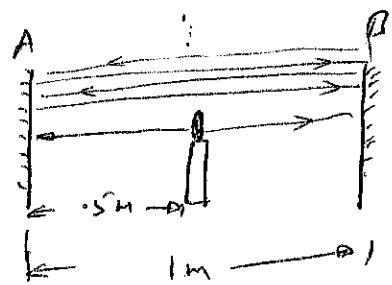CONSIDER THE FOLLOWING ANALOGY: AN OBJECT IS PLACED BETWEEN THE MIRRORS THAT ARE 1m APART.



AS THE LIGHT FROM THE OBJECT FALLS ON THE LEFT MIRROR, ONE COULD SEE A VIRTUAL IMAGE OF THE OBJECT (APPEARS TO BE AT DISTANCE 0.5m BEHIND THE MIRROR), WHICH I CALL THE FIRST VIRTUAL IMAGE. THE LIGHT REFLECTED FROM THE MIRROR A IS ALSO REFLECTED FROM MIRROR B & PROPAGATES TOWARDS THE MIRROR A, PRODUCING A ^{SECOND} VIRTUAL IMAGE (APPEARS TO BE AT DISTANCE 2.5m BEHIND THE MIRROR A). THE BRIGHTNESS OF THE SECOND IMAGE IS LESS THAN THAT OF THE FIRST IMAGE SINCE THE REFLECTIVE COEFFICIENTS Γ_A & Γ_B OF THE MIRRORS IS ALWAYS LESS THAN UNITY. THIS PROCESS CONTINUES & THERE ARE

①

INFINITE NUMBER OF VIRTUAL IMAGES IN BOTH MIRRORS UNDER THE STEADY-STATE CONDITIONS. HOWEVER, WE MAY BE ABLE TO SEE THREE OR FOUR IMAGES DEPENDING IN THE QUALITY OF THE MIRRORS. SIMILARLY, IN THE CASE TRANSMISSION LINES,

~~V_1^-~~ ~~V_2^+~~

... $|V_2^-| < |V_2^+| < |V_1^-| < |V_1^+|$ & HENCE THE

SUM IN EQ. (6) CONVERGES.

AS AN EXAMPLE, LET $R_g = 0$;

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = -1$$

AT $A=0$, IN THIS CASE, VOLTAGE AT THE INPUT OF THE LINE, $V_1^+ = V_0$. FROM (7), THE STEADY-STATE LOAD VOLTAGE IS



$$V_L = \frac{V_0 (1 + \Gamma_L)}{1 - (-1)\Gamma_L} = V_0$$

SO, UNDER THE STEADY-STATE^{CONDITIONS}, THE LOAD IS CHARGED TO THE BATTERY VOLTAGE. NOTE THAT THIS IS A LOSSLESS TRANSMISSION LINE & THERE IS NO VOLTAGE

LOSS IN THE LINE.

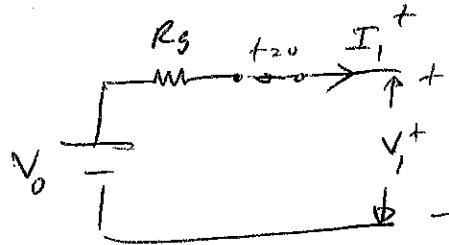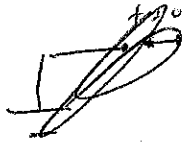(8)

NEXT, LET US CONSIDER A MORE GENERAL CASE $R_g \neq 0$. AT $t=0$.



APPLYING KVL, $V_1^+ = V_0 - I_1^+ R_g$

FOR A FORWARD WAVE: $I_1^+ = V_1^+ / Z_0$

$$V_1^+ (1 + R_g / Z_0) = V_0$$

or

$$V_1^+ = \left(\frac{Z_0}{Z_0 + R_g} \right) V_0$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$$

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0}$$

FROM (7),


$$V_L = \frac{\left(\frac{Z_0}{Z_0 + R_g} \right) V_0 \times \left(1 + \frac{R_L - Z_0}{R_L + Z_0} \right)}{1 - \left(\frac{R_L - Z_0}{R_L + Z_0} \right) \left(\frac{R_g - Z_0}{R_g + Z_0} \right)}$$

(9)


$$V_L = \left(\frac{z_0}{z_0 + R_S} \right) V_0 \times \left(\frac{2R_L}{R_L + z_0} \right)$$

$$\frac{(R_L + z_0)(R_S + z_0) - (R_L - z_0)(R_S - z_0)}{(R_L + z_0)(R_S + z_0)}$$
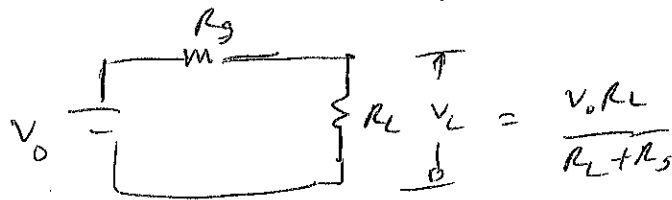
$$= \left(\frac{z_0}{z_0 + R_S} \right) V_0 \times \frac{2R_L \times (R_S + z_0)}{2z_0(R_L + R_S)} = \frac{V_0 R_L}{R_L + R_S}$$



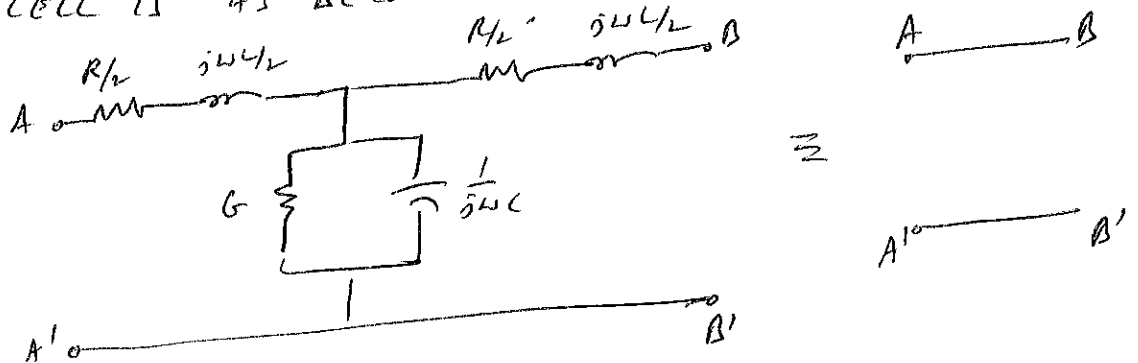UNDER THE STEADY STATE CONDITIONS, VOLTAGE ACROSS THE LOAD CAN BE FOUND FROM THE ~~VOLTS~~ THROUGH SIMPLE VOLTAGE DIVISION RULE, AS IF THE LINE IS A SHORT CIRCUIT. THIS IS BECAUSE, THE EQUIVALENT CIRCUIT OF THE TRANSMISSION LINE UNIT CELL IS AS BELOW



FOR A LOSSLESS LINE, $R = G = 0$. REACTANCE DUE TO INDUCTANCE IS ZERO ($\because \omega = 2\pi f = 0$ for DC).

(10)

THE CONDUCTANCE $G=0 \Rightarrow$ SHUNT RESISTANCE $= \frac{1}{G} = \infty$.
 \Rightarrow OPEN CIRCUIT.

$\omega = 0 \Rightarrow \frac{1}{j\omega L} = \infty \Rightarrow$ OPEN CIRCUIT
(i.e. CAPACITOR BLOCKS THE DC VOLTAGE)

FIG. 6 SHOWS THE VOLTAGE REFLECTION DIAGRAM. TIME IS PLOTTED ON THE VERTICAL AXIS & DISTANCE z IS PLOTTED ON THE HORIZONTAL AXIS.

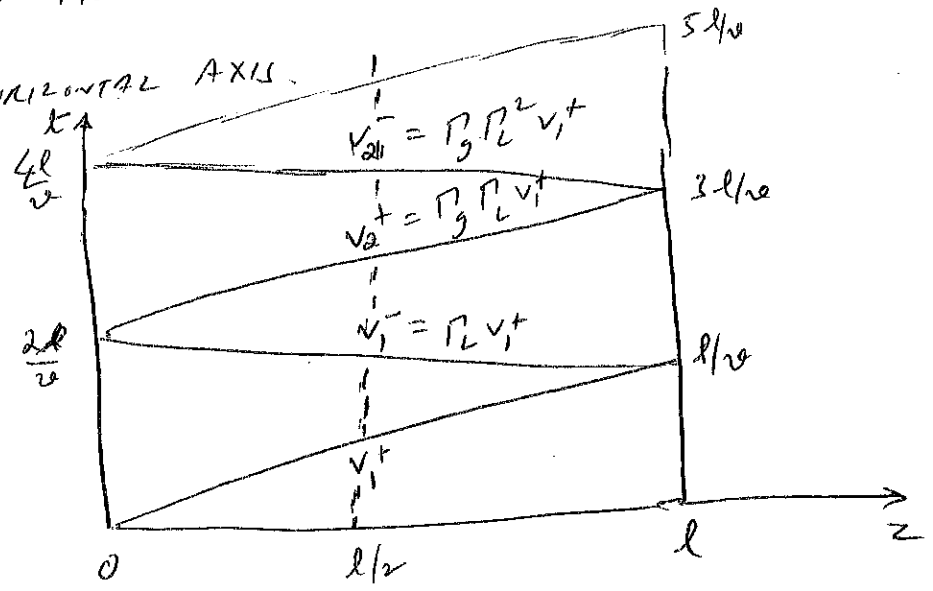


FIG. 6

AT $t=0$, INITIAL VOLTAGE WAVE V_1^+ STARTS AT THE ORIGIN ($t=z=0$). IT REACHES THE LOAD ($z=l$) AT $t=l/v$. THE SLOPE OF THE FIRST DIAGONAL LINE IS $1/v$. V_1^+ IS REFLECTED AT THE LOAD TO PRODUCE A NEW BACKWARD WAVE WITH THE AMPLITUDE $V_1^- = \Gamma_L V_1^+$, WHICH REACHES THE SOURCE AT $t=2l/v$. V_1^- WAVE IS REFLECTED AT THE SOURCE

(11)

TO PRODUCE A NEW ~~WAVE~~ FORWARD WAVE WITH THE

AMPLITUDE $V_2^+ = \frac{1}{5} V_1^-$, WHICH REACHES THE LOAD

AT $t = 3l/v$ & SO ON.

THE VOLTAGE AT ANY POINT ON THE LINE AT

A TIME t_1 , CAN BE FOUND BY ADDING THE VOLTAGES

AT THAT POINT FROM $t=0$ TO t_1 . FOR EXAMPLE,

TO DETERMINE THE VOLTAGE AT THE MIDDLE OF THE

LINE $(z = l/2)$ AT $t = 4l/v$, ADD THE VOLTAGES

AT $z = l/2$ (VERTICAL DASHED LINE) FROM $t=0$ TO $4l/v$, I.E.

$$V(l/2, 4l/v) = V_1^+ + V_1^- + V_2^+ + V_2^-.$$

EXAMPLE 1

(12)

SUPPOSE $R_L = R_g = \frac{1}{3} Z_0$

$$\Gamma_L = \Gamma_g = \frac{R_L - Z_0}{R_L + Z_0} = \frac{(\frac{1}{3} - 1)Z_0}{(\frac{1}{3} + 1)Z_0} = -\frac{1}{2}$$

THE STEADY-STATE LOAD VOLTAGE IS

$$V_L = \frac{V_0 \times R_L}{R_L + Z_0} = \frac{V_0}{2}$$

$$V_1^+ = \frac{V_0 \times Z_0}{R_L + Z_0} = \frac{3}{4} V_0$$

$$V_1^- = \Gamma_L V_1^+ = -\frac{3}{8} V_0$$

$$V_1^+ + V_1^- = \frac{3}{8} V_0$$

$$V_2^+ = \Gamma_g V_1^- = +\frac{3}{16} V_0$$

$$V_1^+ + V_1^- + V_2^+ = \left(\frac{3}{8} + \frac{3}{16}\right) V_0 = \frac{9}{16} V_0$$

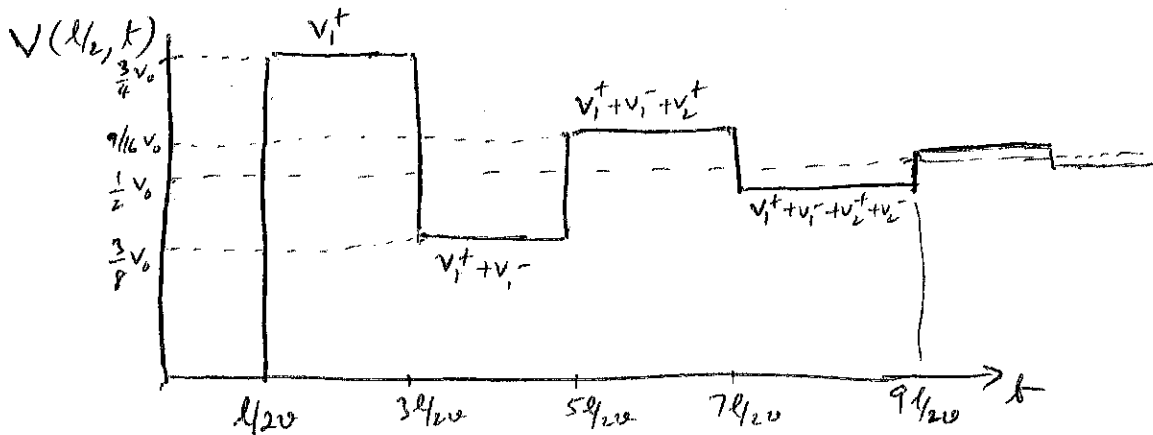


Fig. 7

(12) (13)

FIG. 7 SHOWS THE LINE VOLTAGE AT $z = l/2$. NOTE THAT THE LINE VOLTAGE AT $z = l/2$ IS ZERO FOR $t < l/(2v)$ SINCE IT TAKES $l/(2v)$ SECONDS FOR THE VOLTAGE WAVE TO ARRIVE AT $l/2$ FROM THE BATTERY. THE REFLECTED WAVE IS GENERATED AT THE LOAD AT $t = l/v$ & IT TAKES $l/(2v)$ SECONDS TO ARRIVE AT $z = l/2$ - SO, V_1^- IS ADDED TO V_1^+ AT $t = 3l/(2v)$ & SO ON.

LINE CURRENT CAN BE FOUND ~~FROM~~ IN A SIMILAR WAY THROUGH A CURRENT REFLECTION DIAGRAM. THE FORWARD CURRENT

IS

$$I^+ = \frac{V^+}{Z_0} \quad \rightarrow (*)$$


& THE BACKWARD CURRENT IS

$$I^- = \frac{-V^-}{Z_0} \quad \rightarrow (**)$$

DUE TO OPPOSITE DIRECTION


EQS. (*) & (**) ARE VALID FOR ANY ORDER OF REFLECTIONS, I.E.,
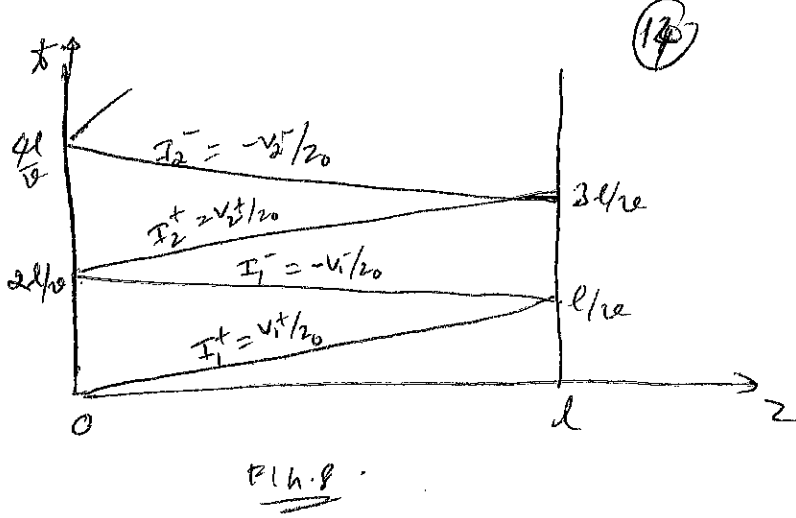
$$I_j^+ = \frac{V_j^+}{Z_0} \quad \& \quad I_j^- = -\frac{V_j^-}{Z_0} \quad \text{FOR } j = 1, 2, \dots$$



IN EXAMPLE 1, (SEE p. 12), $R_L = R_S = \frac{1}{3} Z_0$.

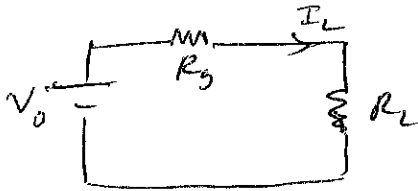THE STEADY STATE ^{LINE/} LOAD CURRENT IS



$$I_L = \frac{V_0}{R_S + R_L} = \frac{3}{2} \left(\frac{V_0}{Z_0} \right) \quad \text{CALL IT } I_0$$

$$= \frac{3}{2} I_0$$

$$I_1^+ = \frac{v_1^+}{Z_0} = \frac{3}{4} \frac{V_0}{Z_0} = \frac{3}{4} I_0$$

$$I_1^- = -\frac{v_1^-}{Z_0} = \frac{3}{8} I_0$$

$$I_2^+ = \frac{v_2^+}{Z_0} = \frac{3}{16} I_0$$

$$I_1^+ + I_1^- = \frac{9}{8} I_0$$

$$I_1^+ + I_1^- + I_2^+ = \frac{21}{16} I_0$$

