

TRANSMISSION LINES

TRANSMISSION LINES ARE USED TO TRANSMIT ELECTRIC SIGNALS

~~ENERGY~~ FROM ONE POINT TO ANOTHER. FOR EXAMPLE, THE

CONNECTION BETWEEN A TRANSMITTER & AN ANTENNA IS A

TRANSMISSION LINE. THE OTHER EXAMPLES INCLUDE THE

CONNECTION BETWEEN A HYDROELECTRIC GENERATING PLANT &

A SUBSTATION SEVERAL ~~HUNDRED~~ HUNDRED KILOMETERS AWAY, AND THE

CONNECTION BETWEEN THE RECEIVER ANTENNA & THE

TELEVISION SET.

IN BASIC CIRCUIT ANALYSIS METHODS, ^{THE LENGTH OF THE} CONNECTION BETWEEN CIRCUIT ELEMENTS (RESISTORS, INDUCTORS & CAPACITORS) IS MUCH SMALLER THAN THE WAVELENGTH & HENCE, THE PROPAGATION

DELAY (OR EQUIVALENTLY PHASE-SHIFT IN PHASOR ANALYSIS)

CAN BE IGNORED. ^{TYPICALLY,} TRANSMISSION LINES ARE USED TO

CONNECT ~~THE~~ SOURCES AND LOADS THAT ARE SEPARATED

BY DISTANCES ~~THE~~ ON THE ORDER OF A WAVELENGTH OR

LARGER.

~~LET US ASSUME THAT THE INPUT VOLTAGE IS SINUSOIDAL &~~

~~CARRY OUT THE PHASOR ANALYSIS.~~

(2)

TRANSMISSION LINE EQUIVALENT CIRCUIT :

WE DEVELOP A CIRCUIT MODEL THAT IS VALID FOR ANY TRANSMISSION LINE. FOR A COAXIAL TRANSMISSION LINE, THE INNER & OUTER CONDUCTORS HAVE A HIGH CONDUCTIVITY, σ_c


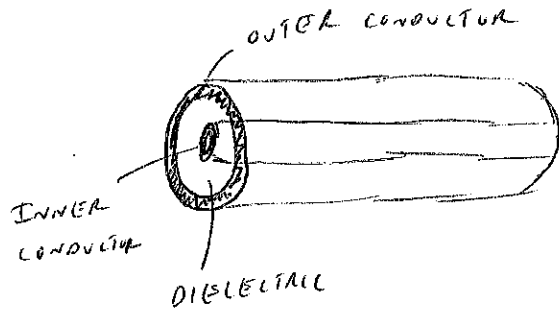


FIG. 1

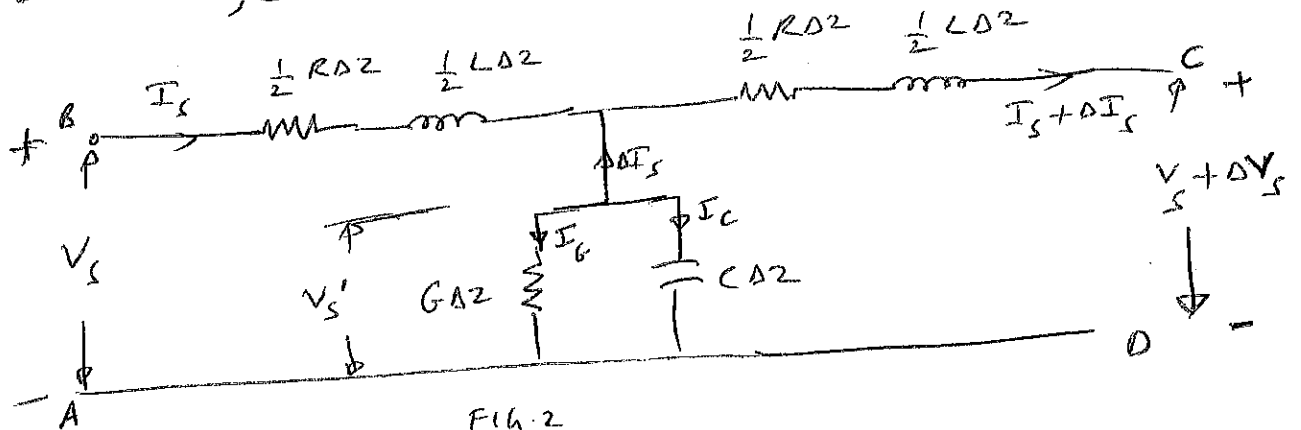INDUCTANCE, L . THE SERIES RESISTANCE R ACCOUNTS FOR



THE CONDUCTIVITY, σ_c ($\because R = \frac{\rho}{\sigma_c A}$). THE SHUNT CONDUCTANCE,

G IS USED TO MODEL THE LEAKAGE CURRENT THROUGH THE DIELECTRIC THAT MAY OCCUR THROUGHOUT THE

TRANSMISSION LINE. THE CAPACITANCE C ACCOUNTS FOR THE

CAPACITOR FORMED DUE TO TWO CONDUCTING CYLINDERS & THE DIELECTRIC BETWEEN THEM. SINCE THE SECTION OF THE TRANSMISSION LINE LOOKS THE SAME FROM EITHER END,

(3)

WE DIVIDE THE SERIES ELEMENTS IN HALF TO PRODUCE A SYMMETRIC NETWORK. NOTE THAT THIS IS NOT THE ONLY POSSIBLE NETWORK — WE COULD AS WELL PLACE HALF THE CONDUCTANCE & HALF THE CAPACITANCE AT EACH END.

LET US ASSUME THAT THE INPUT VOLTAGE IS SINUSOIDAL & CARRY OUT THE PHASOR ANALYSIS.

$$\begin{aligned} V &= \operatorname{Re}\{V_S(z) \cdot e^{j\omega t}\} \\ I &= \operatorname{Re}\{I_S(z) \cdot e^{j\omega t}\} \end{aligned} \quad \rightarrow \textcircled{1}$$

HERE, V_S & I_S ARE PHASORS. A TRANSMISSION LINE IS DIVIDED INTO SECTION OF LENGTH Δz & FIG. 2 SHOWS THE EQUIVALENT CIRCUIT OF THE TRANSMISSION LINE OF LENGTH Δz . HERE, R, L, G & C HAVE VALUES SPECIFIED PER UNIT LENGTH.

(I.E. UNIT OF R IS Ω/m).

APPLYING KVL TO LOOP ABCDA, WE FIND

$$\begin{aligned} V_S - \frac{1}{2}(R+j\omega L)\Delta z I_S - \frac{1}{2}(I_S + \Delta I_S)(R+j\omega L)\Delta z \\ - (V_S + \Delta V_S) = 0 \end{aligned}$$

$$\frac{\Delta V_S}{\Delta z} = -(R+j\omega L)I_S - \frac{1}{2}\Delta I_S(R+j\omega L) \quad \rightarrow \textcircled{2}$$

(4)

As $\Delta z \rightarrow 0$, $\Delta I_s \rightarrow 0$ & THE LAST TERM IN EQ. (2) VANISHES.

$$\lim_{\Delta z \rightarrow 0} \frac{\Delta V_s}{\Delta z} = \frac{dV_s}{dz} = -(R + j\omega L) I_s \rightarrow (3)$$

VOLTAGE ACROSS ~~THE~~ G L C IS

$$V'_s = V_s - I_s \frac{(R + j\omega L) \Delta z}{2}$$

$$\approx V_s \text{ AS } \Delta z \rightarrow 0.$$

$$I_G = V'_s G \Delta z$$

$$I_C = V'_s (j\omega C) \Delta z$$

$$\Delta I_s = -(I_G + I_C) = -V'_s (G + j\omega C) \Delta z$$

$$\approx -V_s (G + j\omega C) \Delta z$$

or

$$\frac{dI_s}{dz} = -(G + j\omega C) V_s \rightarrow (4)$$

TRANSMISSION LINES

(5)

$$V_S$$

$$I_S$$

$$\frac{dI_S}{dz} = -(G + j\omega C) V_S$$

$$\frac{dV_S}{dz} = -(R + j\omega L) I_S$$

FIELDS

$$E_{XS}$$

$$H_{YS}$$

$$\frac{dH_{YS}}{dz} = -(\sigma + j\omega \epsilon) E_{XS}$$

$$\frac{dE_{XS}}{dz} = -j\omega \mu \cdot H_{YS}$$

$$G$$

$$\epsilon$$

$$R + j\omega L$$

$$\sigma$$

$$\epsilon$$

$$j\omega \mu$$

TO ELIMINATE I_S IN (3) + (4), DIFFERENTIATE (3) w.r.t. z ,

LET,

d

LET

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$

SERIES IMPEDANCE

SHUNT ADMITTANCE

(3) $\rightarrow \frac{dV_S}{dz} = -Z I_S \rightarrow (3')$

(4) $\rightarrow \frac{dI_S}{dz} = -Y V_S \rightarrow (4')$

To ELIMINATE I_s IN (3') & (4'), DIFFERENTIATE (3') WITH 2, (6)

$$\frac{d^2 V_s}{dz^2} = -2 \frac{dI_s}{dz} = -2(-Y V_s) \quad \text{from (4')}$$

$$\frac{d^2 V_s}{dz^2} = Y^2 V_s$$

$$Y^2 = YZ = (R + j\omega L)(G + j\omega C)$$

$$V_s = A e^{YZ} + B e^{-YZ} \quad \rightarrow (5)$$

CONSIDER THE SECOND TERM,

$$V_s = B e^{-YZ}$$

$$\text{LET } Y = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$V_s = B \cdot e^{-(\alpha + j\beta)z}$$

$$V = \text{Re} \{ V_s e^{j\omega t} \}$$

$$= B \cdot e^{-\alpha z} \cdot \text{Re} \{ e^{j(\omega t - \beta z)} \}$$

$$V(z) = B e^{-\alpha z} \cos(\omega t - \beta z)$$

FORWARD PROPAGATING WAVE

(7)

THE SPEED v IS

$$v = \frac{\omega}{\beta}$$

FOR THE LOSSLESS CASE, $R=0$, $G=0$.


$$Y = \sqrt{-\omega^2 LC} = \pm j\sqrt{LC}\omega = \alpha + j\beta$$

$$\beta = \pm \omega\sqrt{LC} \rightarrow (6)$$

PICK THE +ve SIGN FOR FORWARD PROPAGATION

$$v = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{LC}} = \frac{1}{\sqrt{LC}}$$
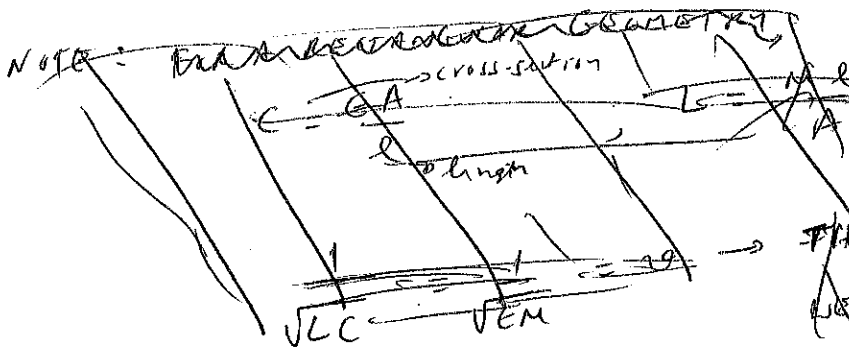
$$\therefore v = \frac{1}{\sqrt{LC}} \rightarrow (7)$$



$$L \rightarrow \mu$$

$$C \rightarrow \epsilon$$

$$\frac{1}{\sqrt{LC}} \rightarrow \frac{1}{\sqrt{\mu\epsilon}}$$

~~THE SAME EQUATION WE HAVE OBTAINED FOR FIELDS.~~

v IS THE SPEED AT WHICH VOLTAGE (OR ELECTRIC FIELD) MOVES. v IS NOT THE SPEED AT WHICH ELECTRONS ARE MOVING.

FROM THE FIRST TERM OF EQ. (5), ~~(7)~~ (8)

$$V_s = A e^{\gamma z} = A e^{(\alpha + j\beta)z}$$

$$V = \operatorname{Re}\{V_s e^{j\omega t}\}$$

$$= A e^{\alpha z} \cos(\omega t + \beta z)$$

BACKWARD PROPAGATING WAVE

NOTE: WHEN $\alpha > 0$, IT IS CALLED THE ATTENUATION

COEFFICIENT - $e^{\alpha z}$ DOES NOT IMPLY THAT IT GROWS

EXPONENTIALLY. THE REASON IS THAT THE WAVE IS PROPAGATING BACKWARDS. IF THE INITIAL FIELD ^{PEAK} IS AT

$z=0$, AT A LATER TIME ~~WAVE~~ ~~MOVES~~ THE ~~FIELD~~ PEAK

WILL BE ~~AT~~ IN THE ~~POSITIVE~~ NEGATIVE z DIRECTION &

HENCE $e^{\alpha z}$ IMPLIES EXPONENTIAL DECAY.

~~HERE~~ FOR A LATER CONVENIENCE, EQ. (5) IS RE-WRITTEN AS

$$V_s = V_0^- e^{\gamma z} + V_0^+ e^{-\gamma z} \rightarrow (5')$$

V_0^+ = B = AMPLITUDE OF THE FORWARD PROP. WAVE

V_0^- = A = " " " BACKWARD " "

HOMWORK: USING (3') & (4'), SHOW THAT (9)

$$\frac{d^2 I_s}{dz^2} = \gamma^2 I_s \rightarrow (8)$$

SO THE SOLUTION OF (8) IS

$$I_s(z) = I_0^- e^{\gamma z} + I_0^+ e^{-\gamma z} \rightarrow (9)$$

CONSIDER THE FORWARD PROPAGATING WAVE

$$V_s(z) = V_0^+ e^{-\gamma z} \rightarrow (10)$$

$$I_s(z) = I_0^+ e^{-\gamma z} \rightarrow (11)$$

~~PROB~~ DIFFERENTIATING (10) & USING (3'), WE FIND

$$\begin{aligned} \frac{dV_s}{dz} &= V_0^+ (-\gamma) e^{-\gamma z} = -\gamma I_s \\ &= -\gamma \cdot I_0^+ e^{-\gamma z} \end{aligned}$$

$$\therefore \frac{V_0^+}{I_0^+} = \frac{\gamma}{Y} ; \quad \text{}$$

$$\gamma^2 = YZ = (R + j\omega L)(G + j\omega C) \quad \text{--- SEE PAGE-6.}$$

THE RATIO OF V_0^+ & I_0^+ IS CALLED THE CHARACTERISTIC

IMPEDANCE, Z_0

$$Z_0 = \frac{V_0^+}{I_0^+} = \frac{\gamma}{Y} = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

(10)

FOR THE LOSSLESS CASE, ($R=G=0$),

$$Z_0 = \sqrt{\frac{L}{C}}$$

~~CHARA~~
NOTE: CHARACTERISTIC IMPEDANCE IS THE ANALOG
OF INTRINSIC IMPEDANCE, η FOR FIELDS.

$$\eta = \frac{E_{x0}^+}{H_{y0}^+} = \sqrt{\frac{\mu}{\epsilon}} \rightarrow \text{PERFECT LOSSLESS DIELECTRIC}$$

BACKWARD PROPAGATING WAVE:

$$V_s(z) = V_0^- e^{yz}$$

$$I_s(z) = I_0^- e^{yz}$$

SHOW THAT,

$$Z_0 = \frac{-V_0^-}{I_0^-} = \sqrt{\frac{Z}{Y}}$$