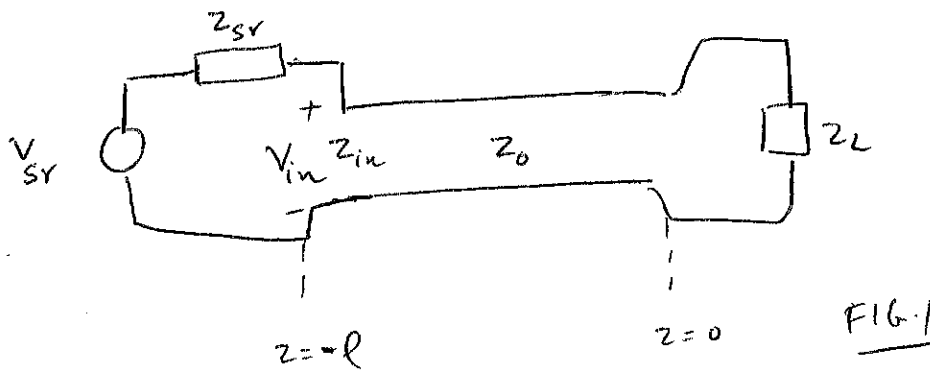


# TRANSMISSION LINES OF FINITE LENGTH



CONSIDER A LOSSLESS TRANSMISSION LINE OF LENGTH  $l$  & IT HAS A CHARACTERISTIC IMPEDANCE  $Z_0$ . THE LOAD IS LOCATED AT  $z=0$  & THE TR. LINE IS LOCATED ALONG THE  $-ve$   $z$  AXIS. THE PHASOR VOLTAGE & CURRENT ARE

$$V_s(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad \rightarrow (1)$$

$$I_s(z) = \frac{V_0^+ e^{-j\beta z} - V_0^- e^{j\beta z}}{Z_0} \quad \rightarrow (2)$$


( $\because$  FOR THE LOSSLESS CASE,  $\alpha=0$ ;  $\gamma = \alpha + j\beta = j\beta$ )

THE WAVE IMPEDANCE IS DEFINED AS

$$Z_w(z) \equiv \frac{V_s(z)}{I_s(z)} = \left( \frac{V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{j\beta z}} \right) Z_0$$

$\hookrightarrow (3)$

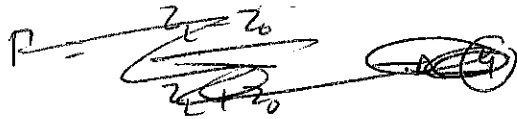NOTE :  $Z_W$  IS DIFFERENT FROM  $Z_0$ . IF THERE IS ONLY A FORWARD PROPAGATING WAVE,  $Z_W = Z_0$ . IF THERE IS ONLY A BACKWARD PROP. WAVE,  $Z_W = -Z_0$ .



$$\Gamma \equiv \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \rightarrow (4)$$

$$\therefore Z_W(z) = Z_0 \frac{Y_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})}{Y_0^+ (e^{-j\beta z} - \Gamma e^{j\beta z})} \rightarrow (5)$$

CONSIDER THE NUMERATOR OF (5),

$$N = Z_0 \left( e^{-j\beta z} + \frac{Z_L - Z_0}{Z_L + Z_0} e^{j\beta z} \right) = \frac{Z_0 \left[ (Z_L + Z_0) e^{-j\beta z} + (Z_L - Z_0) e^{j\beta z} \right]}{Z_L + Z_0}$$

$$= \frac{Z_0}{Z_L + Z_0} Z_L \left( e^{-j\beta z} + e^{j\beta z} \right) + Z_0 \left( e^{j\beta z} - e^{-j\beta z} \right)$$

Euler identities,

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2} ; \sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$N = \frac{2Z_0}{Z_L + Z_0} \left[ Z_L \cos(\beta z) - j Z_0 \sin(\beta z) \right]$$

(3)  
 W/3, THE DENOMINATOR OF (5) IS

$$D = \frac{2}{z+z_0} [z_0 \cos(\beta z) + j z_L \sin(\beta z)]$$

$$\therefore Z_w(z) = z_0 \left[ \frac{z_L \cos(\beta z) - j z_0 \sin(\beta z)}{z_0 \cos(\beta z) + j z_L \sin(\beta z)} \right]$$

AT  $z = -l$ , THE WAVE IMPEDANCE AT THE LINE INPUT,  $Z_{in}$  IS

$$Z_{in} = Z_w(-l) = z_0 \left[ \frac{z_L \cos(\beta l) + j z_0 \sin(\beta l)}{z_0 \cos(\beta l) + j z_L \sin(\beta l)} \right] \rightarrow (6)$$

$$V_s(z=-l) = V_{in}; \quad I_s(z=-l) = I_{in}$$

THE EQUIVALENT CIRCUIT OF FIG. 1 ~~CAN BE WRITTEN AS~~ IS

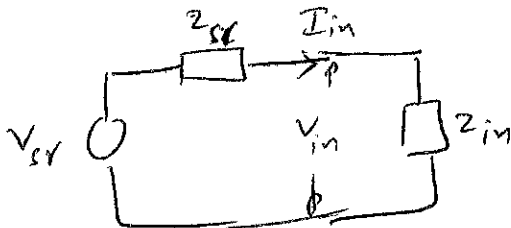


FIG. 2

CASE (i): ~~l is~~ l is HALF-WAVELENGTH (OR <sup>ITS</sup> INTEGER MULTIPLE) ~~HALF-WAVELENGTH~~

$$l = \frac{m\lambda}{2}, \quad m = 1, 2, \dots \rightarrow (7)$$


$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{m\lambda}{2} = m\pi$$

$$\cos(m\pi) = \pm 1; \quad \sin(m\pi) = 0$$

$$Z_{in} = Z_0 \frac{Z_L \cos(m\pi)}{Z_0 \sin(m\pi)} \quad (4)$$

$$\boxed{Z_{in} = Z_L} \quad \text{WHEN } l = m\lambda/2 \quad \rightarrow (8)$$

THE EQUIVALENT CIRCUIT OF FIG. 1 IS

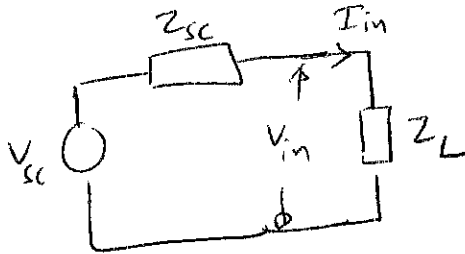

FOR A HALF-WAVE LINE (i.e.  $l = m\lambda/2$ ), ~~THE LINE AND~~ LOAD IMPEDANCE IS PLACED DIRECTLY ACROSS THE INPUT TERMINALS & THE LINE IS COMPLETELY REMOVED.

NOTE: THIS SIMPLIFICATION IS VALID ~~ONLY~~ AT THESE WAVELENGTHS ( $m\lambda$ ) ONLY. IF THE FREQUENCY (EQUIVALENTLY, WAVELENGTH) VARIES CONDITION (7) IS NO LONGER SATISFIED & EQ. (8) IS NOT VALID

CASE (ii):  $l$  IS QUARTER-WAVELENGTH (OR ITS ODD MULTIPLE):

$$l = (2m+1) \frac{\lambda}{4} \quad m = 0, 1, 2, \dots$$

$$\beta = \frac{2\pi}{\lambda}$$


$$\beta l = \frac{2\pi}{\lambda} \cdot (2m+1) \frac{\lambda}{4} = \left( \frac{2m+1}{2} \right) \pi$$

(5)

~~cos((2m+1)π/2) = 0~~

~~cos((2m+1)π/2) = 0~~       $\sin((2m+1)π/2) = 1$

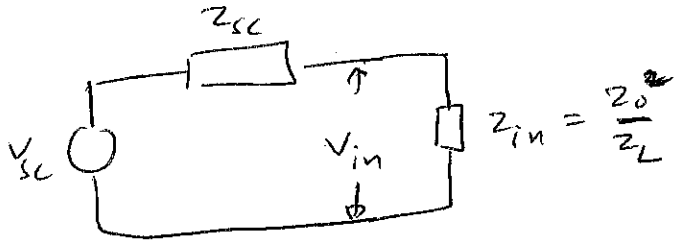$Z_{in} = \frac{Z_0^2}{Z_L}$       WHEN  $l = (2m+1) \frac{\lambda}{4}$       (9)



~~IN THIS CASE, THE IMPEDANCE AT THE LINE INPUT IS~~

~~THE GEOMETRIC MEAN OF~~


IN THIS CASE,  $Z_0$  IS THE GEOMETRIC MEAN OF  $Z_{in}$  &  $Z_L$  i.e.

$Z_0 = \sqrt{Z_{in} Z_L}$       (10)

APPLICATION OF QUARTER-WAVELENGTH LINE: SUPPOSE YOU

NEED TO CONNECT TWO DISSIMILAR TRANSMISSION LINES

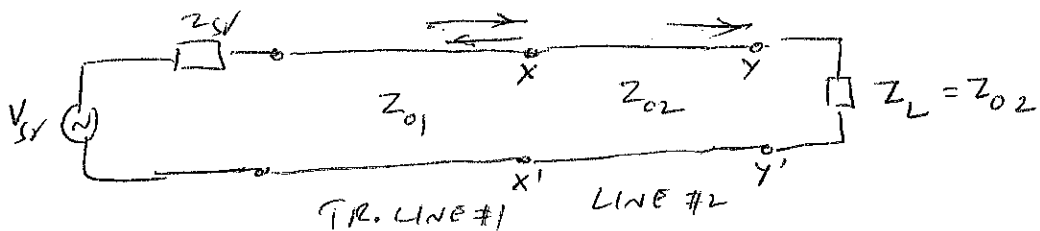OF CHARACTERISTIC IMPEDANCES  $Z_{01}$  &  $Z_{02}$ . IF THEY ARE CONNECTED DIRECTLY AS SHOWN BELOW,




(6)


THERE WOULD BE REFLECTION AT X IF  $Z_{01} \neq Z_{02}$ .

THERE IS NO REFLECTION AT Y SINCE LINE #2 IS MATCHED TO LOAD ( $Z_{02} = Z_L$ ). BECAUSE OF THE REFLECTION AT X, THE POWER TRANSFER TO THE LOAD IS NOT EFFICIENT.

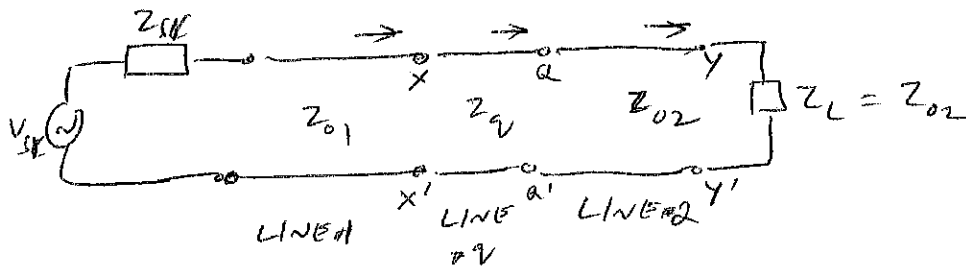TO IMPROVE THE EFFICIENCY, A QUARTER WAVELENGTH TRANSMISSION LINE IS SANDWICHED BETWEEN LINE #1 & LINE #2. THE CHARACTERISTIC IMPEDANCE,  $Z_0$ , OF THIS MIDDLE LINE NEEDS TO BE CALCULATED.



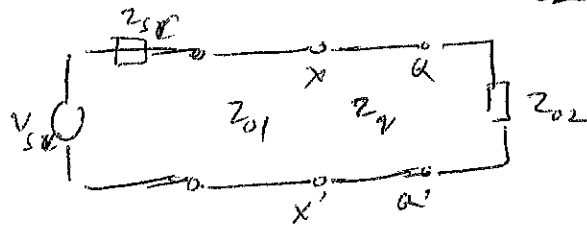
SINCE THE LINE #2 IS MATCHED TO LOAD, THE EFFECTIVE IMPEDANCE BETWEEN Q & Q' IS  $Z_{02}$ .



SINCE LINE 2 IS A  $\lambda/4$  LINE, THE INPUT IMPEDANCE ACROSS X & X' IS (SEE (9))

$$Z_{in} = \frac{Z_0^2}{Z_{02}}$$

(7)

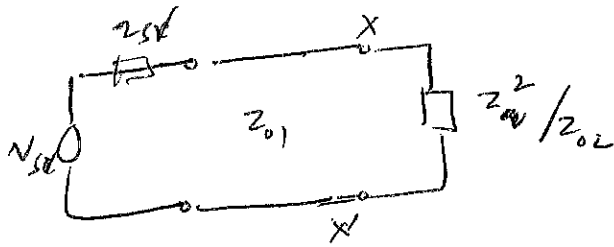


To AVOID REFLECTION AT X (OR X'), THE EFFECTIVE LOAD IMPEDANCE  $Z_{0l}^2 / Z_L$  SHOULD BE EQUAL TO THE CHARACTERISTIC IMPEDANCE  $Z_0$ ,

$$Z_0 = Z_{0l}^2 / Z_L$$

or

$$Z_{0l} = \sqrt{Z_0 Z_L}$$

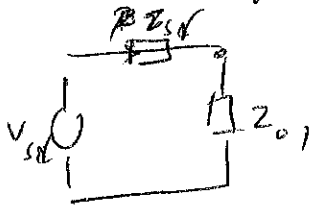

So, THE CHARACTERISTIC IMPEDANCE OF THE ~~MATCH~~ ~~LINE~~ LINE SHOULD BE THE GEOMETRIC MEAN OF  $Z_0$  &  $Z_L$ . THIS TECHNIQUE IS CALLED QUARTER-WAVE MATCHING. AGAIN IT IS LIMITED TO THE FREQUENCY (OR NARROW BAND OF FREQUENCIES) SUCH THAT  $(2M+1)\lambda/4 = l$ .