

VOLTAGE STANDING WAVE RATIO (VSWR)

IN THIS SECTION, WE FOCUS ON LOSSLESS TRANSMISSION LINE.

($R=G=0$). ~~THE~~ IN PRACTICE, TRANSMISSION LINES HAVE LOSSES. HOWEVER, IF THE LENGTH OF THE LINE IS SHORT

AND/OR $R \ll \omega L$ & $G \ll \omega C$, LOSSES CAN BE IGNORED.

IN THIS CASE, ANALYSIS BECOMES MUCH SIMPLER & IN FACT, THE ANALYSIS IS APPLICABLE TO MEASUREMENT OF CHARACTERISTICS OF TRANSMISSION LINES. IN SOME TRANSMISSION LINES, IT IS POSSIBLE TO MEASURE VOLTAGE AS A FUNCTION OF DISTANCE, z . BY

MEASURING THE VOLTAGE MAXIMUM & VOLTAGE MINIMUM, IT IS

POSSIBLE TO CALCULATE REFLECTION COEFFICIENT, Γ , &

CHARACTERISTIC IMPEDANCE, Z_0 , & OTHER IMPORTANT PARAMETERS


OF THE TRANSMISSION ~~CO~~ SYSTEM. TRANSMISSION LINES HAVE

A LONGITUDINAL GAP IN THE OUTER CONDUCTOR ALONG ITS

ENTIRE LENGTH. A VOLTAGE ^{PROBE} ~~PROBE~~ COULD BE INSERTED

BETWEEN THE INNER & OUTER CONDUCTOR THROUGH THE GAP.

(2)

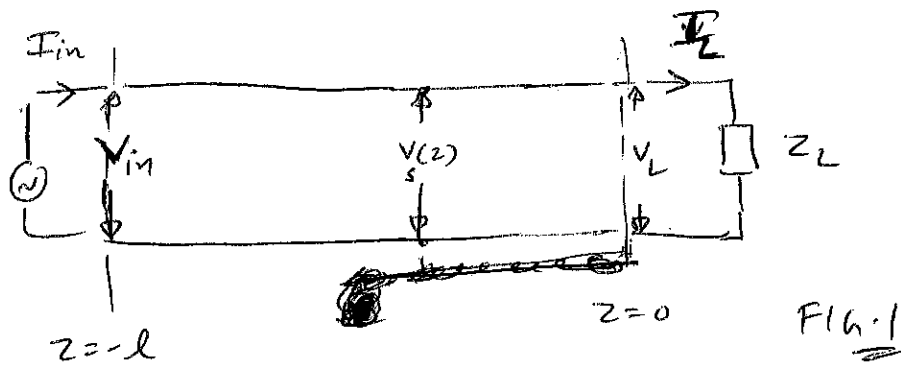

FOR A LOSSLESS ~~TE~~ LINE, THE PHASOR VOLTAGE IS

$$V_s(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \rightarrow (1)$$

$$\left(\because \gamma = \alpha + j\beta z; \alpha = 0, \text{ so } \gamma = j\beta \right)$$

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \rightarrow (2)$$

SO, (1) BECOMES:

$$V_s(z) = V_0^+ \left(e^{-j\beta z} + \Gamma e^{j\beta z} \right) \rightarrow (3)$$

$$\text{LET } \Gamma = |\Gamma| e^{j\phi} \rightarrow (4)$$

MATCHED LOAD: $Z_L = Z_0 \Rightarrow \Gamma = 0$

LOAD IS A SHORT CIRCUIT: $Z_L = 0$, $\Gamma = -1 = 1 \cdot e^{j\pi}$

i.e. $|\Gamma| = 1$ & $\phi = \pi$

LOAD IS AN OPEN CIRCUIT: $Z_L = \infty$; $\Gamma = \frac{Z_L(1 - Z_0/Z_L)}{Z_L(1 + Z_0/Z_L)} = 1$

(3)

$$|\Gamma| = 1 \quad \& \quad \phi = 0$$

Z_L IS REAL & $Z_L < Z_0$:

$$Z_L < Z_0 \Rightarrow \Gamma \text{ IS -VE}$$

NOTE: Z_0 IS REAL ($= \sqrt{\frac{L}{C}}$)

$$\text{LET } \Gamma = -|\Gamma|$$

~~U. LINE~~ FOR LOSSLESS TR. LINE

$$\therefore \phi = \pi$$

Z_L IS REAL & $Z_L > Z_0$:

$$\Gamma \text{ IS +VE.}$$

$$\Gamma = |\Gamma| e^{j0}$$

$$\phi = 0$$

MATCHED LOAD :

$$\Gamma = 0 \Rightarrow$$

$$V_S(z) = V_0^+ e^{-j\beta z}$$

$$I_S(z) = \frac{V_0^+}{Z_0} e^{-j\beta z}$$

$$\frac{V_S(z)}{I_S(z)}$$

= Z_0 AT ANY POINT IN THE TR. LINE.

AT THE ~~END~~ SOURCE, $z = -l$, $V_S(-l) = V_{in} \leftarrow$

$$I_S(-l) = I_{in}$$

(4)

$\frac{V_{in}}{I_{in}} = Z_0 \Rightarrow$ THE EFFECTIVE IMPEDANCE
 "SEEN" AT THE SOURCE TERMINALS
 IS $Z_0 = Z_L$.

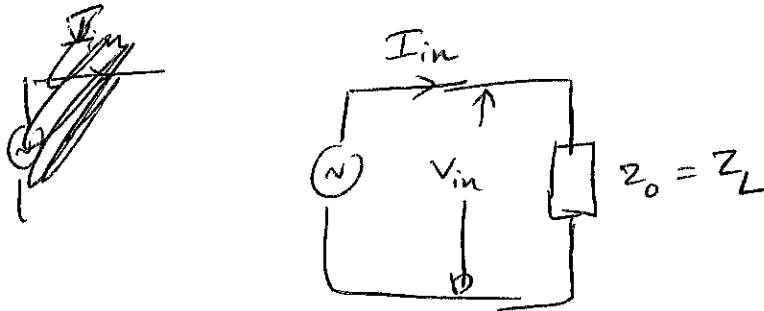


FIG. 2

FIG. 2 IS THE EQUIVALENT CIRCUIT OF THE TRANSMISSION
 SYSTEM SHOWN IN FIG. 1. WHEN THE LOAD IS MATCHED TO
 LINE, THE NET EFFECT IS THAT THE LOAD IS TRANSFERRED
 TO THE SOURCE TERMINAL AS IF ^{THE} TRANSMISSION LINE IS
 ABSENT.

~~LOAD IS A SHORT~~

$(Z_L = 0)$ SHORT CIRCUIT: $\Gamma = -1 = 1 \cdot e^{j\pi}$

FROM (3), $V_S(z) = V_0^+ (e^{-\gamma z} - e^{j\beta z})$

$= -2j V_0^+ \sin(\beta z)$

$= -2 e^{j\pi/2} V_0^+ \sin(\beta z)$


$$V(z,t) = \text{Re} \{ V_s(z) e^{j\omega t} \} \quad (5)$$

ASSUME IT TO
BE REAL.

$$= 2V_0^+ \sin(\beta z) \text{Re} \{ e^{j(\omega t + \pi/2)} \}$$

$$= -2V_0^+ \sin(\beta z) \cos(\omega t + \pi/2)$$
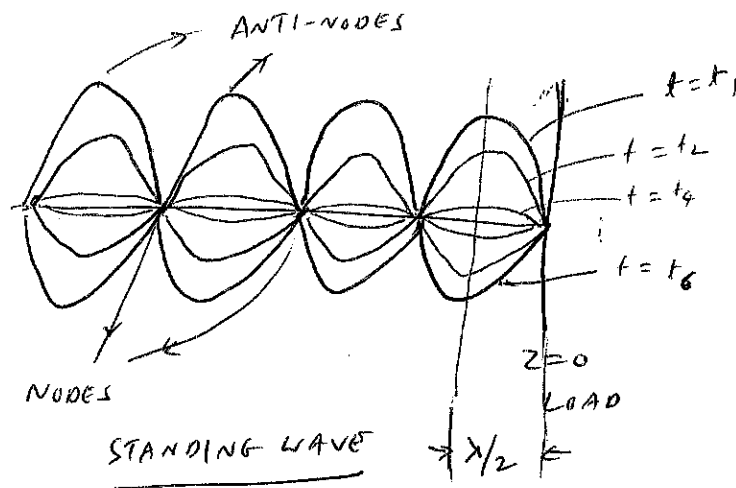
$$V(z,t) = 2V_0^+ \sin(\beta z) \sin(\omega t) \quad \rightarrow (5)$$



AT $z=0$, $\sin(\beta z) = 0$. SO, AT LOAD, THE VOLTAGE IS ZERO ~~AT ALL TIMES~~ AT ANY TIME. IN FACT, IF

$$\beta z = 2m\pi, \quad m = 0, \pm 1, \pm 2, \dots$$

OR

$$z = \frac{2m\pi}{\beta},$$

$V(z,t)$ IS ZERO AT THESE LOCATIONS & THESE ARE

KNOWN AS NODES.

(6)

IF

$$\beta z = 2m\pi \pm \pi/2, \quad m = 0, \pm 1, \pm 2, \dots$$

or

$$z = \frac{2m\pi \pm \pi/2}{\beta}$$

$$\sin(\beta z) = \pm 1.$$

AT THESE LOCATIONS, THE VOLTAGE BECOMES MAXIMUM ($= 2V_0^+$)

AT A CERTAIN TIME, THEN IT STARTS DECREASING & BECOMES

MINIMUM ($-2V_0^+$). THESE POSITIONS ARE ANTI-NODES.

THE DISTANCE BETWEEN A NODE & AN ANTI-NODE IS $\lambda/4$.

THIS CAN BE SHOWN AS FOLLOWS: AT $z=0$, WE HAVE A

NODE. THE NEAREST ANTI-NODE OCCURS AT

$$\beta z = -\pi/2$$

or

$$\frac{2\pi}{\lambda} z = -\pi/2 \Rightarrow z = -\frac{\lambda}{4} \quad \left(\begin{array}{l} \text{NOTE:} \\ \text{THE LINE IS} \\ \text{IN -Z DIRECTION} \end{array} \right)$$

HERE, λ IS THE WAVELENGTH OF THE VOLTAGE WAVE,

$$\lambda = \frac{v}{f} \rightarrow \text{frequency}$$

YOU CAN EASILY VERIFY THAT THE DISTANCE BETWEEN

NODES (OR ANTI-NODES) IS $\lambda/2$.

PARTIAL REFLECTION

(7)

FROM EQS. (3) & (4), WE HAVE

$$\begin{aligned} V_s(z) &= V_0^+ \left[e^{-j\beta z} + |\Gamma| e^{j(\beta z + \phi)} \right] \\ &= V_0^+ e^{j\phi/2} \left[e^{-j(\beta z + \phi/2)} + |\Gamma| e^{j(\beta z + \phi/2)} \right] \quad \text{--- (STEP 2)} \\ &= V_0^+ e^{j\phi/2} \left[(|\Gamma| + (1 - |\Gamma|)) e^{-j\theta} + |\Gamma| e^{j\theta} \right] \quad \text{--- (STEP 3)} \\ &= V_0^+ e^{j\phi/2} \left[2|\Gamma| \cos \theta + (1 - |\Gamma|) e^{-j(\beta z + \phi/2)} \right] \quad \text{--- (STEP 4)} \\ &= V_0^+ \left[e^{j\phi/2} 2|\Gamma| \cos \theta + (1 - |\Gamma|) e^{-j\beta z} \right] \quad \text{--- (STEP 5)} \end{aligned}$$

IN STEP 3, THE INCIDENT WAVE IS SPLIT INTO TWO PARTS,

$|\Gamma|$ & $(1 - |\Gamma|)$. THE FRACTION $|\Gamma| V_0^+$ OF THE INCIDENT WAVE

INTERFERES WITH THE REFLECTED WAVE TO FORM A STANDING

WAVE. THE REST OF THE INCIDENT WAVE REMAINS AS A TRAVELLING

~~WAVE~~ WAVE. THIS CAN BE SEEN BY ~~THE~~ CONVERTING

~~IT~~ IT INTO REAL INSTANTANEOUS FORM:

$$\begin{aligned} v(z, t) &= \text{Re}\{V_s(z) e^{j\omega t}\} = \text{Re}\{V_s(z) e^{j\omega t}\} \\ &= V_0^+ \text{Re}\left\{ 2|\Gamma| \cos \theta \cdot e^{j(\omega t + \phi/2)} + (1 - |\Gamma|) e^{j(\omega t - \beta z)} \right\} \\ &= \underbrace{2|\Gamma| V_0^+ \cos(\beta z + \phi/2) \cdot \cos(\omega t + \phi/2)}_{\text{STANDING WAVE}} + \underbrace{V_0^+ (1 - |\Gamma|) \cos(\omega t - \beta z)}_{\text{TRAVELLING WAVE}} \end{aligned}$$

(8)

VOLTAGE MAXIMUM + MINIMUM:

$$V_s(z) = V_0^+ \left[e^{-j\beta z} + |\Gamma| e^{j(\beta z + \phi)} \right]$$

$$= V_0^+ e^{-j\beta z} \left[1 + |\Gamma| e^{j(2\beta z + \phi)} \right] \rightarrow (6)$$

THE MAXIMUM VOLTAGE ~~IS~~ IS OBTAINED WHEN THE FIRST & SECOND TERMS ADD IN PHASE, I.E.

$$2\beta z + \phi = 2m\pi, \quad m = 0, \pm 1, \pm 2, \dots$$

OR

$$z_{\max} = \frac{2m\pi - \phi}{2\beta} \rightarrow (7a)$$

AT THESE LOCATIONS, THE VOLTAGE IS

$$V_s(z) = V_0^+ e^{-j\beta z} (1 + |\Gamma|)$$

$$v(z, t) = \text{Re} \{ V_s(z) e^{j\omega t} \}$$

$$= V_0^+ [1 + |\Gamma|] \cos(\omega t - \beta z) \rightarrow (7)$$

FROM (7), WE SEE THAT THE AMPLITUDE OF THE VOLTAGE WAVE IS $V_0^+ (1 + |\Gamma|)$. THE ^{INSTANTANEOUS} VOLTAGE AT THESE LOCATIONS IS


$V_0^+ (1 + |\Gamma|)$ AT A CERTAIN TIME t_1 ; IT WILL BECOME 0

AT ~~SOME~~ TIME t_2 & BECOMES $-V_0^+ (1 + |\Gamma|)$ AT TIME t_3 .

THE RMS VOLTAGE AT THESE LOCATIONS IS $V_0^+ [1 + |\Gamma|] / \sqrt{2}$.

(a) $z = z_{\max}$

(9)

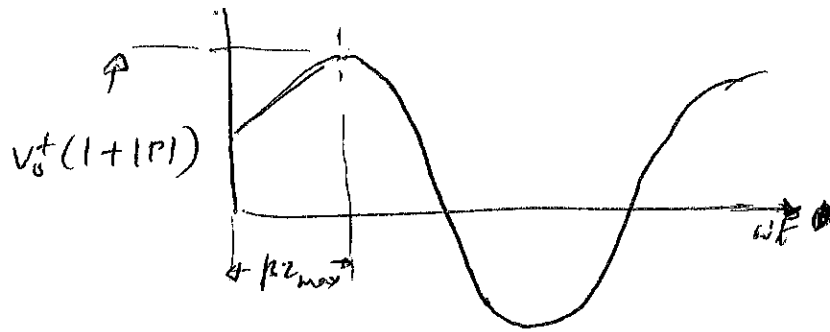

THE MINIMUM VOLTAGE IS OBTAINED WHEN THE FIRST & SECOND TERMS ADD UP DESTRUCTIVELY, i.e.

$$2\beta z + \phi = 2n\pi + \pi \quad n = 0, \pm 1, \pm 2$$

$$e^{j(2\beta z + \phi)} = e^{j(2n\pi + \pi)} = -1$$

$$z_{\min} = \frac{(2n+1)\pi - \phi}{2\beta}$$

AT THESE LOCATIONS, THE VOLTAGE IS

$$V_s(z) = V_0^+ e^{-j\beta z} (1 - |\Gamma|)$$

$$v(z,t) = \text{Re} \{ V_s(z) e^{j\omega t} \}$$

$$= V_0 (1 - |\Gamma|) \cos(\omega t - \beta z) \rightarrow \text{P}$$

FROM (P), WE SEE THAT THE AMPLITUDE (i.e. PEAK) OF THE VOLTAGE WAVE IS $V_0^+ (1 - |\Gamma|)$. THE RMS VOLTAGE IS $V_0^+ (1 - |\Gamma|) / \sqrt{2}$.


(10)

FROM EQ. (6), WE FIND $\Gamma = 1$

$$|V_S| = |V_0^+| |e^{-i\beta z}| \left| (1 + |\Gamma| e^{i(2\beta z + \phi)}) \right|$$

$$|V_S|_{\max} = V_0^+ (1 + |\Gamma|) \rightarrow (9)$$

$$|V_S|_{\min} = V_0^+ (1 - |\Gamma|) \rightarrow (10)$$

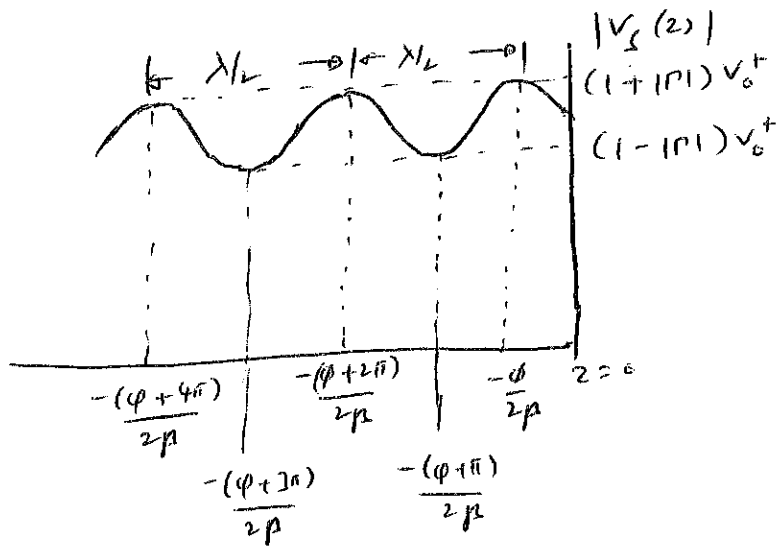

THE FIRST MAXIMUM OCCURS AT

$$z_{\max, 1} = \frac{2m\pi - \phi}{2\beta} \quad \text{when } m=0$$

$$= \frac{-\phi}{2\beta} \rightarrow (11)$$

THE SECOND MAXIMUM OCCURS AT ($m=-1$)

$$z_{\max, 2} = \frac{-2\pi - \phi}{2\beta} \rightarrow (12)$$

NOTE, IF m IS +VE, $z > 0$. HOWEVER, THE LINE IS LOCATED IN THE -VE z AXIS.

DISTANCE BETWEEN SUCCESSIVE VOLTAGE MAXIMA IS

$$|z_{\max,1} - z_{\max,2}| = \frac{2\pi}{2\beta} = \lambda/2 \quad (\because \beta = \frac{2\pi}{\lambda})$$

↳ (13)

(VSWR)

THE VOLTAGE STANDING WAVE RATIO IS DEFINED AS

$$VSWR = S = \frac{|V_s|_{\max}}{|V_s|_{\min}} = \frac{y_0^+ (1 + |\Gamma|)}{y_0^- (1 - |\Gamma|)}$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

↳ (14)

~~FOR A SHORT CIRCUIT, $|\Gamma| = 1$~~

FOR A SHORT CIRCUIT or OPEN CIRCUIT, $|\Gamma| = 1$

& $S = \infty$. FOR A MATCHED LOAD, $\Gamma = 0$ & $S = 1$.

IN PRACTICE, VOLTAGE MAXIMUM & MINIMUM ARE MEASURED

& S IS CALCULATED. ~~USING EQ. (14)~~ USING EQ. (14),

$|\Gamma|$ CAN BE CALCULATED. THE PHASE OF Γ IS

THEN FOUND BY MEASURING THE ^{LOCATION OF THE} FIRST MAXIMUM or MINIMUM (SEE EX. 11)

ONCE Γ IS KNOWN, LOAD IMPEDANCE

CAN BE FOUND IF Z_0 IS ~~KNOWN~~ KNOWN.

EXAMPLE: THE VSWR IN A TRANSMISSION LINE IS 4; THE SPACING BETWEEN SUCCESSIVE VOLTAGE MAXIMA IS 20 CM & THE FIRST MAXIMUM AT A DISTANCE OF 8 CM IN FRONT OF THE LOAD. CALCULATE

(i) REFLECTION COEFFICIENT, Γ (ii) Z_0 , IF THE LOAD IMPEDANCE IS ~~30.68 / 2.926~~ $30.64 / 0.8339$

THE SPACING BETWEEN SUCCESSIVE VOLTAGE MAXIMA = $\frac{\lambda}{2} = 20 \text{ cm}$

$$\therefore \lambda = 40 \text{ cm.}$$

$$\beta = \frac{2\pi}{\lambda} = 15.7 \text{ m}^{-1}$$

THE FIRST MAXIMUM IS LOCATED AT

$$-\frac{\phi}{2\beta} = -8 \text{ cm}$$

$$\therefore \phi = 2 \times 15.7 \times 8 \times 10^{-2} \text{ rad.}$$

$$= 2.512 \text{ rad.}$$

$$\text{VSWR} = S = \frac{1 + |\Gamma|}{1 - |\Gamma|} \Rightarrow S(1 - |\Gamma|) = 1 + |\Gamma|$$

$$S - 1 = |\Gamma|(S + 1)$$

$$\therefore |\Gamma| = \frac{S - 1}{S + 1} = \frac{4 - 1}{4 + 1}$$

$$(i) \quad \therefore |\Gamma| = \frac{s-1}{s+1} = \frac{3}{5} = 0.6$$

$$\Gamma = |\Gamma| e^{i\phi} = 0.6 \angle 2.512$$

(ii)

$$\Gamma = \frac{z_L - z_0}{z_L + z_0} \Rightarrow \Gamma(z_L + z_0) = z_L - z_0$$

$$(\Gamma + 1)z_0 = z_L(1 - \Gamma)$$

$$z_0 = \frac{z_L(1 - \Gamma)}{1 + \Gamma}$$

~~30.64~~

$$\therefore z_0 = \frac{30.64 \angle \overset{0.8219}{\cancel{2.512}} (1 - 0.6 \angle 2.512)}{1 + 0.6 \angle 2.512}$$

$$= 75 \Omega$$