


## WORKED EXAMPLES

EXAMPLE #1. CONSIDER A <sup>LOSSLESS</sup> COAXIAL CABLE OF LENGTH 20 m. THE CHARACTERISTIC IMPEDANCE OF THE LINE IS  $75 \Omega$  & THE SPEED ON THE LINE IS  $2.2 \times 10^8$  m/s. THIS CABLE IS USED TO CONNECT AN ANTENNA & A TV RECEIVER. THE ANTENNA MAY BE REPRESENTED BY ITS THEVENIN EQUIVALENT  $Z = 75 \Omega$  IN SERIES WITH  $V_{SV} = 5$  mV. THE IMPEDANCE OF THE RECEIVER IS  $75 \Omega$ , i.e. IT IS MATCHED TO THE LINE. CALCULATE THE

(i) VOLTAGE AT THE INPUT TO THE LINE & AT THE LOAD

(ii) POWER DELIVERED TO THE INPUT OF THE LINE & TO THE LOAD.

SOLUTION:

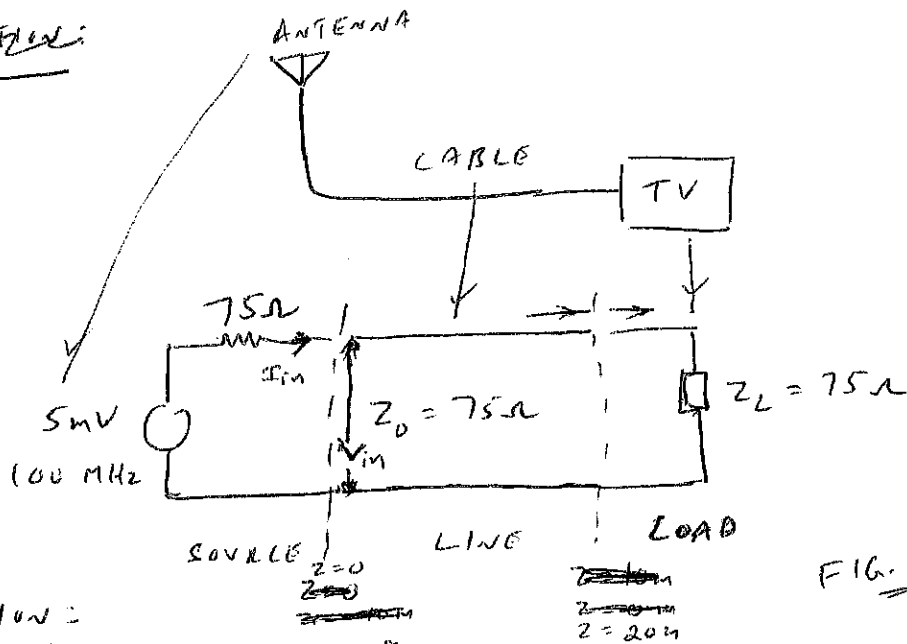

SOLUTION:

$$v = 2.2 \times 10^8 \text{ m/s}$$

$$f = 100 \times 10^6 \text{ Hz}$$

$$\lambda = \frac{v}{f} = \frac{2.2 \times 10^8}{10^8} \text{ m} = 2.2 \text{ m}$$

(2)

PROP. CONSTANT,  $\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{2.2} \text{ rad/m}$

$$= 2.856 \text{ rad/m}$$

$$l = 20 \text{ m}$$

Total phase shift accumulated over a length of 10 m  
 $= \phi = \beta l = 57.1190 \text{ rad.}$

SINCE THE LINE IS MATCHED TO THE LOAD, LOAD CAN BE TRANSFERRED TO THE SOURCE TERMINALS BY REMOVING THE LINE COMPLETELY, i.e. ( $Z_{in} = Z_L$ )

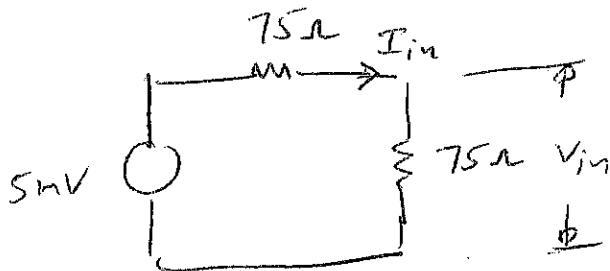


FIG. 2

$$\text{So, } V_{in} = \frac{75}{150} \times 5 \text{ mV} = 2.5 \text{ mV}$$

$$v_{in} = \text{Re}\{V_{in} e^{j\omega t}\} = 2.5 \times 10^{-3} \cos(2\pi 10^8 t) \text{ V}$$

SINCE THERE IS NO REFLECTION, VOLTAGE & CURRENT

EQUATIONS BECOME

$$V_s(z) = V_0^+ e^{-j\beta z} \quad (\because \text{LOSSLESS} \Rightarrow \alpha = 0)$$

$$I_s(z) = \frac{V_0^+}{Z_0} e^{-j\beta z}$$

(3)

As  $z=0$ ,  $V_s(0) = V_0^+ = V_{in}$

$I_s(0) = \frac{V_0^+}{Z_0} = I_{in} = \frac{2.5 \times 10^{-3}}{75} \text{ A} = 3.33 \times 10^{-5} \text{ A}$

At  $z=20 \text{ m}$ ,  $V_s(20 \text{ m}) = V_L = V_{in} e^{-\gamma \beta l} = V_{in} e^{-j\phi}$

$v_L = \text{Re}\{V_L e^{j\omega t}\} = V_{in} \cos(\omega t - \phi)$   
 $= 2.5 \times 10^{-3} \cos(2\pi \cdot 10^8 t - 57.1190)$

$I_s(10 \text{ m}) = I_L = I_{in} e^{-j\phi}$

~~$i_L$~~   $i_L = \text{Re}\{I_L e^{j\omega t}\}$   
 $= I_{in} \cos(\omega t - \phi)$   
 $= 3.33 \times 10^{-5} \cos(2\pi \cdot 10^8 t - 57.1190) \text{ A}$

POWER DELIVERED TO THE INPUT OF LINE =  $P_{in} = \frac{1}{2} \text{Re}\{V_{in} I_{in}^*\}$   
 $= \frac{1}{2} \text{Re}\{2.5 \times 10^{-3} \times 3.33 \times 10^{-5}\}$   
 ~~$= 8.33 \times 10^{-8} \text{ W}$~~   
 $4.16 \times 10^{-8} \text{ W}$

ALTERNATIVELY, FROM FIG. 2, THE POWER DELIVERED TO 75Ω RESISTOR IS,  
 $P_{in} = \frac{|V_{in}|^2}{2R_0} = \frac{(2.5 \times 10^{-3})^2}{2 \times 75} = 4.16 \times 10^{-8} \text{ W}$   
 $R_0 \rightarrow$  Real part of  $Z_0$


NOTE: ~~YOU CAN~~ TO CALCULATE THE POWER, YOU COULD USE ANY OF THE FOLLOWING FORMULAS:

$$P = \frac{1}{2} \operatorname{Re}\{V I^*\} = \frac{|V|^2}{2 \operatorname{Re}(Z)} = \frac{1}{2} |I|^2 \operatorname{Re}(Z)$$

POWER DELIVERED TO THE LOAD IS ALSO ~~6.16~~  $\times 10^{-4} \text{ W}$  SINCE THERE IS NO LOSS IN THE LINE.

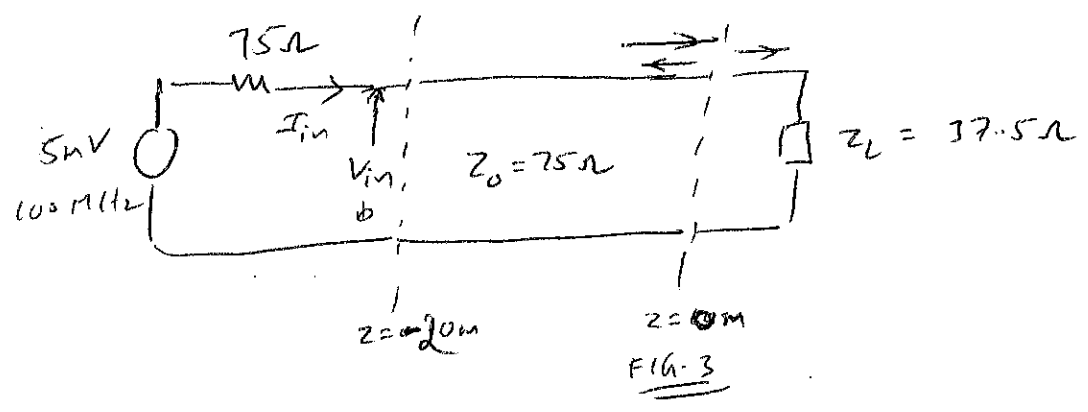EXAMPLE 2: CONNECT A SECOND TV RECEIVER, IDENTICAL TO THE FIRST ONE, ACROSS THE LINE IN PARALLEL WITH THE FIRST ONE. REPEAT EXAMPLE #1.

SOLUTION: THE NET LOAD IMPEDANCE IS  $75 \Omega // 75 \Omega = 37.5 \Omega$



$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{37.5 - 75}{37.5 + 75} = -\frac{1}{3}$$


THE WAVE IMPEDANCE AT THE LINE INPUT (INPUT IMPEDANCE),

$$Z_{in} = Z_0 \left[ \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right] = 75 \left[ \frac{37.5 \cos(57.12) + j 75 \sin(57.12)}{75 \cos(57.12) + j 37.5 \sin(57.12)} \right] \Omega$$

(5)

$$Z_{in} = 58.14 \angle 0.59^\circ \Omega = 48.02 + j 32.76 \Omega$$

THE EQUIVALENT CIRCUIT OF FIG. 3 IS

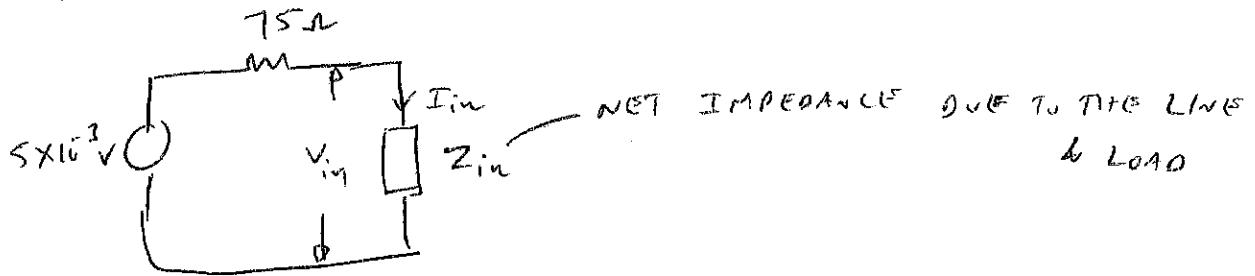

$$I_{in} = \frac{5 \times 10^{-3}}{75 + 48.02 + j 32.76} \text{ A}$$

$$= 2.92 \times 10^{-5} \angle -0.26^\circ \text{ A}$$

$$V_{in} = I_{in} Z_{in} = 2.28 \times 10^{-3} \angle 0.34^\circ \text{ V}$$

POWER DELIVERED TO THE LINE IS

$$P_{in} = \frac{1}{2} |I_{in}|^2 \text{Re}\{Z_{in}\} = \frac{1}{2} (3.92 \times 10^{-5})^2 \times 48.02 \text{ W}$$

$$= 3.7 \times 10^{-8} \text{ W}$$

THE POWER DELIVERED TO THE NET LOAD OF TWO RECEIVERS

IN PARALLEL ( $Z_L = 37.5 \Omega$ ) IS ALSO  $3.7 \times 10^{-8} \text{ W}$  ( $\because$  LOSSLESS

TR. LINE)

SINCE THERE ARE TWO RECEIVERS IN PARALLEL, THE POWER DELIVERED TO EACH RECEIVER IS  $3.7 \times 10^{-8} / 2 \text{ W} = 1.85 \times 10^{-8} \text{ W}$ .

IN EXAMPLE #1, THE POWER DELIVERED TO THE LOAD IS  $4.16 \times 10^{-8} \text{ W}$ .

IN EXAMPLE #2, SINCE THERE ARE TWO RECEIVERS, WE MAY EXPECT THAT THE POWER DELIVERED TO EACH RECEIVER IS  $2.08 \times 10^{-8} \text{ W}$ ; BUT THE

(UNDER IDEAL CONDITIONS)

(6)

ACTUAL POWER DELIVERED IS ONLY  $1.85 \times 10^{-8} \text{ W}$  BECAUSE OF THE REFLECTION (I.E. LOAD & LINE ARE NOT MATCHED)

$$V_S(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

AT THE LOAD,  $z=0$ ,

$$\begin{aligned} V_S(z=0) &= V_L = V_0^+ e^0 + V_0^- e^0 = V_0^+ + V_0^- \\ &= V_0^+ (1 + V_0^-/V_0^+) = V_0^+ (1 + \Gamma) \\ &= \frac{2}{3} V_0^+ \end{aligned}$$

AT THE SOURCE,  $z=-l$ ,

$$\begin{aligned} V_S(z=-l) &= V_{in} = V_0^+ e^{j\beta l} + V_0^- e^{-j\beta l} \\ &= V_0^+ [e^{j\beta l} + \Gamma e^{-j\beta l}] \\ &= V_0^+ [1 \angle 57.11^\circ + \frac{1}{3} \angle -57.11^\circ] \\ &= V_0^+ \times 0.912 \angle 0.909^\circ \\ \therefore V_L &= \frac{2}{3} V_0^+ = \frac{2}{3} \times \frac{V_{in}}{0.912 \angle 0.909^\circ} \quad V = 1.66 \times 10^3 \angle -6.568^\circ \text{ V} \end{aligned}$$

NOTE:  $|V_L| = 1.66 \text{ V} < |V_{in}|$ .

EXAMPLE #3: REPEAT EXAMPLE #1 IF THE SECOND RECEIVED IS CONNECTED IN SERIES WITH THE FIRST ONE.

SOLUTION: THE NET LOAD IMPEDANCE IS  $2 \times 75 \Omega = 150 \Omega$

$$\begin{aligned} Z_{in} &= Z_0 \left[ \frac{Z_L \cos(\beta l) + j Z_0 \sin(\beta l)}{Z_0 \cos(\beta l) + j Z_L \sin(\beta l)} \right] \\ &= 75 \left[ \frac{150 \cos(57.12^\circ) + j 75 \sin(57.12^\circ)}{75 \cos(57.12^\circ) + j 150 \sin(57.12^\circ)} \right] \Omega \\ &= 79.12 - j 54.52 \Omega \end{aligned}$$

$$I_{in} = \frac{5 \times 10^{-3}}{75 + 79.92 - j54.52} \text{ A}$$

$$= 3.044 \times 10^{-5} \angle 0.3284$$

POWER DELIVERED TO THE INPUT OF THE LINE IS (= POWER DELIVERED TO THE NET LOAD)

$$P_{in} = \frac{1}{2} |I_{in}|^2 R_r(z_{in})$$

$$= \frac{1}{2} (3.04 \times 10^{-5})^2 \times 79.92 \text{ W}$$

$$= 3.7 \times 10^{-8} \text{ W}$$

POWER DELIVERED TO EACH RECEIVER IS  $1.85 \times 10^{-8} \text{ W}$ .

NOTE: CONNECTING THE SECOND RECEIVER IN PARALLEL OR SERIES LEADS TO LINE-LOAD MISMATCH. IF A QUARTER WAVE TR. LINE IS INTRODUCED BETWEEN THE COAXIAL LINE & THE RECEIVERS, THE POWER TRANSFER CAN BE MAXIMIZED. HOWEVER, THIS IMPEDANCE-MATCHING IS LIMITED TO 100 MHz FREQUENCY OR A NARROW BAND OF FREQUENCIES CENTERED AROUND 100 MHz.

8

EXAMPLE #4. REPEAT EXAMPLE #1 IF THE LOSSLESS CABLE IS REPLACED WITH A LOSSY CABLE WITH  $R = 0.15 \Omega/m$ ,  $G = 12 \text{ mS/m}$ ,  $L = 0.4 \text{ mH/m}$  &  $C = 71 \text{ pF/m}$ . ASSUME THAT THE LOAD IS MATCHED TO THE LINE SO THAT THERE IS NO REFLECTED WAVE.

SOLUTION:

PART

$$f = 100 \times 10^6 \text{ Hz}$$

$$\omega = 2\pi f = 6.28 \times 10^8 \text{ rad/s}$$

$$Z = 0.15 + j 6.28 \times 10^8 \times 0.4 \times 10^{-6} \Omega/m$$

$$Y = 12 \times 10^{-6} + j 6.28 \times 10^8 \times 71 \times 10^{-12} \text{ S/m}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = 75.058 - j 0.0123 \Omega$$

$$\gamma = \sqrt{ZY} = \underbrace{0.0014}_{\alpha} + j \underbrace{3.3484}_{\beta} \text{ m}^{-1}$$

$$\alpha = 0.0014 \text{ Np/m or } 1/m$$

$$\beta = 3.3484 \text{ rad/m or } 1/m$$

$$v = \frac{\omega}{\beta} = 1.87 \times 10^8 \text{ m/s}$$

( or use  $\beta = \frac{2\pi}{\lambda}$  &  $v = \lambda f$  )



(9)


VOLTAGE &amp; CURRENT PHASORS ARE

$$V_s(z) = V_0^+ e^{-(\alpha + j\beta)z}$$

$$I_s(z) = \frac{V_0^+}{Z_0} e^{-(\alpha + j\beta)z}$$

$$V_s(0) = V_0^+ = V_{in}$$

$$I_s(0) = \frac{V_0^+}{Z_0} = I_{in}$$

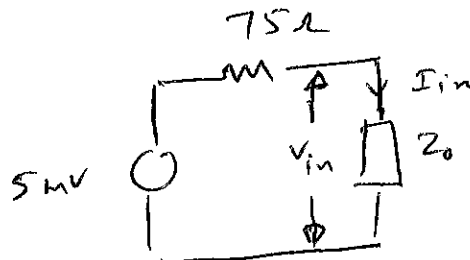

$$V_{in} = \frac{5 \text{ mV} \times Z_0}{Z_0 + 75} = 2.5 \times 10^{-3} - j2.04 \times 10^{-7} \text{ V}$$

$$I_{in} = 3.332 \times 10^{-5} + 2.73 \times 10^{-9} \text{ A}$$

$$P_{in} = \frac{1}{2} |I_{in}|^2 \text{Re}\{Z_0\} = 4.16 \times 10^{-8} \text{ W}$$

$$P_{out} = P_{in} e^{-2\alpha l}$$

POWER  
DISSIPATED  
IN THE LOAD

$$= 4.16 \times 10^{-8} \times e^{-2 \times 0.0014 \times 20}$$

$$= 3.93 \times 10^{-8} \text{ W}$$

$$\text{loss (dB)} = \cancel{10 \log_{10} \frac{P_{in}}{P_{out}}} - 10 \log_{10} \frac{P_{out}}{P_{in}} = 0.25 \text{ dB}$$

(10)

$$V_s(z=20\text{m}) = V_L = \text{LOAD VOLTAGE}$$

$$= V_0^+ \cdot e^{-\gamma z} \quad ; \quad \gamma = \alpha + j\beta$$

$$|V_L| = |V_0^+| e^{-\alpha z}$$

$$= |V_{in}| \cdot e^{-0.0014 \times 20} \quad \checkmark$$

$$= 2.42 \times 10^{-3} \text{ V}$$

$$V_L = |V_L| \cdot e^{-j\phi_L}$$

$$\phi_L = \beta z = 57.11 \text{ rad.}$$

$$\therefore V_L = 2.42 \times 10^{-3} \angle -57.11 \text{ V}$$

EXAMPLE #5

A SINUSOIDAL WAVE ON A TRANSMISSION LINE IS

(11)

SPECIFIED BY VOLTAGE & CURRENT IN PHASOR FORM:

$$V_s(z) = V_0 e^{\alpha z} e^{j\beta z} \quad \& \quad I_s(z) = I_0 e^{\alpha z} e^{j\beta z} e^{j\phi}$$

WHERE  $I_0$  &  $V_0$  ARE BOTH REAL & POSITIVE. (a) IN WHICH

DIRECTION DOES THIS WAVE PROPAGATE & WHY? (b) IT

IS FOUND THAT  $\alpha = 0$ ,  $Z_0 = 50 \Omega$  & THE WAVE VELOCITY IS

$2.5 \times 10^8 \text{ m/s}$ , WITH  $\omega = 10^8 \text{ s}^{-1}$ . EVALUATE  $R$ ,  $G$ ,  $L$ ,  $C$ ,  $\lambda$

&  $\phi$ .

SOLUTION:

(a)  $V_s(z) = V_0 e^{(\alpha + j\beta)z}$

$$v(t) = \text{Re} \{ V_s(z) \cdot e^{j\omega t} \} = e^{\alpha z} \text{Re} \{ e^{j(\omega t + \beta z)} \}$$

$$= \cancel{V_0 e^{\alpha z}} V_0 e^{\alpha z} \cos(\omega t + \beta z) \rightarrow \textcircled{1}$$

$$i(t) = I_0 \text{Re} \{ I_s(z) e^{j\omega t} \}$$

$$= I_0 e^{\alpha z} \cos(\omega t + \beta z + \phi)$$

AT  $t = 0$  &  $z = 0$ ,  $v(t) = V_0$ , ie. THE PEAK OCCURS AT  $z = 0$ .  
~~WHICH IS A PEAK.~~

AT A LATER TIME, SAY AT  $t > 0$ , THE PEAK OCCURS AT

$$\omega t + \beta z = 0 \quad (\because \cos(0) = 1)$$

SINCE,  $\omega$  &  $\beta$  ARE BOTH POSITIVE,  $z$  HAS TO BE

(12)

THEREFORE, THE PEAK MOVES IN THE NEGATIVE  
NEGATIVE: ~~THE PEAK MOVES IN~~

IN  $-z$  DIRECTION & WE SAY THAT THE WAVE PROPAGATES IN  
 $-z$  DIRECTION.

⑤  $\alpha = 0 \Rightarrow R = G = 0;$

$$Z_0 = \sqrt{\frac{L}{C}} = 50 \Omega$$

$$v = \frac{1}{\sqrt{LC}} = 2.5 \times 10^8 \text{ m/s}$$

$$Z_0 v = \frac{1}{C} \Rightarrow C = \frac{1}{2.5 \times 10^8 \times 50} \text{ F}$$
$$= 80 \text{ pF/m}$$

$$\frac{Z_0}{v} = \sqrt{\frac{L}{C}} \cdot \sqrt{LC} = L = \frac{50}{2.5 \times 10^8} \text{ H}$$
$$= 0.2 \text{ mH/m}$$

$$\omega = 2\pi f = 10^9 \text{ s}^{-1}$$

$$\lambda = \frac{v}{f} = \frac{2.5 \times 10^8 \times 2\pi}{10^9} \text{ m} = 15.7 \text{ m}$$

FOR A BACKWARD PROP. WAVE:

$$V_s(z) = V_0^- e^{(\alpha + j\beta)z}$$

$$I_s(z) = -\frac{V_0^-}{Z_0} e^{(\alpha + j\beta)z}$$

$$\therefore V_0^- = V_0; \quad I_0^- = I_0 e^{j\phi} = -\frac{V_0}{Z_0}$$

(13)

$I_0$  is +ve  $\Rightarrow \phi = \pi$ .

$$I_0 = \frac{V_0}{Z_0}$$