

Tutorial 7

Problem 1. A 50-Ω lossless transmission line is terminated by a load impedance $Z_L = 50 - j75\Omega$. If the incident power is 100 mW, find the power dissipated by the load.

Solution: The reflection coefficient is

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 - j75 - 50}{50 - j75 + 50} = 0.36 - j0.48 = 0.6e^{-j0.93}$$

$$P_t = (1 - |\Gamma|^2)P_{in} = (1 - 0.6^2)100 = 64\text{mW}$$

Problem 2. The characteristics of a certain lossless transmission line are $Z_0 = 50\Omega$

and $\gamma = 0 + j0.2\pi\text{m}^{-1}$ at $f = 60\text{MHz}$

(a) Find L and C for the line;

(b) A load $Z_L = 60 + j80\Omega$ is located at $z = 0$. What is the shortest distance from the

load to a point at which $Z_{in} = R_{in} + j0$?

Solution:

(a)

$$Z = R + j\omega L = j\omega L \quad Y = G + j\omega C = j\omega C$$

$$\gamma = \sqrt{ZY} = j\omega\sqrt{LC} \Rightarrow \sqrt{LC} = \frac{\gamma}{j\omega}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{L}{C}}$$

$$L = \sqrt{LC} \cdot \sqrt{\frac{L}{C}} = \frac{\gamma}{j\omega} Z_0 = \frac{0 + j0.2\pi}{j2\pi \times 60 \times 10^6} \times 50 = 8.333 \times 10^{-8} \text{H/m} = 83.33\text{nH/m}$$

$$C = \frac{\sqrt{LC}}{\sqrt{L/C}} = \frac{\gamma}{j\omega Z_0} = \frac{0 + j0.2\pi}{j2\pi \times 60 \times 10^6 \times 50} = 3.333 \times 10^{-11} \text{F/m} = 33.33\text{pF/m}$$

(b)

$$\begin{aligned} Z_{in} &= Z_0 \frac{Z_L + jZ_0 \tan(\beta z)}{Z_0 + jZ_L \tan(\beta z)} = 50 \frac{(60 + j80) + j50 \tan(\beta z)}{50 + j(60 + j80) \tan(\beta z)} \\ &= 50 \frac{60 + j(80 + 50 \tan(\beta z))}{50 - 80 \tan(\beta z) + j60 \tan(\beta z)} \end{aligned}$$

$$\begin{aligned} \text{Im}(Z_{in}) &= 50 \frac{(80 + 50 \tan(\beta z))(50 - 80 \tan(\beta z)) - 60 \times 60 \tan(\beta z)}{(50 - 80 \tan(\beta z))^2 + (60 \tan(\beta z))^2} = 0 \\ \Rightarrow \tan^2(\beta z) + 1.875 \tan(\beta z) - 1 &= 0 \\ \Rightarrow \tan(\beta z) &= \frac{-1.875 \pm \sqrt{1.875^2 + 4}}{2} = 0.4332 \text{ or } -2.3082 \\ \Rightarrow \beta z \pm n\pi &= 0.4088 \text{ or } -1.1620 \\ \Rightarrow z &= 0.65 \pm 5n \text{ or } -1.8494 \pm 5n \\ z_{\min} &= -1.8494 \text{m } (z_{\min} < 0) \end{aligned}$$

Problem 3. A sinusoidal voltage source drives the series combination of an impedance, $Z_g = 50 - j50 \Omega$, and a lossless transmission line of length L , shorted at the load end. The line characteristic impedance is 50Ω , and wavelength λ is measured on the line. (a) Determine, in terms of wavelength, the shortest line length that will result in the voltage source driving a total impedance of 50Ω . (b) Will other line lengths meet the requirements of part (a)? If so, what are they?

Solution:

$$Z_{tot} = Z_g + Z_{in} = 50 - 50j + Z_{in} = 50 \Rightarrow Z_{in} = 50j \Omega$$

$$Z_L = 0, Z_0 = 50 \Omega \Rightarrow$$

$$Z_{in} = Z_0 \frac{Z_L \cos(\beta l) + jZ_0 \sin(\beta l)}{Z_0 \cos(\beta l) + jZ_L \sin(\beta l)} = j50 \tan(\beta l) = j50 \Rightarrow \tan(\beta l) = 1$$

$$\beta l = \frac{2\pi}{\lambda} l = \frac{\pi}{4} + n\pi, n = 0, 1, 2, \dots \Rightarrow l = \frac{\lambda}{8} + n \frac{\lambda}{2}, n = 0, 1, 2, \dots$$

$$l_{\min} = \frac{\lambda}{8}$$

