

Fig. 1 Block diagram of AM modulator - demodulator circuit

# AM Modulator - Demodulator Detailed Schematic

4th-order low-pass Butterworth filter

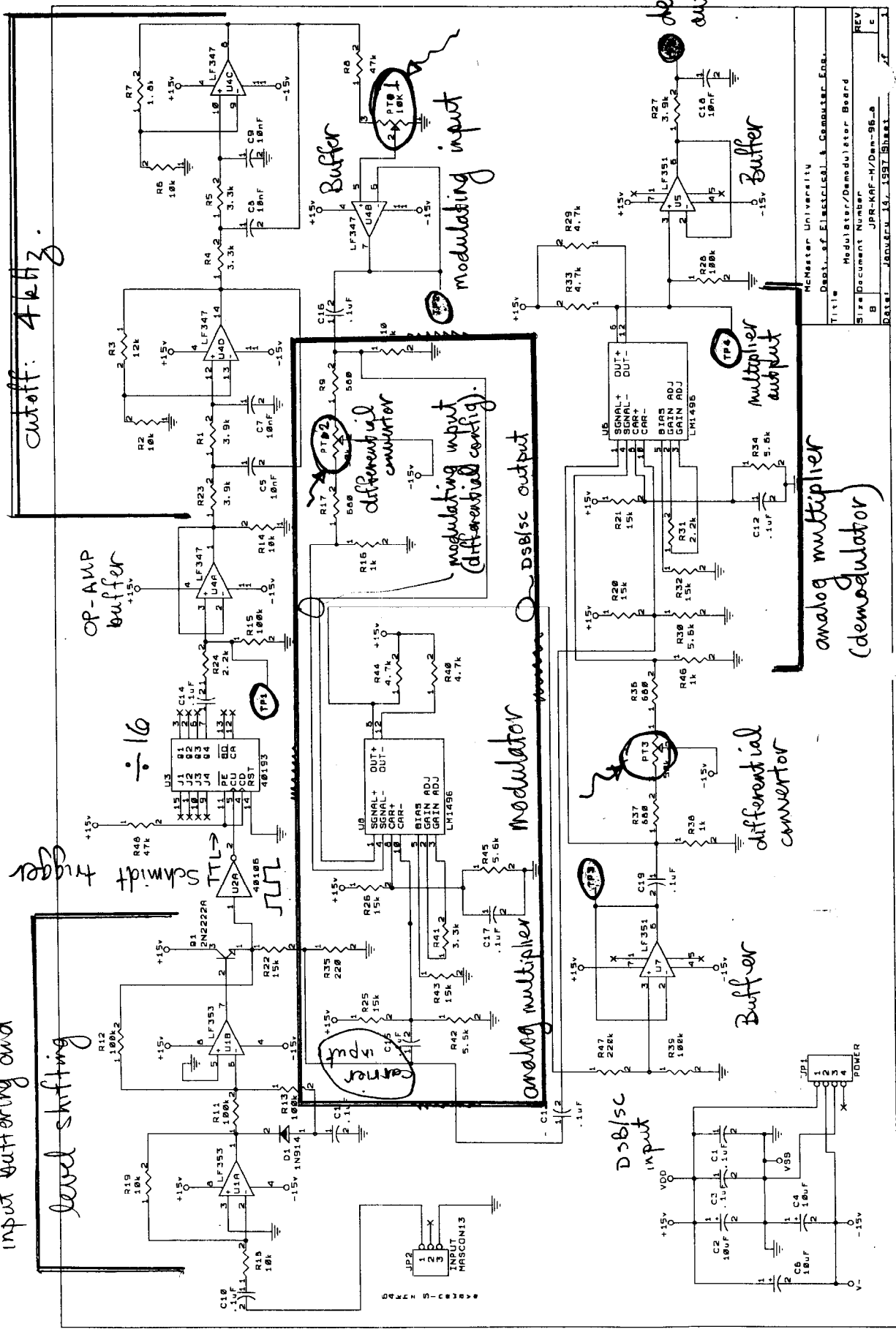


Fig 2