

Logic Design


Chapter 2: Introduction to Logic Circuits




Introduction

- Logic circuits perform operation on digital signal
- Digital signal: signal values are restricted to a few discrete values
- Binary logic circuits: signals can have two values represented by 0 and 1.

Switch networks

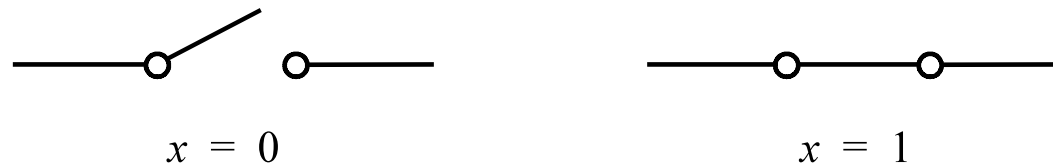


(a) Two states of a switch

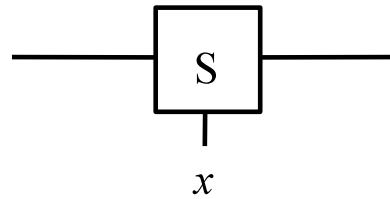


(b) Symbol for a switch

Switch networks

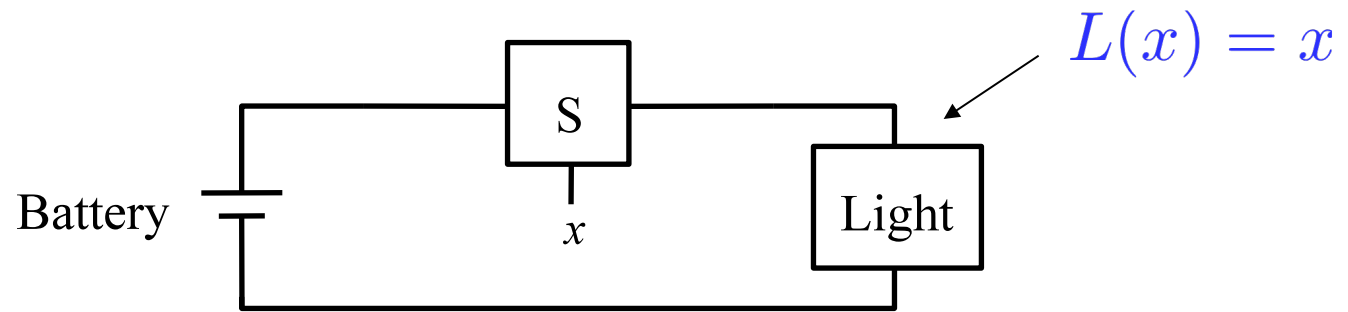


(a) Simple connection to a battery

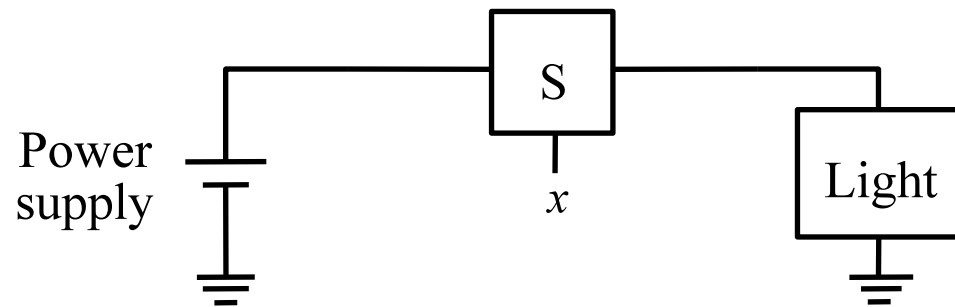


(b) Using a ground connection as the return path

Switch networks

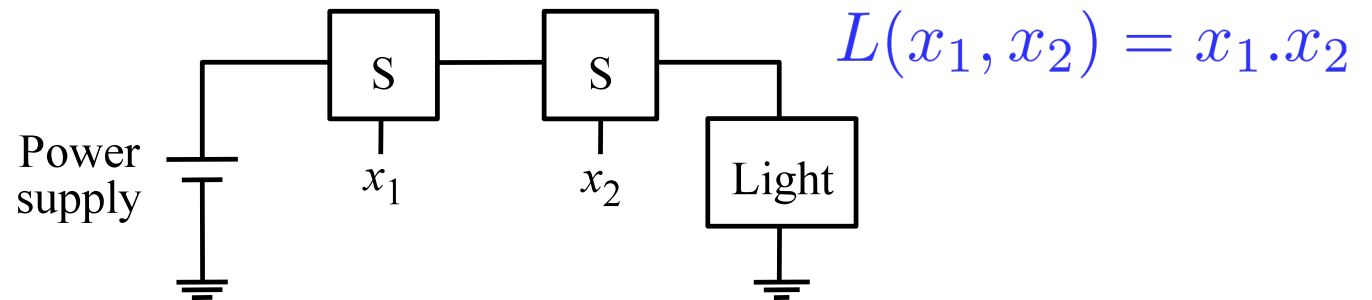


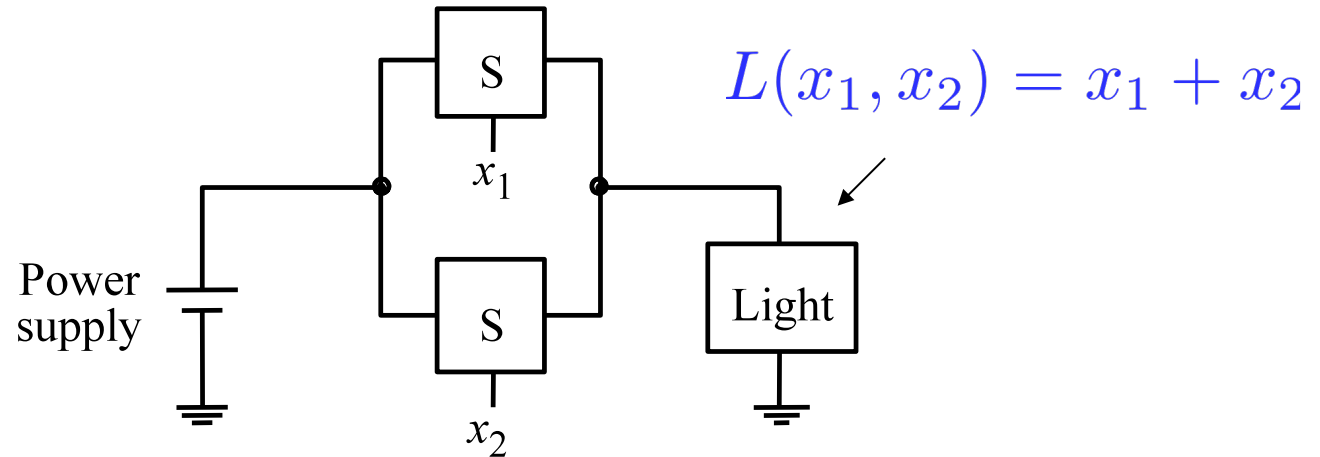(a) The logical AND function (series connection)



(b) The logical OR function (parallel connection)

Switch networks

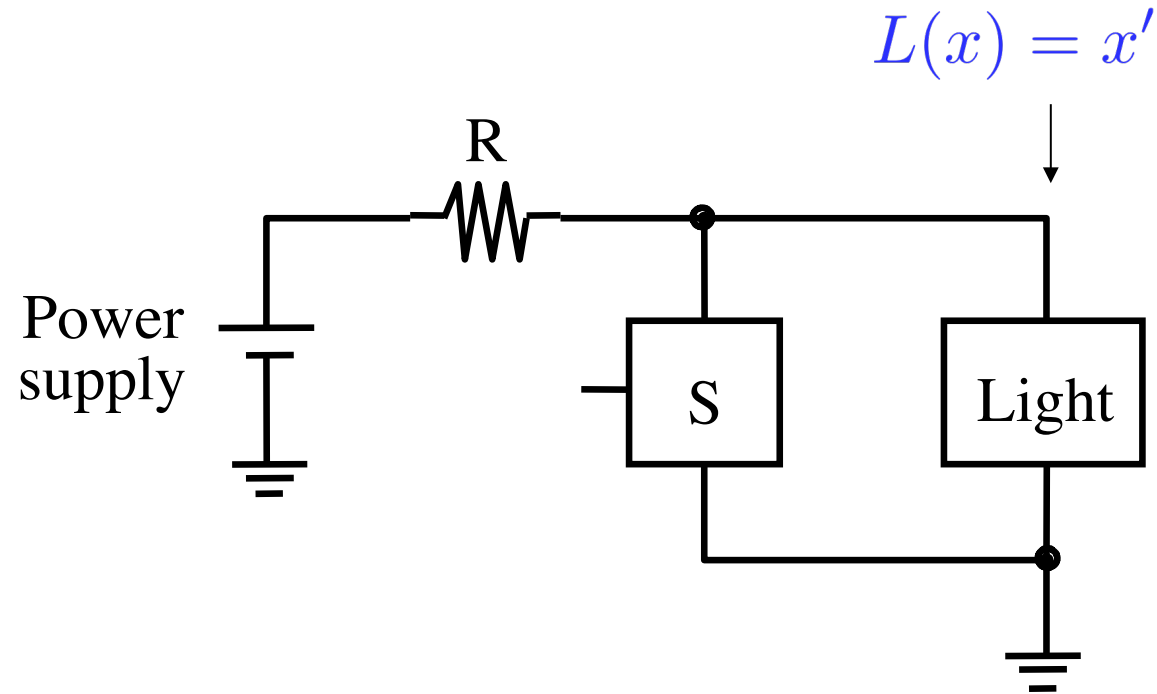

Logic Operations

- The *fundamental* logic operations are:
- AND $F = X.Y$
- OR $F = X + Y$
- NOT $F = X'$ (complement)
- Note:
- X' and \bar{X} are used interchangeably!

Logic Operations

- Don't confuse the AND symbol (\cdot) and OR symbol ($+$) with arithmetic multiplication and addition
- There are some differences:
- Example:
 - Arithmetic addition: $1+1=2$
 - OR operation: $1+1=1$
- Based on the context you should recognize if it is AND/OR or addition/multiplication
- One more thing: sometimes we drop the \cdot symbol
- Example: $a \cdot b$ is the same as ab

Truth table

- The most basic representation of a logic function is a truth table.
- A truth table lists the output of the circuit for every possible input combination.
- There are 2^n rows in a truth table for an n-variable function

Truth table:


X	Y	XY	X + Y	X'
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

Logic Gate

- Binary signals are manipulated using *logic gates*. These are electronic devices whose inputs and outputs are interpreted with only two values, representing logic 0 and logic 1.

Logic Gate

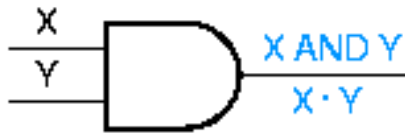
- The bubble on the inverter output denotes “inverting” behavior



X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1




X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

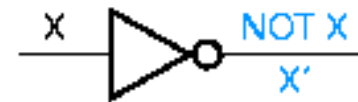

X	NOT X
0	1
1	0

Analysis and Synthesis of a Logic Network

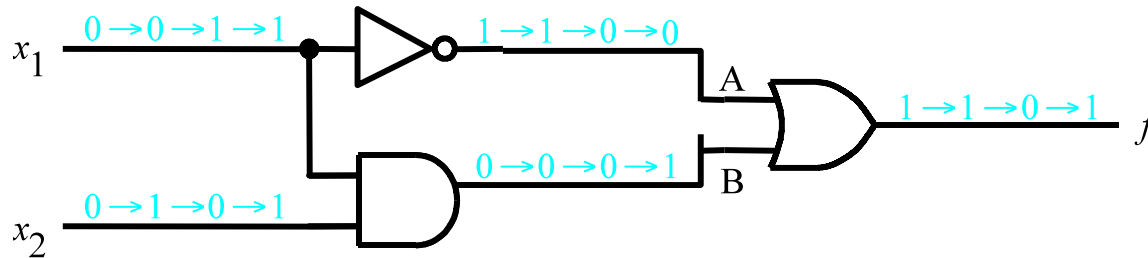
- Combinations of gates form a logic circuit or logic network
- Analysis: For an existing network determine the function performed by the network
- Synthesis: Design a network that implements a desired function




(a) Network that implements $f = \bar{x}_1 + x_1 \cdot x_2$

x_1	x_2	$f(x_1, x_2)$	A	B
0	0	1	1	0
0	1	1	1	0
1	0	0	0	0
1	1	1	0	1

(b) Truth table

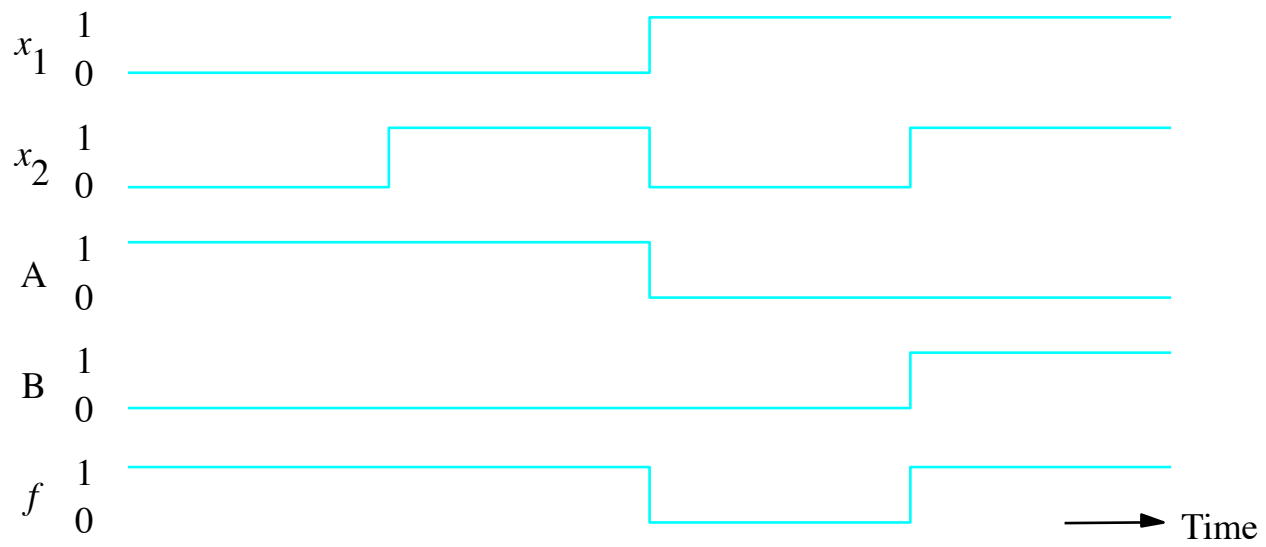

(c) Timing diagram

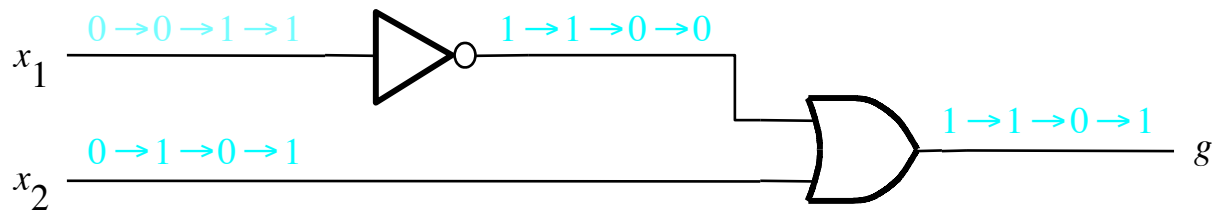

(d) Network that implements $g = \bar{x}_1 + x_2$

Boolean Algebra

- A variety of implementations are available for a logic function
- How to find the best implementation?

Boolean Algebra

- To design logic circuits and describe their operation we use a mathematical tool called *Boolean algebra* (from English mathematician George Boole in 1800's) that operates on two-valued functions.

Axioms of Boolean algebra

- The axioms (or postulates) of a mathematical system are a minimal set of basic definitions that we assume to be true.
- The first three pairs of axioms state the formal definitions of the AND (logical multiplication) and OR (logical addition) operations:
 - (1a) $0 \cdot 0 = 0$ (1b) $1 + 1 = 1$
 - (2a) $1 \cdot 1 = 1$ (2b) $0 + 0 = 0$
 - (3a) $0 \cdot 1 = 1 \cdot 0 = 0$ (3b) $1 + 0 = 0 + 1 = 1$
- The next axioms embody the complement notation:
 - (4a) If $X=0$, then $X'=1$ (4b) If $X=1$, then $X'=0$

Theorems of Boolean algebra

- Theorems are statements, known to be true, that allow us to manipulate algebraic expressions to have simpler analysis or more efficient synthesis of the corresponding circuits.

- Theorems involving a single variable:

$$(5a) X \cdot 0 = 0 \qquad (5b) X + 1 = 1 \qquad (\text{Null elements})$$

$$(6a) X \cdot 1 = X \qquad (6b) X + 0 = X \qquad (\text{Identities})$$

$$(7a) X \cdot X = X \qquad (7b) X + X = X \qquad (\text{Idempotency})$$

$$(8a) X \cdot X' = 0 \qquad (8b) X + X' = 1 \qquad (\text{Complements})$$

$$(9) (X')' = X \qquad (\text{Involution})$$

- These theorems can be proved to be true. Let us prove 6b:

$$[X=0] \quad 0+0=0 \text{ (true, according to 2b)}$$

$$[X=1] \quad 1+0=1 \text{ (true, according to 3b)}$$

Theorems of Boolean algebra

- Theorems involving two or three variables:

$$(10a) X \cdot Y = Y \cdot X \qquad (10b) X + Y = Y + X \qquad \text{(Commutativity)}$$

$$(11a) (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z) \qquad (11b) (X + Y) + Z = X + (Y + Z) \quad \text{(Associativity)}$$

$$(12a) X \cdot Y + X \cdot Z = X \cdot (Y + Z) \qquad (12b) (X + Y) \cdot (X + Z) = X + Y \cdot Z$$

(Distributivity)

$$(13a) X + X \cdot Y = X \qquad (13b) X \cdot (X + Y) = X \qquad \text{(Absorption)}$$

$$(14a) X \cdot Y + X \cdot Y' = X \qquad (14b) (X + Y) \cdot (X + Y') = X \qquad \text{(Combining)}$$

$$(15a) (X_1 \cdot X_2)' = X_1' + X_2'$$

$$(15b) (X_1 + X_2)' = X_1' \cdot X_2'$$

DeMorgan's theorems

$$(16a) X + X' \cdot Y = X + Y \qquad (16b) X \cdot (X' + Y) = X \cdot Y \quad \text{(simplification)}$$

$$(17a) X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z \qquad \text{(Consensus)}$$

$$(17b) (X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$$

Duality

- Theorems were presented in pairs.
- The b version of a theorem is obtained from the a version by swapping “0” and “1”, and “.” and “+”.
- Principle of Duality: Any theorem or identity in Boolean algebra remains true if 0 and 1 are swapped and \cdot and $+$ are swapped throughout.
- Duality is important because it doubles the usefulness of everything about Boolean algebra and manipulation of logic functions.

Consensus theorem

Consensus Theorem:

- $XY + \bar{X}Z + YZ = XY + \bar{X}Z$
 ↑
 redundant

Note: Y and Z are associated with X and \bar{X} , and appear together in the term that is eliminated.

Consensus theorem

- Using duality:

$$(x + y).(y + z).(\bar{x} + z) = (x + y)(\bar{x} + z)$$

Boolean Algebra

$$\mathbf{X + 0 = X}$$

$$\mathbf{X + 1 = 1}$$

$$\mathbf{X + X = X}$$

$$\mathbf{X + X' = 1}$$

$$\mathbf{(X')' = X}$$

$$\mathbf{X + Y = Y + X}$$

$$\mathbf{X + (Y + Z) = (X + Y) + Z}$$

$$\mathbf{X(Y + Z) = XY + XZ}$$

$$\mathbf{X + XY = X}$$

$$\mathbf{X + X'Y = X + Y}$$

$$\mathbf{(X + Y)' = X'Y'}$$

$$\begin{aligned} \mathbf{XY + X'Z + YZ} \\ \mathbf{= XY + X'Z} \end{aligned}$$

$$\mathbf{X \cdot 1 = X}$$

$$\mathbf{X \cdot 0 = 0}$$

$$\mathbf{X \cdot X = X}$$

$$\mathbf{X \cdot X' = 0}$$

$$\mathbf{XY = YX}$$

$$\mathbf{X(YZ) = (XY)Z}$$

$$\mathbf{X + YZ = (X + Y)(X + Z)}$$

$$\mathbf{X(X + Y) = X}$$

$$\mathbf{X(X' + Y) = XY}$$

$$\mathbf{(XY)' = X' + Y'}$$

$$\begin{aligned} \mathbf{(X + Y)(X' + Z)(Y + Z)} \\ \mathbf{= (X + Y)(X' + Z)} \end{aligned}$$

Identity

Idempotent Law

Complement

Involution Law

Commutativity

Associativity

Distributivity

Absorption Law

Simplification

DeMorgan's Law

Consensus Theorem

Boolean Algebra

- Differences between Boolean and ordinary algebra:
- Distributive law of $+$ over $.$ $x+(y.z)=(x+y).(x+z)$ is not valid in ordinary algebra
- Boolean algebra does not have additive or multiplicative inverse so there is no subtraction or division operations


Boolean Algebra

- Boolean algebra is used for manipulating logical functions when designing digital hardware.
- However, today most design is done using Computer-Aided Design (CAD) software that includes schematic capture, logic simplification and simulation.
- Other methods include truth tables, Venn diagrams and Karnaugh Maps.


Venn Diagram

- A graphical tool that can be used for Boolean algebra
- A binary variable s is represented by a contour
- Area within the contour corresponds to $s=1$
- Area outside the contour corresponds to $s=0$
- Two variables are represented by two overlapping circles


Venn Diagram

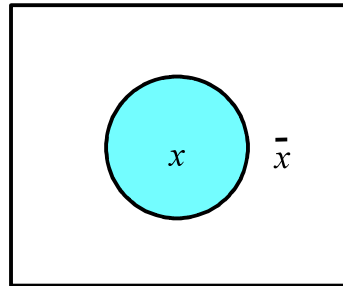


(c) Variable x

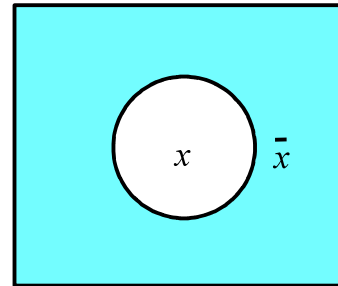


(d) \bar{x}

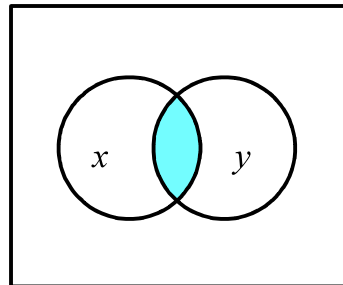


(e) $x \cdot y$

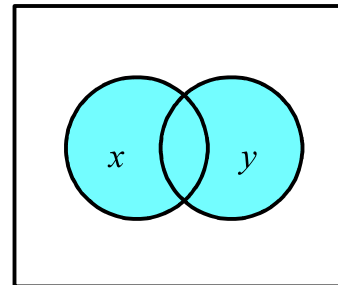

(f) $x + y$

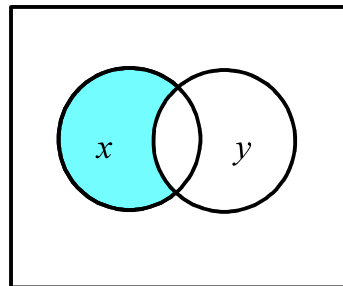


(g) $x \cdot \bar{y}$

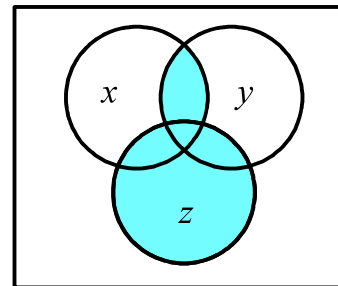

(h) $x \cdot y + z$

Venn Diagram

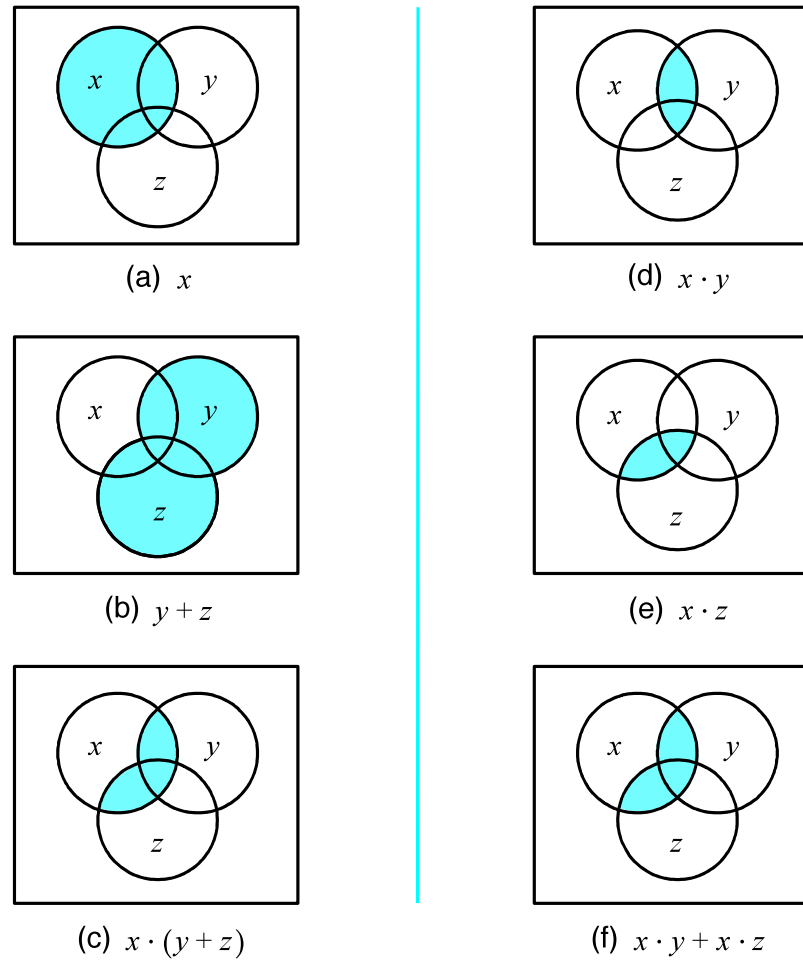

Precedence of operations

- In the absence of parentheses, operations in a logic expression must be performed in the order: NOT, AND, OR
- Example:

$$f = x_1 \cdot x_2 + \bar{x}_1 \bar{x}_2$$

Synthesis using AND, OR and NOT


- One way of designing a logic circuit that implements a truth table is to create a product term that has a value of 1 for each valuation for which the output function has to be 1.
- Then we take the logical sum of these product terms to realize f

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


$$f(x_1, x_2) = \overline{\overline{x_1} x_2} + \overline{x_1} x_2 + x_1 x_2$$

$$f = \overline{x_1} + x_2$$

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

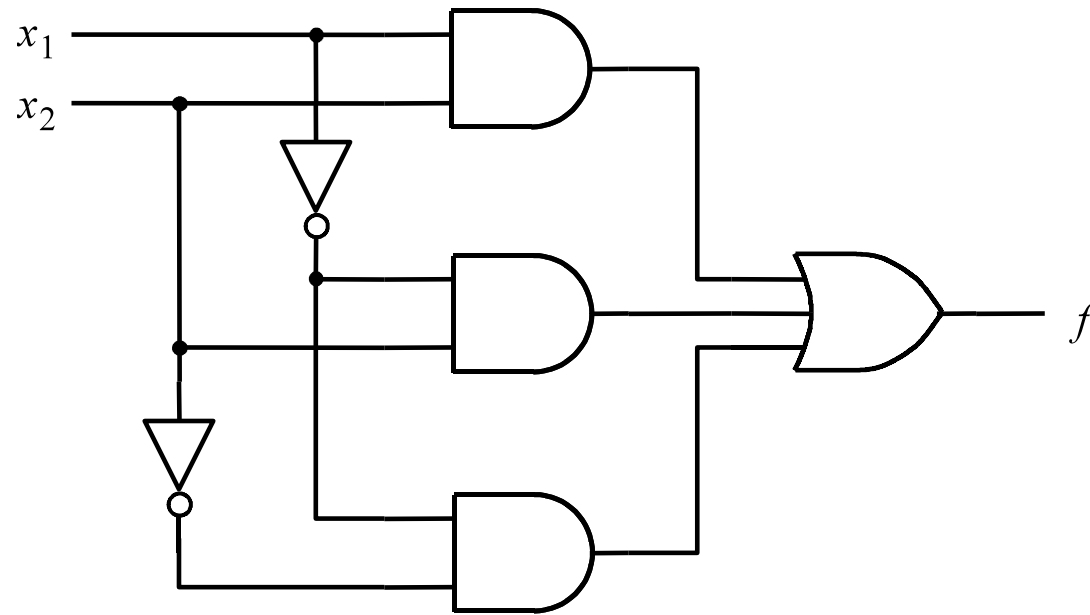

(a) Canonical sum-of-products

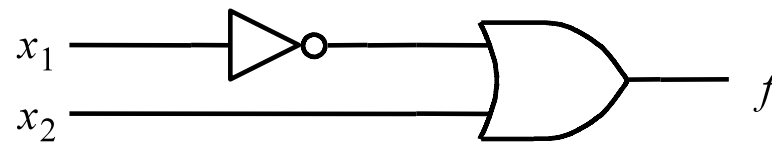

(b) Minimal-cost realization

Minterm, Maxterm

- Minterm
- A product term in which all variables of a function appear exactly once, uncomplemented or complemented.
- Maxterm
- A sum term in which all variables of a function appear exactly once, uncomplemented or complemented.

Minterm, Maxterm

For a Boolean function of n variables, there are 2^n minterms:

$$\mathbf{m_0 \dots m_{2^n - 1}}$$

and 2^n maxterms:

$$\mathbf{M_0 \dots M_{2^n - 1}}$$

Note that: $M_i = \overline{m_i}$

Minterm, Maxterm

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A' B' C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A' B' C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A' B C' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A' B C = m_3$	$A + B' + C' = M_3$
4	1 0 0	$A B' C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$A B' C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$A B C' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$A B C = m_7$	$A' + B' + C' = M_7$

$$M_i = m'_i$$

Canonical Sum of Products Form

- A Boolean function $f(x_1, x_2, x_3)$ can be expressed algebraically as a logical *sum of minterms*:

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Canonical Sum of Products Form

- f can be expressed as sum of product terms (SOP)

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

$$f(x_1, x_2, x_3) = \sum m(1,4,5,6)$$

Canonical Product of Sums Form

- The *complement* of $f(x_1, x_2, x_3)$ can be formed as the logical sum of all minterms not used in $f(x_1, x_2, x_3)$:

$$\bar{f}(x_1, x_2, x_3) = m_0 + m_2 + m_3 + m_7$$

$$f = \overline{m_0 + m_2 + m_3 + m_7}$$

$$f = \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_3} \cdot \overline{m_7}$$

$$f = M_0 \cdot M_2 \cdot M_3 \cdot M_7$$

This is called the product of sum presentation of f

Conversion Between the Canonical Forms

- It is easy to convert from one canonical form to other one, simply use the DeMorgan's theorem.
- Example:

$$F(A,B,C) = \sum(1,4,5,6,7)$$

$$F'(A,B,C) = \sum(0,2,3)$$

$$F(A,B,C) = (m_0 + m_2 + m_3)' = m_0' m_2' m_3' = M_0 M_2 M_3$$

$$F(A,B,C) = \prod(0,2,3)$$

Cost of a Logic Circuit

- Cost of a logic circuit: total number of gates plus total number of inputs to all gates in the circuit
- The canonical SOP and POS implementations described before are not necessarily minimum cost
- We can simplify them to obtain minimum-cost SOP and POS circuits

Reducing Cost

- How can we simplify a logic function?
- There are systematic approaches for doing this (e.g., Karnaugh map) that we will learn later
- The other way is to use theorems and properties of Boolean algebra and do algebraic manipulations.
- Do an example on the board.

Reducing Cost

- The simplified version of SOP is called minimal SOP
- The simplified version of POS is called minimal POS
- We cannot in general predict whether the minimal SOP expression or minimal POS expression will result in the lowest cost.
- It is often useful to check both expressions to see which gives the best result.

Other Logic Operations

- NAND,
- NOR,
- XOR,
- XNOR

NAND

- NAND: a combination of an AND gate followed by an inverter.



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

- Symbol for NAND is \uparrow
- NAND gates have several interesting properties:

$$A \uparrow A = A'$$




$$(A \uparrow B)' = AB$$

$$(A' \uparrow B') = A + B$$

NAND


- These three properties show that a NAND gate with both of its inputs driven by the same signal is equivalent to a NOT gate
- A NAND gate whose output is complemented is equivalent to an AND gate, and a NAND gate with complemented inputs acts as an OR gate.
- Therefore, we can use a NAND gate to implement all three of the *elementary operators* (AND,OR,NOT).
- Therefore, ANY Boolean function can be constructed using only NAND gates.

NAND

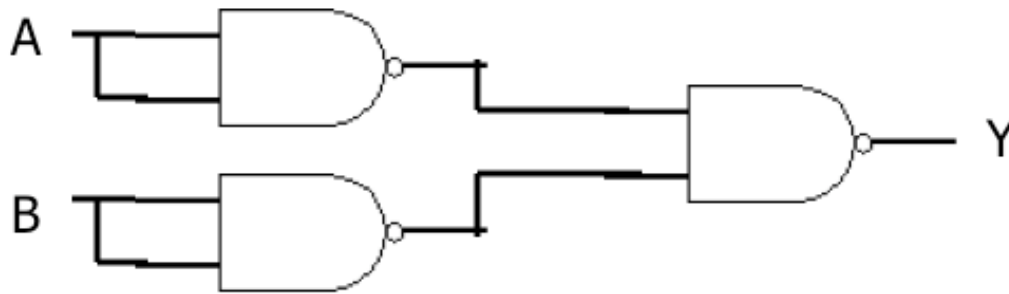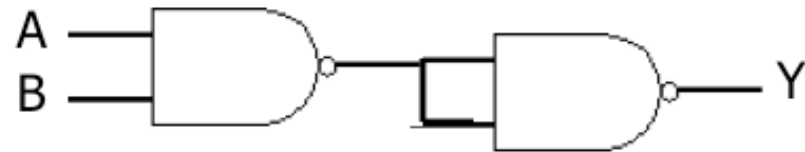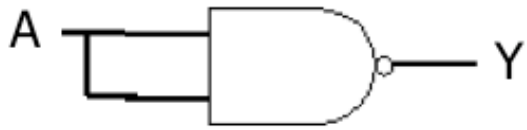

NOR

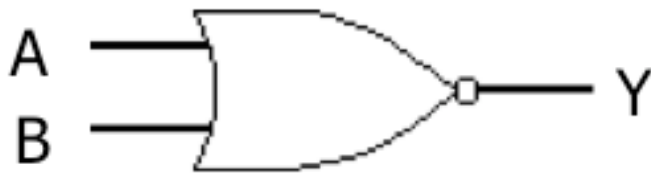- NOR: a combination of an OR gate followed by an inverter.



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

- NOR gates also have several interesting properties:

$$A \downarrow A = A'$$

$$(A \downarrow B)' = A + B$$

$$A' \downarrow B' = AB$$



NOR

- Just like the NAND gate, any logic function can be implemented using just NOR gates.
- Both NAND and NOR gates are very valuable as any design can be realized using either one.
- It is easier to build an IC chip using all NAND or NOR gates than to combine AND, OR, and NOT gates.
- NAND/NOR gates are typically faster at switching and cheaper to produce.


NAND and NOR networks

- NAND and NOR can be implemented by simpler electronic circuits than the AND and OR functions
- Can these gates be used in synthesis of logic circuits?


NAND and NOR networks

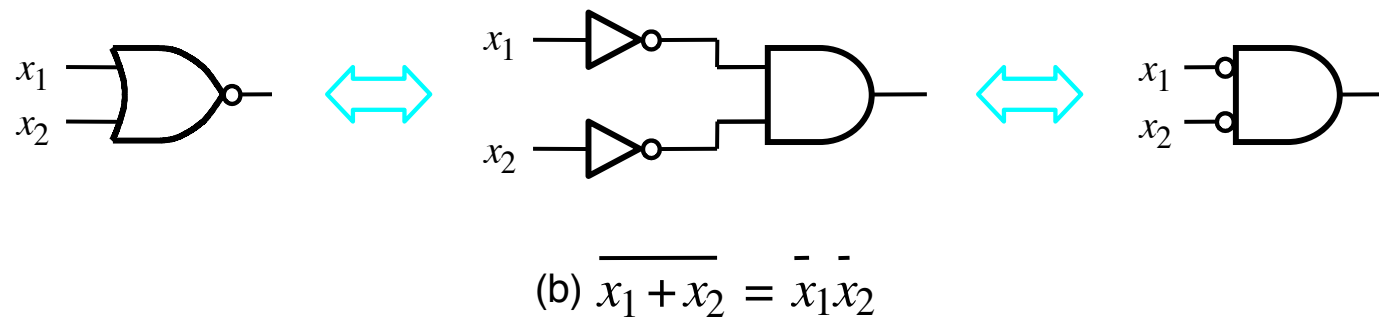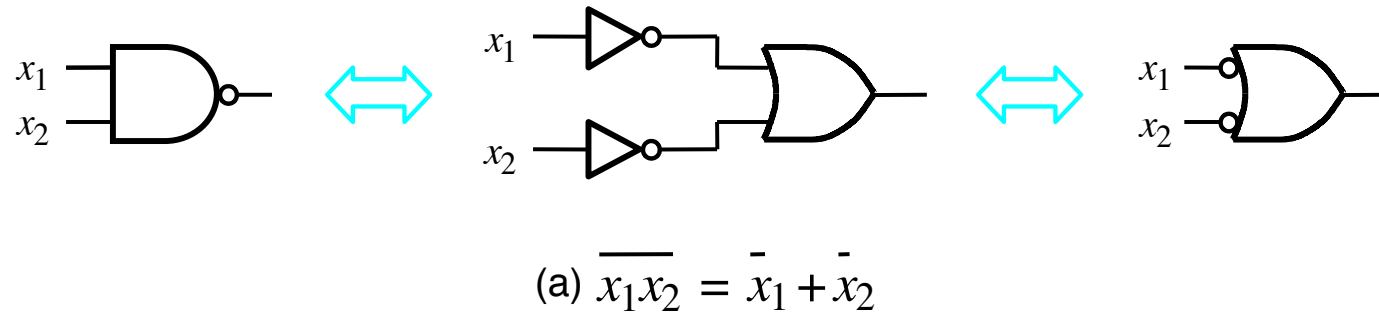

NAND and NOR networks

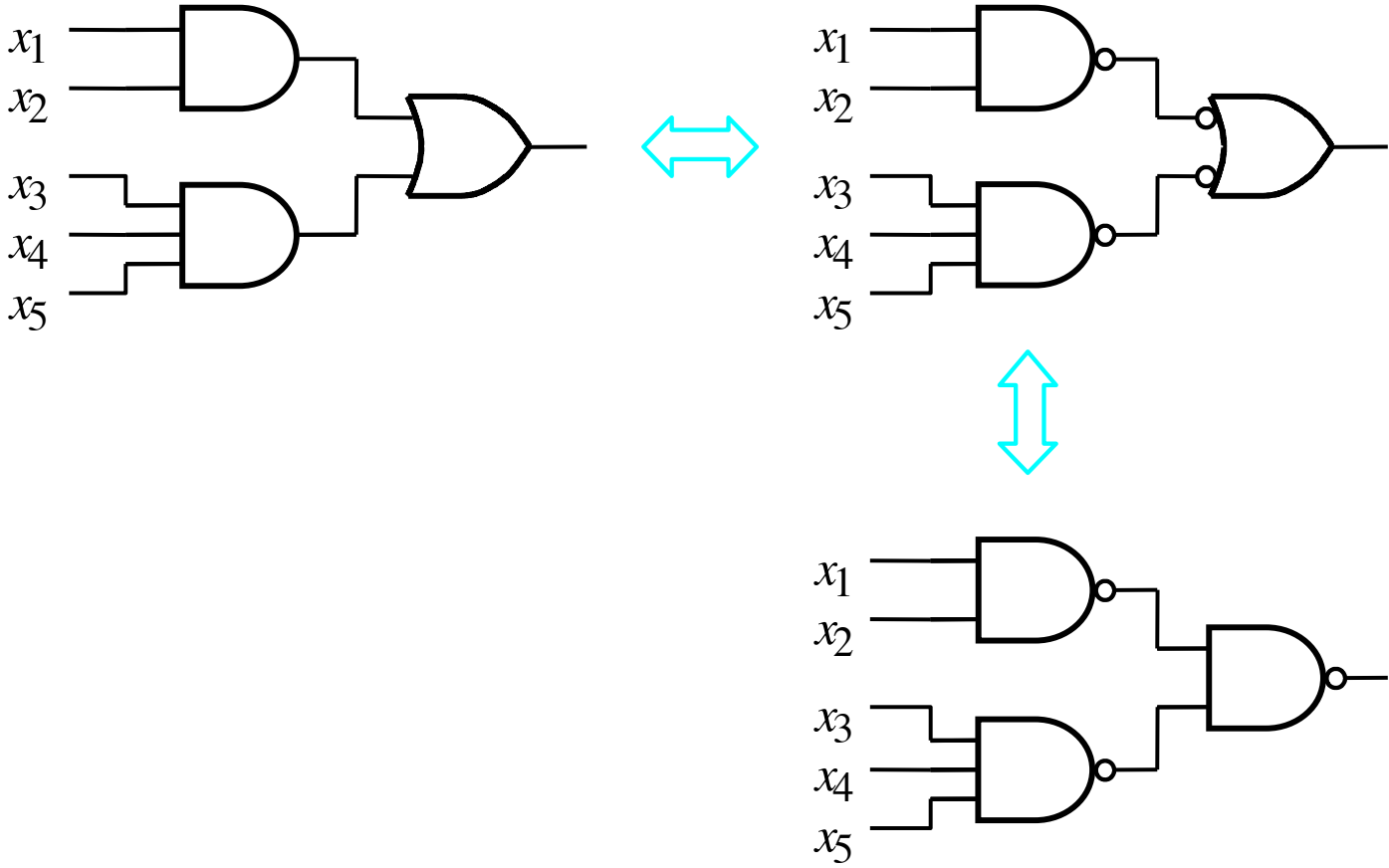

NAND and NOR networks

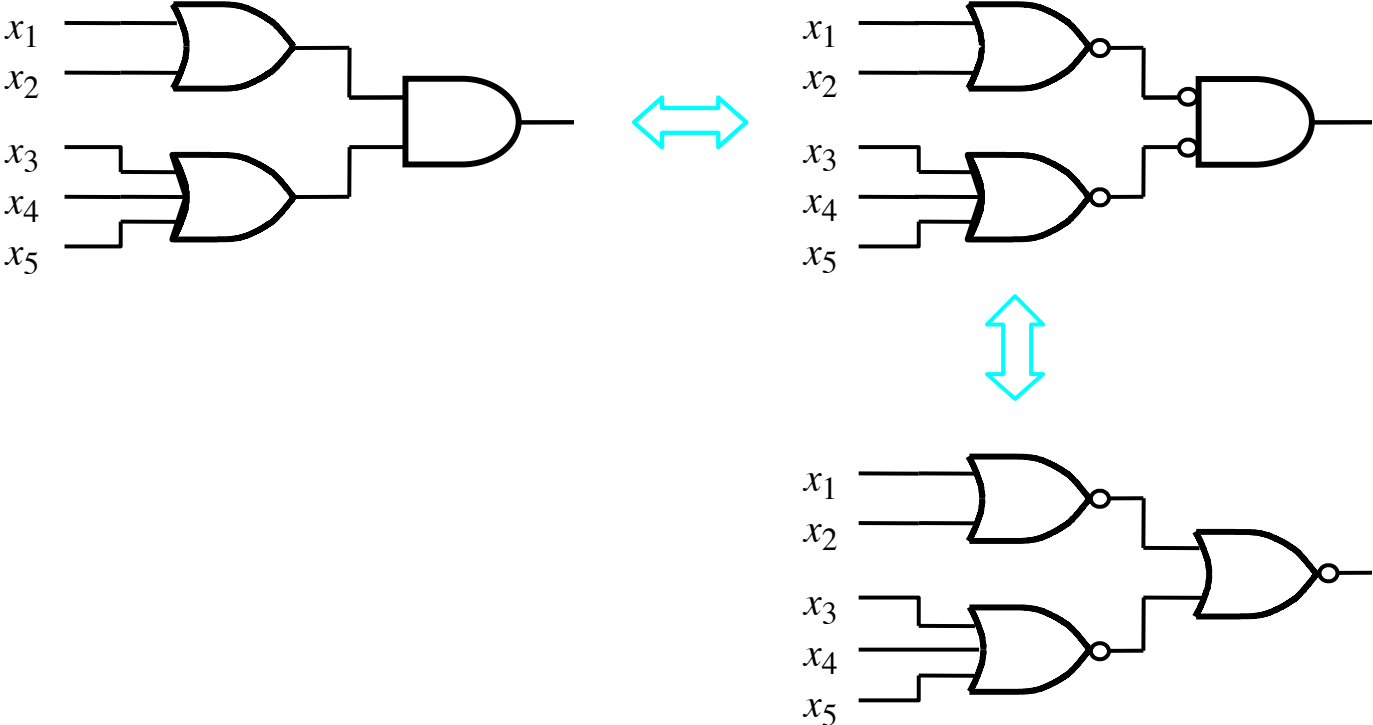


Exclusive OR (XOR)

- The eXclusive OR (XOR) function is an important Boolean function used extensively in logic circuits.
- The XOR function maybe:
 - implemented directly as an electronic circuit (truly a gate) or
 - implemented by interconnecting other gate types (used as a convenient representation)
- The XOR function means:
X OR Y, but NOT BOTH

XOR

- XOR gates assert their output when exactly one of the inputs is asserted, hence the name.
- The symbol for this operation is \oplus

$$Y = A'B + AB'$$

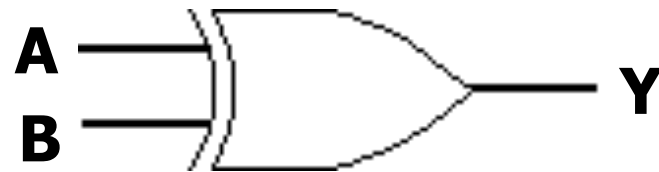

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

- The eXclusive NOR function is the complement of the XOR function
- The symbol for this operation is \odot , i.e. $1 \odot 1 = 1$ and $1 \odot 0 = 0$.




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$Y = A'B' + AB$$


- Why is the XNOR function also known as the *equivalence* function?

XOR Implementations

- A SOP implementation

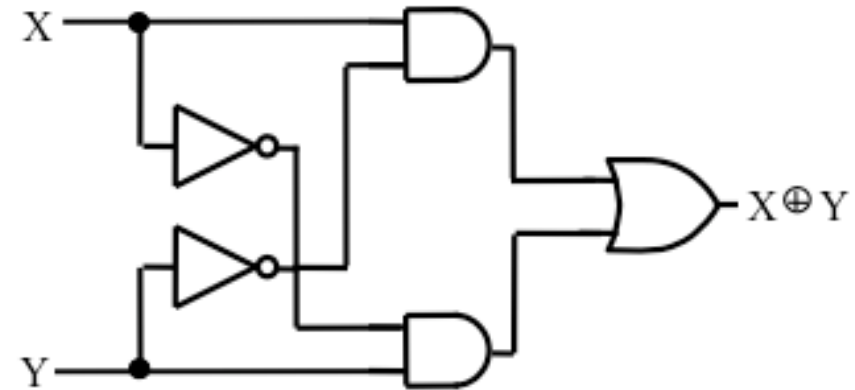

- A NAND implementation

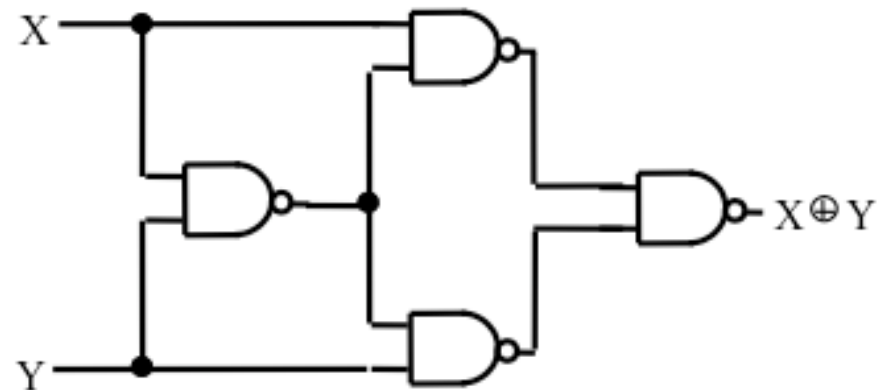

XOR and XNOR

- Uses for the XOR and XNORs gate include:
 - Adders/subtractors/multipliers
 - Counters/incrementers/decrementers
 - Parity generators/checkers

XOR

- XOR identities:

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus Y = Y \oplus X$$

$$X \oplus 1 = X'$$

$$X \oplus X' = 1$$

Gates with more than two inputs

- A gate can be extended to have multiple inputs if the binary operation it represents is commutative and associative.
- AND and OR operations have these two properties
- NAND and NOR are not associative:

$$(A \downarrow B) \downarrow C \neq A \downarrow (B \downarrow C)$$

$$(A \uparrow B) \uparrow C \neq A \uparrow (B \uparrow C)$$

Gates with more than two inputs

- We define multiple input NAND and NOR gates as follows:

$$A \downarrow B \downarrow C = (A + B + C)'$$

$$A \uparrow B \uparrow C = (ABC)'$$

Gates with more than two inputs

- XOR and XNOR are both commutative and associative
- Definition of XOR should be modified for more than two inputs
- For more than 2 inputs, XOR is called an *odd function*: it is equal to 1 if the input variables have an odd number of 1's
- Similarly, for more than 2 inputs, XNOR is called an *even function*: it is equal to 1 if the input variables have an even number of 1's

Learning Objectives

- List the three basic logic operations
- Draw the truth table for the basic logic operations
- Build truth table for an arbitrary number of variables
- Draw schematic for basic logic gates
- Perform analysis on simple logic circuits
- Draw timing diagram for simple logic circuits