

# Logic Design

## Implementation Technology



---

# Outline


- Implementation of logic gates using transistors
- Programmable logic devices
  - Complex Programmable Logic Devices (CPLD)
  - Field Programmable Gate Arrays (FPGA)
- Dynamic operation of logic gates
- Transmission gates

---

# Transistor as a Switch

- Logic circuits are implemented using transistors
- Logic variables (0 and 1) are represented either as levels of current or voltage.
- We will use voltage.
- A threshold is define and any voltage below threshold is one logic value and any voltage above threshold is the other logic value
- Positive logic system: logic zero is represented by low voltage and logic 1 is represented by higher voltage
- Negative logic system: logic zero is represented by high voltage and logic 1 is represented by low voltage

# Transistor as a Switch

 

---


# Transistor as a Switch

- Transistors in logic circuits operates as switches
- Most popular type of transistors: metal oxide semiconductor field effect transistor (MOSFET)
- Two types of MOSFET: n-channel (NMOS) and p-channel (PMOS)
- Terminals: source, drain, gate and substrate
- A MOSFET is controlled by the gate voltage
- NMOS:
  - $V_G$  high  $\rightarrow$  transistor on
  - $V_G$  low  $\rightarrow$  transistor off


# Transistor as a Switch



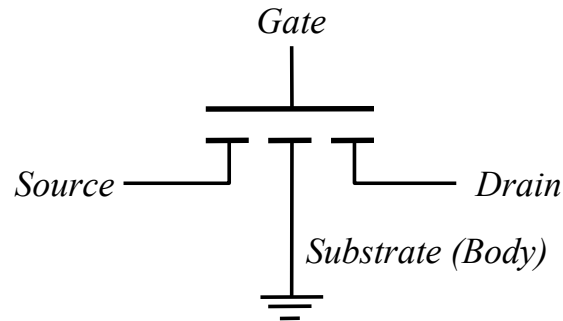(a) A simple switch controlled by the input  $x$



(b) NMOS transistor

 


(c) Simplified symbol for an NMOS transistor


# Transistor as a Switch



 (a) A switch with the opposite behavior of Figure 3.2 a




(b) PMOS transistor

 


(c) Simplified symbol for a PMOS transistor

# Transistor as a Switch

 

(a) NMOS transistor

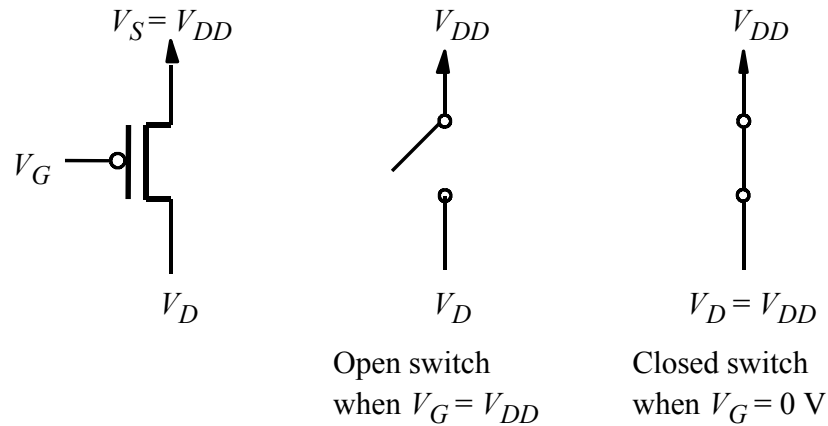


(b) PMOS transistor



 
# NMOS Logic Gates



- Consider  $V_f$  as a function of  $V_x$



(a) Circuit diagram

 


(b) Simplified circuit diagram

  

(c) Graphical symbols


# NMOS Logic Gates

 

(a) Circuit


$x_1$	$x_2$	$f$
0	0	1
0	1	1
1	0	1
1	1	0

(b) Truth table

 

(c) Graphical symbols


# NMOS Logic Gates

 

(a) Circuit


$x_1$	$x_2$	$f$
0	0	1
0	1	0
1	0	0
1	1	0

(b) Truth table

 

(c) Graphical symbols


# NMOS Logic Gates

 

(a) Circuit



$x_1$	$x_2$	$f$
0	0	0
0	1	0
1	0	0
1	1	1

(b) Truth table

 

(c) Graphical symbols


# NMOS Logic Gates

  

(c) Graphical symbols

 
# CMOS Gates

- In NMOS the logic functions are realized by arrangements of NMOS transistors combined with a pull-up device that acts as a resistor.



 
# CMOS Gates

- In CMOS circuits the pull-up device is replaced by a pull-up network (PUN) build using PMOS transistors
- For any valuation of inputs, either PDN pulls  $V_f$  down to Gnd or PUN pulls  $V_f$  up to  $V_{DD}$
- PDN and PUN have equal number of transistors, which are arranged so that the networks are dual



# CMOS Gates

 


(a) Circuit

$x$	$T_1$	$T_2$	$f$
0	on	off	1
1	off	on	0

(b) Truth table and transistor states



# CMOS Gates

 

(a) Circuit

$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

(b) Truth table and transistor states

---


# CMOS Gates

- How to design the transistor circuit for a logic function  $f$ ?
- $f=1$  gives the PUN
- $f=0$  gives the PDN

$$f = (x_1 x_2)' = x_1' + x_2'$$

$$f' = x_1 x_2$$

# CMOS Gates

 

(a) Circuit

$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0


(b) Truth table and transistor states

---

# NOR Gate

$$f = (x_1 + x_2)' = x_1'x_2'$$


$$f' = x_1 + x_2$$

 

(a) Circuit


$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	0
1	0	off	on	on	off	0
1	1	off	off	on	on	0

(b) Truth table and transistor states

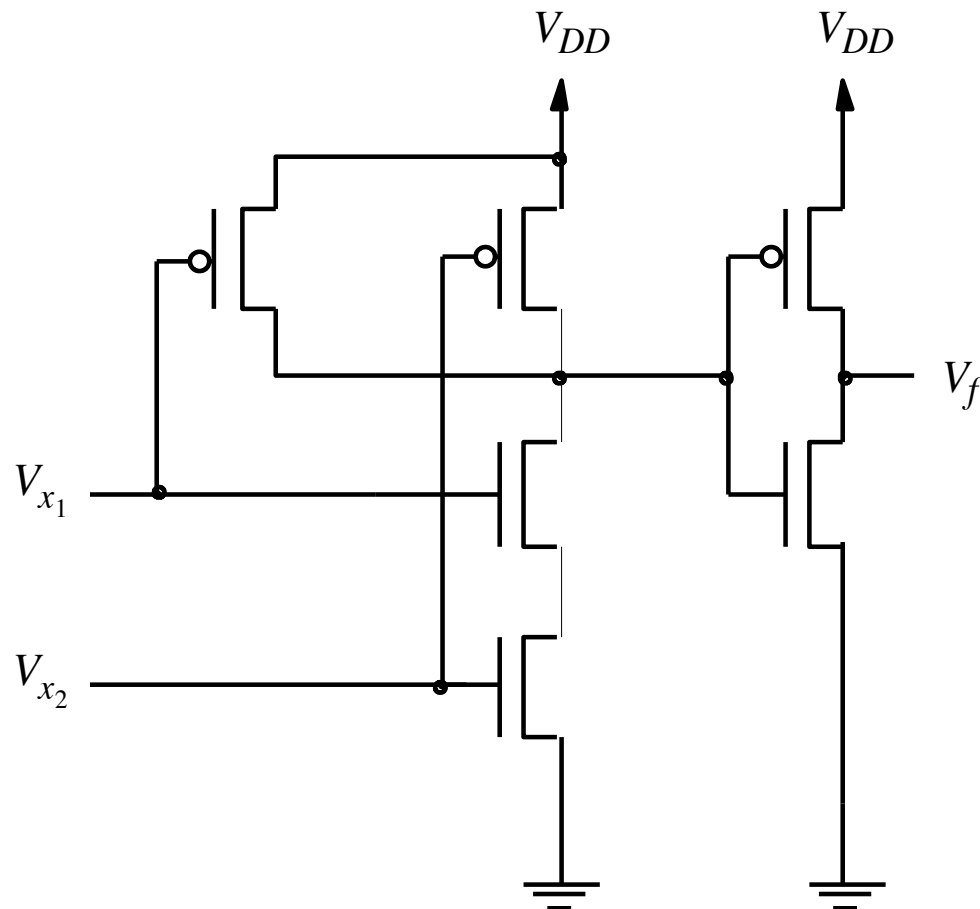


$$f = x'_1 + x'_2x'_3$$
 
$$f' = (x'_1 + x'_2x'_3)' = x_1(x_2 + x_3)$$


 
# Negative Logic System

- Negative logic system: lower voltage represents 1




$V_{x1}$	$V_{x2}$	$V_f$
L	L	H
L	H	H
H	L	H
H	H	L




# Negative Logic System

$x_1$	$x_2$	$f$
0	0	1
0	1	1
1	0	1
1	1	0

 

(a) Positive logic truth table and gate symbol


$x_1$	$x_2$	$f$
1	1	0
1	0	0
0	1	0
0	0	1

 


(b) Negative logic truth table and gate symbol
 
# Standard Chips

- An approach used widely until mid-1980s was to connect chips each containing only a few logic gates
- 7400 series: chips with different logic gates



(a) Dual-inline package

 

(b) Structure of 7404 chip

---

# Standard Chips

- For each specific 7400 series chip several variants are build with different technologies
- 74LS00: build with transistor-transistor logic (TTL)
- 74HC00: build using CMOS technology

# Standard Chips


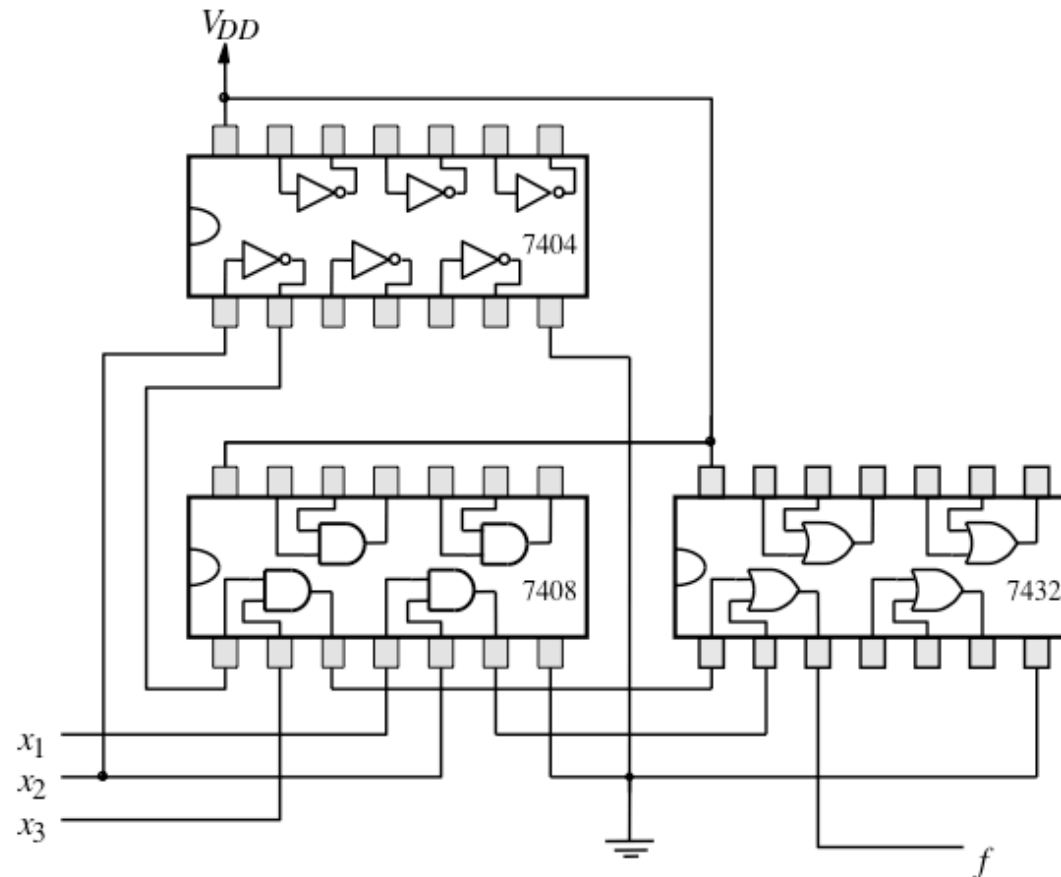


Figure 3.22. An implementation of  $f = x_1x_2 + \bar{x}_2x_3$ .
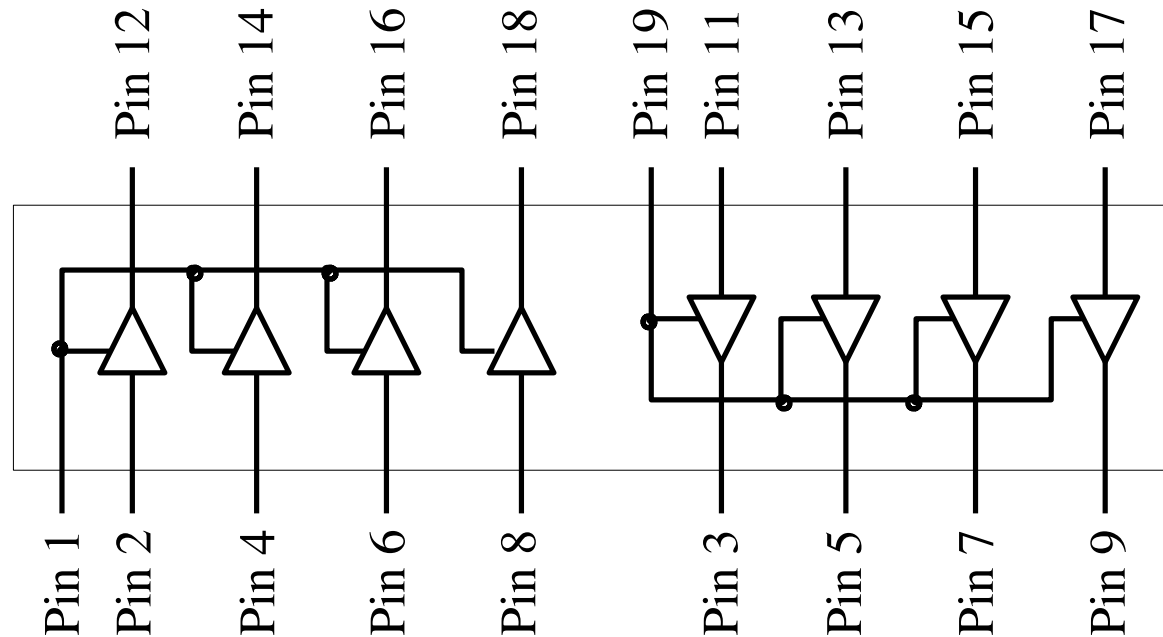
# Standard Chips

- Because of their low capacity, standard chips are seldom used today except for buffers



---


# Programmable Logic Devices

- The function provided by each of the 7400 series parts is fixed
- Each chip contains only a few logic gates
- These chips are inefficient for building large circuits
- Solution: manufacture chips that contain relatively large amount of logic with a structure that is not fixed
- These chips are called programmable logic devices (PLDs)
- Several types of PLDs are available: PLA, PAL, CPLD, and FPGA

---
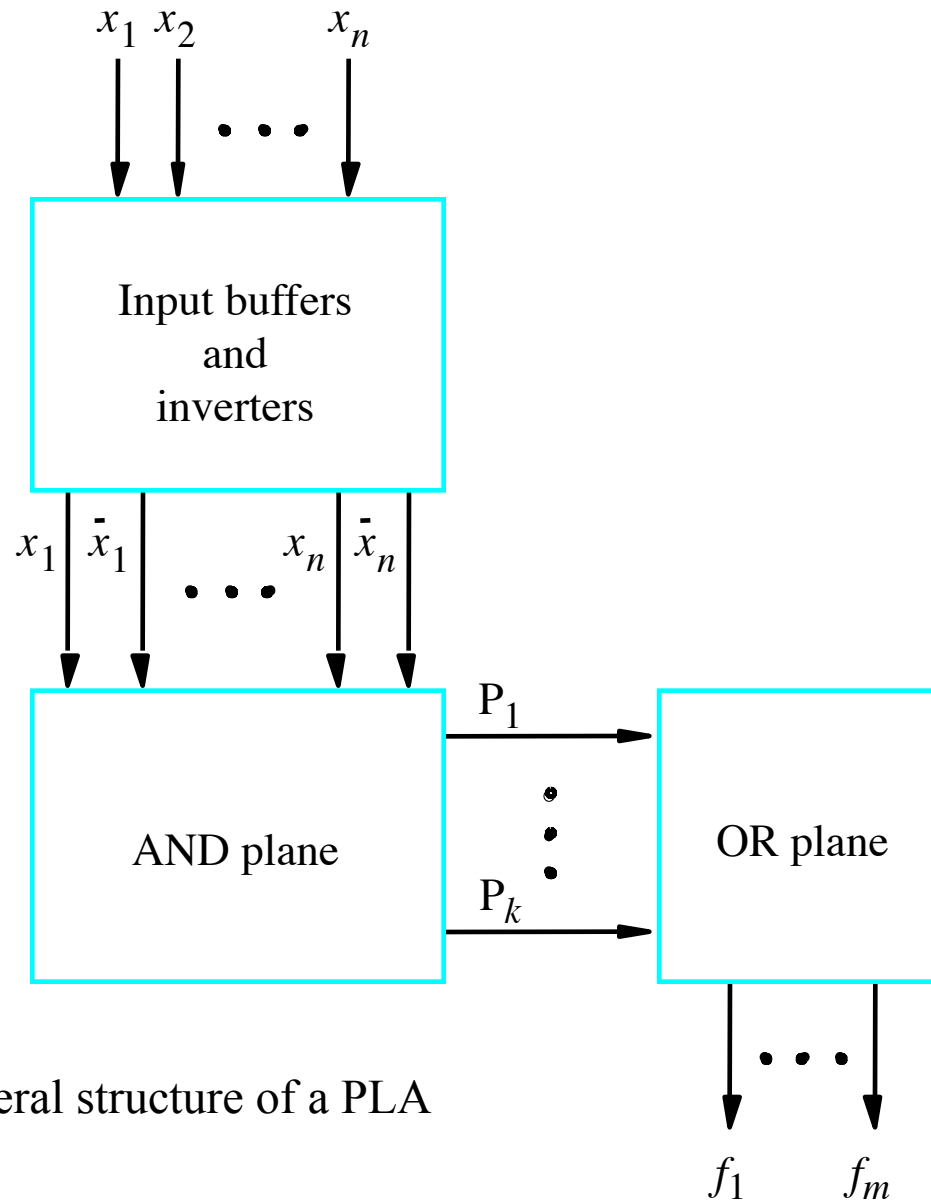
# Programmable Logic Technology

- Simple programmable logic devices (PLDs) such as programmable logic array (PLA) and programmable array logic (PAL) have been in use for over 20 years.
- PLA: the idea is that logic functions can be realized in sum-of-products form



General structure of a PLA



 


Figure 3.26. Gate-level diagram of a PLA.

 


Figure 3.27. Customary schematic for the PLA in Figure 3.26.

---

# Programmable Logic Technology

- Programmable connections (switches) are difficult to fabricate and reduce the speed of circuit
- In PALs the AND plane is programmable but the OR plane is fixed.
- To compensate for reduced flexibility, PALs are manufactured in a range

 


Figure 3.28. An example of a PLA.

---

# Programmable Logic Technology

- On many PLAs and PALs the output of the OR gate is connected to a flip flop whose output can then be feedback as an input into the AND gate array.
- This way simple state machines are implemented

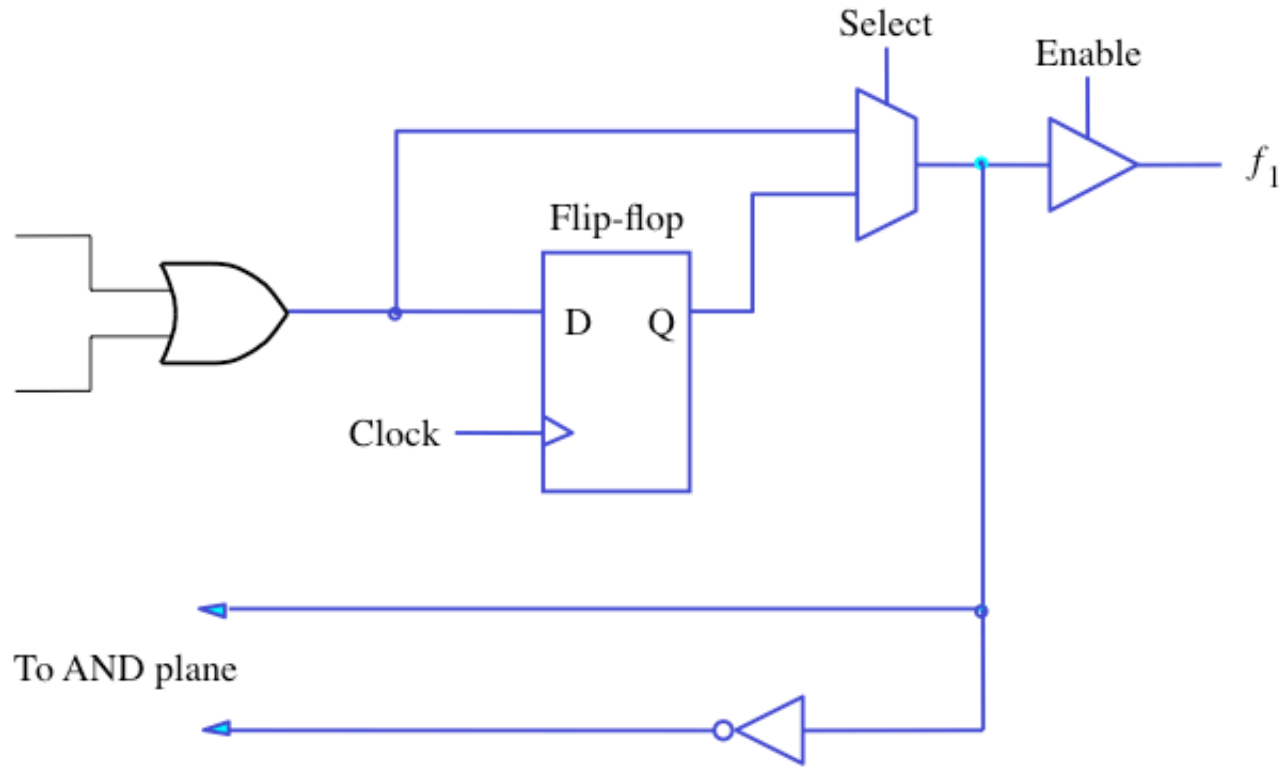


Figure 3.29. Extra circuitry added to OR-gate from Figure 3.28.

---

# Programming PLAs and PALs

- In PLA or PAL switches exist between the inputs and AND gate
- These switches should be programmed to implement a circuit
- There are several thousands programmable switches in commercial chips
- Manual programming is not an option
- CAD systems are employed for this purpose
- CAD is running on a computer that is connected to a programming unit
- CAD generates a file that states how each switch should be to realize the designed circuit

---

# Programming PLAs and PALs

- PLD is placed in the programming unit and the programming file is transferred from the computer system
- Usually PLAs and PALs are part of circuit and are on a printed circuit board
- Usually the chip should be removed from the board for programming
- In system programming is usually not provided for PLAs and PALs but is available for more sophisticated chips



---

# CPLD

- PLAs and PALs are enough for implementing moderate size circuits
- For more sophisticated circuits CPLDs are used
- CPLD: multiple blocks and internal wiring that connects the blocks
- Each block is similar to a PAL or PLA so it is called PAL like block

# CPLD

 


Figure 3.32. Structure of a complex programmable logic device (CPLD).

# CPLD

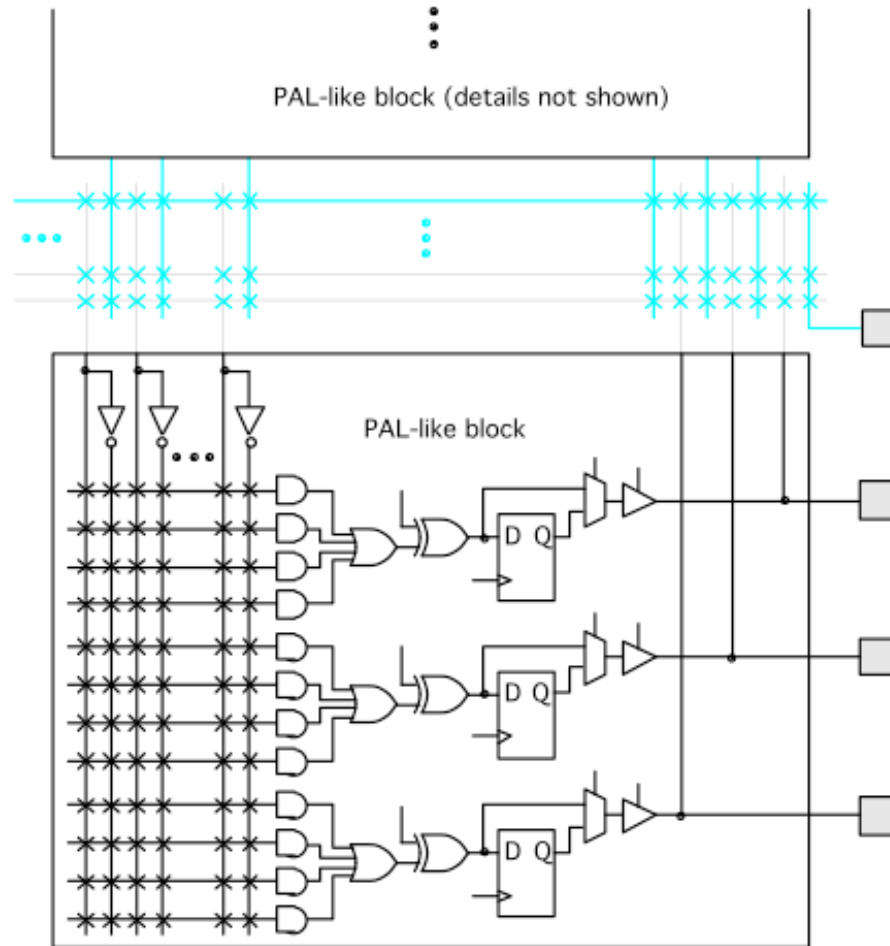



Figure 3.33. A section of the CPLD in Figure 3.32.

---


# CPLD

- Interconnection wiring contains programmable switches that are used to connect PAL-like blocks
- Commercial CPLDs have 2 to 100 PAL-like blocks
- CPLD devices usually support in system programming
- A small connector is place on the board and for programming it is connected to the computer
- The circuit on CPLD that allows this type of programming is called JTAG (Joint Test Action Group).

# CPLD

 

 (a) CPLD in a Quad Flat Pack (QFP) package



(b) JTAG programming

---

# Field Programmable Gate Arrays (FPGA)


- One way to quantify a circuit's size is to assume that the circuit is to be built using only simple gates (e.g., NAND gates) and estimate how many of these gates are needed
- This method is called equivalent gates
- PLA/PAL: 160 gates
- CPLD: 10,000 gates
- Not large by modern standards
- To implement larger circuits we use FPGAs

---


# Field Programmable Gate Arrays (FPGA)

- FPGAs: do not contain AND or OR planes
- FPGA contains three main types of resources:
  - logic blocks
  - I/O blocks for connecting to the pins
  - interconnection wires and switches
- Each logic block in an FPGA has a small number of input and outputs
- The most commonly used logic block is a look-up table (LUT)
- LUT: contains storage cells that are used to implement a small logic function

# FPGA

 


(a) General structure of an FPGA

 

(b) Pin grid array (PGA) package (bottom view)




# FPGA

 

(a) Circuit for a two-input LUT

$x_1$	$x_2$	$f_1$
0	0	1
0	1	0
1	0	0
1	1	1

(b)  $f_1 = \bar{x}_1\bar{x}_2 + x_1x_2$

 

(c) Storage cell contents in the LUT

# FPGA

 


Figure 3.37. A three-input LUT.

# FPGA

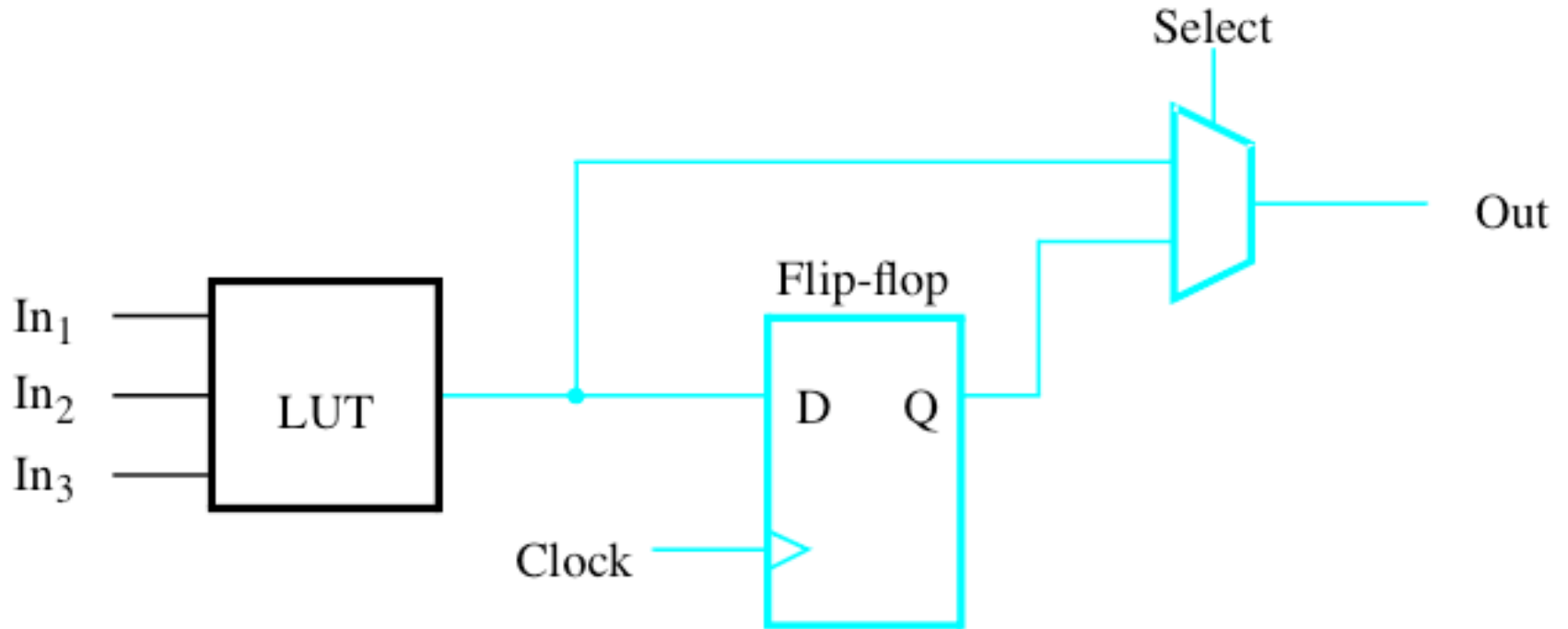


Figure 3.38. Inclusion of a flip-flop in an FPGA logic block.

# FPGA

 



Figure 3.39. A section of a programmed FPGA.

---


# FPGA

- FPGAs are configured by using the in-system programming method
- FPGAs are volatile: they will lose stored contents whenever the power is turned off
- Often a small PROM is included on the board that houses the FPGA and the storage cells are loaded automatically from the PROM when the power is applied

# Dynamic operation of logic gates

 


(a) A NOT gate driving another NOT gate

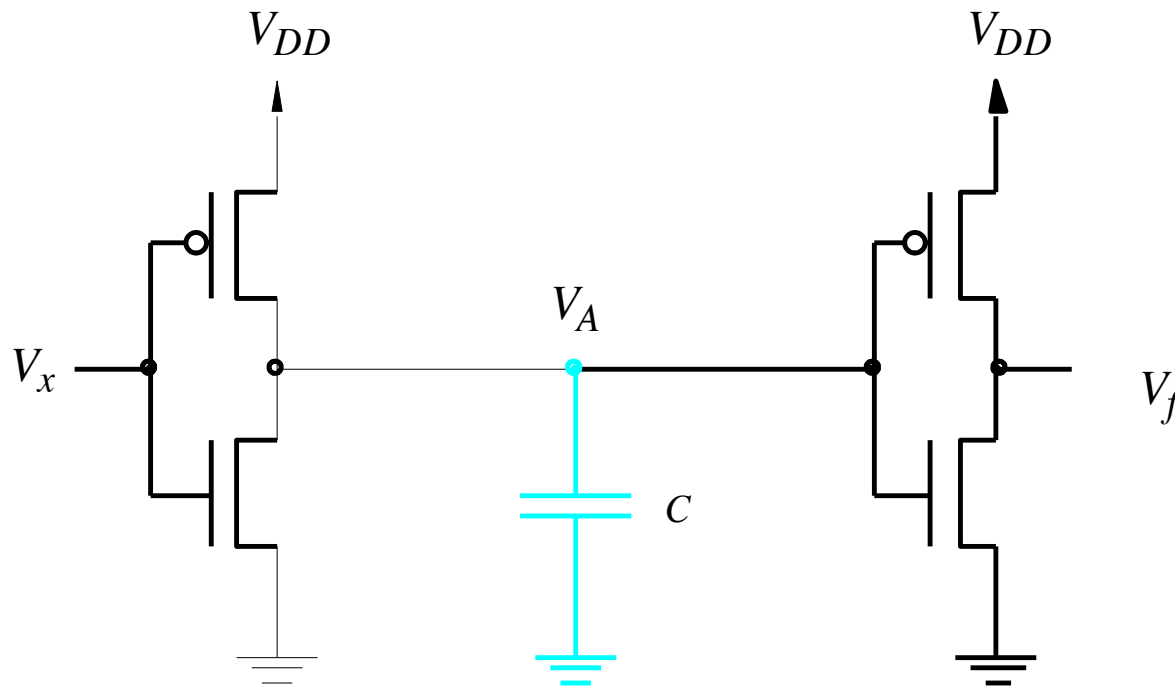


(b) The capacitive load at node A


# Dynamic operation of logic gates

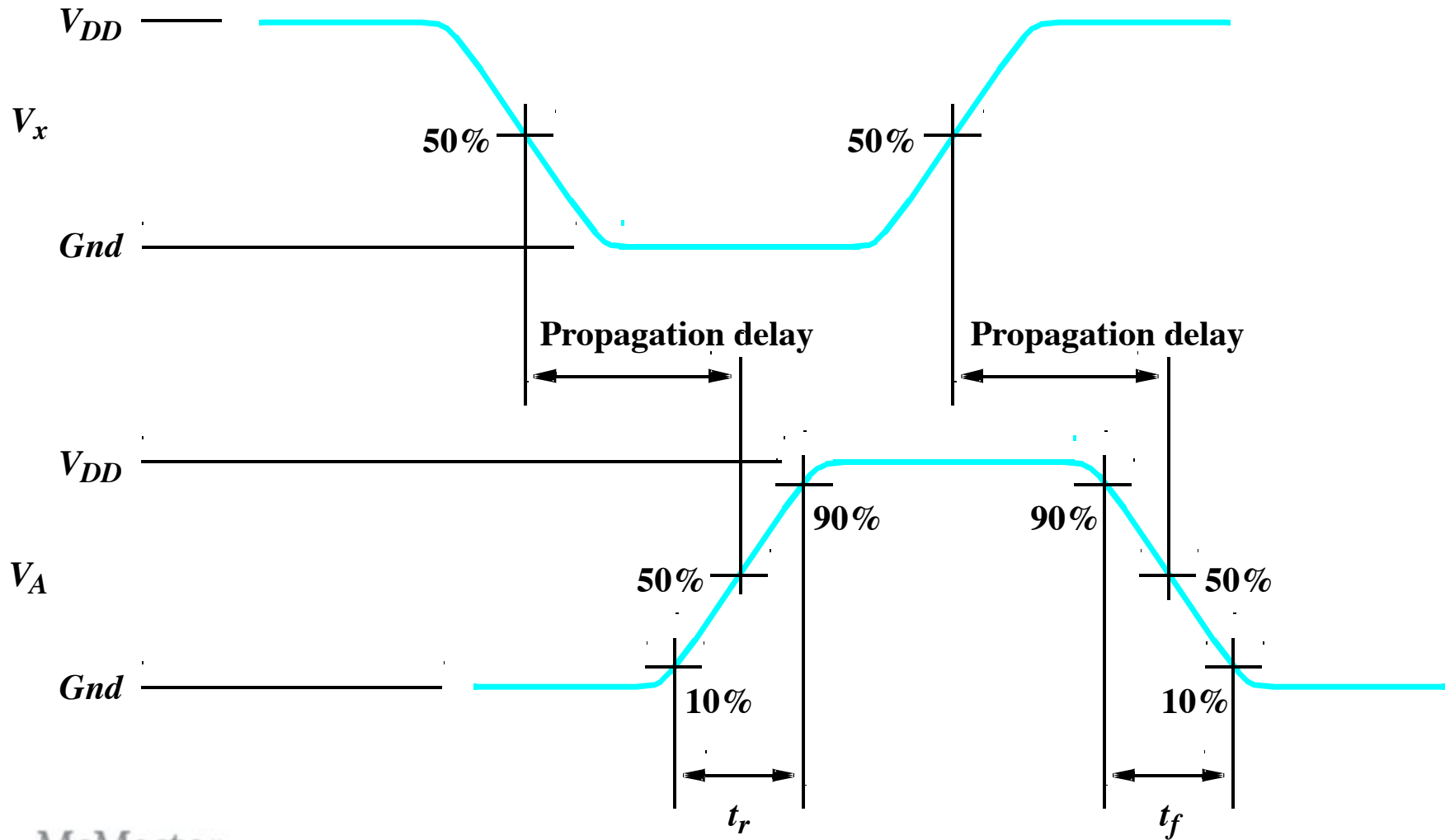

# Buffer

 


(a) Implementation of a buffer

 


(b) Graphical symbol



# Tri-state Buffer

 


**(a) A tri-state buffer**

 

**(b) Equivalent circuit**


<i>e</i>	<i>x</i>	<i>f</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

**(c) Truth table**

 


**(d) Implementation**


# Tri-state Buffer

 


(a)

 

(b)

 


(c)

 


(d)

# Tri-state Buffer

 
 
# Transmission Gate


- It is possible to combine an NMOS and a PMOS transistor into a single switch
- It is called a transmission gate
- $V_s=5$  and  $V_s'=0$  turns the switch on.
- When  $V_x=0$ , NMOS is on and  $V_f$  will be 0
- When  $V_x=5$ , PMOS transistor will be on and  $V_f$  will be 5




(a) Circuit

$s$	$f$
0	Z
1	$x$

(b) Truth table

 

(c) Equivalent circuit

 


(d) Graphical symbol

Figure 3.60. A transmission gate.
 
# XOR

- Implementing XOR using AND and OR and NOT requires 22 transistors.
- This can be reduced using transmission gates



(d) CMOS implementation

# Multiplexer

 


Figure 3.62. A 2-to-1 multiplexer built using transmission gates.

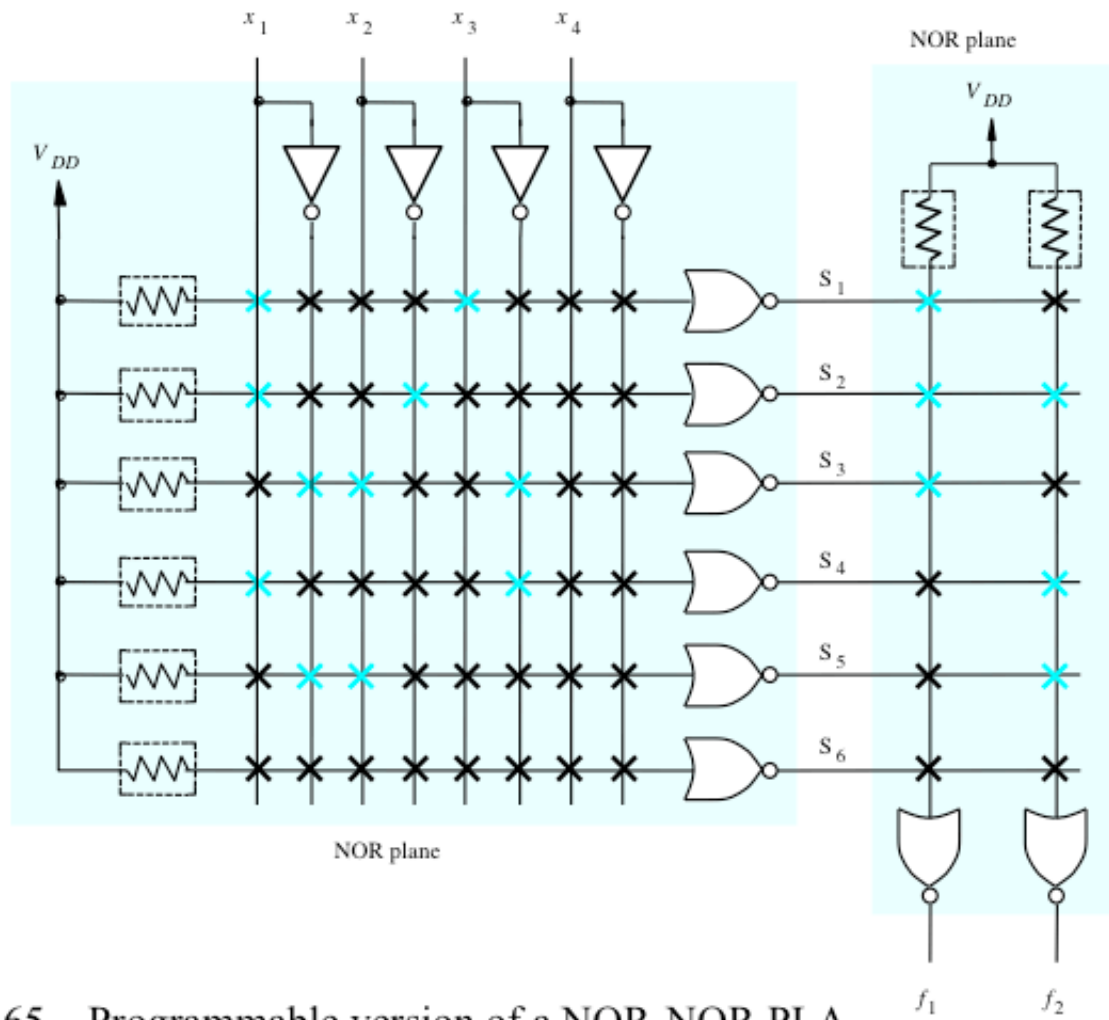


Figure 3.65. Programmable version of a NOR-NOR PLA.

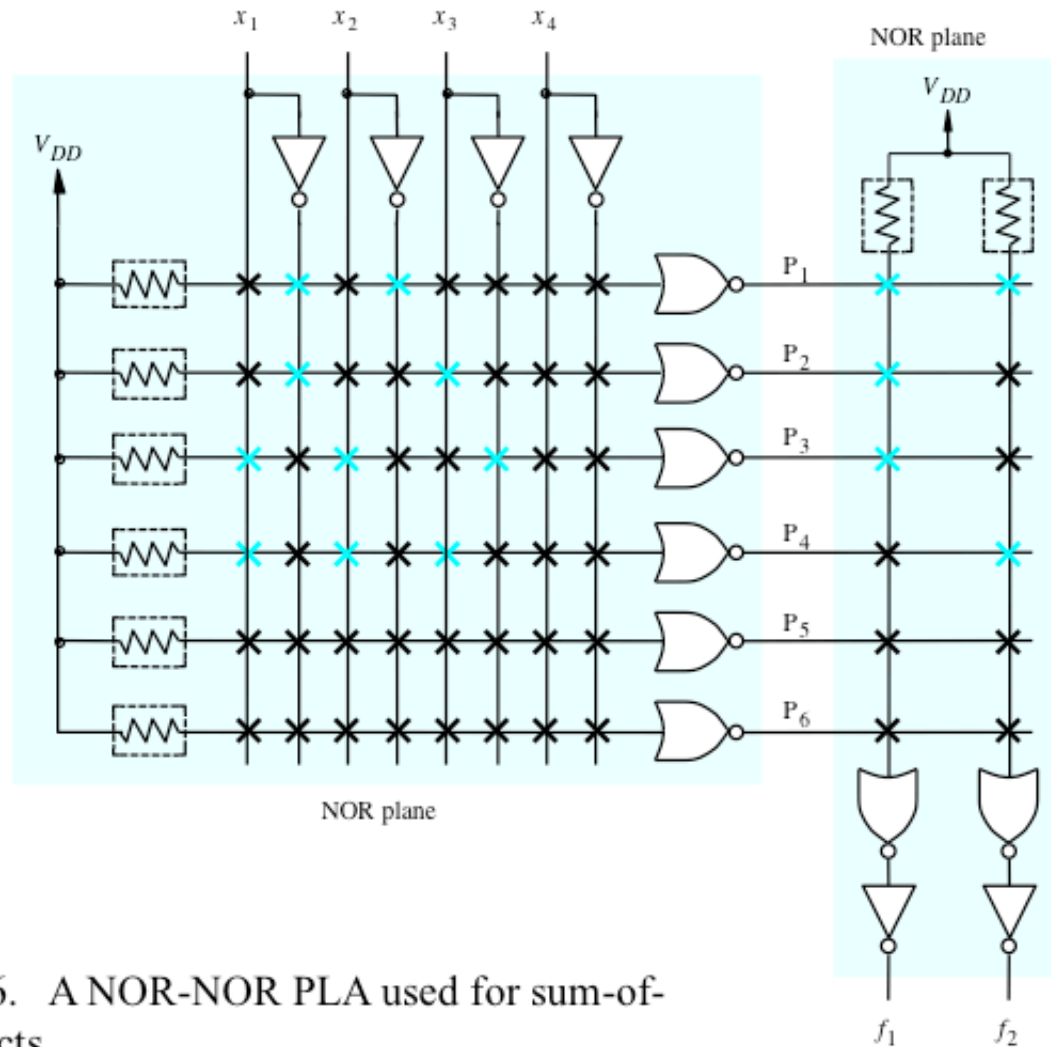


Figure 3.66. A NOR-NOR PLA used for sum-of-products.



 


Figure 3.67. PAL programmed to implement two functions in Figure 3.66.