

Logic Design

Synchronous Sequential Circuits



Introduction

- Combinational circuits: value of each output depends only on the values of inputs
- Sequential Circuits: values of outputs depend on inputs and past behavior of the circuit
- In most cases a clock is used to control the operation of a sequential circuit
- These circuits are called synchronous sequential circuits

-
- Synchronous sequential circuits are realized using combinational logic and one or more flip-flops
 - State: the value of outputs of flip-flops
 - Under the control of clock signal, flip-flop outputs change their state as determined by the combinational logic

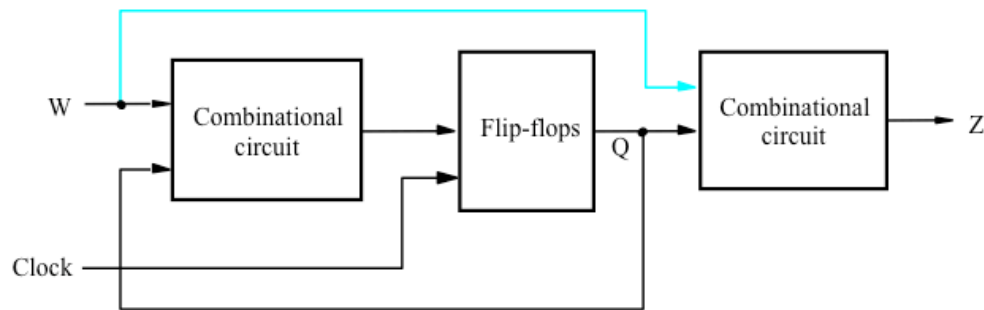


Figure 8.1. The general form of a sequential circuit.

-
- To ensure that only one transition from one state to another takes place during one clock cycle, flip-flops are edge-triggered
 - Outputs are generated by another combinational circuit and are function of present state of the flip-flops and the inputs
 - Outputs do not necessarily have to depend directly on the inputs
 - Moore type: the output depends only on the state of the circuit
 - Mealy type: outputs depend on both the state and the inputs
 - Sequential circuits are also called finite state machines (FSM)

Design Example

- Design a circuit that:
 - Has one input (w) and one output (z)
 - All changes occur on the positive edge of the clock
 - Output z is equal to 1 if during the two immediately preceding clock cycles the input w was equal to 1. Otherwise z is equal to 0.

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Figure 8.2. Sequences of input and output signals.

Design Example

- First step in designing a FSM: determine how many states are needed and which transitions are possible from one state to another
- No set procedure for this task
- A good way is select a starting state (a state that the circuit enters when the power is turned on or a reset signal is applied)
- Starting state A
- As long as w is 0, the circuit should remain in A
- When w becomes 1, the machine should move to a different state (B)

State Diagram

 


Figure 8.3. State diagram of a simple sequential circuit.

State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Figure 8.4. State table for the sequential circuit in Figure 8.3.

Design Example

- When implemented in logic circuits, each state is represented by a particular valuation (combination) of state variables
- Each state variable may be implemented in the form of a flip-flop
- Since there are three states in this example, two state variables are sufficient: y_1 and y_2

Design Example

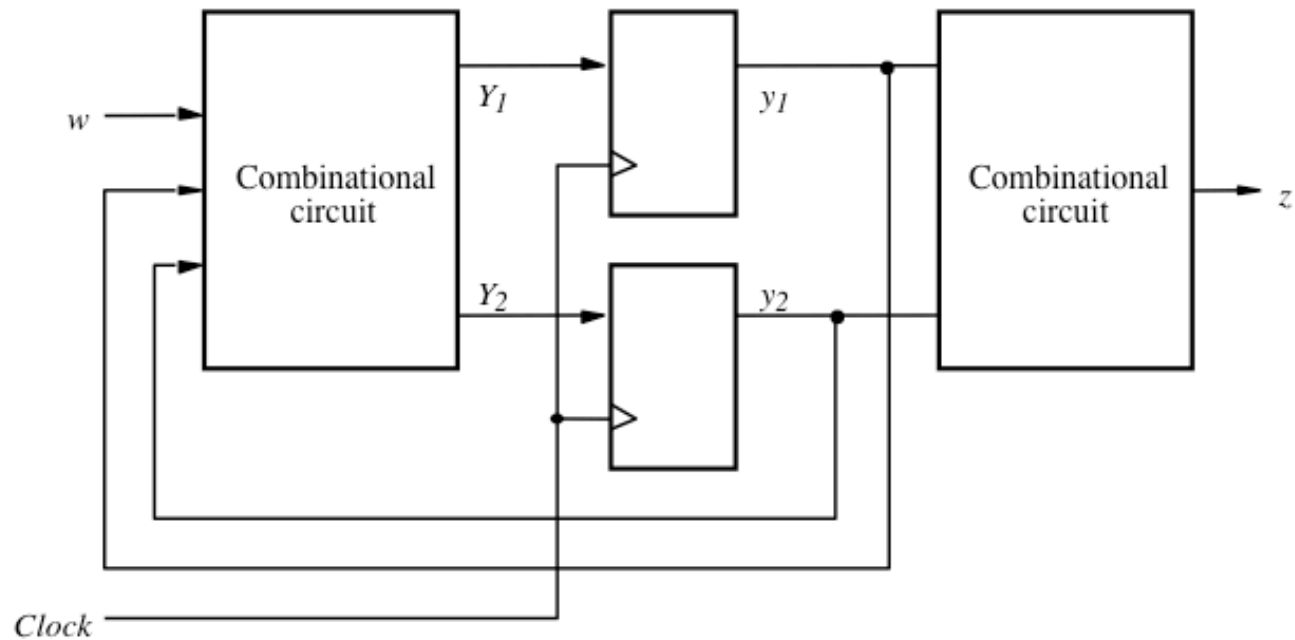


Figure 8.5. A general sequential circuit with input w , output z , and two state flip-flops.

Design Example

- We need to design a combinational circuit with inputs w , y_1 and y_2 such that for all valuations of these signals Y_1 and Y_2 will cause the machine to move to the next state
- We create a truth table by assigning specific valuation of variables y_1 and y_2 to each state

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	<i>dd</i>	<i>dd</i>	<i>d</i>

Design Example

- Choice of flip-flop:
- Most straightforward choice is to use D flip-flops because the values of $Y1$ and $Y2$ are simply clocked into the flip-flops to become the new values of $y1$ and $y2$

Design Example

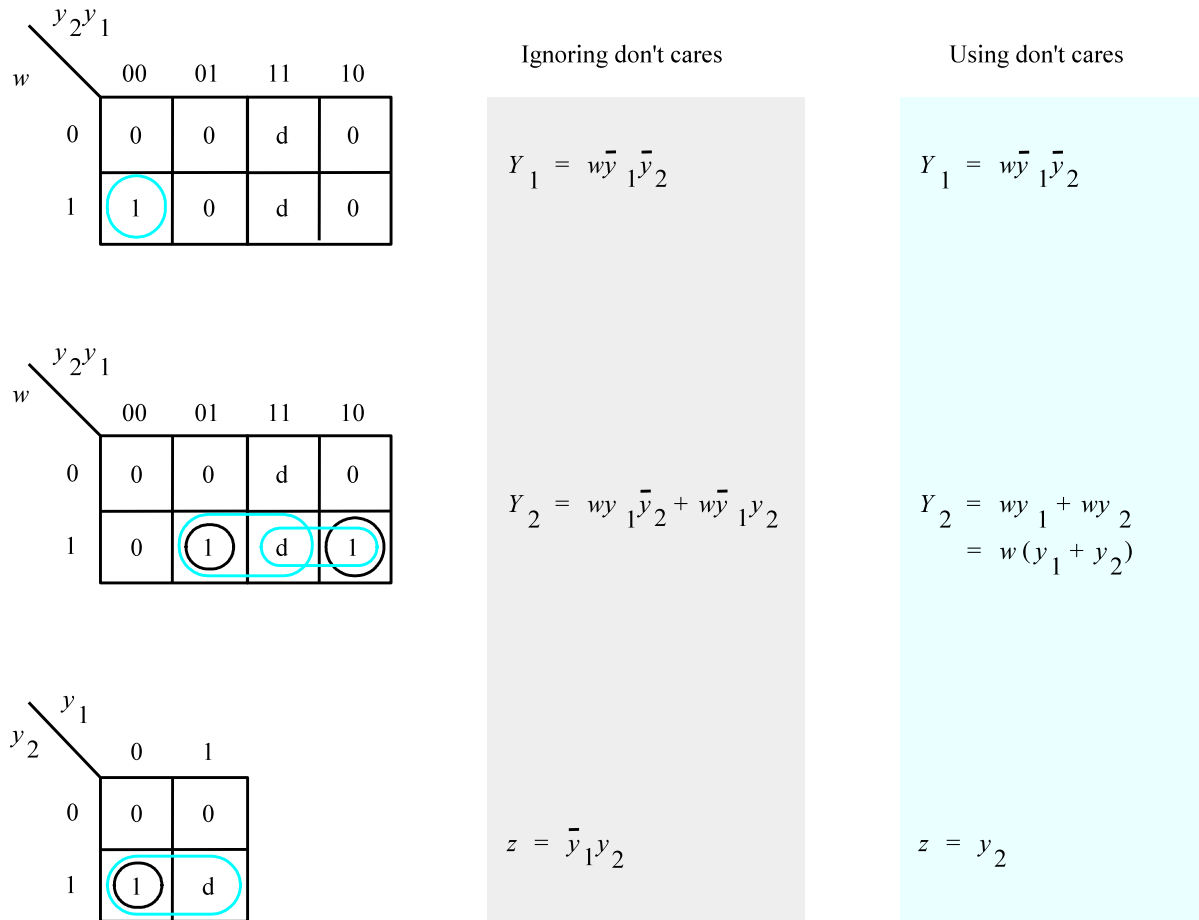


Figure 8.7. Derivation of logic expressions for the sequential circuit in Figure 8.6.

Design Example

 


Figure 8.8. Final implementation of the sequential circuit derived in Figure 8.7.

Design Example

 


Figure 8.9. Timing diagram for the circuit in Figure 8.8.

Bus controller

- Digital systems often contain a set of registers to store data
- Each register is connected to a common set of n wires, used to transfer data into and out of registers
- This common set of wires is called a bus
- In addition to registers other types of circuits would be connected to the bus
- It is essential to ensure that only one circuit block attempts to place data onto the bus wires at any given time
- A control circuit is used to ensure that only one of the tri-state buffers enables is asserted at a given time

Bus Controller

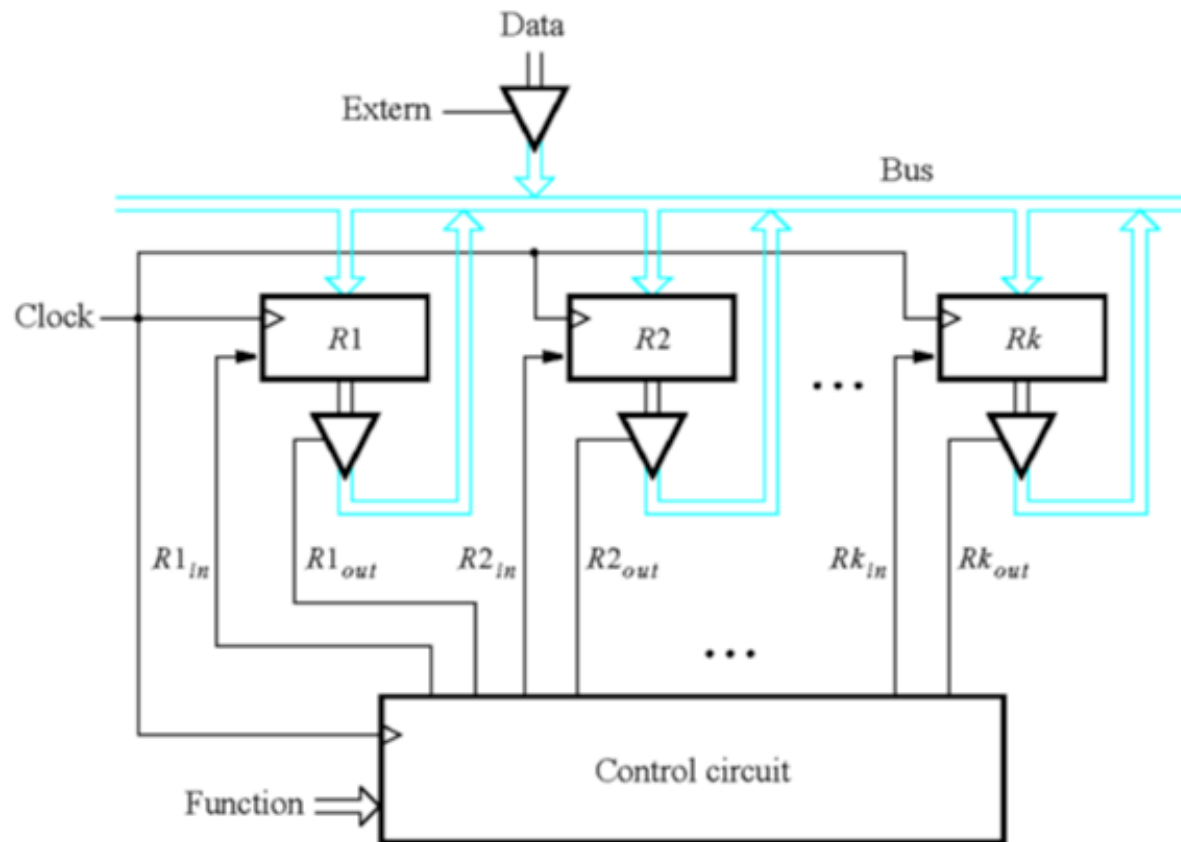


Figure 7.55. A digital system with k registers.

Bus controller

 



Figure 7.56. Details for connecting registers to a bus.

Bus controller


- An example: consider a system that has three registers, R1, R2 and R3. We want to swap the content of R1 and R2
- Steps:
 - Copy R2 to R3
 - Copy R1 to R2
 - Transfer R3 to R1

Bus controller

 - Content of R2 is loaded into R3 using $R2_{out}=1, R3_{in}=1$
- Content of R1 is transferred into R2 using $R1_{out}=1, R2_{in}=1$
- Content of R3 is transferred into R1 using $R3_{out}=1, R1_{in}=1$
- We will indicate the completion of the task by setting a signal $Done=1$



Bus controller

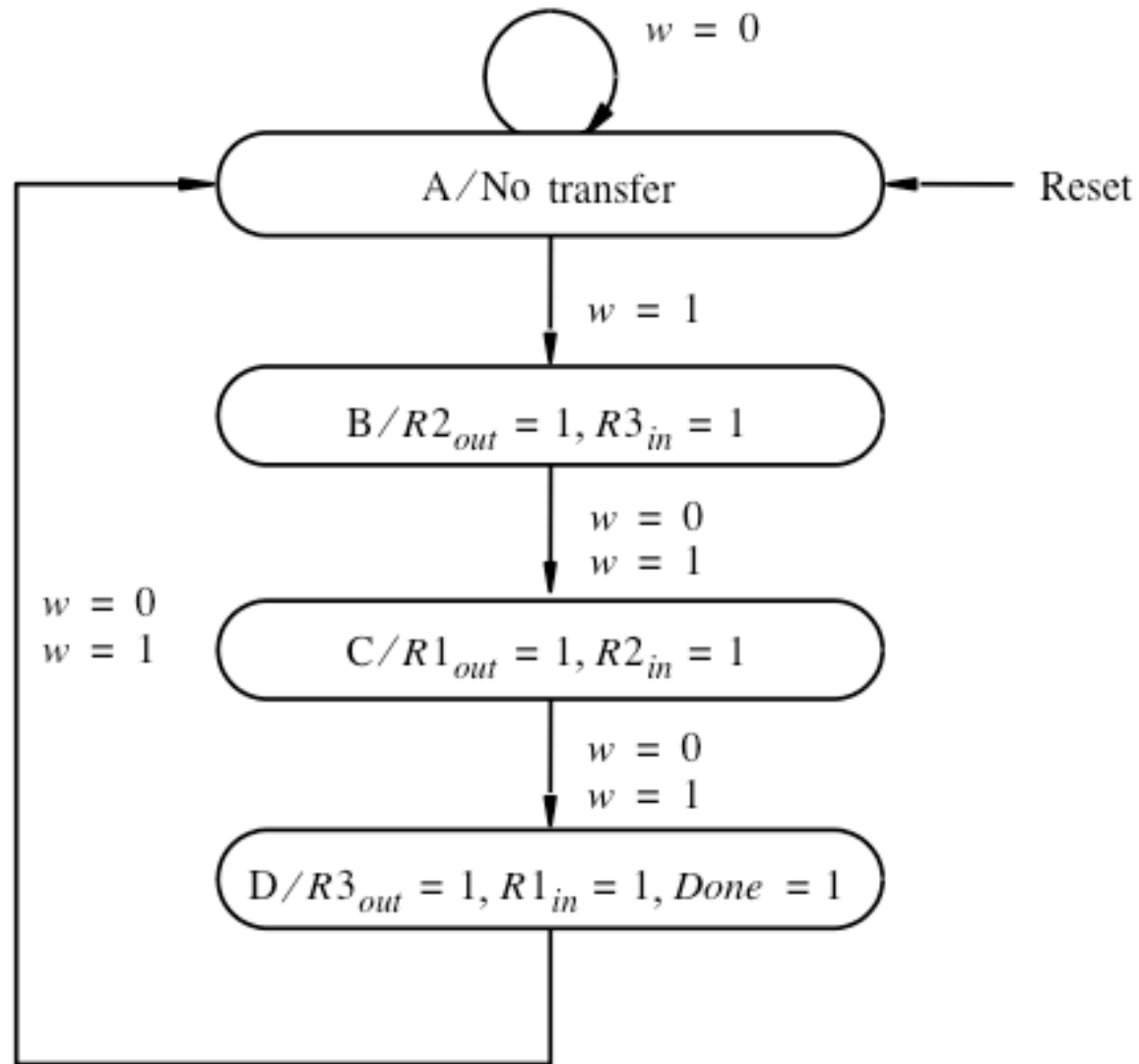


Bus controller

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1


Bus controller

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	y_2y_1	Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	01	0	0	0	0	0	0	0
B	01	10	10	0	0	1	0	0	1	0
C	10	11	11	1	0	0	1	0	0	0
D	11	00	00	0	1	0	0	1	0	1

Bus controller

 

$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

 

$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$


Bus controller

$$R1out = R2in = \overline{y_1}y_2$$

$$R1in = R3out = Done = y_1y_2$$

$$R2out = R3in = y_1\overline{y_2}$$

Bus controller

 

State Assignment Problem


- Some state assignment might be better than the others
- It is often impossible to find the best state assignment for a large circuit
- Exhaustive search is not practical because the number of available state assignments is huge

State Assignment Problem

- $Y_1 = D_1 = w$
- $Y_2 = D_2 = wy_1$
- $z = y_2$

	Present state	Next state		Output z
		$w = 0$	$w = 1$	
	y_2y_1	Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	<i>dd</i>	<i>dd</i>	<i>d</i>

State Assignment Problem

 

State Assignment Problem

- We now consider a different state assignment for the bus controller example

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	y_2y_1	Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	01	0	0	0	0	0	0	0
B	01	11	11	0	0	1	0	0	1	0
C	11	10	10	1	0	0	1	0	0	0
D	10	00	00	0	1	0	0	1	0	1

State Assignment Problem

w	y_2y_1	00	01	11	10
0			1		
1		1	1		

$$Y_1 = w\bar{y}_2 + y_1\bar{y}_2$$

w	y_2y_1	00	01	11	10
0			1	1	
1			1	1	

$$Y_2 = y_1$$

One-hot coding

- One possibility is to use as many state variables as there are states
- For each state all but one of the state variables are equal to 0
- This approach is known as one-hot coding

One-hot coding

- $Y_1 = w'$
- $Y_2 = wy_1$
- $Y_3 = wy_1'$
- $z = y_3$

	Present state $y_3y_2y_1$	Nextstate		Output z
		$w = 0$	$w = 1$	
		$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$	
A	001	001	010	0
B	010	001	100	0
C	100	001	100	1

One-hot coding

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

One-hot coding

$$Y1 = \bar{w}y1 + y4$$

$$Y2 = wy1$$

$$Y3 = y2$$

$$Y4 = y3$$

$$R1out = R2in = y3$$

$$R1in = R3out = Done = y4$$

$$R2out = R3in = y2$$

Mealy State Model

- Mealy state machine: output values are generated based on both the state and the inputs
- Example: design a sequential circuit that the output z is equal to 1 in the same clock cycle when the second occurrence of w (input) is detected

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Mealy State Model

 


Figure 8.23. State diagram of an FSM that realizes the task in Figure 8.22.

Mealy State Model

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1


Figure 8.24. State table for the FSM in Figure 8.23.

Mealy State Model


Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
A 0	0	1	0	0
B 1	0	1	0	1

Figure 8.25. State-assigned table for the FSM in Figure 8.24.

Mealy State Model

 

(a) Circuit

 

(b) Timing diagram

Figure 8.26. Implementation of FSM in Figure 8.25.

Mealy State Model

 


Figure 8.28. State diagram for Example 8.4.

Mealy State Model

$$Y1 = \bar{w}y1 + y3$$

$$Y2 = wy1$$

$$Y3 = y2$$