

# Logic Design

## Asynchronous Sequential circuits




---

# Asynchronous Sequential Circuits

- Synchronous sequential circuits: operation is controlled by a clock pulse (operates in pulse mode)
- Sequential circuits that do not operate in pulse mode and do not use flip-flops
- In asynchronous sequential circuits changes in state are not triggered by clock pulses but by change in the inputs
- Conditions:
  - Inputs must change one at a time
  - Sufficient time exists between changes in input signals so all internal signals stop changing
- Above conditions true: circuit is operating in the fundamental mode

# Asynchronous behavior

 

(b) Circuit with modeled gate delay

Present state $y$	Next state			
	$SR = 00$	01	10	11
	$Y$	$Y$	$Y$	$Y$
0	0	0	1	0
1	1	0	1	0

(b) State-assigned table

Figure 9.1. Analysis of the SR latch.

---


# Asynchronous behavior

- Because of the feedback the circuit is sequential
- Box labeled  $\Delta$  represents combined propagation delays through two NOR gates
- $y$  is the current state
- $Y$  is the next state
- After a  $\Delta$  time delay  $y$  takes the value of  $Y$
- If for a particular input  $y$  is not equal to  $Y$ , the circuit is not stable
- Stable states are indicated by circles
- We can derive state table and state diagram

# Asynchronous behavior

Present state	Next state				Output Q
	$SR = 00$	01	10	11	
A	(A)	(A)	B	(A)	0
B	(B)	A	(B)	A	1

(a) State table

 

(b) State diagram

---

# Asynchronous behavior

- Consider the opposite task: synthesis of an asynchronous circuit
- Using the state assigned table to find minimal SOP yields:
- $Y=R'.(S+y)$
- If we were doing synchronous circuits we would use a D flip-flop
- Here, we create a circuit that realizes the expression and we feed back the output signal as the present state input  $y$

---

# Asynchronous behavior


- In asynchronous circuits:
  - State table => flow table
  - State-assigned table => transition table or excitation table

---
 
## Gated D latch

- We consider the clock signal to be one of the input signals
- $Y = CD + C'y + Dy$
- Using the consensus theorem:  $Y = CD + C'y$






(a) Circuit

Present state	Next state				Q
	CD = 00	01	10	11	
y	Y	Y	Y	Y	
0	0	0	0	1	0
1	1	1	0	1	1

(b) Excitation table

Present state	Next state				Q
	CD = 00	01	10	11	
A	A	A	A	B	0
B	B	B	A	B	1

(c) Flow table

 

(d) State diagram

Figure 9.4. The gated D latch.

---

# Master Slave D Flip-flop

- $Y_m = CD + C'y_m$
- $Y_s = C'y_m + Cys$

---

# Master Slave D Flip-flop

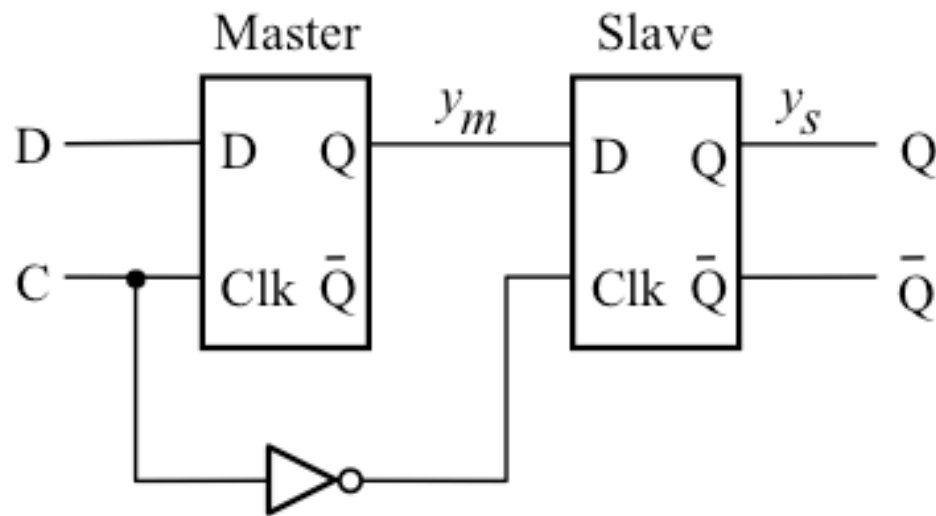


Figure 9.5. Circuit for the master-slave D flip-flop.

Present state $y_m y_s$	Next state				Output Q
	$CD = 00 \quad 01 \quad 10 \quad 11$				
	$Y_m Y_s$				
00	⓪⓪	⓪⓪	⓪⓪	10	0
01	00	00	⓪1	11	1
10	11	11	00	⓪10	0
11	⓪11	⓪11	01	⓪11	1

(a) Excitation table

Present state	Next state				Output Q
	$CD = 00 \quad 01 \quad 10 \quad 11$				
S1	⓪1	⓪1	⓪1	S3	0
S2	S1	S1	⓪2	S4	1
S3	S4	S4	S1	⓪3	0
S4	⓪4	⓪4	S2	⓪4	1

(b) Flow table

Present state	Next state				Output Q
	$CD = 00 \quad 01 \quad 10 \quad 11$				
S1	⓪1	⓪1	⓪1	S3	0
S2	S1	-	⓪2	S4	1
S3	-	S4	S1	⓪3	0
S4	⓪4	⓪4	S2	⓪4	1

(c) Flow Table with unspecified entries



Figure 9.6. Excitation and flow tables for Example 9.2.

# Master Slave D Flip-flop

 


Figure 9.7. State diagram for the master-slave D flip-flop.

---

## Master Slave D Flip-flop

- Since we assumed that inputs must change one at a time, if the circuit is stable in state S2 for which  $CD=10$  it cannot go to S1 under the input valuation  $CD=01$  because simultaneous change in both inputs cannot happen
- These changes are labeled unspecified in the table.

## An other example

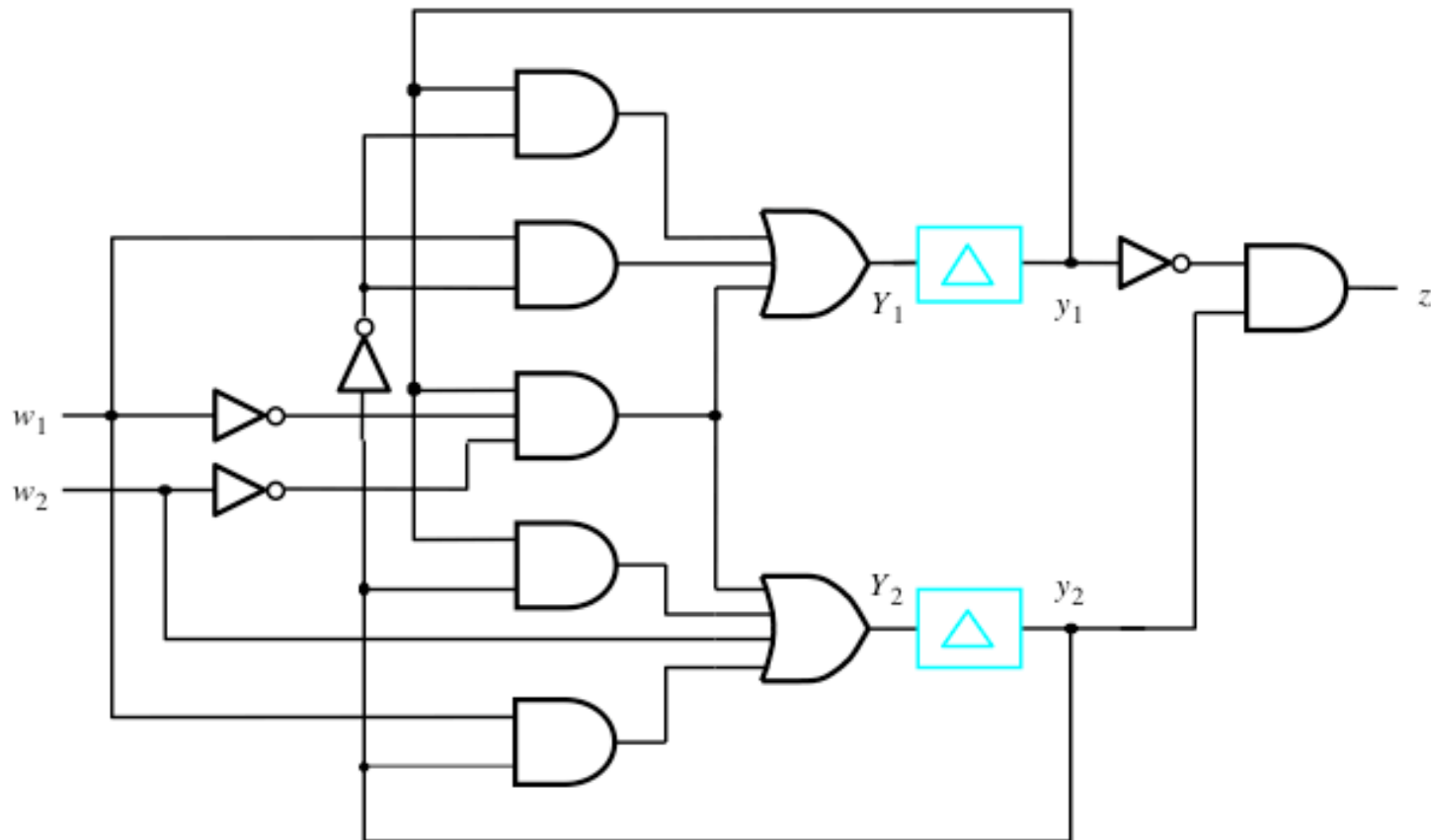


Figure 9.8. Circuit for Example 9.3.

- 
- $Y_1 = y_1 y_2' + w_1 y_2' + w_1' w_2' y_1$
  - $Y_2 = y_1 y_2 + w_1 y_2 + w_2 + w_1' w_2' y_1$
  - $Z = y_1' y_2$



Present state $y_2 y_1$	Next state				Output $z$
	$w_2 w_1 = 00$	01	10	11	
	$Y_2 Y_1$	$Y_2 Y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
00	00	01	10	11	0
01	11	01	11	11	0
10	00	10	10	10	1
11	11	10	10	10	0

(a) Excitation table

Present state	Next state				Output $z$
	$w_2 w_1 = 00$	01	10	11	
A	A	B	C	D	0
B	D	B	D	D	0
C	A	C	C	C	1
D	D	C	C	C	0

(b) Flow table

---

Present state	Next state				Output $z$
	$w_2 w_1 = 00$	01	10	11	
A	Ⓐ	B	C	—	0
B	D	Ⓑ	—	D	0
C	A	Ⓒ	Ⓒ	Ⓒ	1
D	Ⓓ	C	C	C	0

Figure 9.10. Modified flow table for Example 9.3.

 


Figure 9.11. State table for Example 9.3.

---

# Analysis Process

- Each feedback path is cut and a delay element is inserted at the point where the cut is made.
  - The input to the delay is a next state variable  $Y_i$  and the output is present state variable  $y_i$
  - Cut can be made anywhere in the loop
  - The number of cuts is the smallest number that results in being no feedback anywhere in the circuit (cut set)
- Next state and output expressions are derived from the circuit
- Excitation table is derived
- Flow table is obtained
- State diagram is derived

---

# Synthesis

1. Devise a state diagram for an FSM that realizes the required functional behavior
  2. Derive the flow table and reduce the number of states if possible
  3. Perform the state assignment and derive the excitation table
  4. Obtain the next state and output expressions
  5. Construct a circuit that implements these expressions
- Note: When devising a state diagram, it is essential to ensure when the circuit is in stable state correct output signals are generated. Should it be necessary to pass through an unstable state, this state must not produce an undesirable output

---

# Serial Parity Generator


- We want to design a circuit with input  $w$  and output  $z$  such that  $z$  is equal to 0 if the number of previously applied pulses to  $w$  is even and  $z$  is equal to 1 if the number of pulses is odd.

---

# Serial Parity Generator

- State A: an even number of pulses have arrived and the current value of the input is 0
- State B: an odd number of pulses have arrived and the current value of the input is 1
- State C: an odd number of pulses have arrived and the current value of the input is 0
- State D: an even number of pulses have arrived and the current value of the input is 1

# Serial Parity Generator

 

(a) State diagram

Present State	Next state		Output $z$
	$w = 0$	$w = 1$	
A	(A)	B	0
B	C	(B)	1
C	(C)	D	1
D	A	(D)	0

(b) Flow table



---

# Serial Parity Generator

- States B and C cannot be combined because it is impossible to have B both stable under  $w=1$  and change to D for  $w=1$

# Serial Parity Generator

Present state $y_2 y_1$	Next state		Output $z$
	$w = 0$	$w = 1$	
	$Y_2 Y_1$		
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

(a) Poor state assignment

Present state $y_2 y_1$	Next state		Output $z$
	$w = 0$	$w = 1$	
	$Y_2 Y_1$		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

(b) Good state assignment

---

# Serial Parity Generator

- Problem with the first state assignment:
- Assume circuit is stable in state 11 with  $w=1$
- Input changes to  $w=0$
- State should change from 11 to 00.
- Both state variables must change their values
- In asynchronous circuits values of the next states are determined by logic gates with varying propagation delays.
- One variable will change slightly before the other

---

# Race condition

- Scenario 1:  $y_1$  changes first
  - Circuit goes from 11 to 10.
  - As soon as it reaches 10 with  $w=0$  it will stay there
- Scenario 2:  $y_2$  changes first
  - Circuit goes from 11 to 01
  - According to the table with  $w=0$  it will try to change to 10
  - This again requires both  $y$ 's to change.
  - If  $y_1$  changes first the circuit is going to be stable in 00 with  $w=0$
- Uncertainty caused by multiple changes in the state variables in response to input: race condition

# Serial Parity Generator

 


Figure 9.15. Circuit that implements the FSM in Figure 9.13b.

# Modulo-4 counter

 


Figure 9.17. State diagram for a modulo-4 counter.

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	(A)	B	0
B	C	(B)	1
C	(C)	D	1
D	E	(D)	2
E	(E)	F	2
F	G	(F)	3
G	(G)	H	3
H	A	(H)	0

(a) Flow table

Present state $y_3 y_2 y_1$	Next state		Output $z_2 z_1$	Mod-8 output $z_3 z_2 z_1$
	$w = 0$	$w = 1$		
	$Y_3 Y_2 Y_1$			
000	(000)	001	00	000
001	011	(001)	01	001
011	(011)	010	01	010
010	110	(010)	10	011
110	(110)	111	10	100
111	101	(111)	11	101
101	(101)	100	11	110
100	000	(100)	00	111

(b) Excitation table

(c) Output for counting the edges



Figure 9.18. Flow and excitation tables for a modulo-4 counter.

---

# Hazards

- In asynchronous sequential circuits it is important to avoid glitches
- Glitches caused by the structure of a given circuit and propagation delays are referred to as hazard
- Two types of hazards: static and dynamic



---

# Hazards

- Static hazard: a signal is supposed to remain at a particular logic value when an input changes its value but instead the signal undergoes a momentary change
- Dynamic hazard: a signal is supposed to change from 0 to 1 (or 1 to 0) but the change involves a short oscillation

 


Figure 9.61. Definition of hazards.

---


# Hazards

- Consider the circuit in the next slide
- Let's assume  $x_1=x_2=x_3=1$ ,  $f=1$
- Suppose  $x_1$  changes to 0
- Point  $p$  will see the change before point  $q$
- For a short time both  $p$  and  $q$  are zero dropping  $f$  to zero before recovering back to 1


$$f = x_1x_2 + \bar{x}_1x_3$$

$$f = x_1x_2 + \bar{x}_1x_3 + x_2x_3$$


# Hazards

 

(a) Circuit with a hazard

 

(b) Karnaugh map

 

(c) Hazard-free circuit

# Master Slave D Flip Flop

Present state $y_m y_s$	Next state				Output Q
	$CD = 00$	01	10	11	
	$Y_m Y_s$				
00	00	00	00	10	0
01	00	00	01	11	1
10	11	11	00	10	0
11	11	11	01	11	1


(a) Excitation table

$$Y_m = CD + \bar{C} y_m$$


$$= (C \uparrow D) \uparrow (\bar{C} \uparrow y_m)$$

$$Y_s = C y_s + \bar{C} y_m$$

 
$$= (C \uparrow y_s) \uparrow (\bar{C} \uparrow y_m)$$



(a) Minimum-cost circuit

 

 (b) Karnaugh maps for  $Y_m$  and  $Y_s$  in Figure 9.6a



(c) Hazard-free circuit



Figure 9.63. Two-level implementation of master-slave D flip-flop.

---

$$\begin{aligned} Y_m &= CD + \bar{C} y_m + D y_m \\ &= (C \uparrow D) \uparrow ((C \uparrow \bar{D}) \uparrow y_m) \end{aligned}$$

$$\begin{aligned} Y_s &= C y_s + \bar{C} y_m + y_m y_s \\ &= ((\bar{C} \uparrow \bar{y}_m) \uparrow y_s) \uparrow (\bar{C} \uparrow y_m) \end{aligned}$$

---

# Dynamic Hazard

- A dynamic hazard is caused by the structure of the circuit where there exist multiple paths for a given signal change to propagate along
- Dynamic hazards are encountered in multilevel circuits obtained using factoring or decomposition techniques
- Dynamic hazards are neither easy to detect nor easy to deal with
- They can be avoided using two-level circuits and ensuring that there are not static hazards