

Dr. Nicola Nicolici **EE2DI4 Midterm Test #2** *Mar 23, 2004*

Instructions: This examination paper includes 12 pages and 20 multiple-choice questions starting on page 3. You are responsible for ensuring that your copy of the paper is complete. Bring any discrepancy to the attention of your invigilator. The answers for all the questions must be indicated by filling the corresponding circle on the optical scanning (OMR) examination sheet. **This OMR examination sheet is the only page to be handed in.** The instructions for completing the OMR examination sheet are provided on page 2. Read and follow these instructions with care! There is one mark for each question. Answer all questions. There is no penalty for guessing. This is a closed book exam. No reference material of any kind is permitted. No calculators of any kind are permitted. **Time allowed is 50 minutes.**

Note: A' and \bar{A} are used interchangeably.

OMR examination instructions

Multiple choice questions (numbered 1 to 20) – indicate your answer by filling the corresponding circle on the OMR answer sheet

 


Figure 1 - CMOS circuit for question 1.

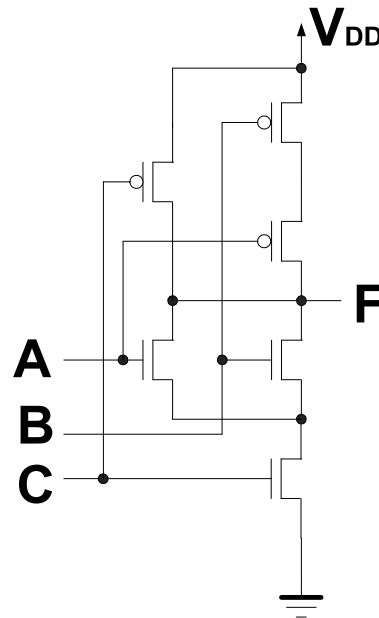


Figure 2 - CMOS circuit for question 2.

1. The complementary metal-oxide semiconductor (CMOS) circuit shown in Figure 1 is:

1. a 3 input XOR gate
2. a 3 input XNOR gate
3. a 2-to-1 multiplexer
4. a 4-to-1 multiplexer
5. none of the above

2. The logic function $F(A,B,C)$ implemented by the CMOS circuit shown in Figure 2 is:

1. $AB + C$
2. $AC + BC$
3. $A'B' + C'$
4. $A' + B'C'$
5. none of the above

3. The function implemented using 2 two-input look-up tables (LUT) as shown in Figure 3 is:

1. $F(A,B,C) = \Sigma m(0,1,3,4)$
2. $F(A,B,C) = \Sigma m(0,1,6,7)$
3. $F(A,B,C) = \Sigma m(1,2,3,6)$
4. $F(A,B,C) = \Sigma m(1,3,4,6)$
5. none of the above

 


Figure 3 – Circuit for question 3.

4. The programmable array logic (PAL) implementation of function F shown in Figure 4 is:

1. $F(A,B,C) = \Sigma m(0,1,2,3,5,7)$
2. $F(A,B,C) = \Sigma m(0,1,2,5,7)$
3. $F(A,B,C) = \Sigma m(0,1,2,7)$
4. $F(A,B,C) = \Sigma m(0,1,7)$
5. none of the above

 


Figure 4 – Circuit for question 4. An X indicates that the wires are connected, i.e., the vertical signal is an input to the corresponding horizontal AND gate.

5. 64 bytes are equal to:

1. 1 Kbits
2. 2 Kbits
3. 3 Kbits
4. 4 Kbits
5. none of the above

6. Consider a read-only memory (ROM) that performs binary to 4-digit BCD conversion as follows. The binary number is applied on the input address lines and the equivalent 4-digit BCD number is read on the output data lines. The capacity of the *smallest* ROM, in terms of the total number of bits that can be stored in it, which can be used for the conversion is:

1. 16 Kbits
2. 16 Kbytes
3. 32 Kbits
4. 32 Kbytes
5. none of the above

Tip for question 6: Note, the range of the unsigned decimal numbers that are converted from their binary representation to their *4-digit BCD* representation is 0 to 9999. First you should determine the values for the *smallest* number of the input address lines and the *smallest* number of the output data lines that are required to perform the binary to 4-digit BCD conversion using a ROM. Then, using these two values (and knowing that for every possible combination on the input address lines you can access a different memory location that stores a number of bits equal to the number of output data lines) you can derive the capacity of the ROM.

7.

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.all;

ENTITY question7 IS
    PORT (A, B, C: IN STD_LOGIC;
          F:      OUT STD_LOGIC);
END question7;

ARCHITECTURE Behavior OF question7 IS
    SIGNAL W: STD_LOGIC_VECTOR(0 TO 2);
BEGIN
    W(2) <= A;
    W(1) <= B;
    W(0) <= C;
    WITH W SELECT
        F <= '0' WHEN "001",
            '0' WHEN "110",
            '1' WHEN OTHERS;
END Behavior;

```

The above VHDL code describes:

1. $F(A,B,C) = A'BC + AB'C'$
2. $F(A,B,C) = (A'+B+C)(A+B'+C')$
3. $F(A,B,C) = A'B'C + ABC'$
4. $F(A,B,C) = (A'+B'+C)(A+B+C')$
5. none of the above

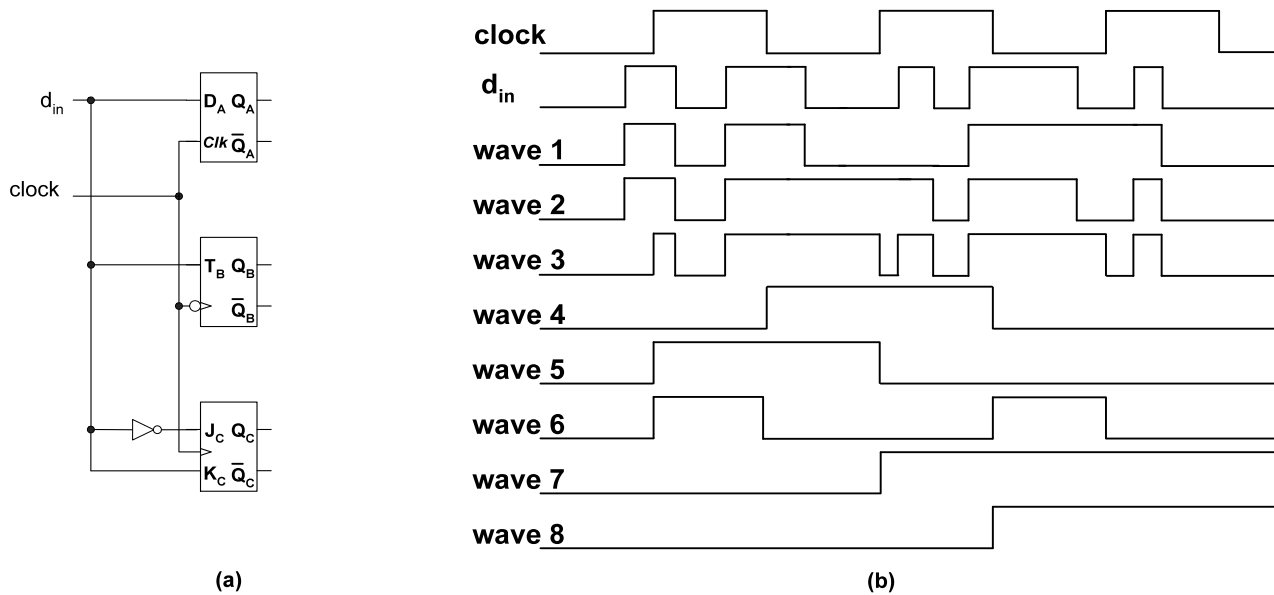


Figure 5 - Sequential (or storage) elements and signal waveforms for questions 8, 9 and 10. Note, the initial value of all the storage elements is zero and they are assumed to be ideal, i.e., the propagation delays and setup/hold times are considered to be zero.

8. Given the **clock** and **d_{in}** waveforms in Figure 5(b) the waveform for **Q_A** from Figure 5(a) is:

1. wave 1 from Figure 5(b)
2. wave 2 from Figure 5(b)
3. wave 3 from Figure 5(b)
4. wave 4 from Figure 5(b)
5. wave 5 from Figure 5(b)

9. Given the **clock** and **d_{in}** waveforms in Figure 5(b) the waveform for **Q_B** from Figure 5(a) is:

1. wave 4 from Figure 5(b)
2. wave 5 from Figure 5(b)
3. wave 6 from Figure 5(b)
4. wave 7 from Figure 5(b)
5. wave 8 from Figure 5(b)

10. Given the **clock** and **d_{in}** waveforms in Figure 5(b) the waveform for **Q_C** from Figure 5(a) is:

1. wave 4 from Figure 5(b)
2. wave 5 from Figure 5(b)
3. wave 6 from Figure 5(b)
4. wave 7 from Figure 5(b)
5. wave 8 from Figure 5(b)

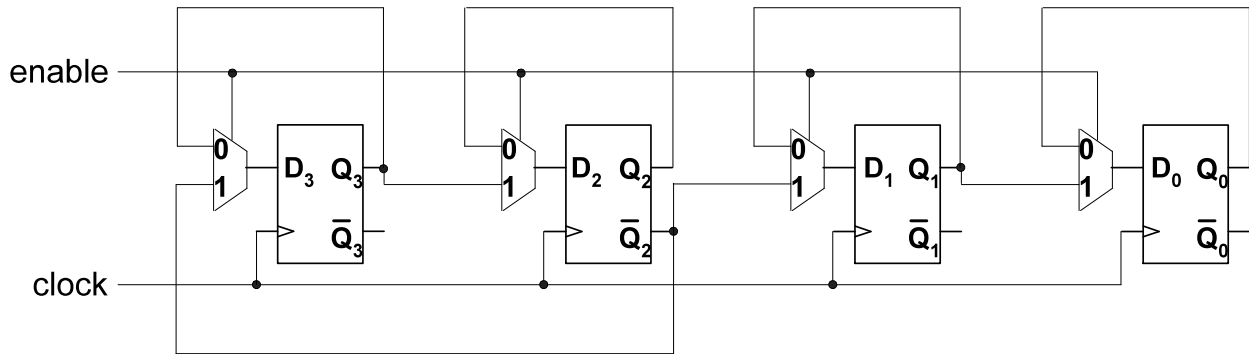


Figure 6 - Circuit for question 11.

11. In Figure 6, if enable=1 and the current (or present) state is $Q_3Q_2Q_1Q_0=0101$, then the next state will be:

1. 1111
2. 1010
3. 1100
4. 0011
5. 0000

12. In Figure 7, if the current state is $Q_3Q_2Q_1Q_0=0101$, then after the next positive edge of the **clock** signal the new state will be:

1. 0110
2. 1111
3. 1011
4. 1010
5. 1110

 


Figure 7- Circuit for question 12.

Note for question 12: Because NOT all the flip-flops' clock inputs share the same **clock** signal, it is considered that the new state value will be observed only when all the flip-flops' outputs have become stable, i.e., after *all* the events triggered by the positive edge of the **clock** signal have been completed.

 


Figure 8 - Circuit for question 13 (it is assumed that after power up the state is 000).

13. The periodic sequence $Q_2Q_1Q_0$ generated by the circuit shown in Figure 8 is:

1. 000,110,001,111
2. 000,101,010,111
3. 000,100,001,111
4. 000,110,011,111
5. none of the above

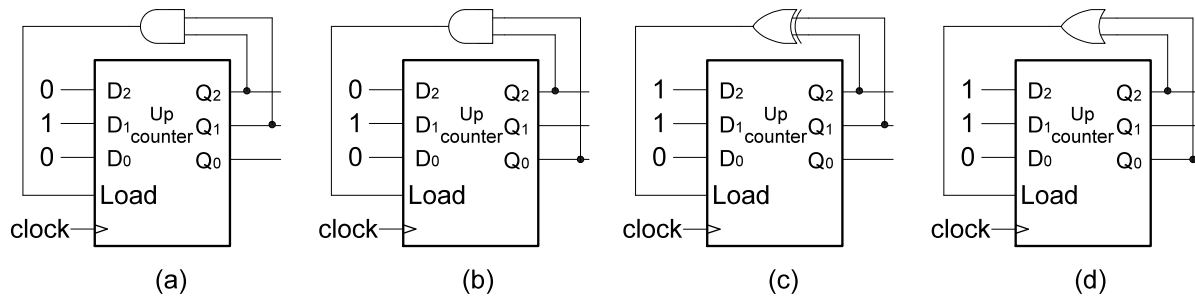


Figure 9 - Circuits for question 14 (it is assumed that after power up the state is 010).

14. Using a 3-bit synchronous up counter with parallel load capability (Q_2 and D_2 are the most significant bits) we can generate a counting sequence 2, 3, 4, 5, 6 using the circuit shown in:

1. Figure 9(a)
2. Figure 9(b)
3. Figure 9(c)
4. Figure 9(d)
5. none of the above

15. Which of the circuits shown in Figure 10 (see next page) are equivalent?

1. Figure 10(a) and Figure 10(c)
2. Figure 10(a) and Figure 10(d)
3. Figure 10(b) and Figure 10(c)
4. Figure 10(b) and Figure 10(d)
5. none of the above


 


Figure 10 - Circuits for question 15.

Present State	Next State	Use this area for the truth tables of the flip-flops' inputs
000	010	
001	101	
010	011	
011	001	
100	000	
101	111	
110	100	
111	110	

(a)

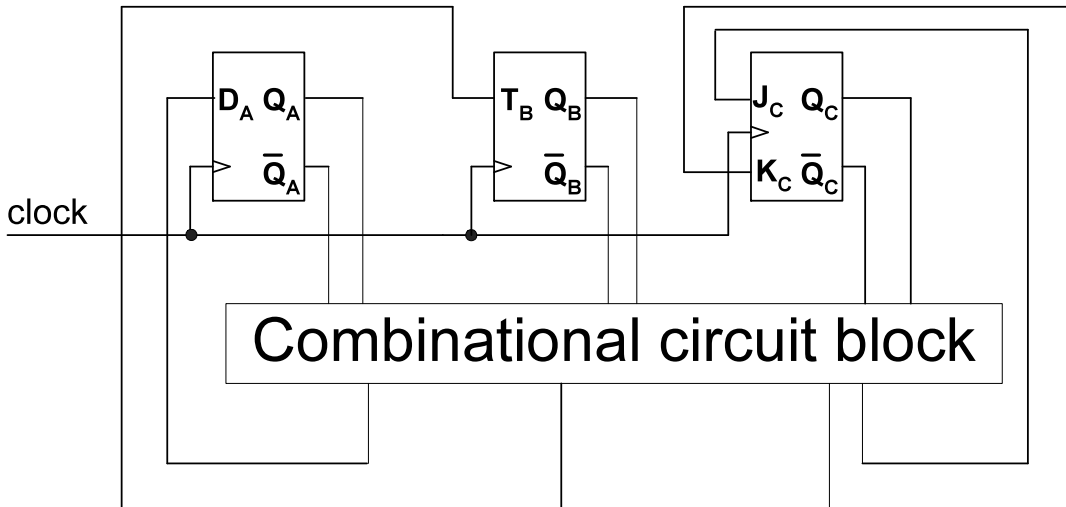

(b)

Figure 11 - State table and circuit for questions 16, 17 and 18. Note, Q_A is the most significant bit. Tip: fill in the truth tables and use K-maps for logic minimization.

 


Figure 12 - Circuit implementations for questions 16, 17 and 18.

16. Consider the state transition table of a sequential circuit shown in Figure 11(a) (see previous page). If in our technology library we have only one **JK** flip-flop, one **D** flip-flop and one **T** flip-flop, then a generic implementation is shown Figure 11(b) (see previous page). Based on the state transition table and circuit topology shown in Figure 11, the logic function, which drives the *input D_A of the leftmost flip-flop from Figure 11(b)* is shown in:

1. Figure 12(a)
2. Figure 12(b)
3. Figure 12(c)
4. Figure 12(d)
5. Figure 12(e)

17. Consider the state transition table of a sequential circuit shown in Figure 11(a) (see previous page). If in our technology library we have only one **JK** flip-flop, one **D** flip-flop and one **T** flip-flop, then a generic implementation is shown Figure 11(b) (see previous page). Based on the state transition table and circuit topology shown in Figure 11, the logic function, which drives the *input T_B of the center flip-flop from Figure 11(b)* is shown in:

1. Figure 12(a)
2. Figure 12(b)
3. Figure 12(c)
4. Figure 12(d)
5. Figure 12(e)

18. Consider the state transition table of a sequential circuit shown in Figure 11(a) (see previous page). If in our technology library we have only one **JK** flip-flop, one **D** flip-flop and one **T** flip-flop, then a generic implementation is shown Figure 11(b) (see previous page). Based on the state transition table and circuit topology shown in Figure 11, the logic function, which drives the *input K_C of the rightmost flip-flop from Figure 11(b)* is shown in:

1. Figure 12(a)
2. Figure 12(b)
3. Figure 12(c)
4. Figure 12(d)
5. Figure 12(e)

 


Figure 13 - Circuit for question 19.

19. Consider the sequential circuit shown in Figure 13. Consider the following state assignment: **A** stands for $Q=0$, **B** stands for $Q=1$. The state transition diagram for the circuit from Figure 13 is shown in:

1. Figure 14(a)
2. Figure 14(b)
3. Figure 14(c)
4. Figure 14(d)
5. none of the above

 


Figure 14 - State transition diagrams for question 19.

 


Figure 15 - Circuit for question 20.

20. Consider the sequential circuit shown in Figure 15. Consider the following state assignment: **A** stands for $Q=0$, **B** stands for $Q=1$. The state transition diagram for the circuit from Figure 15 is shown in:

1. Figure 16(a)
2. Figure 16(b)
3. Figure 16(c)
4. Figure 16(d)
5. none of the above

 


Figure 16 - State transition diagrams for question 20.

- THE END -