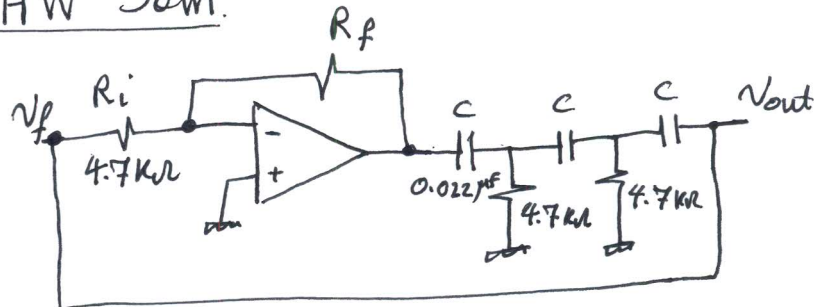


11) R_f ??, for oscillation ; f_r ??



$$\therefore A_{cl} = \frac{R_f}{R_i}$$

$$\therefore R_f = R_i A_{cl}$$

$$\therefore \text{for oscillation: } A_{cl} B = 1 \quad ; \quad B = \frac{1}{29} = \frac{V_f}{V_{out}}$$

$$\therefore A_{cl} = \frac{1}{B} = 29$$

$$\therefore R_f = 4.7k\Omega \times 29$$

$$\therefore R_f = 136.3k\Omega$$


$$\therefore f_r = \frac{1}{2\pi\sqrt{6}R_iC} = \frac{1}{2\pi\sqrt{6} \times 4.7 \times 10^3 \times 0.022 \times 10^{-6}}$$

$$\therefore f_r \approx 628.4 \text{ Hz}$$

↑ phase-shift oscillat -or

12) Type of oscillator ??, f_r ??

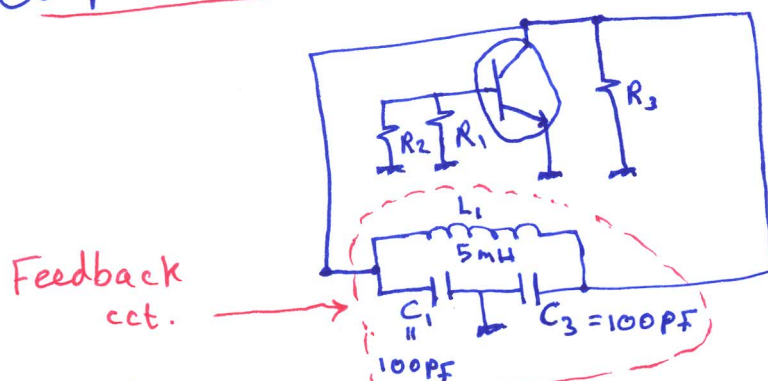a) Colpitts Oscillator, as for ac-analysis we can redraw cct. as follows



where, C_2 & C_4 are almost O.C.

$$\therefore f_o = \frac{1}{2\pi\sqrt{L_1 C_T}}$$


$$; \quad C_T = \frac{C_1 C_3}{C_1 + C_3} = \frac{100 \text{ pF} \times 1000 \text{ pF}}{1100 \text{ pF}} = 90.91 \text{ pF}$$

$$\therefore f_o = \frac{1}{2\pi\sqrt{5 \times 10^{-3} \times 90.91 \times 10^{-12}}}$$

$$\approx 236.1 \text{ KHz}$$

$$\therefore f_o = 236.1 \text{ KHz}$$

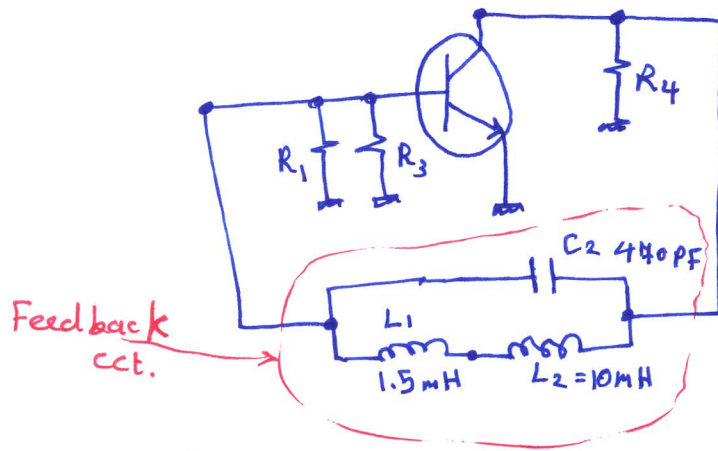b) Hartley oscillator, as the cct. can be drawn, in ac-analysis, as follows:




$$\therefore f_o = \frac{1}{2\pi\sqrt{L_T C_2}} \quad ; \quad L_T = L_1 + L_2 = 1.5 + 10 = 11.5 \text{ mH}$$

$$\therefore f_o = \frac{1}{2\pi\sqrt{11.5 \times 10^{-3} \times 440 \times 10^{-12}}} \approx 68.5 \text{ KHz}$$

$$\therefore f_o = 68.5 \text{ KHz}$$

13 $A_v = ??$ for sustained oscillation.

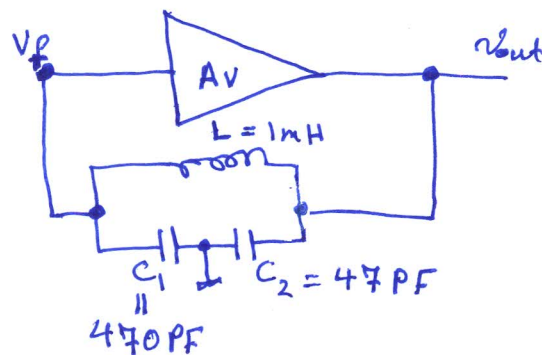The given Colpitts oscillator is equivalent to:



of attenuation, $B = \frac{-C_2}{C_1} = \frac{-47 \text{ pF}}{470 \text{ pF}} = -0.1$

To have oscillation :

$$A_{cl} = A_v B = 1 \quad \therefore A_v = \frac{1}{B} = \frac{1}{-0.1}$$

$$\therefore A_v = -10$$