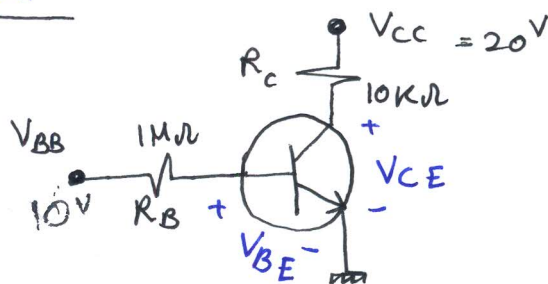


# Ch.5 HW Soln.

[6]

$$I_B = 20 \mu A, \beta_{DC} = 50$$

$$V_{BB} = ?, \text{ Q-point: } V_{CE}, I_c = ??$$



$$\therefore V_{BB} = V_{BE} + I_B R_B$$

$$= 0.7 + 20 \times 10^{-6} \times 1 \times 10^6$$

$$\therefore V_{BB} = 20.7 \text{ V}$$

$$\therefore I_c = \beta_{DC} I_B = 50 \times 20 \mu A = 1000 \mu A$$

$$\therefore I_c = 1 \text{ mA}$$

$$\therefore V_{CE} = V_{CC} - I_c R_c$$

$$= 20 - 1 \times 10^{-3} \times 10 \times 10^3$$


$$\therefore V_{CE} = 10 \text{ V}$$

[7]

$$V_{BB} = V_{CC} = 10, I_c = 5 \text{ mA}, V_{CE} = 4 \text{ V}, \beta_{DC} = 100$$

$$R_B? R_c? P_{min}?$$

Assume a base-biased-transistor circuit:

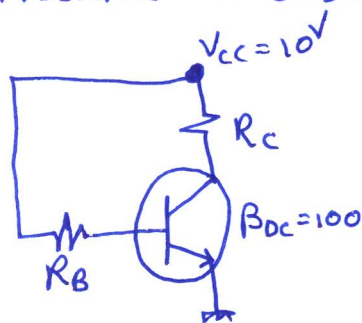

$$\therefore V_{CE} = V_{CC} - I_c R_c$$

$$\therefore R_c = \frac{V_{CC} - V_{CE}}{I_c} = \frac{10 - 4}{5 \times 10^{-3}}$$

$$\therefore R_c = 1.2 \text{ k}\Omega$$

$$\therefore V_{BB} = V_{BE} + I_B R_B = V_{BE} + \frac{I_c}{\beta_{DC}} R_B$$

$$\therefore R_B = \beta_{DC} \frac{V_{CC} - V_{BE}}{I_c} = 100 \frac{10 - 0.7}{5 \times 10^{-3}}$$

$$\therefore R_B = 186 \text{ k}\Omega$$

$$\therefore \text{minimum diss Power} = P_{min} = V_{CE} I_c = 4 \text{ V} \times 5 \text{ mA}$$

$$\therefore P_{min} = 20 \text{ mW}$$


8

$$\therefore I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{8V}{390\Omega}$$

$$\therefore I_{C(sat)} = 20.5 \text{ mA}$$

$$\therefore V_{BB} = V_{BE} + I_B R_B$$
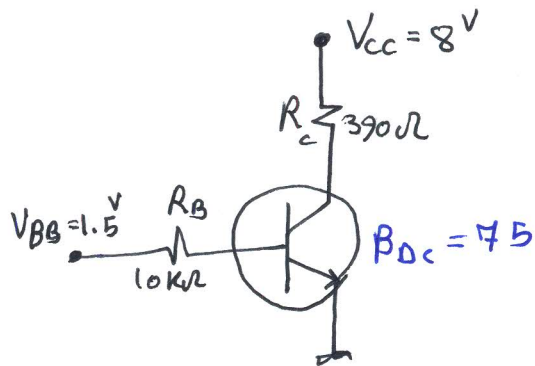
$$\therefore I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{1.5 - 0.7}{10k} = 0.08 \text{ mA} = 80 \mu\text{A}$$



if transistor were in linear region:-

$$I_C = \beta_{DC} I_B = 75 \times 80 \mu\text{A} = 6000 \mu\text{A}$$

$$\therefore I_C = 6 \text{ mA}$$


$$\text{as } 0 < 6 \text{ mA} < I_{C(sat)} = 20.5$$

cut-off  $\uparrow$  sat.  $\uparrow$

$\therefore$  The transistor is biased in linear region

12  $R_{2|min}$  ?? , for saturation
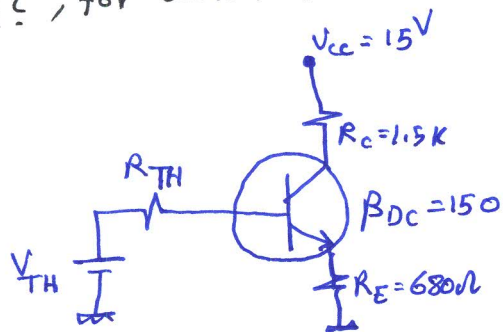
$$R_{TH} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




$$V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{V_{CC}}{R_1} \left( \frac{R_1 R_2}{R_1 + R_2} \right) = V_{CC} \frac{R_{TH}}{R_1}$$

$$\therefore V_{TH} = I_C R_E + V_{BE} + I_B R_{TH}$$

$$\therefore \frac{V_{CC}}{R_1} R_{TH} = I_C R_E + V_{BE} + \frac{I_C}{\beta_{DC}} R_{TH}$$

$$\therefore R_{TH} \left( \frac{V_{CC}}{R_1} - \frac{I_C}{\beta_{DC}} \right) = I_C R_E + V_{BE}$$
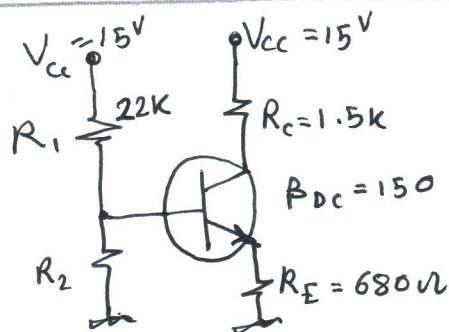
$$\text{or } R_{TH} = \frac{I_C R_E + V_{BE}}{\frac{V_{CC}}{R_1} - \frac{I_C}{\beta_{DC}}}$$



$$\therefore I_{E(sat)} = \frac{V_{CC}}{R_C + R_E} = \frac{15}{1.5 \times 10^3 + 680} \approx 6.88 \text{ mA} \quad (3)$$

$$\therefore R_{TH} = \frac{6.88 \times 10^{-3} \times 680 + 0.7}{\frac{15}{22 \times 10^3} - \frac{6.88 \times 10^{-3}}{150}}$$

$$\therefore R_{TH} \approx 8.457 \text{ k}\Omega$$

$$\therefore R_{TH} = R_1 \parallel R_2 \quad \therefore \frac{1}{R_{TH}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\therefore R_2 = \frac{1}{\frac{1}{R_{TH}} - \frac{1}{R_1}} = \frac{1}{\frac{1}{8.457 \text{ k}} - \frac{1}{22 \text{ k}}}$$


$$\therefore R_2|_{\min} \approx 13.74 \text{ k}\Omega$$

[13]  $I_C$  ?  $V_{CE}$  ?

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2}{22 + 2} \times 15$$

$$\therefore V_{TH} = 1.25 \text{ V}$$
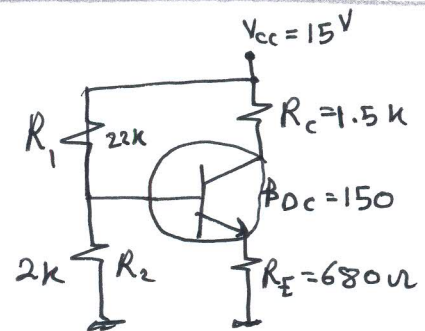
$$R_{TH} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{2 \times 22}{22 + 2} = \frac{11}{6} \text{ k}\Omega$$



$$\therefore V_{TH} = I_E R_E + V_{BE} + I_B R_{TH}$$

$$\approx I_C R_E + V_{BE} + I_C R_{TH} / \beta_{DC}$$

$$\therefore I_C = \frac{V_{TH} - V_{BE}}{R_E + \frac{R_{TH}}{\beta_{DC}}} = \frac{1.25 - 0.7}{680 + \frac{11/6 \times 10^3}{150}}$$

$$\therefore I_C \approx 794.5 \mu\text{A}$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$= 15 - 794.5 \times 10^{-6} (1.5 \times 10^3 + 680)$$

$$\therefore V_{CE} \approx 13.27 \text{ V}$$

17) a)  $V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{-12 \times 5.6K}{33K + 5.6K} \approx -1.74V$

$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{33K \times 5.6K}{38.6K} \approx 4.79K\Omega$

$V_{TH} = -I_B R_{TH} - V_{EB} - I_E R_E$

$\approx -\frac{I_C}{\beta_{DC}} R_{TH} - V_{EB} - I_C R_E$

$\therefore I_C = \frac{-V_{TH} - V_{EB}}{R_E + \frac{R_{TH}}{\beta_{DC}}} = \frac{1.74 - 0.7}{560 + \frac{4.79 \times 10^3}{150}} \approx 1.76 \text{ mA}$

$\therefore I_C = 1.76 \text{ mA}$


$V_{CE} = V_C - V_E = (V_{CC} + I_C R_C) - (-I_C R_E) = V_{CC} + I_C (R_C + R_E)$

$= -12 + 1.76 \times 10^{-3} (1.8 \times 10^3 + 560)$

$\therefore V_{CE} = -7.85V$

b)  $P_{D(min)} = I_C V_{CE} = |I_C V_{CE}| = |1.76 \text{ mA} \times -7.85|$

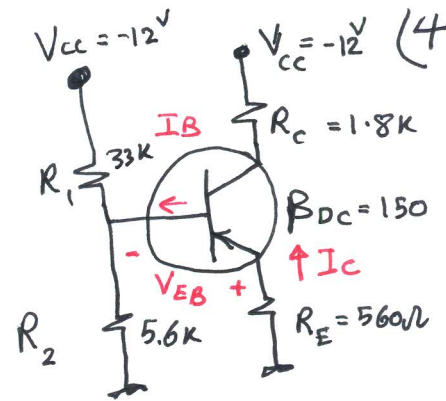$\therefore P_{D(min)} = 13.81 \text{ mW}$



23)  $I_C, V_{CE} ??$

$V_{EE} = I_E R_E + V_{EB} + I_B R_B$

$\approx I_C R_E + V_{EB} + I_C \frac{R_B}{\beta_{DC}}$

$\therefore I_C = \frac{V_{EE} - V_{EB}}{R_E + \frac{R_B}{\beta_{DC}}} = \frac{10 - 0.7}{470 + \frac{10 \times 10^3}{100}}$


$\therefore I_C \approx 16.32 \text{ mA}$

$V_{CE} = (V_{CC} + I_C R_C) - (-I_C R_E + V_{EE})$

$= V_{CC} - V_{EE} + I_C (R_C + R_E)$

$= -10 - (10) + 16.32 \times 10^{-3} (330 + 470)$


$\therefore V_{CE} = -6.94V$

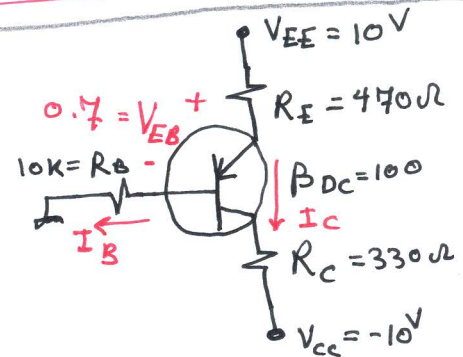

24  $V_B?$ ,  $V_C?$ ,  $I_C?$

as  $V_{BE} = 0.7$ ,  $V_E = 0V$
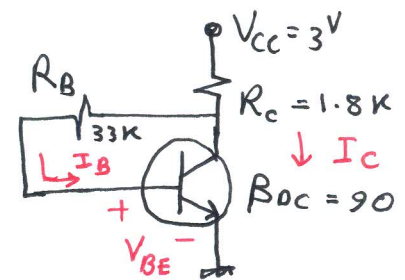
$$\therefore V_B = V_{BE} - V_E = \underline{0.7V}$$



$$\begin{aligned} \therefore V_{CC} &= (I_C + I_B)R_C + I_B R_B + V_{BE} \\ &\approx I_C R_C + \frac{I_C}{\beta_{DC}} R_B + V_{BE} \end{aligned}$$

$$\therefore I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}} = \frac{3 - 0.7}{1.8 \times 10^3 + \frac{33 \times 10^3}{90}}$$

$$\therefore I_C \approx 1.06 \text{ mA}$$

$$\therefore V_C = V_{CE} = V_{CC} - (I_C + I_B)R_C$$

$$\approx V_{CC} - I_C R_C$$

$$= 3 - 1.06 \times 10^{-3} \times 1.8 \times 10^3$$

$$\therefore V_C = 1.09V$$