

Ch. 6 HW Soln

13

DC-analysis:

$$a) V_{TH} = \frac{R_2 V_{CC}}{R_1 + R_2} \approx 3.66 \text{ V}$$

$$R_{TH} = R_1 // R_2 \approx 9.56 \text{ k}\Omega$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta_{DC}} = \frac{3.66 - 0.7}{1 \times 10^3 + \frac{9.56 \times 10^3}{45}}$$

$$\therefore I_E \approx 2.63 \text{ mA}$$


$$b) V_E = I_E R_E \quad \therefore V_E = 2.63 \text{ V}$$

$$c) V_B = V_{BE} + V_E = 0.7 + 2.63 \quad \therefore V_B = 3.33 \text{ V}$$

$$d) I_C \approx I_E = 2.63 \text{ mA} \quad \therefore V_C = 9.32 \text{ V}$$

$$e) V_C = V_{CC} - I_C R_C \quad \therefore V_{CE} = 6.69 \text{ V}$$

$$f) V_{CE} = V_C - V_E$$

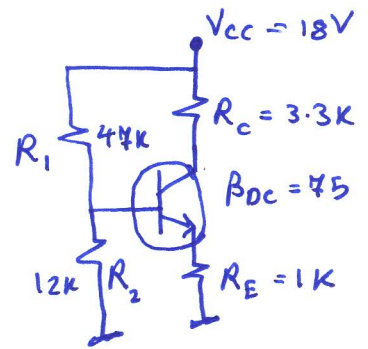

DC-circuit
"all c's are o.c."

14

AC-analysis:-

$$a) \therefore R_{in(base)} = \beta_{ac} r_e'$$

$$\text{as } r_e' = \frac{25 \text{ mV}}{I_E} = \frac{25 \times 10^{-3}}{2.63 \times 10^{-3}} \approx 9.51 \Omega$$

$$\therefore R_{in(base)} = 40 \times 9.51 = 665.7 \Omega$$


$$b) R_{in(tot)} = R_{TH} // R_{in(base)}$$

$$= \frac{9.56 \times 10^3 \times 665.7}{9.56 \times 10^3 + 665.7}$$

$$c) A_v = \frac{R_C // R_L}{r_e'} = \frac{33 \text{ k} // 10 \text{ k}}{9.51 \Omega}$$

$$d) A_i = \beta_{ac} = 40, \quad e) A_p = A_v A_i = 260.9 \times 40$$

$$\therefore A_p = 18263$$

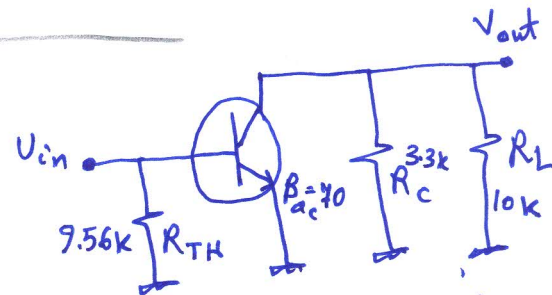

AC-circuit
"all c's & dc-supplies, or S.C. are ac-grounds"

$$\therefore R_{in(tot)} \approx 622.4 \Omega$$

$$\therefore A_v = 260.9$$

15

$$R_s = 600 \Omega, V_{in} = 12 \mu V \text{ (rms)}$$

$$A_v = ??, V_{out} ??, \theta ??$$

$$\therefore \text{Attenuation} = \frac{V_{in}}{V_b} = \frac{R_s + R_{in(tot)}}{R_{in(tot)}} = \frac{600 + 622.4}{622.4} \approx 1.964$$

$$\therefore A_v' = \frac{A_v}{\text{Attenuation}} = \frac{260.9}{1.964} = 132.8$$

$$\therefore A_v' = 132.8$$

$$\therefore V_{out|ac} = A_v' V_{in}$$

$$\therefore V_{out|ac} = 1.594 \text{ mV (rms)}$$

$$V_{out|dc} = V_C = 9.32 \text{ V}$$

$$\text{Phase shift, } \theta = 180^\circ$$

20

$$\therefore A_v = \frac{R_E}{r_e' + R_E}; r_e' = \frac{25 \text{ mV}}{I_E}$$

dc-analysis:

$$R_{TH} = R_1 // R_2 \approx 3.2 \text{ k}\Omega$$


$$V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2} \approx 1.76 \text{ V}$$

$$\text{as, } V_{TH} = \frac{I_E}{\beta_{DC}} R_{TH} + V_{BE} + I_E R_E$$

$$\therefore I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta_{DC}} = \frac{1.76 - 0.7}{1\text{k} + \frac{3.2\text{k}}{90}} \approx 1.024 \text{ mA}$$

$$\therefore A_v = \frac{1 \times 10^3}{\frac{25 \times 10^{-3}}{1.024 \times 10^{-3}} + 1 \times 10^3} \approx 0.976$$

$$\therefore A_v = 0.976$$

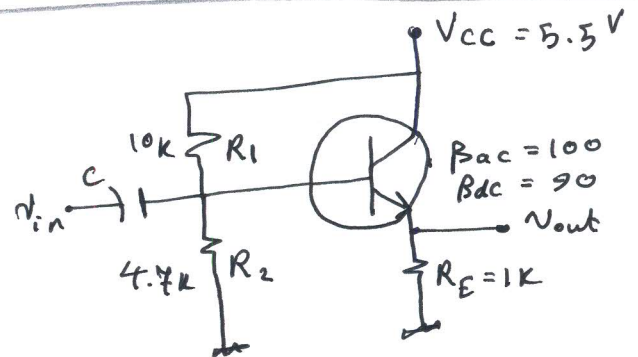

$$[21] R_{in(tot)} = ?, V_{out|dc} = ?$$

$$V_{out|dc} = V_E = I_E R_E = 1.024 \text{ mA} \times 1\text{k}$$

$$\therefore V_{out|dc} = 1.024 \text{ V}$$

$$R_{in(tot)} = R_{TH} // R_{in(base)}$$

$$R_{in(base)} = \beta_{ac} (r_e' + R_E) = 100 \left(\frac{25}{1.024} + 1 \times 10^3 \right) = 102.4 \text{ k}\Omega$$

$$\therefore R_{in(tot)} \approx 3.1 \text{ k}\Omega$$

22

if $R_L < \infty$, A_v increase or decreases??

(3)

$$\therefore A_v = \frac{R_E \parallel R_L}{R_E \parallel R_L + r_e'} = \frac{\frac{R_E R_L}{R_E + R_L}}{\frac{R_E R_L}{R_E + R_L} + r_e'}$$

$$A_v = \frac{R_E R_L}{R_E R_L + R_E r_e' + R_L r_e'}$$

$$\therefore A_v = \frac{R_E}{R_E + r_e' + \frac{R_E r_e'}{R_L}}$$

$\therefore$ as $R_L \downarrow$, denominator (A_v) $\uparrow$, as a result $A_v \downarrow$

if R_L is "o.c" $\rightarrow A_v = \frac{R_E}{R_E + r_e'}$

as $R_L < \infty \rightarrow A_v < \frac{R_E}{R_E + r_e'} = A_{v1}$

23

$A_v = 0.9$, $R_L = ??$

$$\therefore A_v = \frac{R_E}{R_E + r_e' + \frac{R_E r_e'}{R_L}}$$

$$\therefore \frac{R_E r_e' A_v}{R_L} = R_E - A_v (R_E + r_e')$$

$$\therefore R_L = \frac{R_E r_e' A_v}{R_E - A_v (R_E + r_e')} ; r_e' = \frac{25 \text{ mV}}{1.024 \text{ mA}} = 24.4 \Omega$$

$$= \frac{1 \text{ k} \times 24.4 \Omega \times 0.9}{1 \text{ k} - 0.9 (1 \text{ k} + 24.4)}$$

$$= \frac{21960 \Omega^2}{78.04 \Omega}$$

$$\therefore R_L = 281.4 \Omega$$

a) i) dc-analysis: "for both Q_1 & Q_2 ccts"

$$V_{TH} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{8.2K * 15}{8.2K + 33K} \approx 2.99V$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{33K * 8.2K}{33K + 8.2K} \approx 6.54K\Omega$$


$$I_E = \frac{V_{TH} - V_{BE}}{R_E + \frac{R_{TH}}{\beta_{DC}}} = \frac{2.99 - 0.7}{1K + \frac{6.54K}{175}} = 2.21mA$$

$$r_e' = \frac{25mV}{I_E} = \frac{25mV}{2.21mA} = 11.3\Omega$$

ii) ac-analysis:

$$A_{V_1} = \frac{R_C \parallel R_{TH} \parallel R_{in(base)}|_{Q_2}}{r_e'}$$

$$R_{in(base)}|_{Q_2} = \beta_{ac} r_e' = 175 * 11.3 = 1.98K\Omega$$

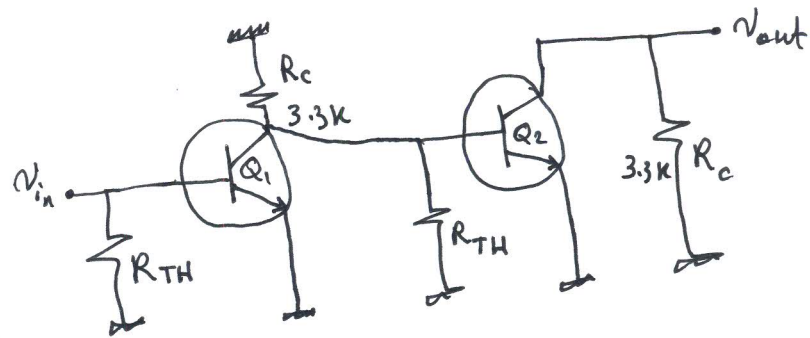

$$\therefore A_{V_1} = \frac{1}{\frac{1}{33K} + \frac{1}{6.54K} + \frac{1}{1.98K}} \cdot \frac{1}{11.3}$$

$$\therefore A_{V_1} \approx 92.16$$

$$\therefore A_{V_1} \approx 92.16$$

$$A_{V_2} = \frac{R_C}{r_e'} = \frac{3.3K}{11.3\Omega}$$

$$\therefore A_{V_2} = 292.04$$

b) $A_{V(tot)} = A_{V_1} * A_{V_2} = 26914.41$

c) $A_{V|dB} = 20 \log_{10}(A_V)$

$$\therefore A_{V_1|dB} = 39.3dB$$

$$A_{V_2|dB} = 49.3dB$$

$$A_{V(tot)|dB} = 20 \log(A_{V(tot)}) = A_{V_1|dB} + A_{V_2|dB} = 88.6dB$$

32


$$R_S = 75 \Omega, V_{in} = 50 \mu V, R_L = 18 k\Omega$$

5

a)

$$A_{V_1} = \frac{R_C \parallel R_{TH} \parallel R_{in(base)}|_{Q_2}}{r_e'}$$

$$= 92.16$$

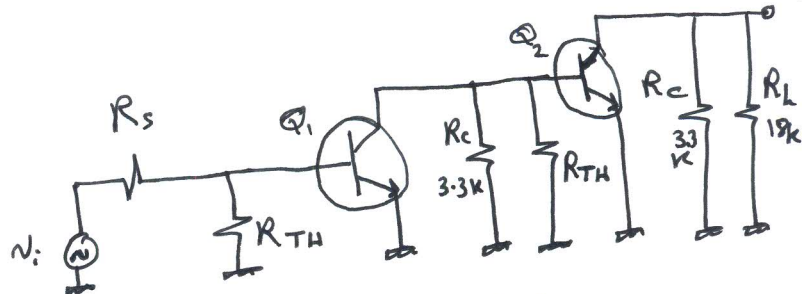

$$A'_{V_1} = \frac{A_{V_1}}{\text{Attenuation}} \quad \text{Attenuation} = \frac{R_S + (R_{TH} \parallel R_{in(base)}|_{Q_1})}{R_{TH} \parallel R_{in(base)}|_{Q_1}}$$

$$\therefore \text{Attenuation} = \frac{75 \Omega + (6.54 k \parallel 1.98 k)}{(6.54 k \parallel 1.98 k)}$$

$$\approx \frac{75 \Omega + 1.52 k}{1.52 k} = 1.049$$

$$\therefore A'_{V_1} = \frac{92.16}{1.049} = \underline{\underline{87.86}}$$

$$A_{V_2} = \frac{R_C \parallel R_L}{r_e'} = \frac{3.3 k \parallel 18 k}{11.3 \Omega} = \underline{\underline{246.79}}$$

$$b) \quad A_{V(tot)} = A'_{V_1} * A_{V_2} = 21682.97$$

$$c) \quad A'_{V_1}|_{dB} = 20 \log(87.86) = \underline{\underline{38.9 \text{ dB}}}$$

$$A_{V_2}|_{dB} = 20 \log(246.79) = \underline{\underline{47.8 \text{ dB}}}$$

$$A_{V(tot)}|_{dB} = 38.9 + 47.8 = \underline{\underline{86.7 \text{ dB}}}$$

33) i) dc-analysis:-

$$V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{12 * 22K}{100K + 22K} = 2.16V$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{100K * 22K}{100K + 22K} \approx 18.03K$$

$$I_{E1} = \frac{V_{TH} - V_{BE}}{R_4 + \frac{R_{TH}}{\beta_{DC}}} = \frac{2.16 - 0.7}{4.7K + \frac{18.03K}{125}}$$

$$\therefore I_{E1} = 301.4 \mu A$$

$$\therefore V_{E1} = I_{E1} R_4 = 301.4 * 10^{-6} * 4.7 * 10^3$$

$$V_{B1} = V_{BE} + V_{E1} = 0.7 + 1.42$$

$$V_{C1} = V_{CC} - I_{C1} R_3$$

$$\approx V_{CC} - I_{E1} R_3 = 12 - 301.4 * 10^{-6} * 22 * 10^3$$

$$\therefore V_{C1} = 5.37V$$

$$V_{B2} = V_{C1} \quad \therefore V_{B2} = 5.37V$$

$$V_{E2} = V_{B2} - V_{BE} = 5.37 - 0.7$$

$$I_{E2} = \frac{V_{E2}}{R_6} = \frac{4.67}{10K} = 467 \mu A$$

$$V_{C2} = V_{CC} - I_{C2} R_5 \approx V_{CC} - I_{E2} R_5 = 12 - 467 * 10^{-6} * 10 * 10^3$$

$$\therefore V_{C2} = 7.33V$$


$$r_{e1}' = \frac{25mV}{I_{E1}} = 82.95 \Omega, \quad r_{e2}' = \frac{25mV}{I_{E2}} = 53.53 \Omega$$

ii) ac-analysis:-

$$A_{V1} = \frac{R_3 \parallel R_{in(base)Q2}}{r_{e1}'} = \frac{R_3 \parallel \beta_{AC} r_{e2}'}{r_{e1}'}$$

$$= \frac{22K \parallel 125 * 53.53}{82.95} = 61.9$$
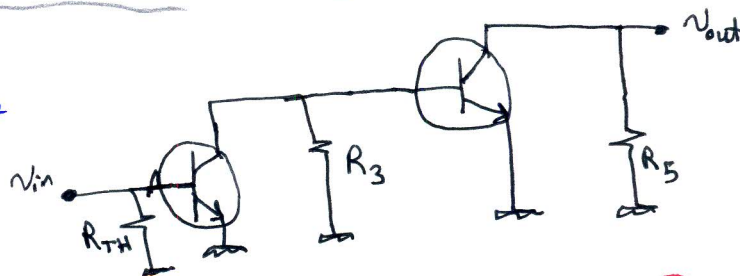
$$A_{V2} = \frac{R_5}{r_{e2}'} = \frac{10K}{53.53 \Omega} = 186.8$$



$$\therefore A_{V1 \text{ tot}} = 11562.9 = 81.3 \text{ dB}$$