

Chapter 4

Bipolar Junction Transistors

Section 4-1 Bipolar Junction Transistor (BJT) Structure

1. Majority carriers in the base region of an *npn* transistor are **holes**.
2. Because of the narrow base region, the minority carriers invading the base region find a limited number of partners for recombination and, therefore, move across the junction into the collector region rather than out of the base lead.

Section 4-2 Basic BJT Operation

3. The base is narrow and lightly doped so that a small recombination (base) current is generated compared to the collector current.
4. $I_B = 0.02I_E = 0.02(30 \text{ mA}) = 0.6 \text{ mA}$
 $I_C = I_E - I_B = 30 \text{ mA} - 0.6 \text{ mA} = 29.4 \text{ mA}$
5. The base must be negative with respect to the collector and positive with respect to the emitter.
6. $I_C = I_E - I_B = 5.34 \text{ mA} - 475 \mu\text{A} = 4.87 \text{ mA}$

Section 4-3 BJT Characteristics and Parameters

7. $\alpha_{DC} = \frac{I_C}{I_E} = \frac{8.23 \text{ mA}}{8.69 \text{ mA}} = 0.947$
8. $\beta_{DC} = \frac{I_C}{I_B} = \frac{25 \text{ mA}}{200 \mu\text{A}} = 125$
9. $I_B = I_E - I_C = 20.5 \text{ mA} - 20.3 \text{ mA} = 0.2 \text{ mA} = 200 \mu\text{A}$
 $\beta_{DC} = \frac{I_C}{I_B} = \frac{20.3 \text{ mA}}{200 \mu\text{A}} = 101.5$
10. $I_E = I_C + I_B = 5.35 \text{ mA} + 50 \mu\text{A} = 5.40 \text{ mA}$
 $\alpha_{DC} = \frac{I_C}{I_E} = \frac{5.35 \text{ mA}}{5.40 \text{ mA}} = 0.99$
11. $I_C = \alpha_{DC}I_E = 0.96(9.35 \text{ mA}) = 8.98 \text{ mA}$

12. $I_C = \frac{V_{R_C}}{R_C} = \frac{5 \text{ V}}{1.0 \text{ k}\Omega} = 5 \text{ mA}$
 $\beta_{DC} = \frac{I_C}{I_B} = \frac{5 \text{ mA}}{50 \mu\text{A}} = 100$
13. $\alpha_{DC} = \frac{\beta_{DC}}{\beta_{DC} + 1} = \frac{100}{101} = 0.99$
14. $I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} = 23 \mu\text{A}$
 $I_C = \beta_{DC} I_B = 200(23 \mu\text{A}) = 4.6 \text{ mA}$
 $I_E = I_C + I_B = 4.6 \text{ mA} + 23 \mu\text{A} = 4.62 \text{ mA}$
 $V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (4.6 \text{ mA})(1.0 \text{ k}\Omega) = 5.4 \text{ V}$
15. I_C = does not change.
 For $V_{CC} = 10 \text{ V}$:
 $V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (4.6 \text{ mA})(1.0 \text{ k}\Omega) = 5.4 \text{ V}$
 For $V_{CC} = 15 \text{ V}$:
 $V_{CE} = 15 \text{ V} - (4.6 \text{ mA})(1.0 \text{ k}\Omega) = 10.7 \text{ V}$
 $\Delta V_{CE} = 10.7 \text{ V} - 5.4 \text{ V} = 5.3 \text{ V}$ increase
16. $I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{4 \text{ V} - 0.7 \text{ V}}{4.7 \text{ k}\Omega} = \frac{3.3 \text{ V}}{4.7 \text{ k}\Omega} = 702 \mu\text{A}$
 $I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{24 \text{ V} - 8 \text{ V}}{470 \Omega} = 34 \text{ mA}$
 $I_E = I_C + I_B = 34 \text{ mA} + 702 \mu\text{A} = 34.7 \text{ mA}$
 $\beta_{DC} = \frac{I_C}{I_B} = \frac{34 \text{ mA}}{702 \mu\text{A}} = 48.4$
17. (a) $V_{BE} = 0.7 \text{ V}$
 $I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{4.3 \text{ V}}{3.9 \text{ k}\Omega} = 1.1 \text{ mA}$
 $I_C = \beta_{DC} I_B = 50(1.1 \text{ mA}) = 55 \text{ mA}$
 $V_{CE} = V_{CC} - I_C R_C = 15 \text{ V} - (55 \text{ mA})(180 \Omega) = 5.10 \text{ V}$
 $V_{CB} = V_{CE} - V_{BE} = 5.10 \text{ V} - 0.7 \text{ V} = 4.40 \text{ V}$
- (b) $V_{BE} = -0.7 \text{ V}$
 $I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{-3 \text{ V} - (-0.7 \text{ V})}{27 \text{ k}\Omega} = \frac{-2.3 \text{ V}}{27 \text{ k}\Omega} = -85.2 \mu\text{A}$
 $I_C = \beta_{DC} I_B = 125(-85.2 \mu\text{A}) = -10.7 \text{ mA}$
 $V_{CE} = V_{CC} - I_C R_C = -8 \text{ V} - (-10.7 \text{ mA})(390 \Omega) = -3.83 \text{ V}$
 $V_{CB} = V_{CE} - V_{BE} = -3.83 \text{ V} - (-0.7 \text{ V}) = -3.13 \text{ V}$

Chapter 4

18. (a) $I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{15 \text{ V}}{180 \Omega} = 83.3 \text{ mA}$
 $I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{3.9 \text{ k}\Omega} = 1.1 \text{ mA}$
 $I_C = \beta_{DC} I_B = 50(1.1 \text{ mA}) = 55 \text{ mA}$
 $I_C < I_{C(sat)}$
 Therefore, the transistor is **not saturated**.

(b) $I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{8 \text{ V}}{390 \Omega} = 20.5 \text{ mA}$
 $I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3 \text{ V} - 0.7 \text{ V}}{27 \text{ k}\Omega} = 85.2 \mu\text{A}$
 $I_C = \beta_{DC} I_B = 125(85.2 \mu\text{A}) = 10.7 \text{ mA}$
 $I_C < I_{C(sat)}$
 Therefore, the transistor is **not saturated**.

19. $V_B = 2 \text{ V}$
 $V_E = V_B - V_{BE} = 2 \text{ V} - 0.7 \text{ V} = 1.3 \text{ V}$
 $I_E = \frac{V_E}{R_E} = \frac{1.3 \text{ V}}{1.0 \text{ k}\Omega} = 1.3 \text{ mA}$
 $I_C = \alpha_{DC} I_E = (0.98)(1.3 \text{ mA}) = 1.27 \text{ mA}$
 $\beta_{DC} = \frac{\alpha_{DC}}{1 - \alpha_{DC}} = \frac{0.98}{1 - 0.98} = 49$
 $I_B = I_E - I_C = 1.3 \text{ mA} - 1.27 \text{ mA} = 30 \mu\text{A}$

20. (a) $V_B = V_{BB} = 10 \text{ V}$
 $V_C = V_{CC} = 20 \text{ V}$
 $V_E = V_B - V_{BE} = 10 \text{ V} - 0.7 \text{ V} = 9.3 \text{ V}$
 $V_{CE} = V_C - V_E = 20 \text{ V} - 9.3 \text{ V} = 10.7 \text{ V}$
 $V_{BE} = 0.7 \text{ V}$
 $V_{CB} = V_C - V_B = 20 \text{ V} - 10 \text{ V} = 10 \text{ V}$
 (b) $V_B = V_{BB} = -4 \text{ V}$
 $V_C = V_{CC} = -12 \text{ V}$
 $V_E = V_B - V_{BE} = -4 \text{ V} - (-0.7 \text{ V}) = -3.3 \text{ V}$
 $V_{CE} = V_C - V_E = -12 \text{ V} - (-3.3 \text{ V}) = -8.7 \text{ V}$
 $V_{BE} = -0.7 \text{ V}$
 $V_{CB} = V_C - V_B = -12 \text{ V} - (-4 \text{ V}) = -8 \text{ V}$

21. For $\beta_{DC} = 100$:
 $I_E = \frac{V_B - V_{BE}}{R_E} = \frac{10 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 930 \mu\text{A}$
 $\alpha_{DC} = \frac{\beta_{DC}}{1 + \beta_{DC}} = \frac{100}{101} = 0.990$
 $I_C = \alpha_{DC} I_E = (0.990)(930 \mu\text{A}) = 921 \mu\text{A}$

For $\beta_{DC} = 150$:

$$I_E = 930 \mu\text{A}$$

$$\alpha_{DC} = \frac{\beta_{DC}}{1 + \beta_{DC}} = \frac{150}{151} = 0.993$$

$$I_C = \alpha_{DC} I_E = (0.993)(930 \mu\text{A}) = 924 \mu\text{A}$$

$$\Delta I_C = 924 \mu\text{A} - 0.921 \mu\text{A} = 3 \mu\text{A}$$

$$22. \quad P_{D(\max)} = V_{CE} I_C$$

$$V_{CE(\max)} = \frac{P_{D(\max)}}{I_C} = \frac{1.2 \text{ W}}{50 \text{ mA}} = 24 \text{ V}$$

$$23. \quad P_{D(\max)} = 0.5 \text{ W} - (75^\circ\text{C})(1 \text{ mW}/^\circ\text{C}) = 0.5 \text{ W} - 75 \text{ mW} = 425 \text{ mW}$$

Section 4-4 The BJT as an Amplifier

$$24. \quad V_{out} = A_v V_{in} = 50(100 \text{ mV}) = 5 \text{ V}$$

$$25. \quad A_v = \frac{V_{out}}{V_{in}} = \frac{10 \text{ V}}{300 \text{ mV}} = 33.3$$

$$26. \quad A_v = \frac{R_C}{r'_e} = \frac{560 \Omega}{10 \Omega} = 56$$

$$V_c = V_{out} = A_v V_{in} = 56(50 \text{ mV}) = 2.8 \text{ V}$$

$$27. \quad I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2.5 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} = 18 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = 250(18 \mu\text{A}) = 4.5 \text{ mA}$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{9 \text{ V} - 4 \text{ V}}{4.5 \text{ mA}} = 1.1 \text{ k}\Omega$$

$$28. \quad \text{(a) DC current gain} = \beta_{DC} = 50$$

$$\text{(b) DC current gain} = \beta_{DC} = 125$$

Chapter 4

Section 4-5 The BJT as a Switch

29. $I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{5 \text{ V}}{10 \text{ k}\Omega} = 500 \mu\text{A}$
 $I_{B(min)} = \frac{I_{C(sat)}}{\beta_{DC}} = \frac{500 \mu\text{A}}{150} = 3.33 \mu\text{A}$
 $I_{B(min)} = \frac{V_{IN(min)} - 0.7 \text{ V}}{R_B}$
 $R_B I_{B(min)} = V_{IN(min)} - 0.7 \text{ V}$
 $V_{IN(min)} = R_B I_{B(min)} + 0.7 \text{ V} = (3.33 \mu\text{A})(1.0 \text{ M}\Omega) + 0.7 \text{ V} = 4.03 \text{ V}$
30. $I_{C(sat)} = \frac{15 \text{ V}}{1.2 \text{ k}\Omega} = 12.5 \text{ mA}$
 $I_{B(min)} = \frac{I_{C(sat)}}{\beta_{DC}} = \frac{12.5 \text{ mA}}{50} = 250 \mu\text{A}$
 $R_{B(min)} = \frac{V_{IN} - 0.7 \text{ V}}{I_{B(min)}} = \frac{4.3 \text{ V}}{250 \mu\text{A}} = 17.2 \text{ k}\Omega$
 $V_{IN(cutoff)} = 0 \text{ V}$

Section 4-6 The Phototransistor

31. $I_C = \beta_{DC} I_A = (200)(100 \mu\text{A}) = 20 \text{ mA}$
32. $I_A = (50 \text{ lm/m}^2)(1 \mu\text{A/lm/m}^2) = 50 \mu\text{A}$
 $I_E = \beta_{DC} I_A = (100)(50 \mu\text{A}) = 5 \text{ mA}$
33. $I_{out} = (0.30)(100 \text{ mA}) = 30 \text{ mA}$
34. $\frac{I_{OUT}}{I_{IN}} = 0.6$
 $I_{IN} = \frac{I_{OUT}}{0.6} = \frac{10 \text{ mA}}{0.6} = 16.7 \text{ mA}$

Section 4-7 Transistor Categories and Packaging

35. See Figure 4-1.

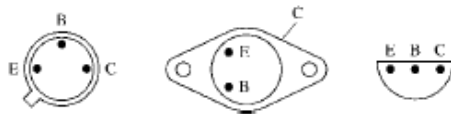


Figure 4-1

36. (a) Small-signal
 (b) Power
 (c) Power
 (d) Small-signal
 (e) RF