

Lecture 2

From Section 2.2 of Textbook


Solve E2.2 – E2.7, 2.11, 2.14,

2.16, 2.18, 2.20

Kirchhoff's Current Law

- * The sum of currents entering a node is zero
- * The sum of currents leaving a node is zero
- * The sum of currents entering a node is equal to the sum of currents leaving the node

Example

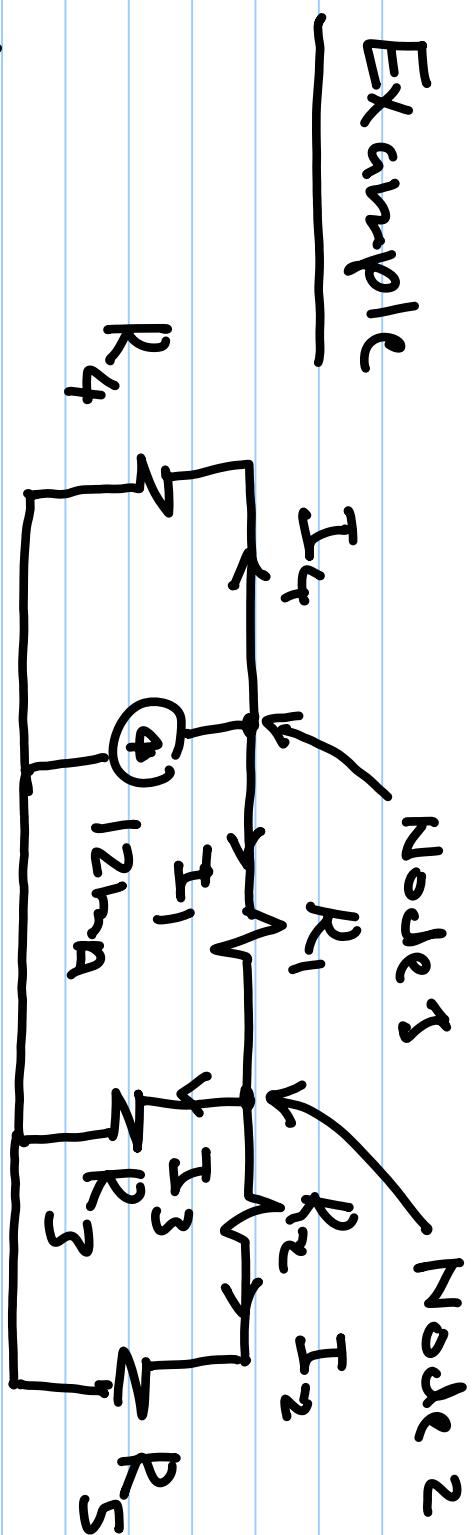

at Node 1

$$12 * 10^{-3} - I_1 - I_4 = 0$$

at Node 2

$$I_1 - I_2 - I_3 = 0$$

or $I_1 + I_4 - 12 * 10^{-3} = 0$
or $I_2 + I_3 = I_1 + I_4$
or $I_1 = I_2 + I_3$

* Currents flowing in are true and Currents flowing out are -ve !

Origin of KCL


* The charge continuity

equation of electromagnetism

states that


$$\oint \mathbf{J} \cdot d\mathbf{s} = -\frac{d}{dt} \iint_{S'} Q_r dv$$

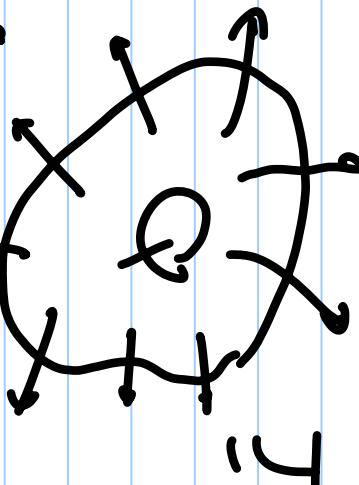$\int \mathbf{J} \cdot d\mathbf{s}$
 S'
 A/m^2
 m^2
 C/m^3



* at sufficiently low frequencies, the RHS is negligible $\rightarrow \oint \mathbf{J} \cdot d\mathbf{s} = 0 \rightarrow$ **Sum of currents leaving $\Delta = 0$**

Example

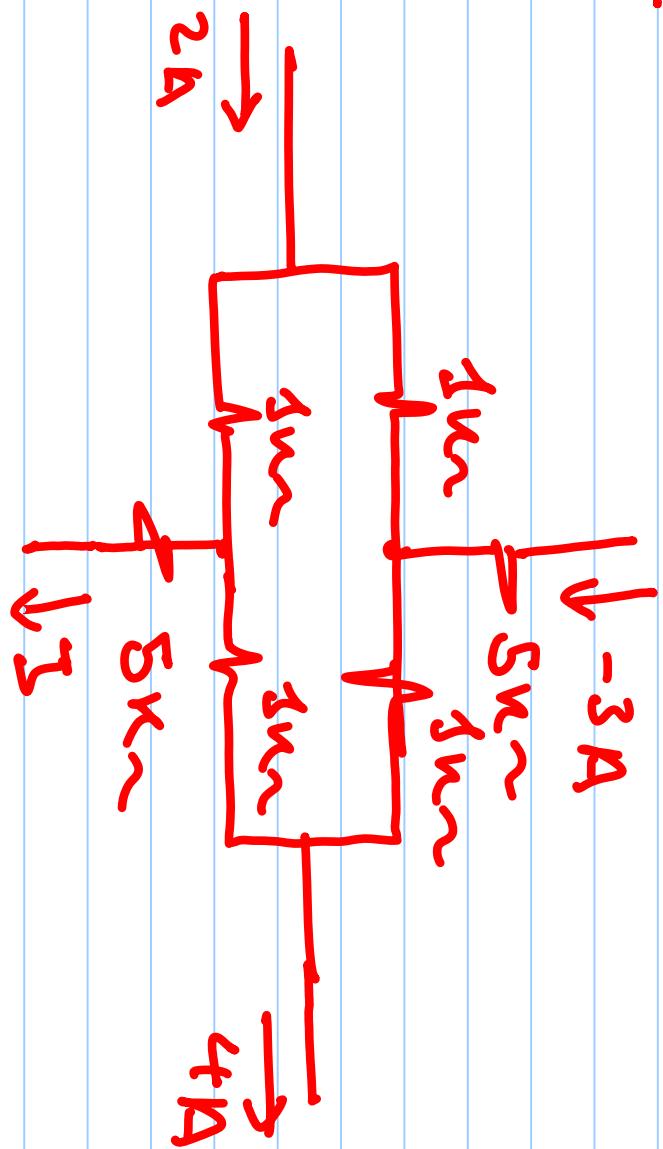


Find the current I in the shown Circuit

Kirchhoff's Voltage Law (KVL)

- * The algebraic sum of the voltages in the clockwise direction of a loop is zero
- * The algebraic sum of the voltages in counter clockwise direction of a loop is zero
- * The algebraic sum of voltages in the cw direction equals the algebraic sum in the ccw direction

Example

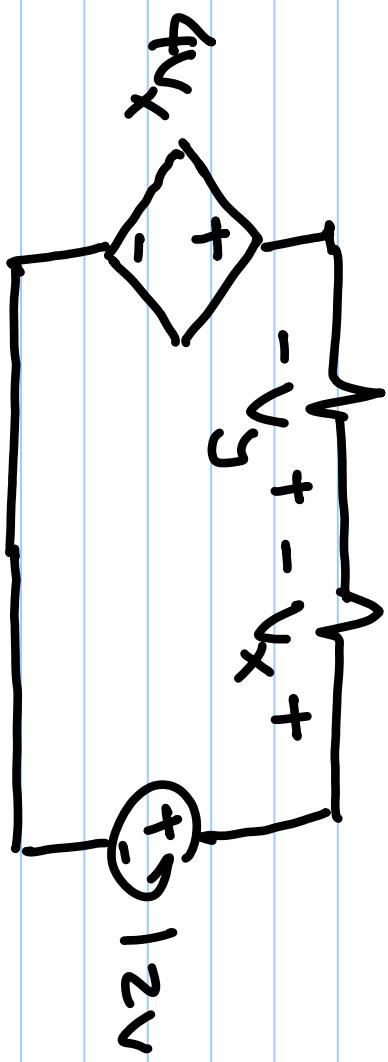

- * CW direction: $V_y + V_x - 12 + 4Vx = 0$
- * CCW direction: $12 - V_x - V_y - 4Vx = 0$
- * Third formulation: $V_x + V_y + 4Vx = 12$

X A Voltage is given w/ the sign if you encounter its low terminal first in that direction!


Origin of KVL

$$* V_{ab} = V_a - V_b = \int_a^b \mathbf{E} \cdot d\ell \quad (\text{E is electric field } \text{V/m}^2)$$

* From Faraday's Law

$$\oint_L \mathbf{E} \cdot d\ell = - \frac{d}{dt} \iint_S \mathbf{B} \cdot d\ell$$


↑
magnetic field

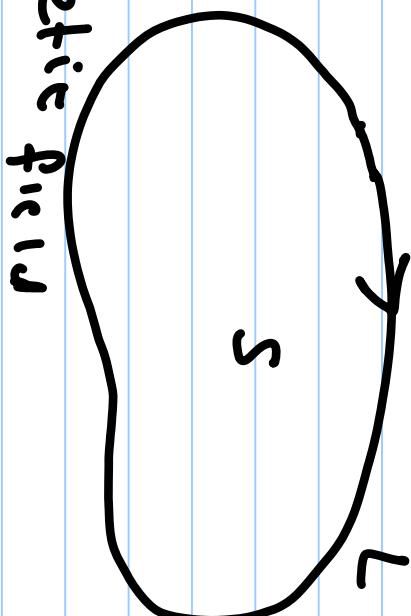


* at sufficiently low frequencies RHS is negligible
 $\Rightarrow \oint_L \mathbf{E} \cdot d\ell = 0 \Rightarrow \text{sum of voltages is zero}$

Example

Find the voltage V_i using KVL

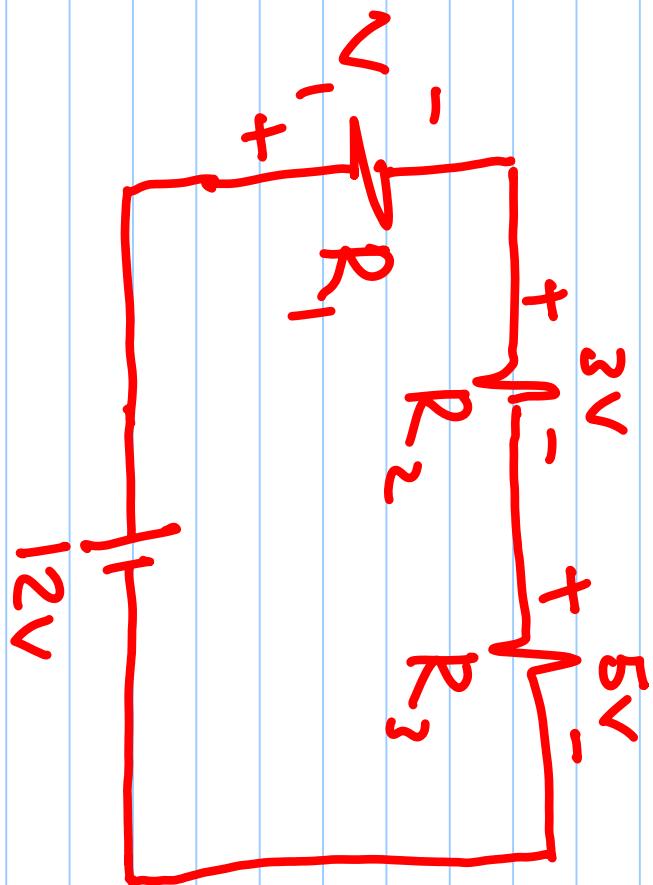


Example

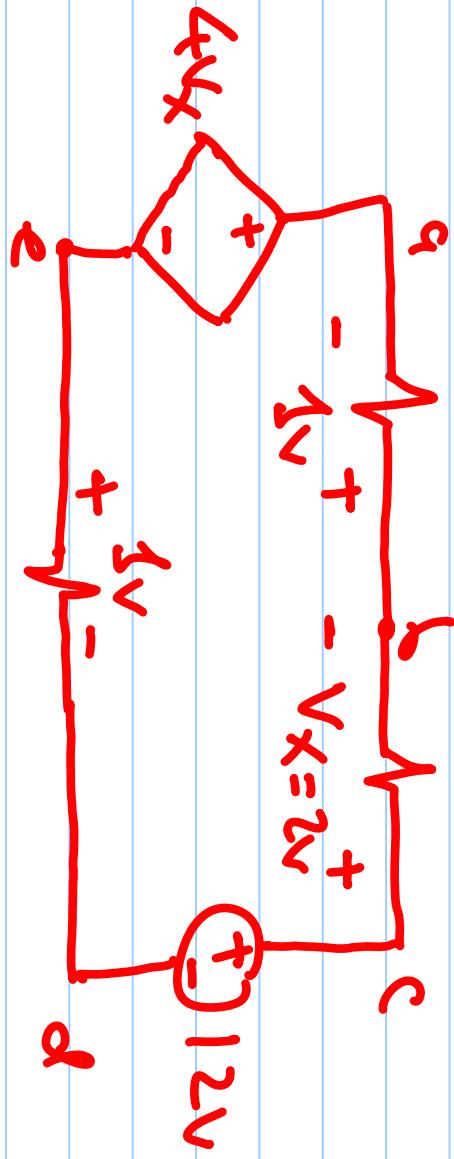

Using KVL find V_{da} and V_{be}

Example

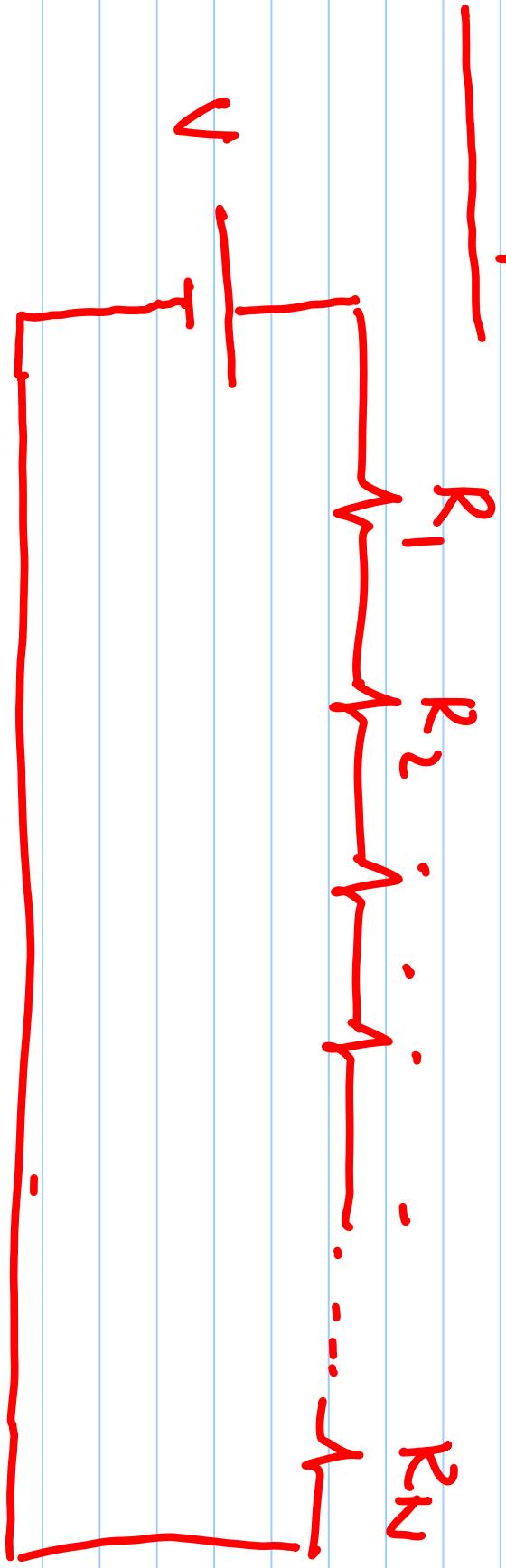

Use Ohm's Law, KCL and KVL

to find the equivalent resistance of the shown series resistor

