

Dr. Mohamed Bakr, EE2C15, 2007

Note Title

9/24/2007

Lecture 8

From Section 3.2 of Textbook

Solve: E3.8, 3.62, 3.64, 3.67,
3.70


Loop analysis

* Loop analysis solves for the current in each loop (mesh) of the circuit

* For each loop, we write KVL to get one equation

* For a circuit with B branches and N nodes, there are $B - N + 1$ linearly independent KVL equations


Example

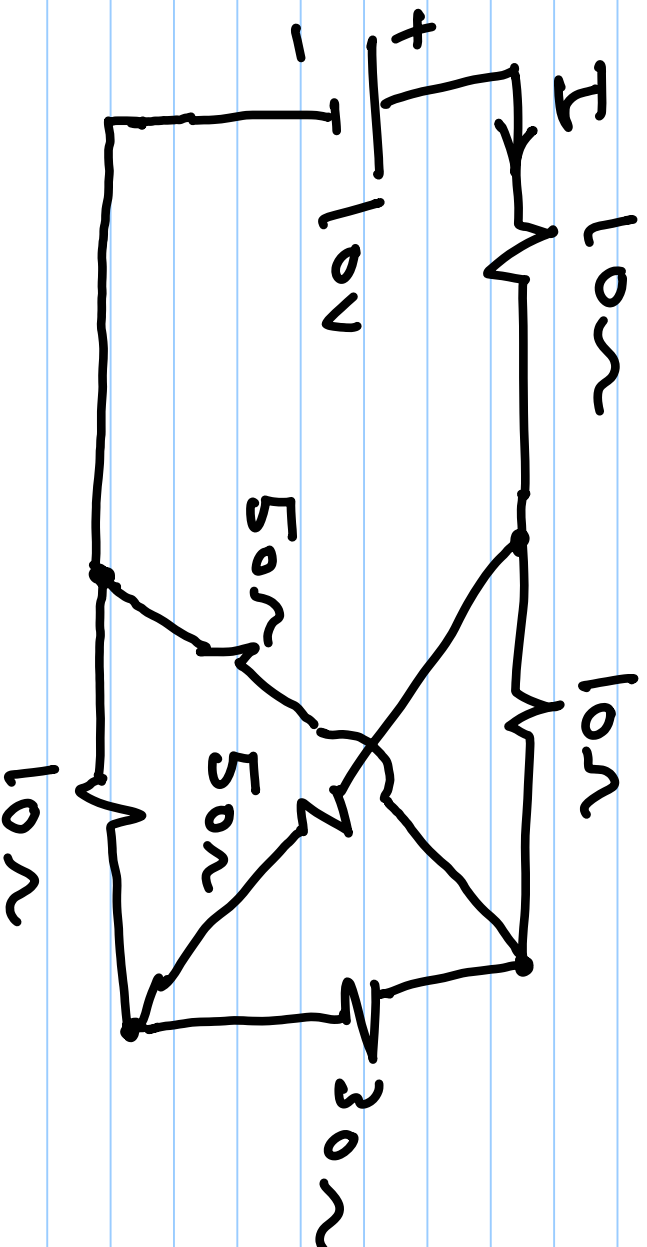

Determine the Current I supplied
by the source

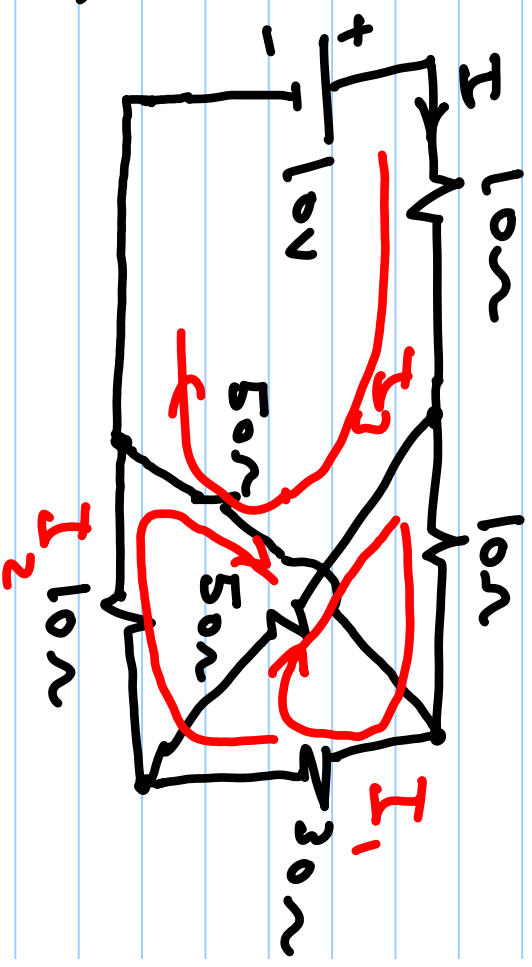Example (Cont'd)


* This circuit contains 4 nodes and 6 branches



* We need $6 - 4 + 1 = 3$ equations to solve for the 3 unknown currents

* We choose these currents to be I_1, I_2 and I_3 in the shown direction

Example (Cont'd)

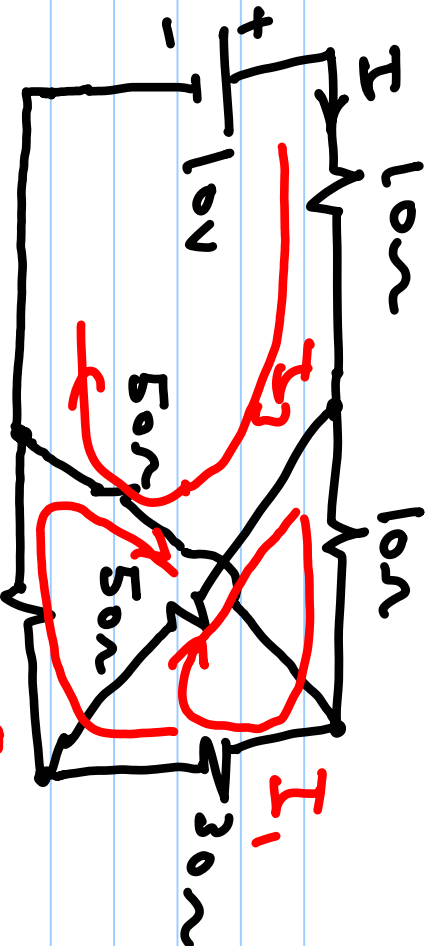

* For loop 3

$$10V = 10I_3 + 50(I_3 - I_1) + 10(I_3 + I_2).$$

$$\Rightarrow -50I_1 + 10I_2 + 70I_3 = 10 \Rightarrow$$

$$-5I_1 + I_2 + 7I_3 = 1 \quad \text{--- (1)}$$

For loop 2: $50I_2 + 30(I_1 + I_2) + 10(I_2 + I_3) = 0$

$$\Rightarrow 3I_1 + 9I_2 + I_3 = 0 \quad \text{--- (2)}$$


Example (Cont'd)

For loop 1, we have -

$$10I_1 + 30(I_1 + I_2)$$

$$+ 50(I_1 - I_3) = 0$$
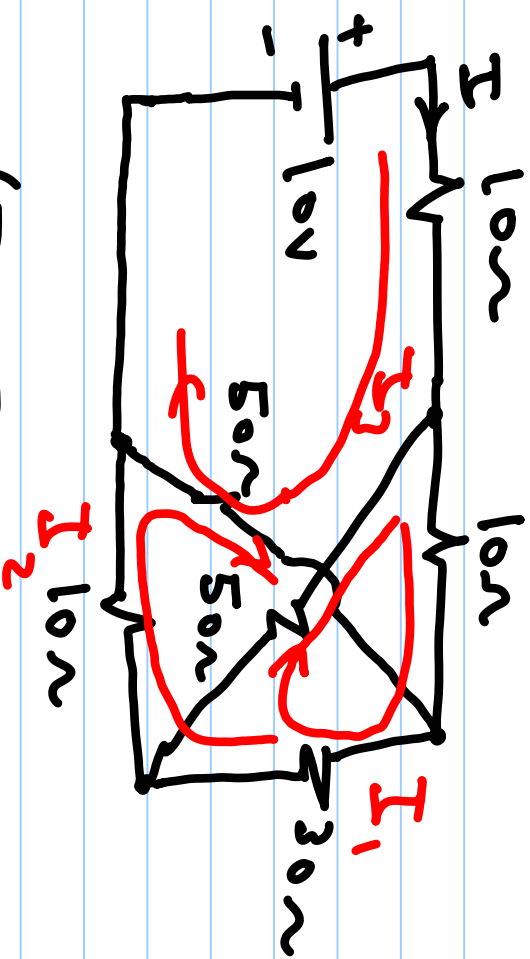
$$9I_1 + 3I_2 - 5I_3 = 0 \quad \text{--- (2)}$$



Example (Cont'd)

$$-5I_1 + I_2 + 7I_3 = 4 \quad (1)$$

$$3I_1 + 9I_2 + 5I_3 = 0 \quad (2)$$

$$9I_1 + 3I_2 - 5I_3 = 0 \quad (3)$$

3 equations in 3 unknowns

Example (Cont'd)


$\textcircled{-5}$	1	7	1
3	9	1	0
9	3	-5	0
<hr/>			
1	$-\frac{1}{5}$	$-\frac{7}{5}$	$-\frac{1}{5}$
0	$\textcircled{\frac{49}{5}}$	$\frac{24}{5}$	$\frac{3}{5}$
0	$\frac{24}{5}$	$\frac{36}{5}$	$\frac{9}{5}$
<hr/>			
1	$-\frac{1}{5}$	$\frac{7}{5}$	$-\frac{1}{5}$
0	1	$\frac{26}{5}$	$\frac{11}{5}$
0	0	$\frac{25}{5}$	$\frac{15}{10}$

$$\frac{25}{5}I_3 = \frac{15}{10}$$

$$I_3 = \frac{3}{10} = 0.3 \text{ A}$$

$$I = I_3 = 0.3 \text{ A}$$

Example

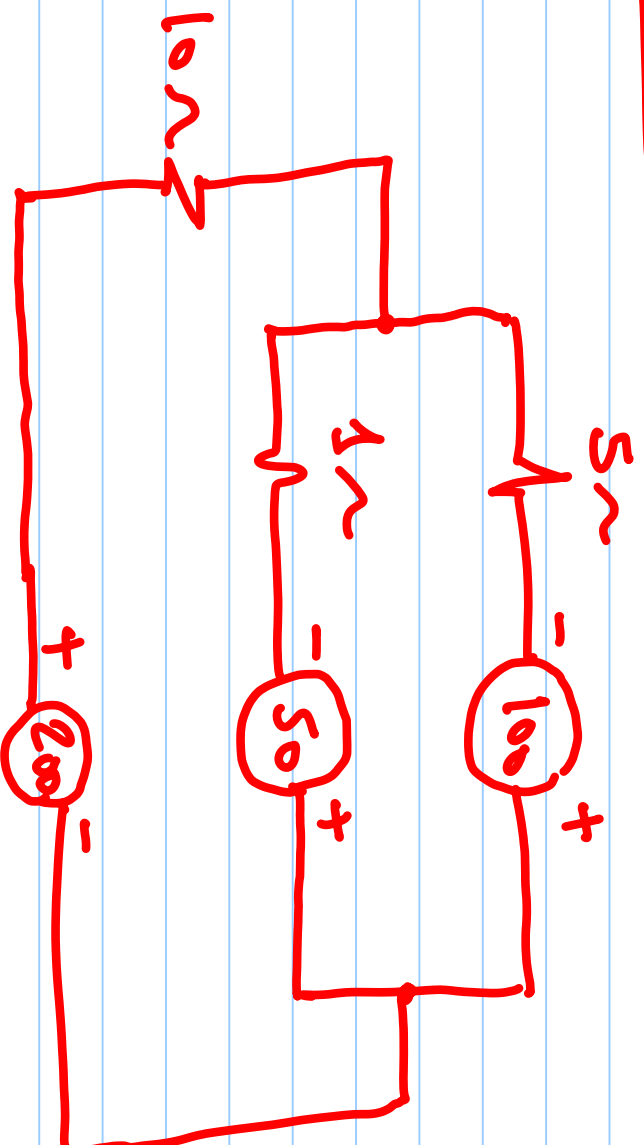


For the shown circuit find the power supplied by each voltage source

Circuit with independent CSs

* The presence of current sources usually simplifies loop analysis

* Some of the unknown loop currents are expressed in terms of the known current sources

Example

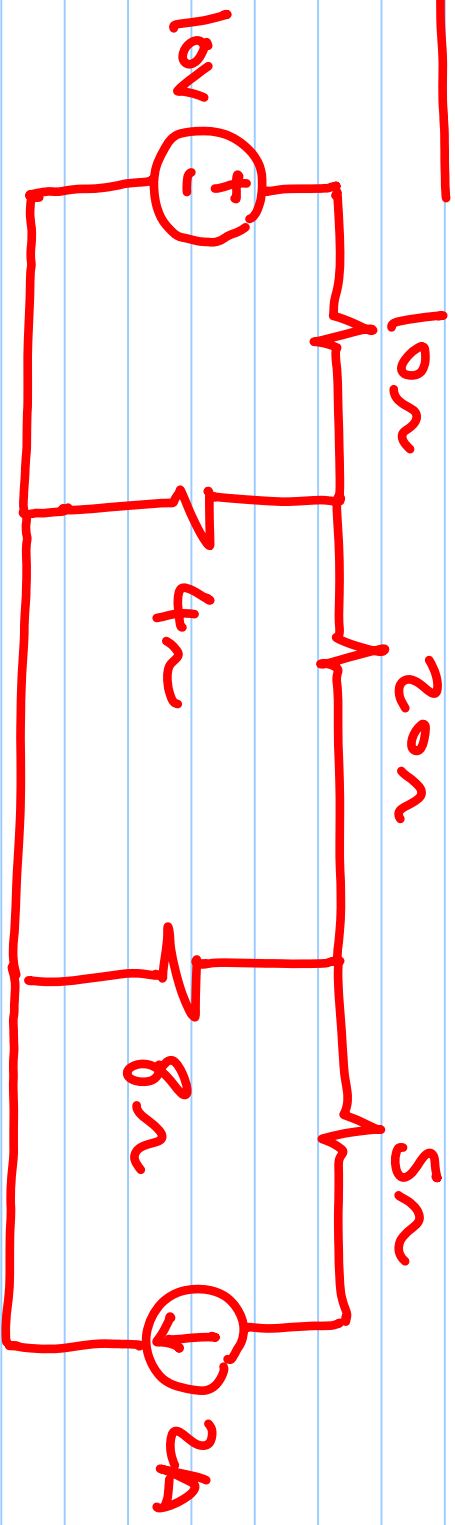

Find the power dissipated in the 10Ω resistor using loop analysis

