

Lecture #6

Operational Amplifiers (Op Amps)

Outline/Learning Objectives:

- Analyze and design simple signal-conditioning circuits based on OpAmps.
- Assess and understand some practical limitations of OpAmps.
- Use the electronics laboratory to investigate the electrical behavior of simple circuits and devices in co-requisite course.

From Chapter 11 in Jaeger, Chapter 5 in Spencer

Selected problems:

11.7, 11.13, 11.15, 11.41, 11.58, 11.78, 11.87

Why study operational amplifiers?

The operational amplifier is a fundamental building block of analog circuit design.

The name “**operational amplifier**” originates from the use of this type of amplifier to perform specific electronic circuit functions or operations, such as scaling, summation, and integration, in analog computers.

The Differential Amplifier



$$v_o = A(v_+ - v_-) = A \cdot v_{id}$$

$$v_o = 6V$$


For 741 OA: $v_o = 2 \times 10^5 v_{id} \Rightarrow v_{id} = 30 \mu V$

For OP 77 OA: $v_o = 1.2 \times 10^7 v_{id} \Rightarrow v_{id} = 0.5 \mu V$
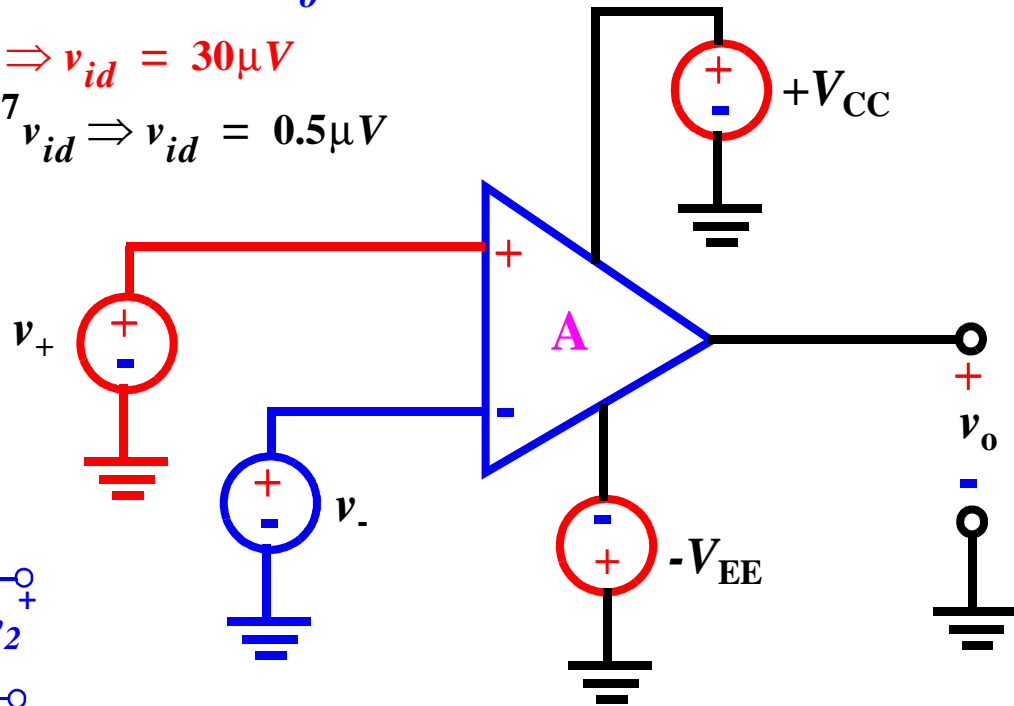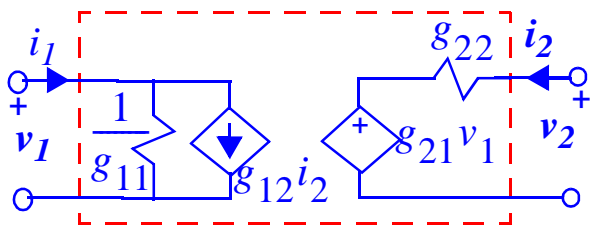
$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \cdot \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$



The Differential Amplifier_

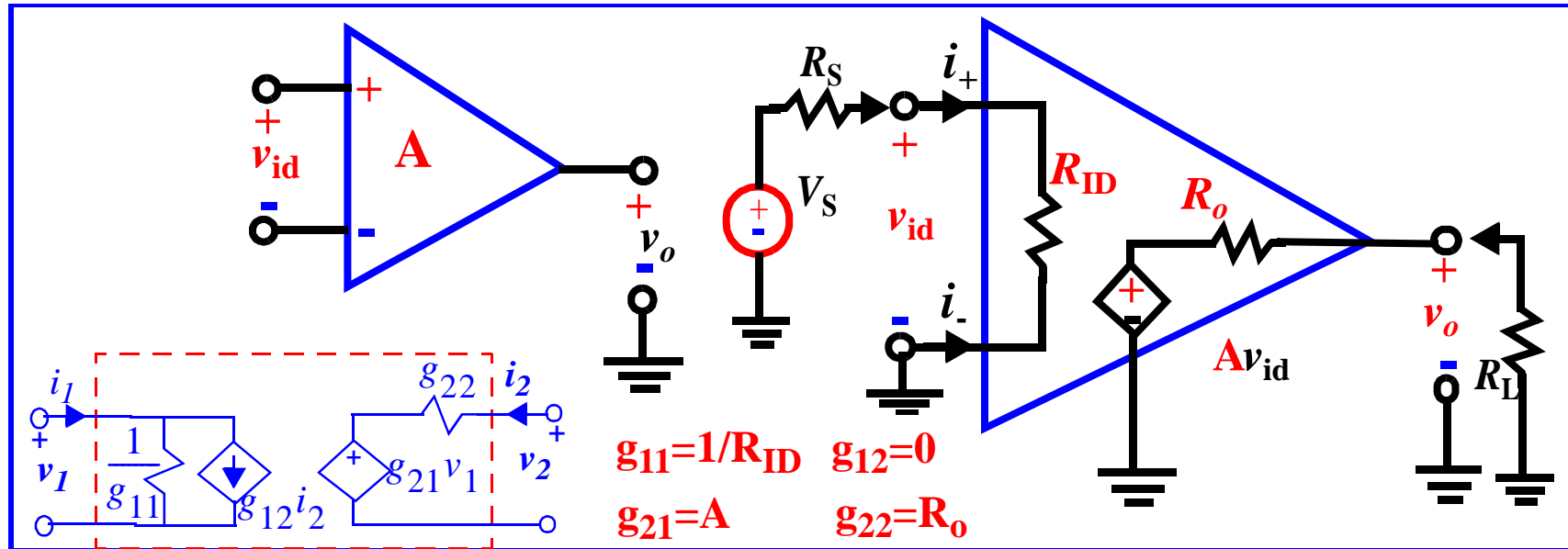

Define - A , v_{id} , R_{ID} and R_o .

Explain the simplified g-parameter representation of the diff. amp.

Diff. amp., $v_o = A v_{id} \cdot \frac{R_L}{R_o + R_L}$; $v_{id} = v_s \cdot \frac{R_{ID}}{R_{ID} + R_s}$. Note $v_s = v_{id} \cdot \frac{R_{ID} + R_s}{R_{ID}}$


Therefore, $A_V = \frac{v_o}{v_s} = A \frac{R_L}{R_o + R_L} \cdot \frac{R_{ID}}{R_{ID} + R_s}$.

In an ideal diff. amp, $R_{ID} \gg R_s$ and $R_o \ll R_L$ (fully mismatched R case), we have

$v_o = A v_{id}$, $v_{id} = v_s$ and $A_V = A$.

The Ideal Differential Amplifier

- Infinite gain (A); $A \rightarrow \infty \Rightarrow v_{id} \rightarrow 0$.
- Infinite input resistance; $R_{ID} \rightarrow \infty$.
- Zero output resistance; $R_O \rightarrow 0$.
- Zero input-offset voltage; $\pm v_{os} \rightarrow 0$.
- Zero IP-bias currents & offset current; $i_+ \rightarrow 0$; $i_- \rightarrow 0$; $i_{os} \rightarrow 0$ ($i_{os} = i_+ - i_-$).
- Infinite common-mode rejection ratio (CMRR).
- Infinite power supply rejection ratio (PSRR).
- Infinite output voltage range.
- Infinite output current capability.
- Infinite open-loop bandwidth.
- Infinite slew-rate.

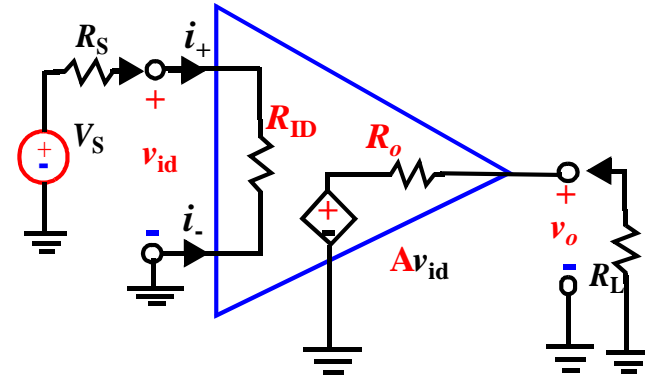


Real OA depart from ideal. However, the ideal characteristics implies that we need not be bothered by, for example, the OP loading characteristics.

Some conceptualizations to simplify OA analysis

- (1) For V purposes, IP port appears as a SC, i.e., $v_{id} \rightarrow 0$
- (2) For I purposes, IP port appears as an OC, i.e., $i_+ \rightarrow 0$; $i_- \rightarrow 0$.

The Inverting Amplifier

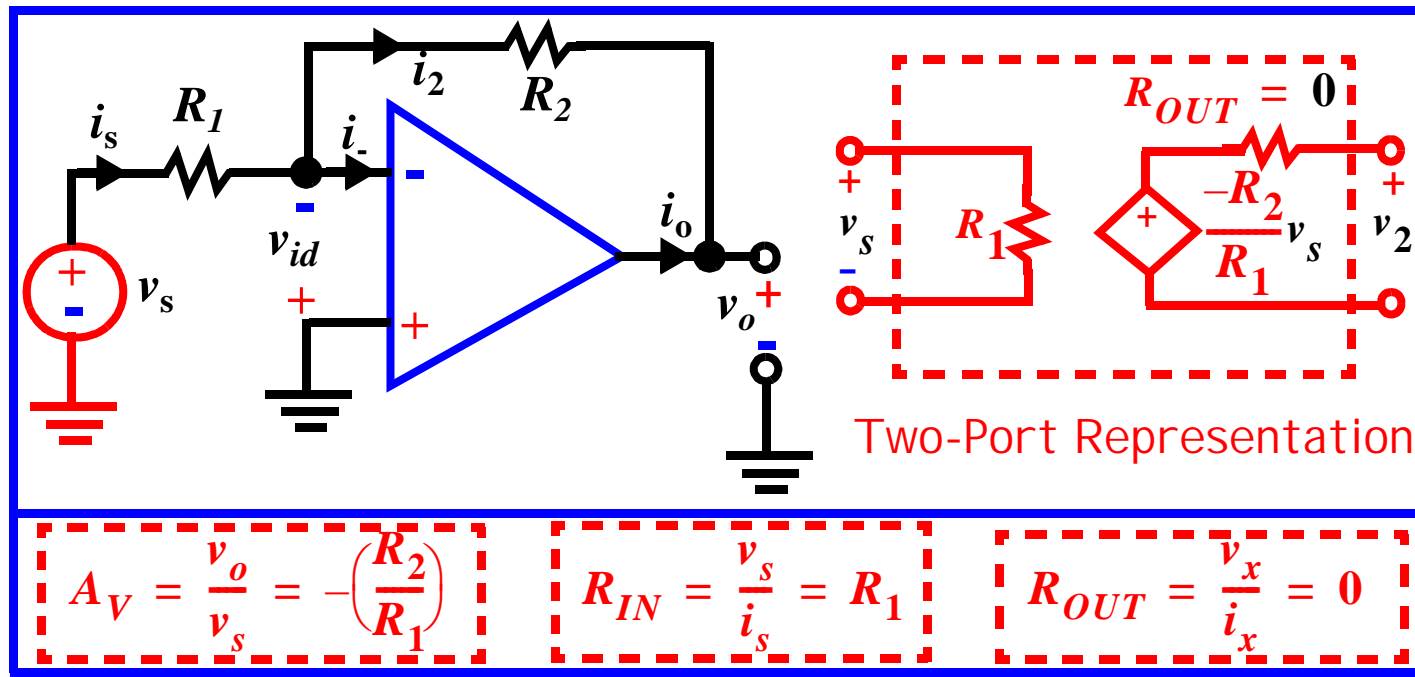

$$v_+ = 0 \text{ and } v_- = \frac{R_2}{R_1 + R_2} v_s + \frac{R_1}{R_1 + R_2} v_o = (1 - \beta)v_s + \beta v_o$$

For inv. amp., $A_V = \frac{v_o}{v_s} = \left(1 - \frac{1}{\beta}\right) \cdot \frac{1}{1 + (A\beta)^{-1}} \cdot \beta$ - feedback factor.

$$A_{V,ideal} = \lim_{A\beta \rightarrow \infty} (A_V) = \left(1 - \frac{1}{\beta}\right) = -\frac{R_2}{R_1}$$

The Inverting Amplifier

Suffers from low R_{IN} since cannot make R_{IN} too large because of A_V .

OP is phase shifted by π radians (180°) from IP. A_V depends only on the ratio of R's. This is important, e.g., R's can vary with temperature, but their ratio remains the same. That is, we can make a stable circuit using unstable components.


Example: Refer to the inverting amplifier circuit on the previous page, what is the voltage gain A_V if $R_1 = 80 \Omega$, $R_2 = 8 \text{ k}\Omega$, and $v_S(t) = 0.15 \sin(3000t) \text{ V}$. Write an expression for the current $i_S(t)$ and output voltage $v_O(t)$.

$$A_V = -\frac{R_2}{R_1} = -\frac{8k}{80} = -100$$


$$I_S = \frac{V_S}{R_1} = \frac{0.15}{80} = 1.875 \text{ mA}$$

$$\therefore i_S(t) = 1.875 \sin(3000t) \text{ mA}$$

$$v_O(t) = -15 \sin(3000t) \text{ V}$$

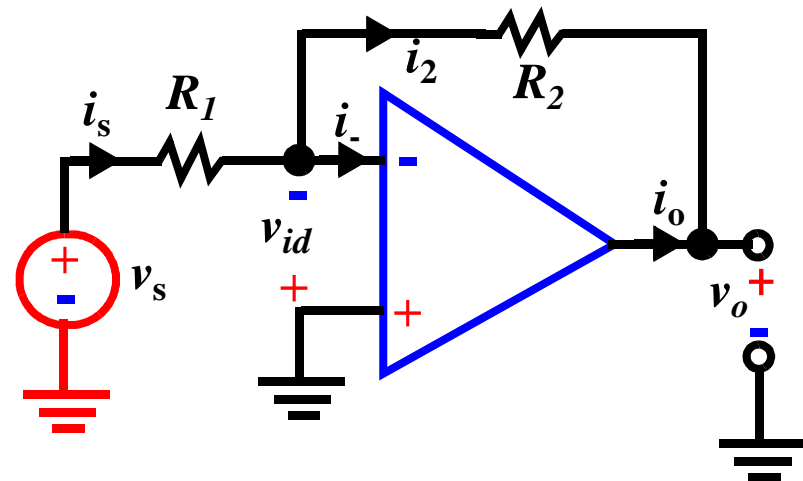

PSPI CE EXAMPLE

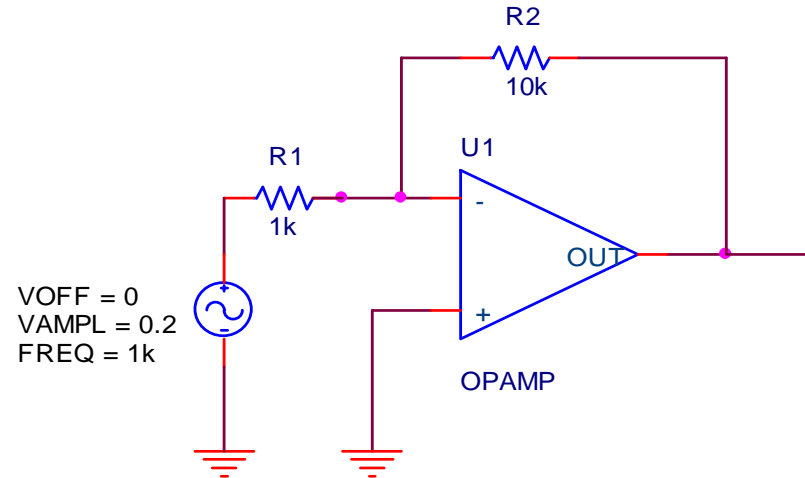

Libraries:

* Local Libraries :

* From [PSPI CE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:

```
.lib "nom.lib"
```

*Analysis directives:

```
.TRAN 0 20ms 0
```

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
```

```
.INC ".\example2-SCHEMATIC1.net"
```

```
**** INCLUDING example2-SCHEMATIC1.net ****
```

```
* source EXAMPLE2
```

PSPI CE EXAMPLE (Cont'd)

E_U1 N00043 0 VALUE {LIMIT(V(0,N00136)*1E6,-15V,+15V)}

R_R2 N00136 N00043 10k

R_R1 N00248 N00136 1k

V_V1 N00248 0

+SIN 0 0.2 1k 0 0 0

**** RESUMING example2-SCHEMATIC1-Example2Profile.sim.cir ****

.END

