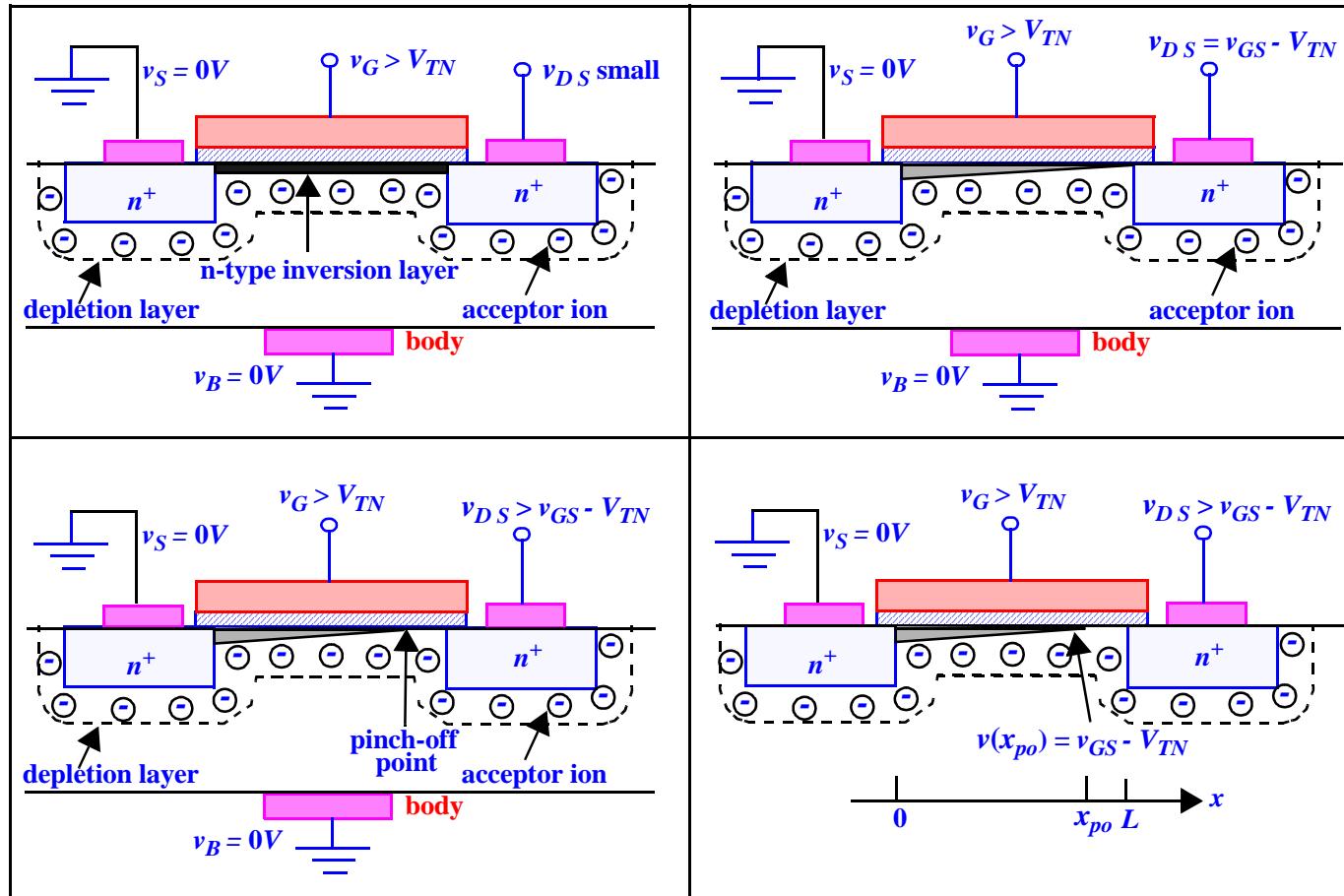


Saturation of the I-V Characteristics




At pinch-off, the voltage is

$$v_{GS} - v(x_{po}) = V_{TN}$$


Current is $i_{DS} = \frac{K_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2$ for $v_{DS} \geq v_{GS} - V_{TN} \geq 0$

The saturation drain voltage is $v_{DSAT} = v_{GS} - V_{TN}$

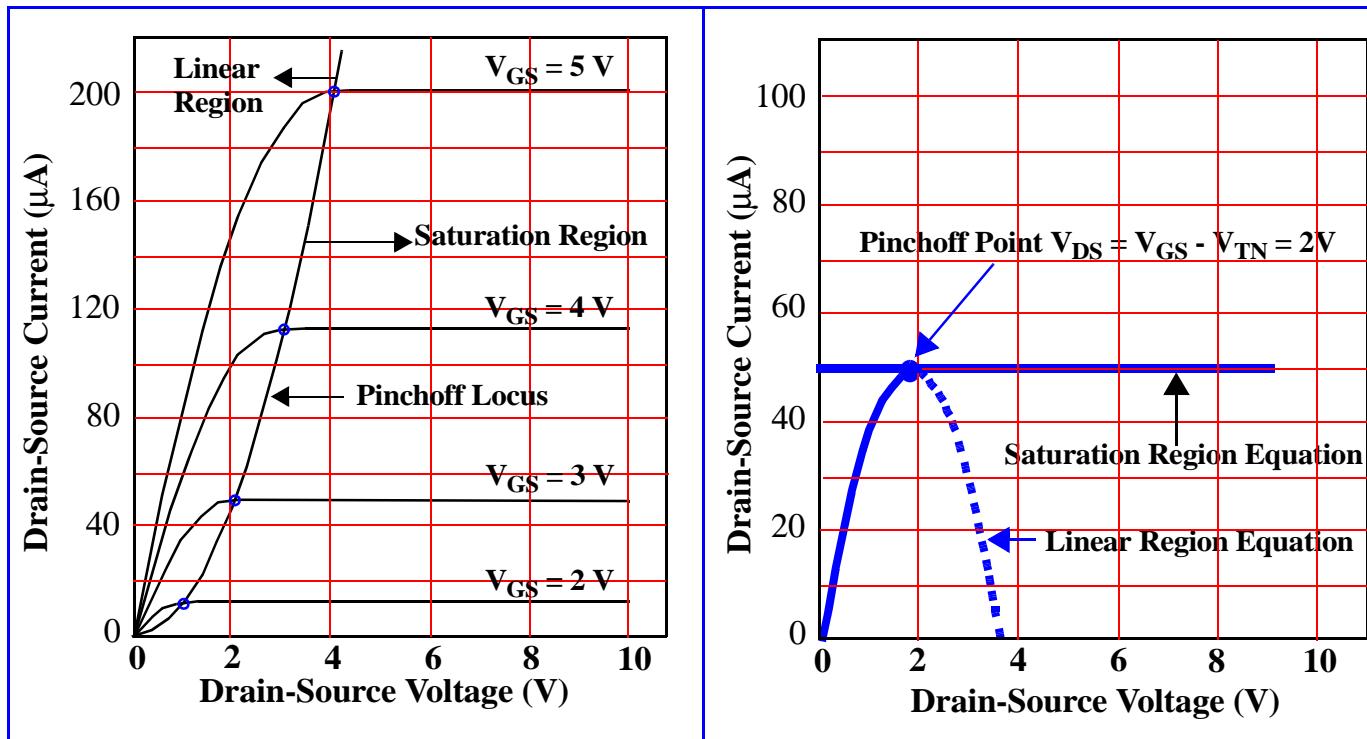Current is $i_{DS} = [WC_{ox}\left(\frac{v_{GS} - V_{TN}}{2}\right)] \cdot [\mu_n\left(\frac{v_{GS} - V_{TN}}{L}\right)]$



Channel Length Modulation

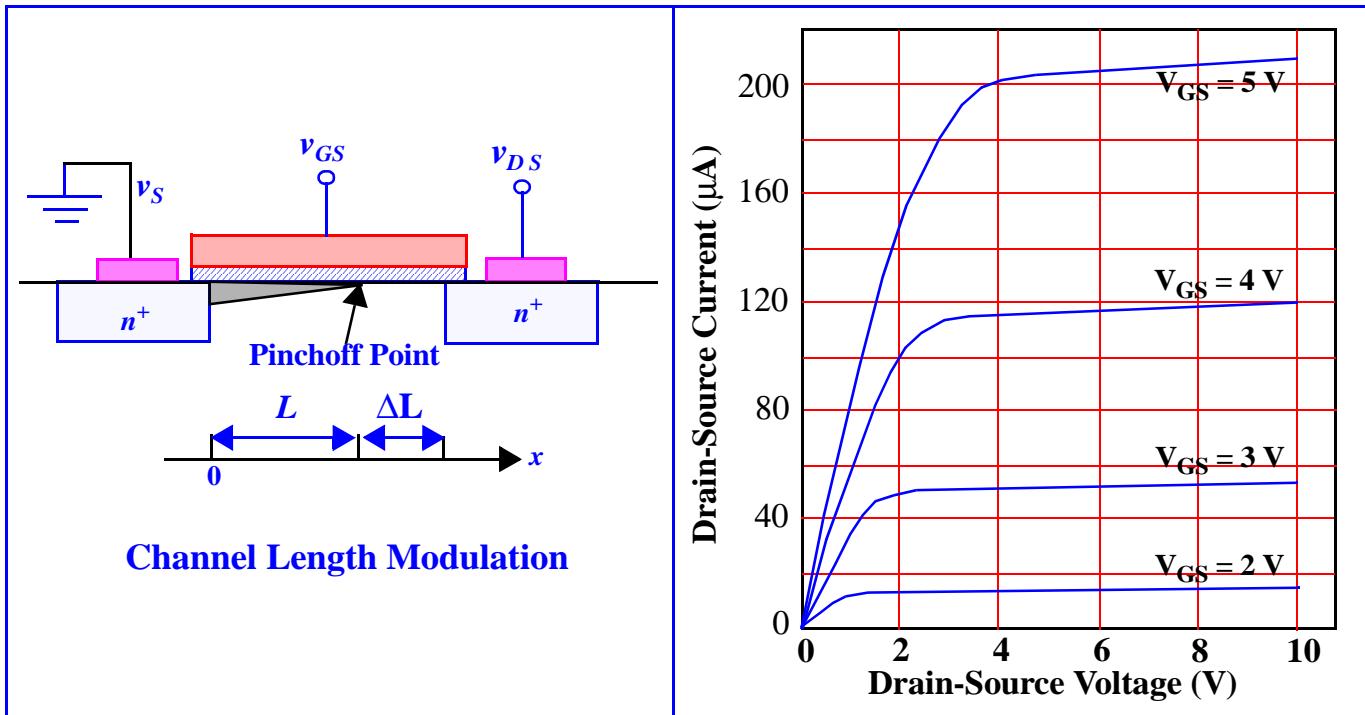

Current is $i_{DS} = \frac{K_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$

and $0.001 \text{ V}^{-1} \leq \lambda \leq 0.1 \text{ V}^{-1}$

In saturation, the on-resistance R_{on} and transconductance g_m

$$R_{on} = \left[\frac{\partial i_{DS}}{\partial v_{DS}} \right]^{-1} = \frac{1}{\frac{K_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 \lambda} \approx \frac{1}{\lambda i_{DS}} \text{ in } \Omega$$

$$g_m = \left[\frac{\partial i_{DS}}{\partial v_{GS}} \right] = K_n \frac{W}{L} (v_{GS} - V_{TN})(1 + \lambda v_{DS}) \text{ in S or A/V.}$$

Example: An enhancement NMOSFET has $V_{TN} = 1.5V$, $K_n \frac{W}{L} = 0.2 \frac{mA}{V^2}$ and $\lambda = 0.02V^{-1}$. It is operated at $V_{GS} = 3.5V$. If $V_{DS} = 2V$, find I_{DS} , R_{on} and g_m .

Since $2 = 3.5 - 1.5 \Rightarrow v_{DS} \geq v_{GS} - V_{TN} \geq 0$, operates in saturation region.

$$\therefore I_{DS} = \frac{K_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS}) = \frac{0.2m}{2} (3.5 - 1.5)^2 (1 + 0.02 \times 2) = 0.416mA$$

$$R_{on} = \frac{1}{\frac{K_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 \lambda} = \frac{1}{\frac{0.2m}{2} (3.5 - 1.5)^2 (0.02)} = 125k\Omega$$

$$g_m = K_n \frac{W}{L} (v_{GS} - V_{TN})(1 + \lambda v_{DS}) = 0.2m(3.5 - 1.5)(1 + 0.02 \times 2) = 0.416mS$$

Summary of NMOS FET Mathematical Model Expressions

$$K_n = \mu_n C_{ox} \frac{W}{L}, \quad i_G = 0, \quad i_B = 0$$

Cut-off Region - $i_{DS} = 0$ for $v_{GS} \leq V_{TN}$


Linear region - $v_{GS} - V_{TN} \geq v_{DS} \geq 0$

$$i_{DS} = K_n \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS}$$

Saturation region - $v_{DS} \geq v_{GS} - V_{TN} \geq 0$


$$i_{DS} = \frac{K_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$

Depletion Mode MOSFET

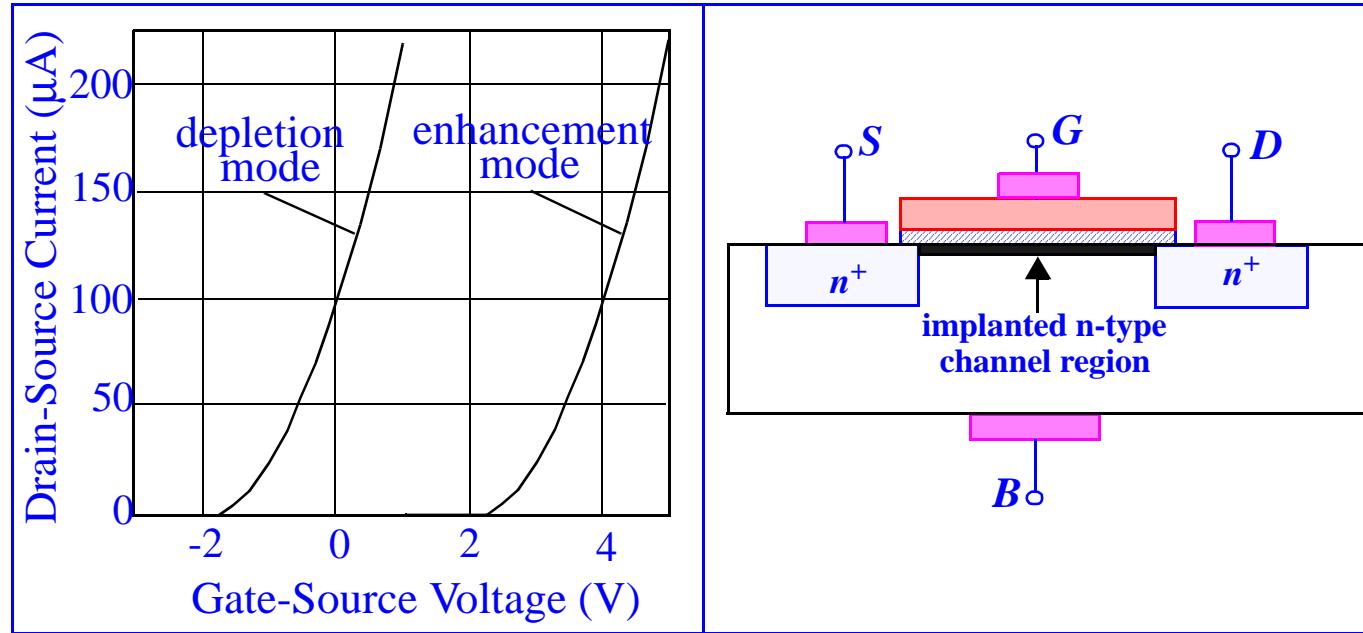

In depletion mode MOSFETs, a channel is present for $V_{GS} = 0$ V. In n-channel depletion mode devices, V_{TN} is negative.

PSpice Example

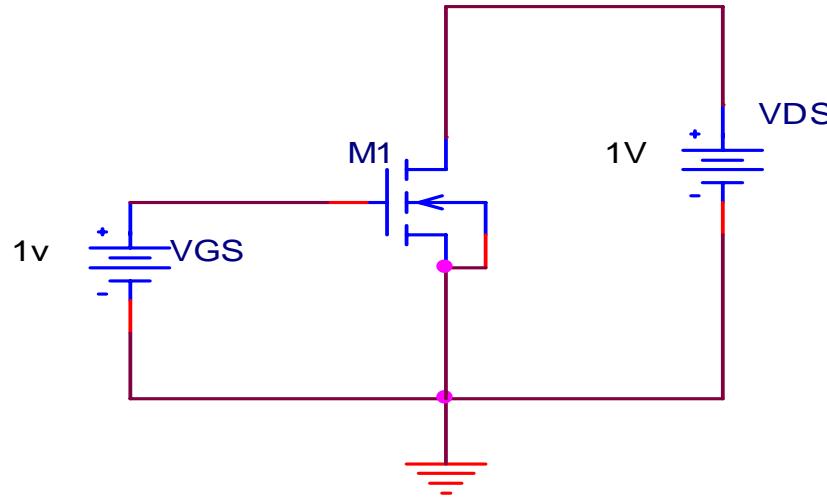

*Libraries:

* Local Libraries :

.LIB ".\example6.lib"

* From [PSpICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:

.lib "nom.lib"

*Analysis directives:

.DC LIN V_VDS 0 5 0.1

+ LIN V_VGS 0 5 1

.PROBE V(*) I(*) W(*) D(*) NOISE(*)

.INC ".\example6-SCHEMATIC1.net"

**** INCLUDING example6-SCHEMATIC1.net ****

* source EXAMPLE6

PSpice EXAMPLE (Cont'd)

M_M1 N00072 N00091 0 0 Mbreakn

V_VGS N00091 0 1v

V_VDS N00072 0 1V

**** RESUMING example6-SCHEMATIC1-Example6Profile.sim.cir ****

.END

**** MOSFET MODEL PARAMETERS

Mbreakn

NMOS

LEVEL 1

L 100.000000E-06

W 100.000000E-06

VTO 1

KP 50.000000E-06

GAMMA 0

PHI .6

LAMBDA 0

IS 10.000000E-15

JS 0

PB .8

PSPI CE EXAMPLE (Cont'd)

```
PBSW .8
CJ 0
CJSW 0
CGSO 0
CGDO 0
CGBO 0
TOX 0
XJ 0
UCRIT 10.000000E+03
DIOMOD 1
VFB 0
LETA 0
WETA 0
U0 0
TEMP 0
VDD 0
XPART 0
```

