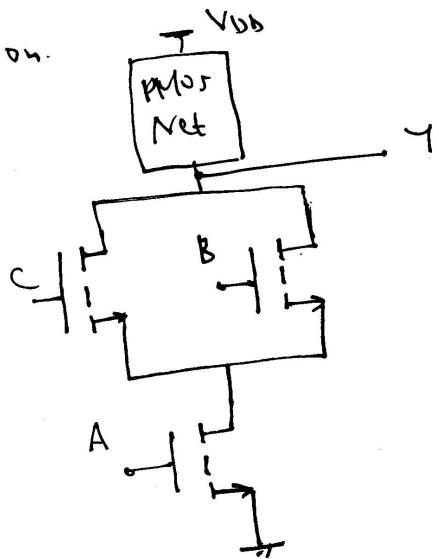



* Design a CMOS Logic gate that implements the logic function $Y = \overline{AB + AC}$. Design the different delays in the circuit to match that of a reference inverter.

ANSWER NMOS network supplier the zeros of the function.



Connections are reversed for the PMos Network

(2)

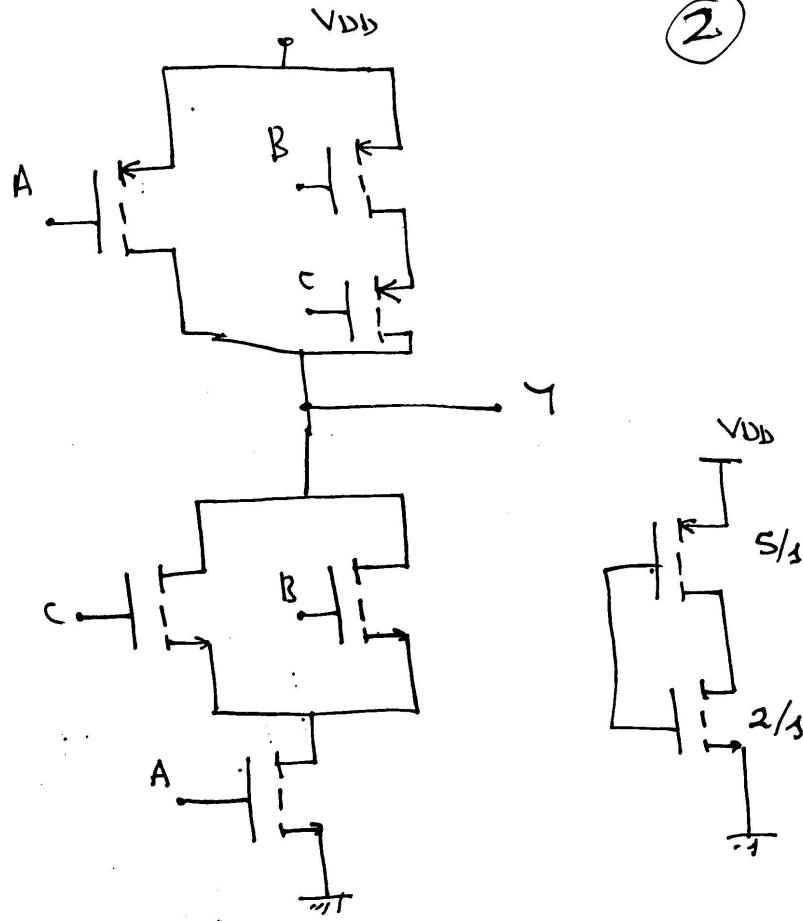

$$R_{on,n} = R_{on3} + R_{on2}$$

$$\frac{1}{(T_e)_n} = \frac{1}{(T)_3} + \frac{1}{(T)_2}$$

$$\frac{1}{(T_e)} = \frac{1}{(T)_3} + \frac{1}{(T)_2}$$

$$\Rightarrow (T)_{A,N} = (T)_{B,N} = (T)_{C,N} = 4/1$$


for the PMOS part, we have

$$\frac{1}{(T)_{\text{en}}} = \frac{1}{(T)_1} + \frac{1}{(T)_2}$$

$$\frac{1}{(S_1)} = \frac{1}{(W/L)_1} + \frac{1}{(W/L)_2} \Rightarrow (W/L)_{A,P} = (W/L)_{B,P} = (W/L)_{C,P} = 10/1$$

* What is the logic function implemented by the shown gate?

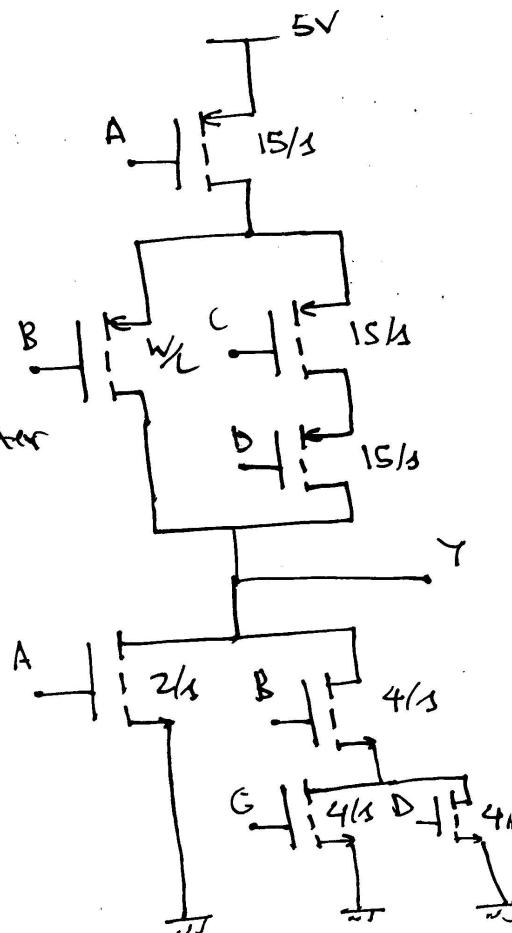* What is W/L to have a worst case delay equal to that of a reference CMOS Inverter



(4)

* Zeros of the function determine its nature

$$Y = \overline{A + BC + BD}$$

* To get Worst Case delay equivalent to that of a reference inverter, we must have

$$\frac{1}{(5/3)} = \frac{1}{(T)}_A + \frac{1}{(T)}_B$$

$$\frac{1}{(5/3)} = \frac{1}{(15/1)} + \frac{1}{(T)}_B$$

$$\frac{1}{(T)}_B = \frac{1}{(15/2)} = \frac{1}{(7.5/1)}$$

Student Name:


ID:

- 1) The value of V_o for the shown circuit is

- a) 5.0 V
- b) 4.7 V
- c) 3.7 V
- d) 3.3 V
- e) 2.7 V

The only consistent state is that D_3 is on,
 D_1 and D_2 are off

$$\Rightarrow V_o = 2.7V$$

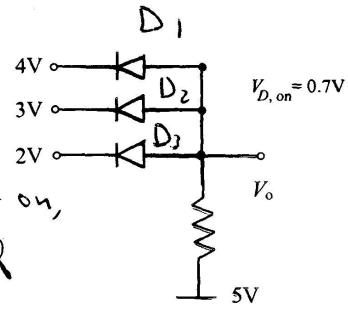


- 2) In the shown circuit, the value of the current I is

- a) -1.25 mA
- b) 2.0 mA
- c) 1.25 mA
- d) -2.0 mA
- e) -1.5 mA

The output is saturated by the 2V input



$$\Rightarrow V_o = 5V$$

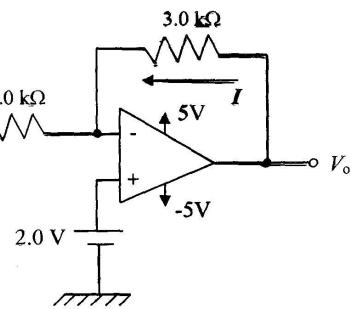

- 3) The circuit to the right shows the ac equivalent circuit of an amplifier. The transistor has an operating point (I_{SD} , V_{SD}) = (2.0 mA, 6.0 V). The parameters of the transistor are $K_p = 1.0 \text{ mA/V}^2$, $\lambda = 0 \text{ V}^{-1}$ and $V_{TP} = -1.0 \text{ V}$. The small signal gain v_o/v_s is equal to

- a) 7.800
- b) -7.800
- c) 0.886
- d) 0.805**
- e) 0.655

$$g_m = 2 \text{ mA/V}$$

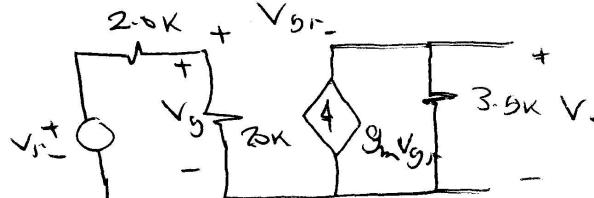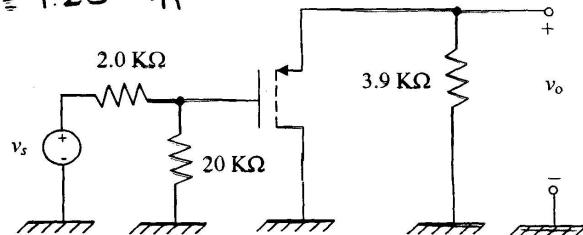

$$v_o = g_m V_{gS} * 3.9K$$

$$= g_m (V_g - V_o) * 3.9K$$

$$8.8V_o = 7.8V_g \Rightarrow V_o = \frac{7.8}{8.8} V_g$$

$$\Rightarrow V_o = \frac{7.8}{22} * \frac{20}{22} V_s \Rightarrow A_v = 0.805$$


Student Name:

ID:

- 4) What is the largest value of R_s such that the transistor remains on and saturated?

- a) 1.5 kΩ
- b) 2.5 kΩ
- c) 3.5 kΩ
- d) 4.5 kΩ
- e) None of the above


transistor is
always on and
saturated

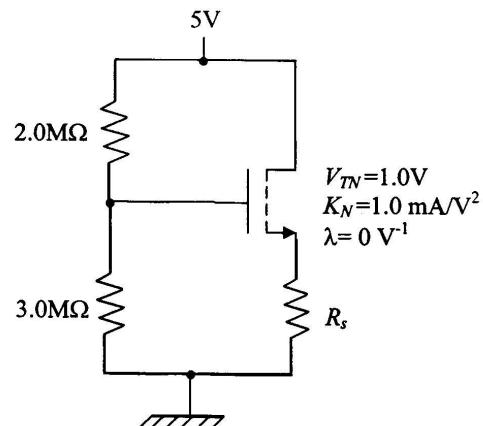

- 5) The current I_{SD} is equal to

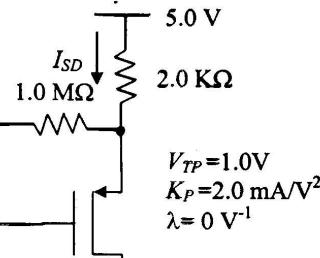- a) 0 mA
- b) 1.0 mA**
- c) 1.5 mA
- d) 2.5 mA
- e) None of the above


$$V_{SG} = 0 > -V_{TP} \\ \therefore \text{transistor is on}$$



$$I_{SD} = \frac{K_P}{2} (V_{SG} + V_{TP})^2 \\ = 1.0 \times 10^{-3} (1)^2 = 1.0 \text{ mA}$$

- 6) For the shown circuit, if the resistor R_L is small enough, the current I_2 is

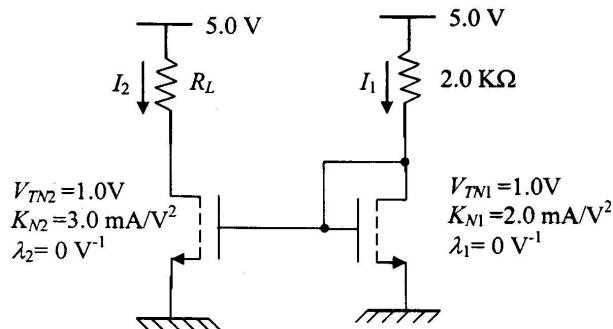- a) 1.406 mA
- b) 2.110 mA**
- c) 2.855 mA
- d) 1.000 mA
- e) 3.367 mA



~~A₂~~ $\frac{5 - V_{GS}}{2.0 \text{ k}} = \frac{K_N}{2} (V_{GS} - V_{TN})^2$

$$\frac{5 - V_{GS}}{2 \text{ k}} = 10^{-3} (V_{GS} - 1)^2$$

$$5 - V_{GS} = 2 (V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.186 \text{ V}$$

$$I_1 = 1.406 \text{ mA} \quad I_2 = 2.11 \text{ mA}$$

Student Name:

ID:


- 7) The diode in the shown circuit has a reverse current $I_s = 1.0 \text{e-12 A}$. If the DC current I is equal to $1.0 \mu\text{A}$, the total voltage v_o appearing across the diode is

- a) $0.345 + 0.0025 \sin \omega t \text{ V}$
- b) $0.707 + 0.0025 \sin \omega t \text{ V}$
- c) $0.345 - 0.0025 \sin \omega t \text{ V}$
- d) $0.707 - 0.0025 \sin \omega t \text{ V}$
- e) $0.345 + 0.003 \sin \omega t \text{ V}$

$$\text{DC Analysis: } I = I_s \exp\left(\frac{V_D}{V_T}\right) \Rightarrow V_D = V_T \ln \frac{I}{I_s}, \quad V_D = 0.345 \text{ V}$$


$$\frac{\partial I}{\partial V_D} = I_s \frac{\exp\left(\frac{V_D}{V_T}\right)}{V_T} \Rightarrow R_D = \left(\frac{\partial I}{\partial V_D}\right)^{-1} = \frac{V_T}{I_D}$$
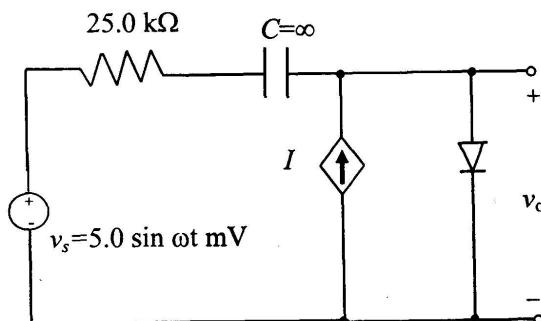
$$R_D = \frac{0.025}{10^{-6}} = 25 \text{ K} \Rightarrow V_o = 0.345 + 2.5 \sin \omega t \text{ mV}$$



- 8) The source V_s is a sinusoidal source with an amplitude of 10 volts. The minimum and maximum values of the output voltage V_o are, respectively,

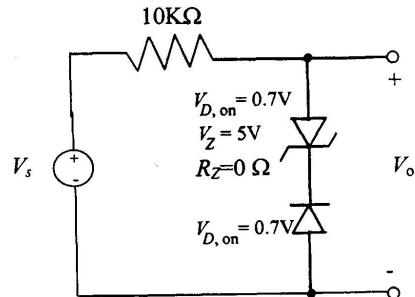- a) -1.4 V, 4.3 V
- b) -4.3 V, 10 V
- c) -5.7 V, 10 V
- d) -5.7 V, 1.4 V
- e) -1.4 V, 5.7 V



for positive voltage both diodes are off and $V_{o,\max} = 10 \text{ V}$

$$< -5.7 \text{ V}$$

for negative voltage Zener is breakdown

and diode is forward biased

$$V_{o,\min} = -5.7 \text{ V}$$