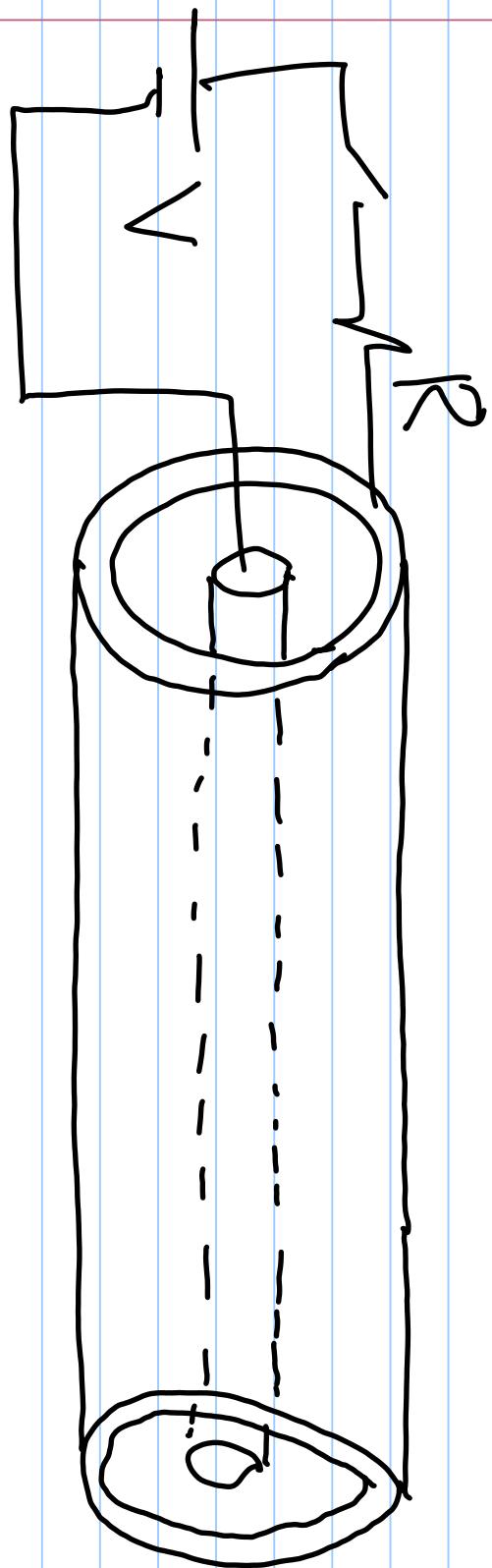


Lecture 14


from Sections 11.1 - 11.3

Solve 11.4 - 11.16


Transmission Lines



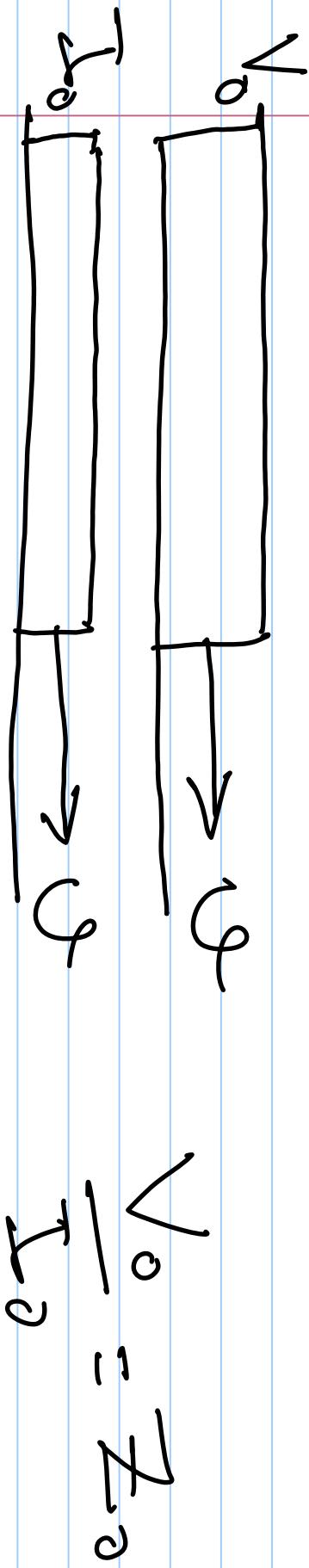* When switch is closed, voltage and current waves are excited.



Equivalent Circuit Model

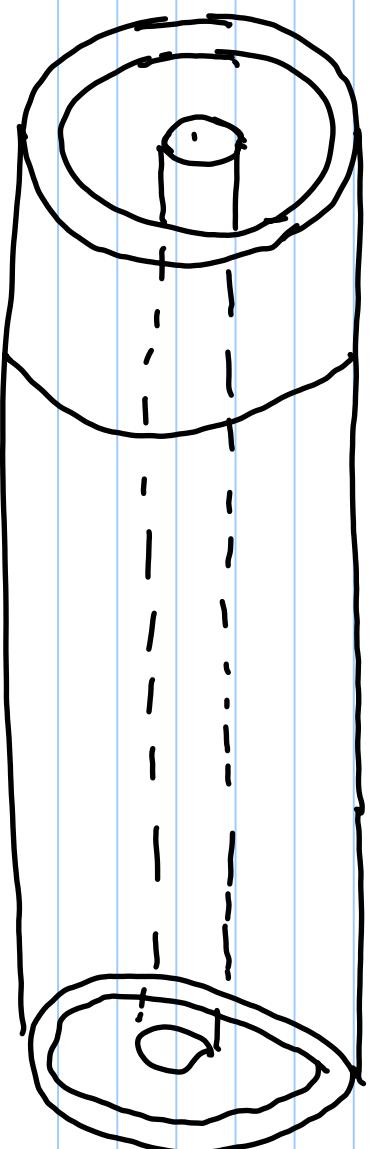

$\leftarrow \Delta z \rightarrow$

Yuket Yukoz Yukoz
Yuket Yukoz Yukoz
T T T T T T T T T T T T

R: Resistance per unit length
G: Conductance per unit length

G₀ T C₀ T

C: Capacitance per unit length
L: Inductance per unit length

Differential Equations of TL_r

$$V = \frac{1}{2} R I \Delta Z + \frac{1}{2} L \frac{\partial I}{\partial t} \Delta Z + \frac{1}{2} L \left(\frac{\partial I}{\partial t} + (I + \Delta I) \right) \Delta Z$$

$$+ \frac{1}{2} R (I + \Delta I) \Delta Z + (V + \Delta V)$$

$$\rightarrow \frac{\partial V}{\partial Z} = \frac{\Delta V}{\Delta Z} = - (R I + L \frac{\partial I}{\partial t}) \leftarrow (1$$

* By applying KCL, we get

$$I = G \Delta Z \left(V + \frac{\Delta V}{2} \right) + C \Delta Z \frac{\partial I}{\partial t} \left(V + \frac{\Delta V}{2} \right) + (I + \Delta I)$$

$$\frac{\partial I}{\partial Z} = \lim_{\Delta Z \rightarrow 0} \frac{\Delta I}{\Delta Z} = - (G V + C \frac{\partial V}{\partial t}) \leftarrow (2$$

Differential Equations (Cont'd)

* Differentiating (1) w.r.t. Z and eliminating $\frac{dI}{dt}$ and $\frac{d^2I}{dt^2}$, we get

$$\frac{\partial^2 V}{\partial Z^2} = LC \frac{\partial^2 V}{\partial t^2} + (LG + RC) \frac{\partial V}{\partial t} + RGV$$

* Similarly we can obtain for the current I ,

$$\frac{\partial^2 I}{\partial Z^2} = LC \frac{\partial^2 I}{\partial t^2} + (LG + RC) \frac{\partial I}{\partial t} + RG I$$

The Lossless Case

* For the lossless case we have

$$R = G = 0$$

$$\rightarrow \frac{\partial^2 V}{\partial Z^2} = L C \frac{\partial^2 V}{\partial t^2} \text{ and } \frac{\partial^2 I}{\partial Z^2} = L C \frac{\partial^2 I}{\partial t^2}$$

* The solution of this 1D wave equation is

$$V(Z, t) = f_1\left(t - \frac{Z}{v}\right) + f_2\left(t + \frac{Z}{v}\right)$$

$$\text{with } v = \sqrt{\frac{1}{LC}}$$

The Lossless Case (Cont'd)

$$\begin{aligned} V(z, t) &= V^+ + V^- \\ I(z, t) &= I^+ + I^- \end{aligned}$$

I⁺ and I⁻ are not independent

$$\frac{\partial I}{\partial t} = - \frac{\partial V}{\partial z} = - \frac{\partial}{\partial z} \left[f_1(t + \frac{z}{v}) + f_2(t + \frac{z}{v}) \right]$$

$$\frac{\partial I}{\partial t} = - \frac{\partial}{\partial z} \left[f_1(t - \frac{z}{v}) - f_2(t + \frac{z}{v}) \right]$$

$$\begin{aligned} I &= \frac{1}{Lc} \left(f_1(t - \frac{z}{v}) - f_2(t + \frac{z}{v}) \right) \\ I^+ &= \frac{V^+}{Lc} = \frac{V^+}{L * \sqrt{Lc}} = \frac{V^+}{\sqrt{Lc}} \\ I^- &= \frac{V^-}{Lc} = \frac{V^-}{L * \sqrt{Lc}} = \frac{V^-}{\sqrt{Lc}} \end{aligned}$$

Characteristic Impedance

$$Z_0 = \sqrt{\frac{L}{C}} = \text{characteristic impedance}$$

$$\text{also } I = -\frac{V^-}{Z_0}$$

$$V = V^+ + V^- \rightarrow I = \frac{V^+}{Z_0} - \frac{V^-}{Z_0}$$



The Sinusoidal Case

* If we take $f_1(z) = \cos(\omega z + \phi)$ a possible solution of the Telegrapher's equation is $V(z,t) = \cos\left(\omega(t - \frac{z}{\beta}) + \phi\right)$

$$\Rightarrow V_z(z,t) = \cos(\omega t - \beta z + \phi), \quad \beta = \frac{\omega}{\rho}$$

* The backward wave is given by

$$V(-z,t) = \cos(\omega t + \beta z + \phi)$$

* The corresponding phasors are

$$\vec{V} = \vec{V}_+ + \vec{V}_- + V_o e^{j\beta z} + V_o e^{-j\beta z}$$

The Lossy Case

- * This case is easier to address in the frequency domain
- * The Voltage Satisfier

$$\frac{d^2V}{dt^2} = L \frac{d^2V}{dt^2} + (LG + RC) \frac{dV}{dt} + RGV$$

using phasor for $(\frac{d^2}{dt^2} + j\omega)^2$, $\frac{d^2V}{dt^2} = -\omega^2 V$

$$\frac{d^2V}{dt^2} = -\omega^2(LCV + (LG + RC)V + RGV)$$

$$\Rightarrow \frac{d^2V}{dt^2} = ((R + j\omega L)(G + j\omega C))V$$

$$Z = \underbrace{R + j\omega L}_{Z_L}$$

$$Y = \underbrace{G + j\omega C}_{Y_C}$$

The Lossy Case (Cont'd).

$$\frac{d^2V}{dz^2} = \sum V_i V_i = \delta^2 V$$

$$\downarrow \quad \delta = \sqrt{(R+jw)(G+jw)}$$

* The general Solution is given by

$$V(t) = \sqrt{\delta} e^{+j\delta t} + \sqrt{\delta} e^{-j\delta t}$$

$$\Rightarrow V(z) = (\sqrt{\delta^+}) e^{-\alpha z} e^{-j\beta z + j\phi^+}$$

$$+ (\sqrt{\delta^-}) e^{\alpha z} e^{j\beta z + j\phi^-}$$

$$\Rightarrow V(z,t) = |\sqrt{\delta^+}| e^{-\alpha z} (\cos(\omega t - \beta z + \phi^+)) + |\sqrt{\delta^-}| e^{\alpha z} \cos(\omega t + \beta z + \phi^-)$$

The Current Phactor

$$\frac{\partial V}{\partial Z} = - (R \dot{I} + \frac{d \dot{I}}{dt}) \rightarrow \frac{\partial^2 V}{\partial Z^2} = -(R + j\omega L) \dot{I}^2$$

$$-jV_o e^{-jZ} + jV_o e^{jZ} = -(R + j\omega L) \dot{I}^2$$

$$\dot{I} = \frac{j}{Z} V_o e^{-jZ} - \frac{j}{Z} V_o e^{jZ}$$

$$\dot{I}_c = \left\{ \begin{array}{l} \dot{I}_+ \\ \dot{I}_- \end{array} \right\}$$

$$\dot{I}_o = \frac{V_o}{Z_o} + \frac{Z_o}{Z} = \frac{Z_o}{Z} = \sqrt{\frac{Z_o}{Z}}$$

$$Z_o = \sqrt{\frac{R_o + j\omega L}{G_o + j\omega C}} \quad (\text{similarly } \dot{I}_o = \frac{V_o}{Z_o})$$