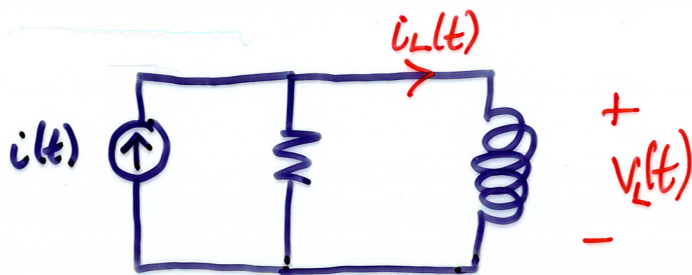


Now consider a coil of wire



- flowing current establishes magnetic field
- when current changes, field changes
- when field changes, what happens?
- Lenz & Faraday  $\Rightarrow$  induced voltage

For linear coils that don't change in time,

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$\Rightarrow i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L(x) dx$$

if  $i_L(-\infty) = 0$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(x) dx$$

Does this element store energy?


$$\begin{aligned} p(t) &= v_L(t) i_L(t) \\ &= L i_L(t) \frac{di_L(t)}{dt} \end{aligned}$$

$$\begin{aligned} E(t) &= \int_{-\infty}^t L i_L(x) \frac{di_L(x)}{dx} dx \\ &= L \int_{i_L(-\infty)}^{i_L(t)} i_L(x) di_L(x) \end{aligned}$$

if  $i_L(-\infty) = 0$

$$E(t) = \frac{1}{2} L i_L(t)^2$$

## PROPERTIES

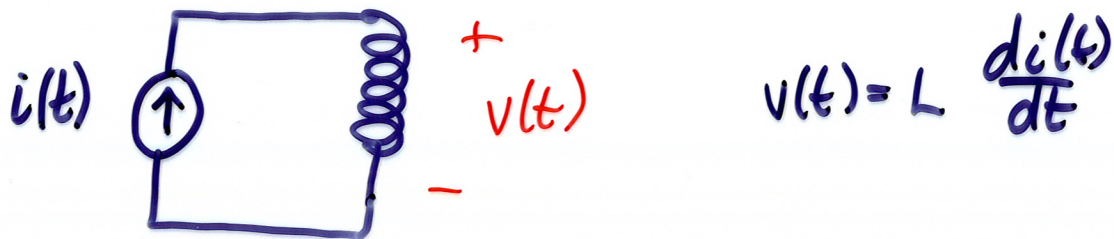


- If  $i(t)$  is constant,  
 $v(t) = 0$  no matter how big  $i(t)$  is  
⇒ short circuit
- If  $i(t)$  changes rapidly  
 $v(t)$  can be large, even if  $i(t)$  is small  
⇒ open circuit

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(x) dx$$

⇒ current is continuous

## CONNECTIONS - SERIES

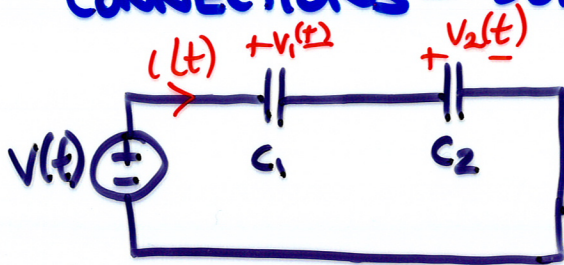


$$v_i(t) = v_i(t_0) + \frac{1}{C_i} \int_{t_0}^t i(x) dx$$

KVL:  $v(t) = v_1(t) + v_2(t)$


$$\Rightarrow v(t) = [v_1(t_0) + v_2(t_0)] + \left[ \frac{1}{C_1} + \frac{1}{C_2} \right] \int_{t_0}^t i(x) dx$$

$\Rightarrow$  circuit is equivalent to

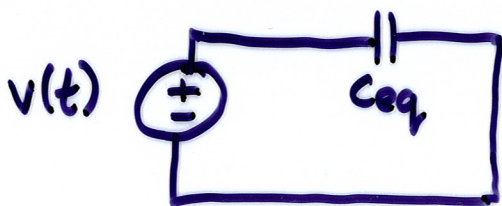

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$


## PARALLEL

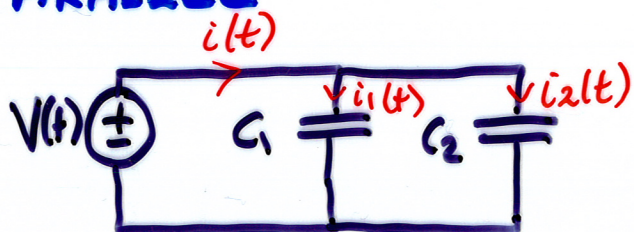

KCL  $i(t) = i_1(t) + i_2(t)$


$$i_k(t) = C_k \frac{dv(t)}{dt}$$
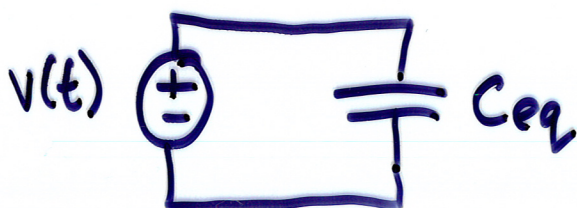
$$\Rightarrow i(t) = [C_1 + C_2] \frac{dv(t)}{dt}$$




$$C_{eq} = C_1 + C_2$$

SERIES

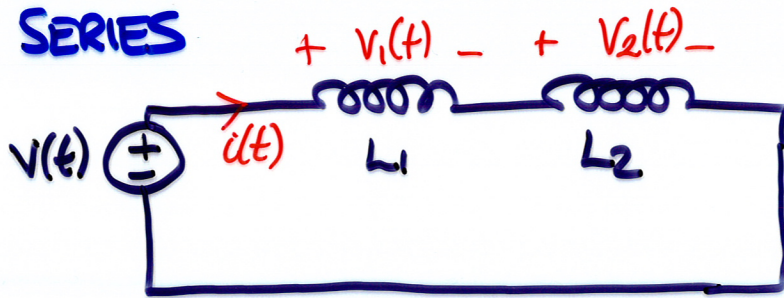


$$v_L(t) = L \frac{di(t)}{dt}$$

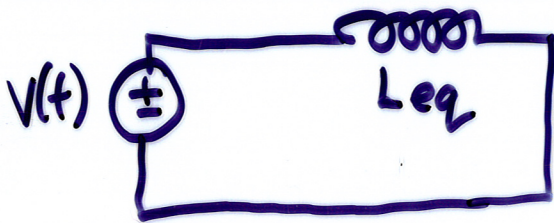KVL:  $v(t) = v_1(t) + v_2(t)$   
 $= (L_1 + L_2) \frac{di(t)}{dt}$



$$L_{eq} = L_1 + L_2$$


PARALLEL

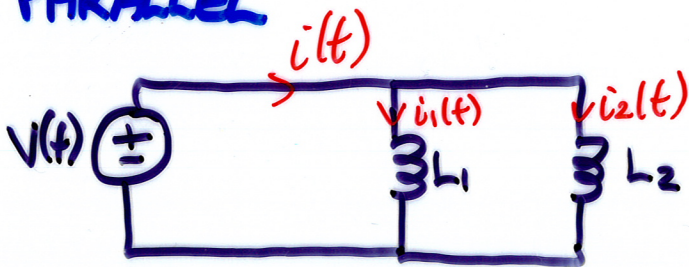

$$i_L(t) = i_2(t) + \frac{1}{L_R} \int_{t_0}^t v(x) dx$$


KCL:
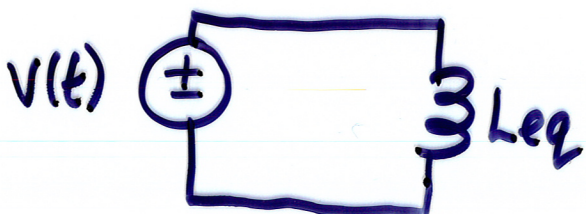
$$i(t) = i_1(t) + i_2(t)$$
$$= [i_1(t_0) + i_2(t_0)] + \left[ \frac{1}{L_1} + \frac{1}{L_2} \right] \int_{t_0}^t v(x) dx$$



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

## FLASH DISCHARGE

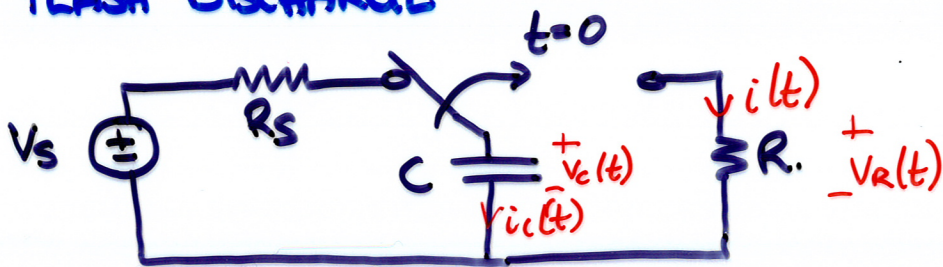

Assume switch has been in current position for a long time

$$\Rightarrow V_c(t) \Big|_{t=0^-} = V_s$$

What happens after that?

Voltage is continuous for a capacitor  $\Rightarrow V_c(t) \Big|_{t=0^+} = V_s$

~~...~~

KCL:  $i_c(t) + i(t) = 0$

$$C \frac{dV_c(t)}{dt} + \frac{1}{R} V_R(t) = 0 \quad ; \text{ but } V_c(t) = V_R(t)$$

$$\Rightarrow \frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = 0$$

$$\Rightarrow V_c(t) = V_s e^{-t/RC}$$

$$\Rightarrow i_c(t) = + \frac{V_s}{R} e^{-t/RC}$$