

FORCED RESPONSE OF A SECOND-ORDER CIRCUIT

- Recall the differential equation, with $a_2 = 1$.

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_0 x(t) = f(t)$$

- The solution is of the form

$$x(t) = x_n(t) + x_f(t)$$

- Since the left hand side of $\boxed{\square}$ = 0 for $x_n(t)$
then the left hand side of $\boxed{\square}$ = $f(t)$ for $x_f(t)$

- What might we expect $x_f(t)$ to be?

if $f(t)$ is a constant: Derivatives of a constant
are zero, so perhaps $x_f(t)$ is a constant

if $f(t)$ is an exponential: Derivatives of an exponential
are also exponentials, perhaps $x_f(t)$ is exponential

if $f(t)$ is a sinusoid: Derivatives of sinusoids are
sinusoids, perhaps $x_f(t)$ is a sinusoid.

Hence, for some simple, but important forcing functions, $x_f(t)$ has the same shape as $f(t)$.

Forcing function, $f(t)$	$x_f(t)$
K	A
Kt	$At + B$
Kt^2	$At^2 + Bt + C$
$K \sin \omega t$	$A \sin \omega t + B \cos \omega t$
$K e^{-\alpha t}$	$A e^{-\alpha t}$

- We will use the initial/boundary conditions to determine A, B, C
- Sometimes you may find that $x_f(t)$ is proportional to a component of $x_n(t)$; (e.g. $f(t) = \text{exponential case}$).
- In that case you must replace $x_f(t)$ above by $t^\rho x_f(t)$ where ρ is the smallest integer such that $x_f(t)$ is no longer proportional to any component of $x_n(t)$

SUMMARY:

COMPLETE RESPONSE OF A SECOND-ORDER CIRCUIT

Given

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_0 x(t) = f(t)$$

we have seen how to find the shape of

$$x(t) = x_n(t) + x_f(t)$$

① Solve characteristic equation


$$s^2 + a_1 s + a_0 = 0$$

② Use solutions to determine the shape of $x_n(t)$.

③ Determine the shape of $x_f(t)$ from the table. (i.e., $x_f(t)$ "looks" like $f(t)$)

- The resulting $x_n(t)$ and $x_f(t)$ contain unknown parameters.
- These can be determined by evaluating $x(0)$ and $\left.\frac{dx(t)}{dt}\right|_{t=0}$ and using knowledge from the circuit
- When the input $f(t)$ is a constant, $x(\infty)$ can also be determined + used here

EXAMPLE : 9.9-1

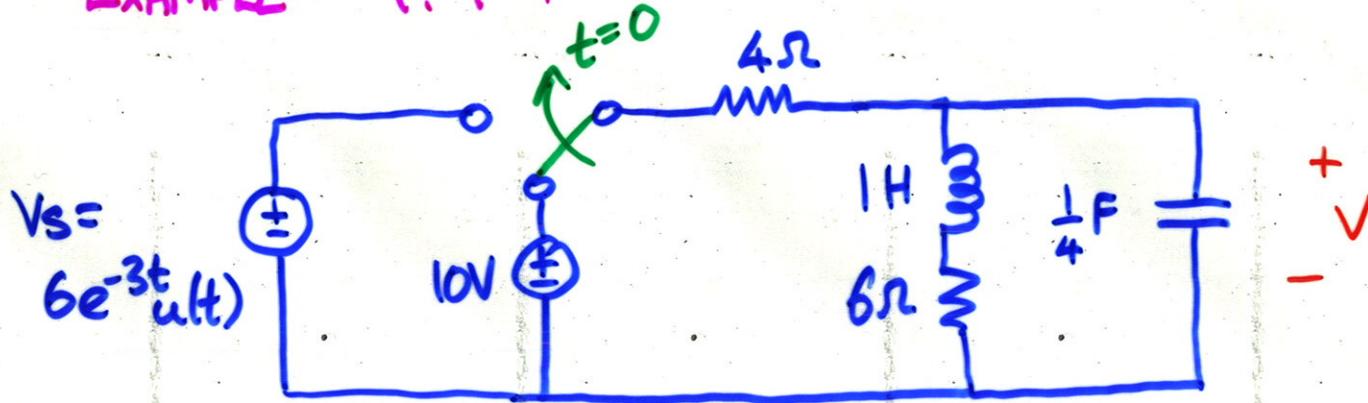

Find $v(t)$ for $t > 0$, assuming circuit is in steady state at $t=0$.

Note $u(t)$ is the unit step function


$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & \text{otherwise} \end{cases}$$

STEP 1 Determine initial conditions

at time $t=0^-$ circuit is in steady state.


⇒ since source is constant, no current flows through the capacitor

Equivalent circuit

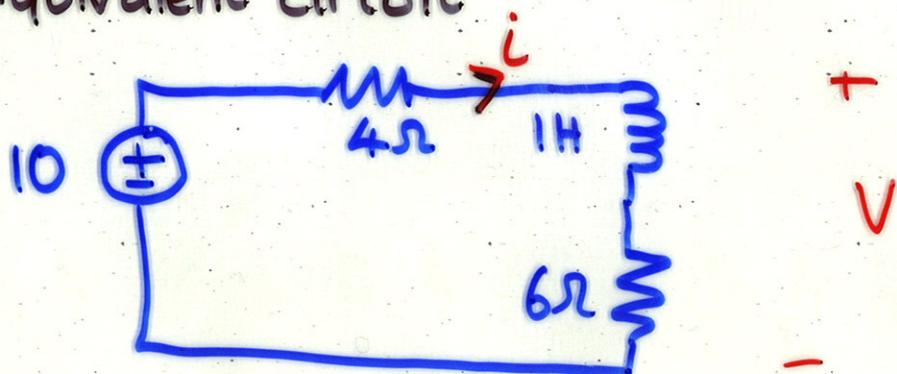

Since the source is constant, in steady state there is no voltage drop over inductor

New equivalent circuit

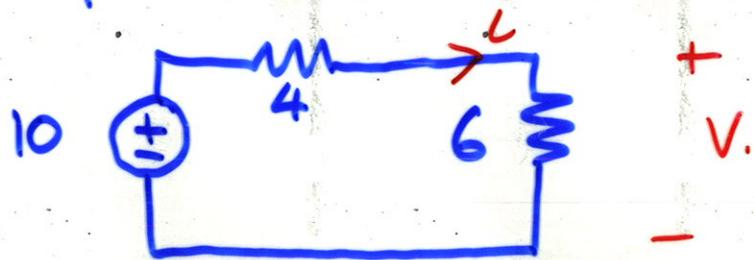

$$\text{By voltage division, } V(0) = \frac{6}{10} \times 10 \\ = 6V$$

$$i = i_L(0^-) \Rightarrow i_L(0^-) = 1A.$$

⇒ Initial conditions are:

$$V(0^-) = 6V$$


$$i_L(0^-) = 1A$$

Both these quantities are continuous

$$\Rightarrow V(0^+) = 6V$$

$$i_L(0^+) = 1A$$

After switching we have:

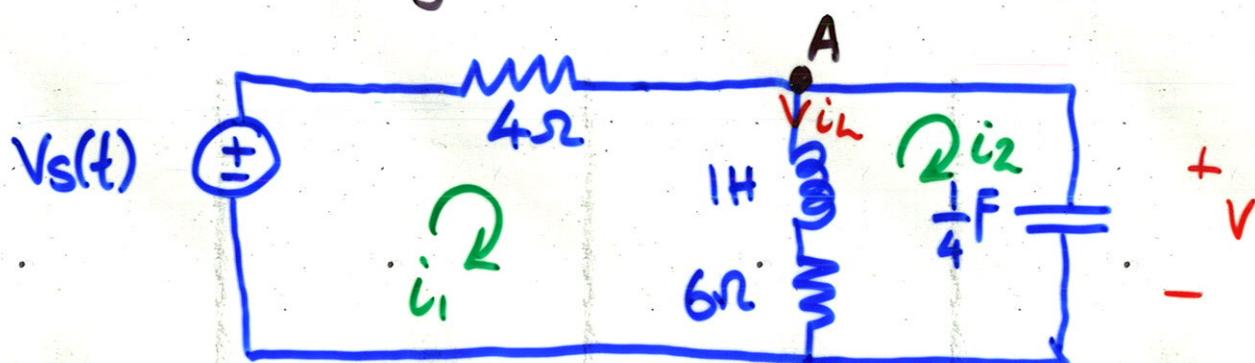

Note: i_1, i_2 not used directly!

KVL loop 2

$$-V(t) + \frac{di_L(t)}{dt} + 6i_L(t) = 0 \quad \textcircled{1}$$

KCL, node A

$$\frac{V(t) - Vs(t)}{4} + i_L(t) + \frac{1}{4} \frac{dV(t)}{dt} = 0 \quad \textcircled{2}$$

$$\textcircled{2} \Rightarrow i_L(t) = \frac{Vs(t) - V(t)}{4} - \frac{1}{4} \frac{dV(t)}{dt}$$

Substitute into \textcircled{1}

$$\Rightarrow \frac{d^2V(t)}{dt^2} + 7\frac{dV(t)}{dt} + 10V = \frac{dVs(t)}{dt} + 6Vs(t)$$

This is the differential equation we must solve

Find Natural Response

Characteristic equation is

$$s^2 + 7s + 10 = 0.$$

$\Rightarrow s = -2, s = -5 \Rightarrow$ overdamped circuit

$$\Rightarrow V_n(t) = A_1 e^{-2t} + A_2 e^{-5t} \quad \text{for } t \geq 0$$

Find Forced Response

Forcing function $f(t) = \frac{dV_s(t)}{dt} + 6V_s(t)$
 $= 18e^{-3t}, t \geq 0$

$$\Rightarrow V_f(t) = Be^{-3t}$$

This is not proportional to any component of $V_n(t)$ so it does not need to be modified

Now we must find A_1, A_2, B .

Since the natural response vanishes (goes to zero) on the left hand side of the differential equation, we have that

$$\frac{d^2V_f(t)}{dt^2} + 7 \frac{dV_f(t)}{dt} + 10V_f(t) = 18e^{-3t}$$

$$\Rightarrow 9Be^{-3t} - 21Be^{-3t} + 10Be^{-3t} = 18e^{-3t}.$$

$$\Rightarrow B = 9.$$

Therefore

$$V(t) = A_1 e^{-2t} + A_2 e^{-5t} - 9e^{-3t}$$

Now find A_1, A_2 from the facts that


$$V(0) = 6V$$

$$i_L(0) = 1A.$$

$$v(t) = A_1 e^{-2t} + A_2 e^{-5t} - 9e^{-3t}$$

$$\Rightarrow v(0) = A_1 + A_2 - 9 = 6.$$

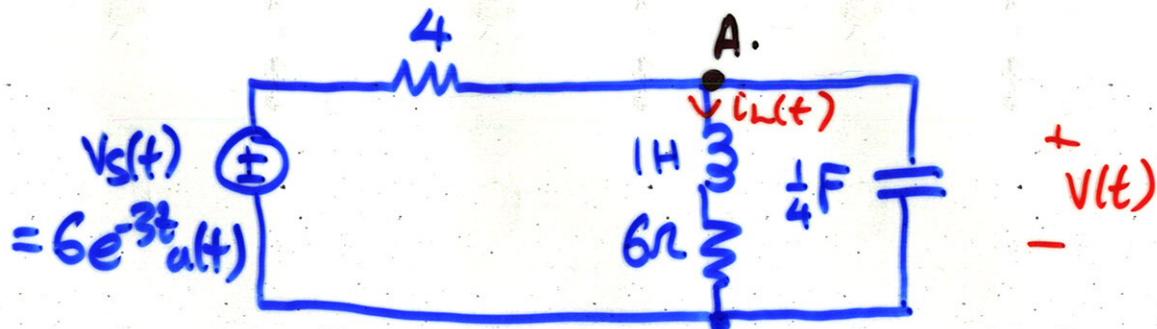To find another equation we need to relate $v(t)$ to $i_L(t)$.



KCL at A,



$$i_L(t) = \frac{V_S(t) - V(t)}{4} - \frac{1}{4} \frac{dV(t)}{dt}$$

$$\Rightarrow i_L(0) = \frac{V_S(0)}{4} - \frac{V(0)}{4} - \frac{1}{4} \left. \frac{dV(t)}{dt} \right|_{t=0}$$

$$\Rightarrow 1 = \frac{6}{4} - \frac{6}{4} - \frac{1}{4}(-2A_1 - 5A_2 + 27)$$

$$\Rightarrow 2A_1 + 5A_2 = 31.$$

Thus we have :

$$\begin{cases} A_1 + A_2 = 15 \\ 2A_1 + 5A_2 = 31 \end{cases} \Rightarrow \begin{cases} A_1 = \frac{44}{3} \\ A_2 = \frac{11}{3} \end{cases}$$

$$\Rightarrow v(t) = \frac{44}{3} e^{-2t} + \frac{1}{3} e^{-5t} - 9e^{-3t} \text{ for } t \geq 0$$

Sanity Checks.

i). $V_s(t)$ decays to zero, Does $V(t)$ decay to zero?

Yes!