


EE2C15 SWITCHING CIRCUIT EXAMPLE

Prior to time t_1 , the switch in the following circuit was in the illustrated position for a long time


At time t_1 , the switch flips and at time $t_2 > t_1$, it flips back

Find $V_C(t)$ for $t > t_1$

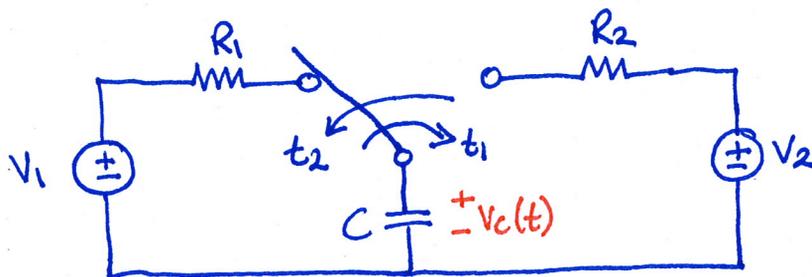Sketch $V_C(t)$. For your sketch, assume $V_1 < V_2$, $R_1 < R_2$



For $t < t_1$

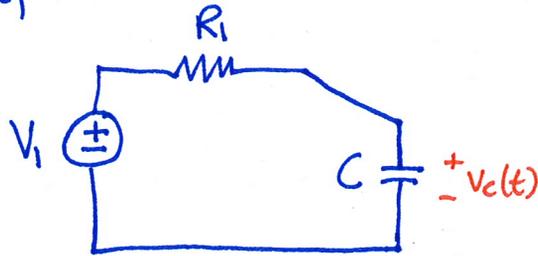


Switch ~~is~~ has been in this position for a long period of time
Since source is constant, there is no current

$$\Rightarrow V_c(t_1^-) = V_1$$

But capacitor voltage is continuous $\Rightarrow V_c(t_1^+) = V_1$

For $t_1 < t < t_2$

$$V_c(t_1^+) = V_1$$

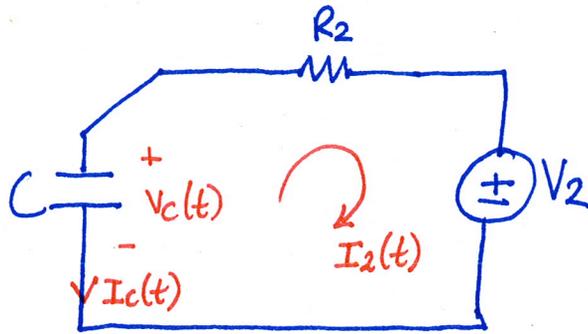

$$\text{KVL: } -V_c(t) + R_2 I_2(t) + V_2 = 0$$

$$\text{Capacitor: } I_c(t) = C \frac{dV_c(t)}{dt}$$

$$\text{Currents: } I_c(t) = -I_2(t)$$

$$\Rightarrow R_2 I_2(t) + V_c(t) = V_2$$

$$\Rightarrow R_2 C \frac{dV_c(t)}{dt} + V_c(t) = V_2$$

$$\Rightarrow \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R_2 C} = \frac{V_2}{R_2 C}$$

$$\text{Let } \tau_2 = R_2 C$$

$$\Rightarrow V_c(t) = K_2 e^{-t/\tau_2} + N_2$$

$$\text{Initial condition } V_c(t_1) = V_1 \Rightarrow K_2 e^{-t_1/\tau_2} + N_2 = V_1$$

Final condition, using the fact that source is constant

$$\text{If the circuit would not change, as } t \rightarrow \infty \quad V_c(t) \rightarrow V_2$$

$$\Rightarrow N_2 = V_2$$

So, we have, for $t_1 < t < t_2$

$$V_c(t) = K_2 e^{-t/\tau_2} + N_2$$

with $K_2 e^{-t_1/\tau_2} + N_2 = V_1$

$$N_2 = V_2.$$

$$\Rightarrow K_2 = (V_1 - V_2) e^{t_1/\tau_2}$$

$$\Rightarrow V_c(t) = (V_1 - V_2) e^{-(t-t_1)/\tau_2} + V_2$$

for $t_1 < t < t_2$.


Note that at $t = t_2^-$ we have

$$V_c(t_2^-) = (V_1 - V_2) e^{-(t_2-t_1)/\tau_2} + V_2$$

For convenience let V_x denote $V_c(t_2^-)$

For $t > t_2$

$$V_c(t_2^+) = V_x$$

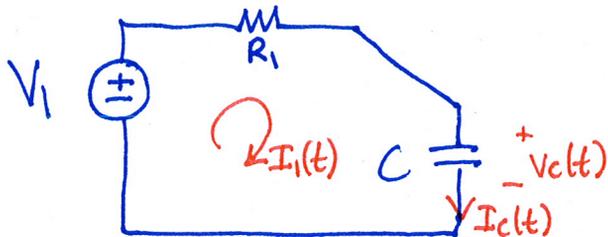

KVL: $-V_1 + R_1 I_1(t) + V_c(t) = 0$

Capacitor: $I_c(t) = C \frac{dV_c(t)}{dt}$

Currents: $I_c(t) = I_1(t)$

$$\Rightarrow \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R_1 C} = \frac{V_1}{R_1 C}$$

Let $\tau_1 = R_1 C$

$$\Rightarrow V_c(t) = K_1 e^{-t/\tau_1} + N_1$$

Initial condition $V_c(t_2^+) = V_x \Rightarrow K_1 e^{-t_2/\tau_1} + N_1 = V_x$

Final condition, using the fact that the source is constant,

$$V_c(t) \Big|_{t \rightarrow \infty} = V_1$$

$$\Rightarrow N_1 = V_1$$

So, for $t > t_2$.

$$V_c(t) = k_1 e^{-t/\tau_1} + N_1$$

with $k_1 e^{-t_2/\tau_1} + N_1 = V_x$

$$N_1 = V_1$$

$$\Rightarrow V_c(t) = (V_x - V_1) e^{-(t-t_2)/\tau_1} + V_1$$

Summary

$$\text{Let } V_x = (V_1 - V_2) e^{-\frac{(t_2 - t_1)}{\tau_2}} + V_2.$$

$$V_c(t) = \begin{cases} V_1 & t \leq t_1 \\ (V_1 - V_2) e^{-\frac{(t - t_1)}{\tau_2}} + V_2 & t_1 \leq t \leq t_2 \\ (V_x - V_1) e^{-\frac{(t - t_2)}{\tau_1}} + V_1 & t \geq t_2. \end{cases}$$

Sketch, with $V_1 < V_2$, $R_1 < R_2$.

Note $R_1 < R_2 \Rightarrow \tau_1 < \tau_2$.

