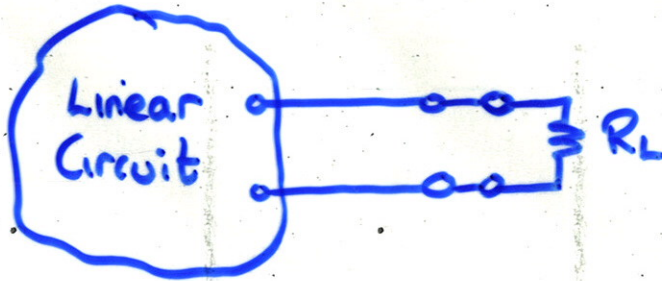



MAXIMUM POWER TRANSFER



What value of R_L should we choose in order to maximize the power in this load?

Where to start?

How about Thevenin equivalent?

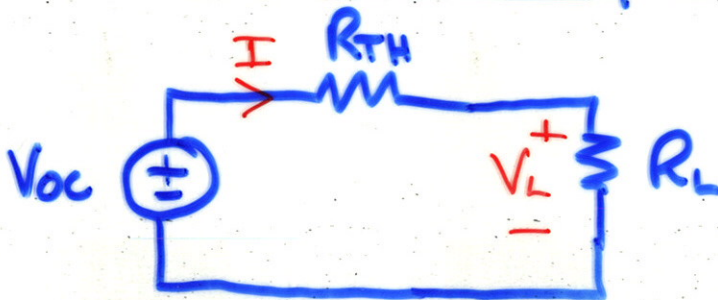

$$\begin{aligned} \text{Power in load} &= V_L \cdot I_L \\ &= I^2 R_L \\ &= \left(\frac{V_{oc}}{R_{TH} + R_L} \right)^2 R_L \end{aligned}$$

How to maximize?

First determine stationary points

$$\frac{dP_L}{dR_L} = \frac{(R_{TH} + R_L)^2 V_{oc}^2 - 2V_{oc}^2 R_L (R_{TH} + R_L)}{(R_{TH} + R_L)^4}$$

Denominator is positive (assuming $R_{TH} > 0$)


⇒ STATIONARY POINT is $R_L = R_{TH}$

⇒ Max. Power Transfer when

$$R_L = R_{TH}$$

- Efficiency?

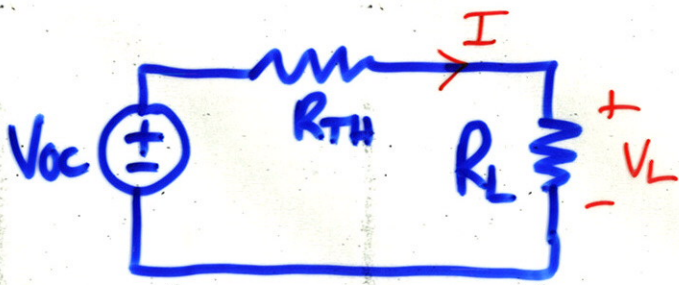WHAT ABOUT OTHER LOAD-MATCHING OBJECTIVES



$$I = \frac{V_{oc}}{R_{TH} + R_L} \rightarrow \text{decreases with } R_L$$

$$V_L = \frac{R_L V_{oc}}{R_{TH} + R_L} = \frac{V_{oc}}{1 + R_{TH}/R_L} \rightarrow \text{Increases with } R_L \text{ towards } V_{oc}$$

$$P_L = V_L I = \frac{V_{oc}^2}{R_L (1 + R_{TH}/R_L)^2}$$

for small R_L , $R_L \ll R_{TH}$

$$P_L \approx \frac{V_{oc}^2}{R_L (R_{TH}/R_L)^2} = \frac{R_L V_{oc}^2}{R_{TH}^2}$$

\rightarrow Increases with R_L

for large R_L , $R_L \gg R_{TH}$

$$P_L \approx \frac{V_{oc}^2}{R_L} \rightarrow \text{Decreases with } R_L$$

Turning point? $R_L = R_{TH}$

What about efficiency

$$\frac{P_L}{P_{s,gen}}$$

$$P_L = \frac{V_{oc}^2}{R_L (1 + R_{TH}/R_L)^2}$$

$$P_{s,gen} = V_{oc} I = \frac{V_{oc}^2}{R_L + R_{TH}} = \frac{V_{oc}^2}{R_L (1 + R_{TH}/R_L)}$$

$$\Rightarrow \text{Efficiency} = \frac{1}{1 + \frac{R_{TH}}{R_L}}$$

What is efficiency at max power transfer?