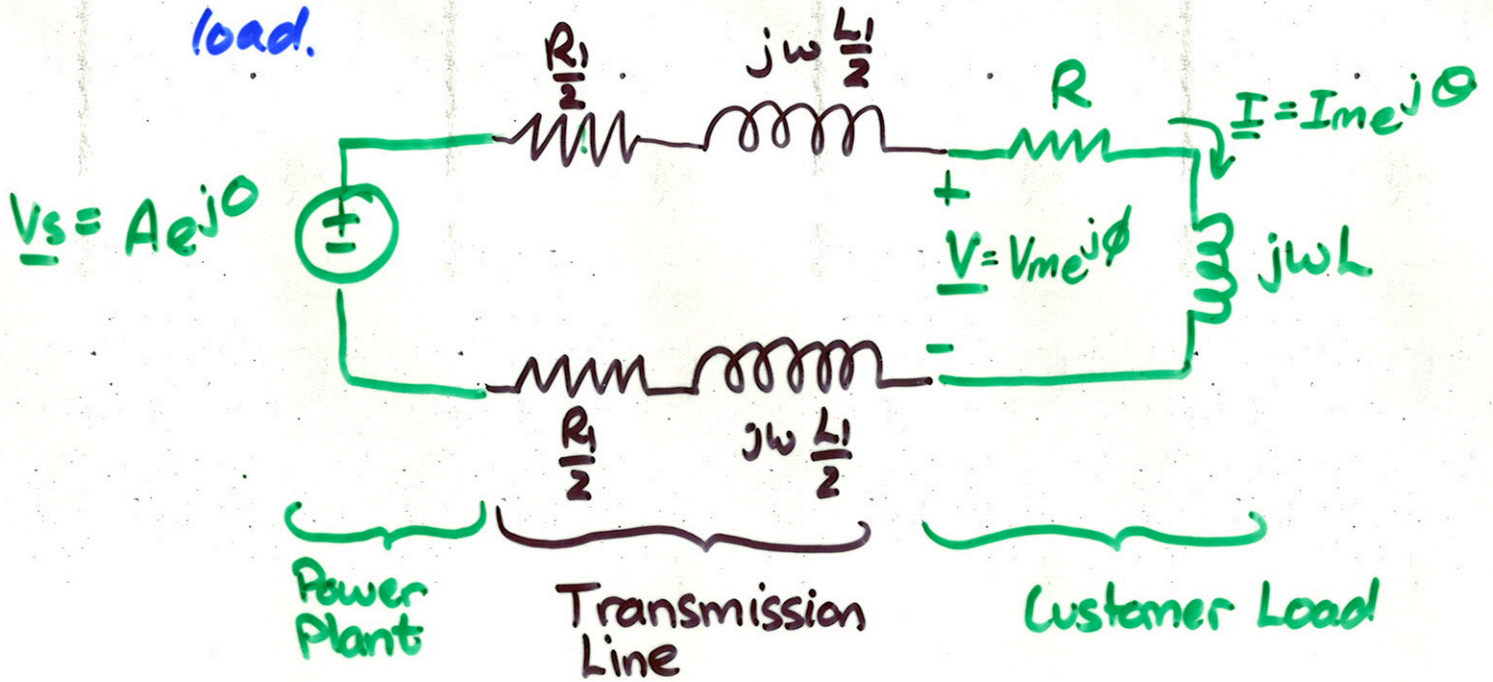


Application

consider the following frequency-domain model of a power plant, transmission line and customer load.



$$\text{Impedance of line} = \underline{Z}_{\text{LINE}} = R_1 + j\omega L_1$$

$$\text{Power absorbed by line} = \frac{I_m^2}{2} \text{Re}\{\underline{Z}_{\text{LINE}}\} = \frac{I_m^2 R_1}{2}$$

The power company has to supply power at a specified voltage V . However some of the power is absorbed by the line. ~~How~~ How much is absorbed in the line? let V_c and P_c be the voltage and average power requested by the customer

$$P_{cs} = \frac{V_m I_m}{2} \text{ pf}$$


$$\Rightarrow I_m = \frac{2P}{V_m \text{ pf}}$$

Hence power dissipated in the line is

$$P_{\text{LINE}} = 2 \left(\frac{P}{V_m \text{ pf}} \right)^2 R_l$$


Hence higher the power factor, the less power is lost in the line
#

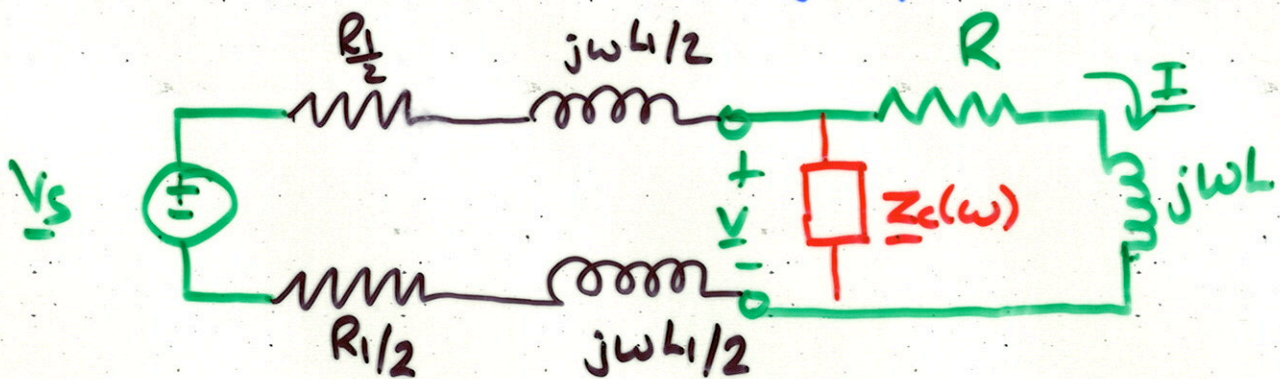- * In practice, power companies charge extra for low power factor loads (large power factor angle)
- * As a result, customers often try to "correct" their power factor using a parallel impedance



POWER FACTOR CORRECTION - AGAIN

Consider a load:

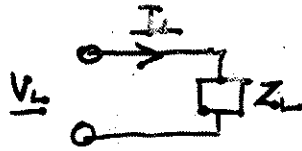

Complex power


$$\begin{aligned} S_L &= \frac{V_L I_L^*}{2} \\ &= |S_L| e^{j \angle S_L} \\ &= P_{av,L} + j Q_L \end{aligned}$$

Power factor: $\cos(\angle S_L)$

if $\angle S_L > 0$: lagging

if $\angle S_L < 0$: leading

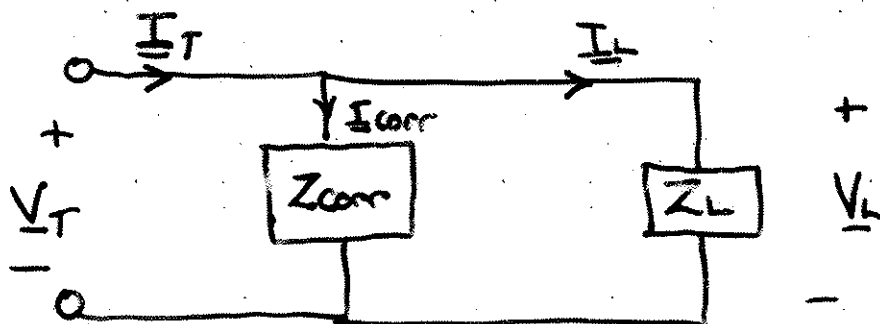- Now suppose we want to increase the power factor while keeping the average power the same.
- We will try to do this with an element in parallel.



$$S_T = P_{AV,L} + j Q_T$$

and desired power factor is $\cos(\theta_T) = \text{pfc}$

What is Q_{corr} ?

$$Q_{\text{corr}} = Q_T - Q_L$$

$$= P_{AV,L} \tan(\theta_T) - Q_L$$

$$= P_{AV,L} \tan(\cos^{-1}(\text{pfc})) - Q_L$$

~~to find~~

$$Q_{\text{corr}} = \text{Im} \left\{ \frac{\underline{V}_T \underline{I}_{\text{corr}}^*}{2} \right\}$$

If $Q_{\text{corr}} < 0$ it will be a capacitor

$$\Rightarrow \underline{I}_{\text{corr}} = j\omega C \underline{V}_T$$

$$\Rightarrow Q_{\text{corr}} = - \frac{|\underline{V}_T|^2 \omega C}{2}$$

Seeing as we have found Q_{corr} we can find C

Recall $S_L = P_{AV,L} + j Q_L$

Recall that complex powers are additive

$$\Rightarrow S_T = \frac{V_T I_T^*}{2} = S_L + S_{corr} \quad (*)$$

How to choose Z_{corr} so that S_T has the desired power factor.

Eqn (*) is a complex sum.

- we want the real part to stay the same and the imaginary part to change in order to obtain the new power factor.

Consider the case where both S_L and S_T have lagging power factors.

