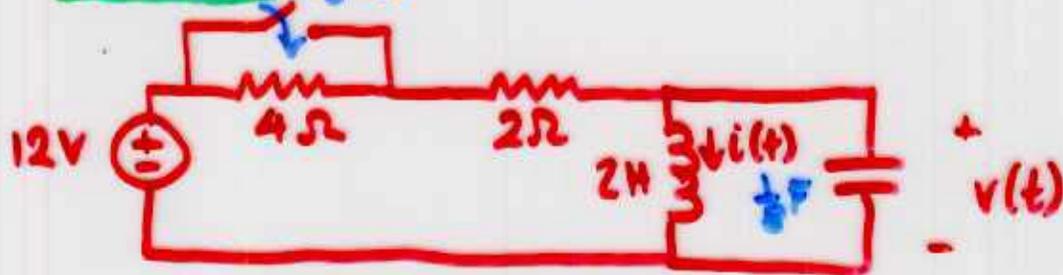


CIRCUIT ANALYSIS in the "s-domain"


- ① Transform all signals into "s-domain"
- ② Replace circuit elements by their "s-domain" equivalents; eg impedance + initial condition
- ③ Do node/mesh analysis in "s-domain" to obtain Laplace transform of desired signal
- ④ Take inverse Laplace Transform to obtain time domain signal.

Example: $t=0$



Find $v(t)$, $t \geq 0$

Steps ① and ②, for $t \geq 0$ we have

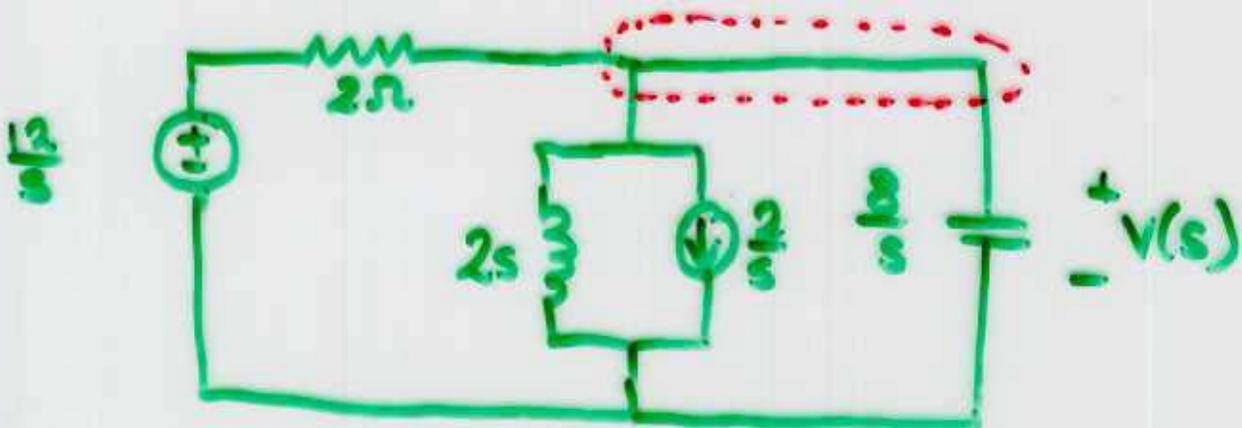

NOTE THAT $i(0) = 2A$, $v(0) = 0V$


③ KCL at marked node.



$$\Rightarrow v(s) = \frac{32}{s^2 + 4s + 4} = \frac{32}{(s+2)^2}$$

Using tables + linearity $\Rightarrow v(t) = 32t e^{-2t} u(t)$

EXAMPLE:

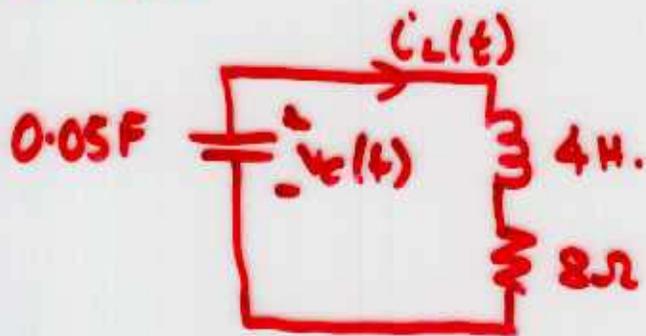

Find $i_L(t)$, $t \geq 0$ if $v_c(0) = 8V$ and $i_L(0) = 1A$.

EQUIVALENT MODEL.



KVL


$$\frac{8}{s} - \frac{1}{Cs} I(s) = 4sI(s) - 4 + 8I(s)$$

$$\Rightarrow I(s) = \frac{4 + 8/s}{\frac{1}{5}s + 4s + 8} = \frac{s+2}{s^2 + 2s + 5}$$

$$= \frac{s+1}{(s+1)^2 + 4} + \frac{1}{2} \left(\frac{2}{(s+1)^2 + 4} \right)$$

$$\Rightarrow i_L(t) = \left[e^{-t} \cos 2t + \frac{1}{2} e^{-t} \sin 2t \right] u(t)$$


EXAMPLE

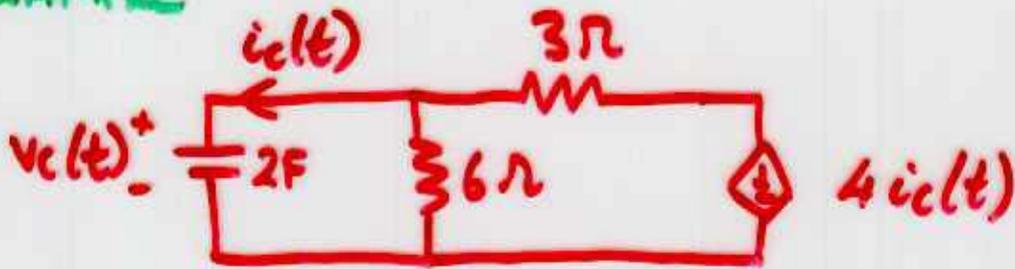

Find $v_c(t)$ for $t \geq 0$ if $v_c(0) = 4V$

SOLUTION

Equivalent diagram

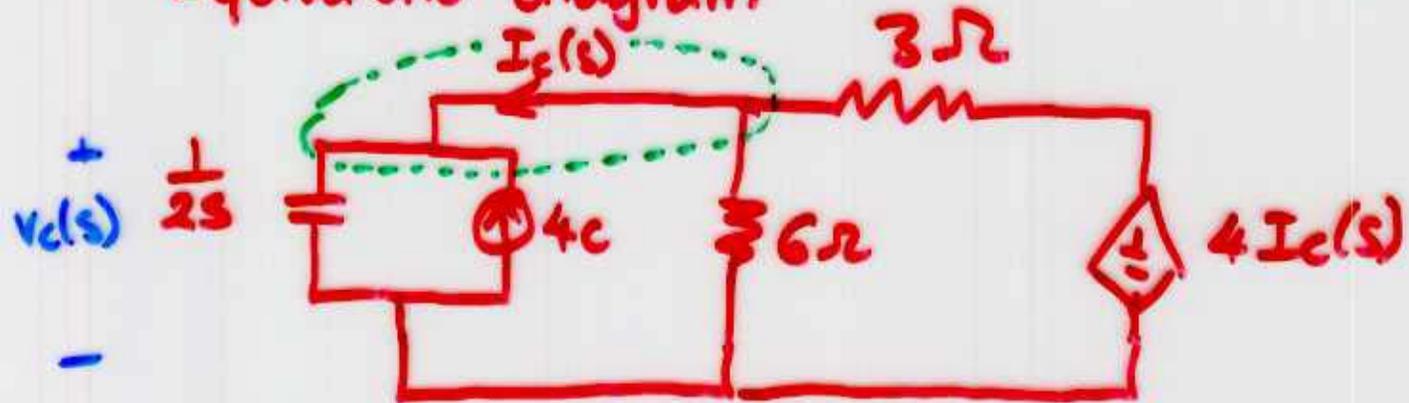

KCL at green node

Capacitor current $I_c(s) =$

$$\Rightarrow V_c(s) = \frac{4}{s - 3/4}$$

$$\Rightarrow v_c(t) =$$

Does this ring alarm bells?

TRANSFER FUNCTION

The transfer function of a circuit is defined as the ratio

$$H(s) = \frac{\text{Laplace Transform of output signal}}{\text{Laplace Transform of input signal}}, \quad (\leftrightarrow)$$

provided all initial conditions are zero.

- * This is sometimes called the "zero-state response"
- * It is closely related to the "network function" for the steady state response to sinusoidal signals.
- * If the signals are voltages, then (\leftrightarrow) implies that

$$V_{out}(s) = H(s) V_{in}(s).$$

So once we have $H(s)$ we can find the zero state response to almost any input signal

A particularly important signal is the unit step. The response is called the "step response"

$$\text{since } \mathcal{L}\{u(t)\} = \frac{1}{s}$$

if $V_{sr}(t)$ denotes the step response, then

$$V_{sr}(s) = \frac{H(s)}{s}$$

• When input is a current and output is a voltage, $H(s)$ is often said to be an "impedance"


$$H(s) = Z(s) = \frac{V_{out}(s)}{I_{in}(s)}$$

• When input is a voltage and output is a current, $H(s)$ is often said to be an "admittance"


$$H(s) = Y(s) = \frac{I_{out}(s)}{V_{in}(s)}$$

STEP RESPONSE EXAMPLE

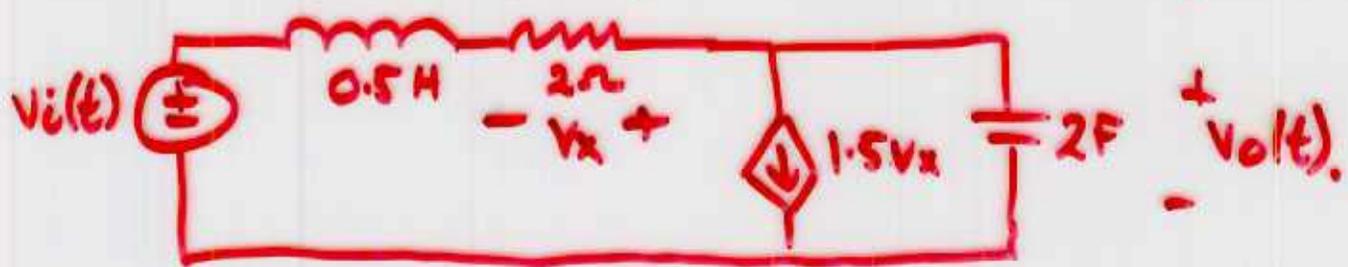Determine the step response of the following circuit



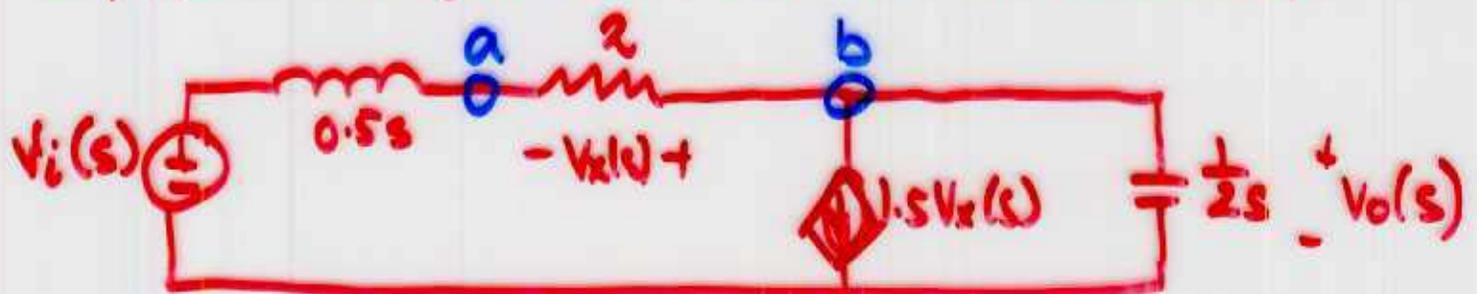Equivalent diagram with zero initial conditions



Node equations at a and b.



$$\Rightarrow V_b(s) = \frac{4}{(s+2)^2} V_i(s)$$

Since $V_b = V_o$, $H(s) = \frac{4}{(s+2)^2}$

Step response = $\mathcal{L}^{-1} \left\{ \frac{H(s)}{s} \right\}_0$

= $\mathcal{L}^{-1} \left\{ \right\}$

$$\Rightarrow \text{stepresponse} = [1 - e^{-2t} - 2te^{-2t}] u(t)$$