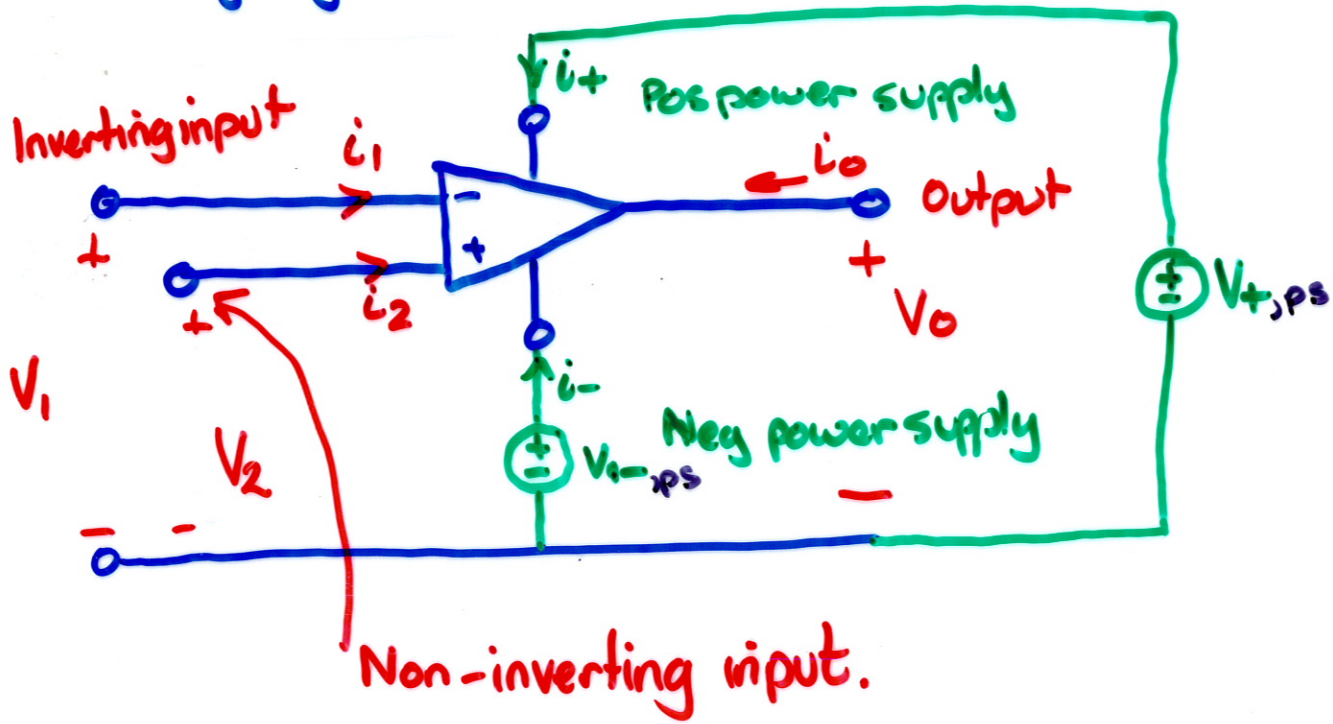


OPERATIONAL AMPLIFIERS

- an important integrated circuit for analog circuit design
- originally designed for analog computation
- Simply speaking, a very good voltage amplifier

CHAPTER 6: OPERATIONAL AMPLIFIERS (OP-AMPS)

- high gain active circuit element (Fig. 6.3-2)




- Power supplies – bias the amplifier, but have few other effects.
 - often omitted from simplified models, but we must be careful to include them where needed
 - Example: KCL implies that

$$i_1 + i_2 + i_0 + i_+ + i_- = 0$$

- Hence try to avoid KCL at op amps.


How do we model op amps?

Typical characteristic

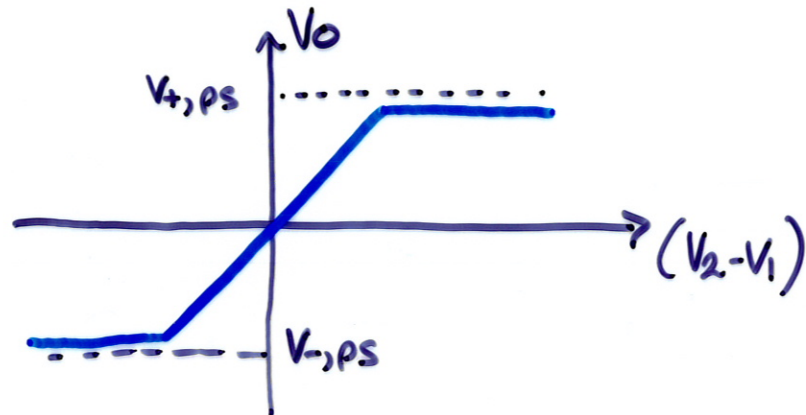


Hence, for input voltages such that $|v_o| < V_{sat}$
for output loads such that $(i_o) < i_{sat}$

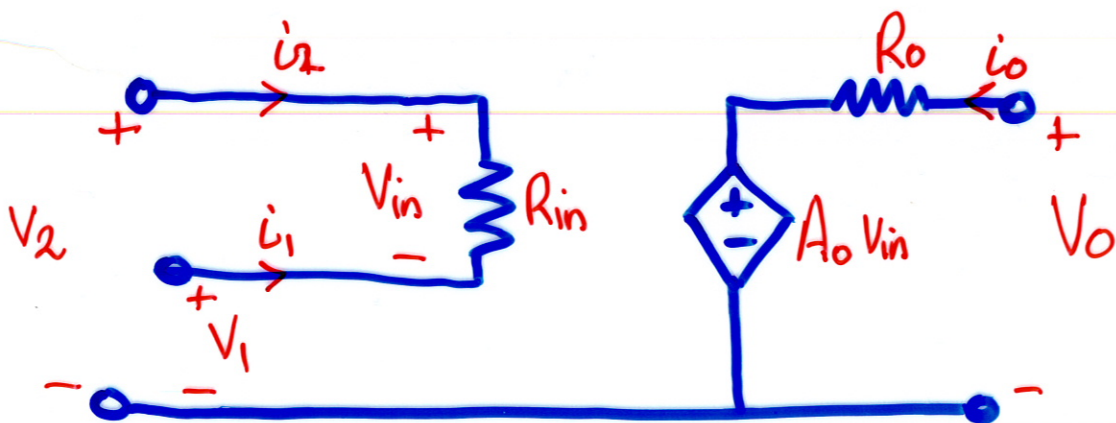
The op amp can be approximated by a simple linear model.



CONSIDER THE OP AMP IN A SIMPLE CIRCUIT

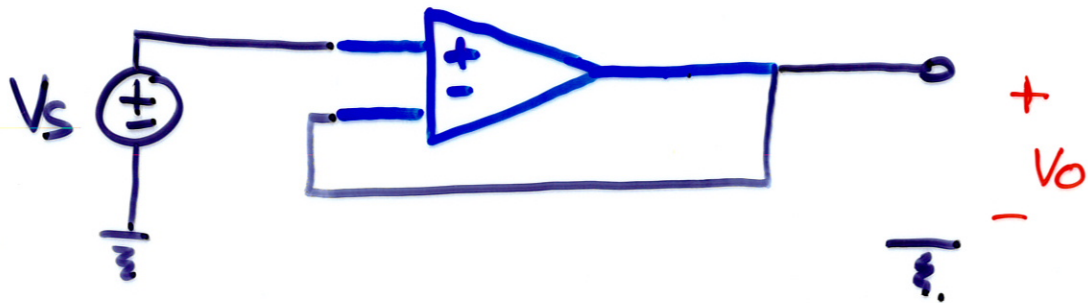

Replace op amp by its model.

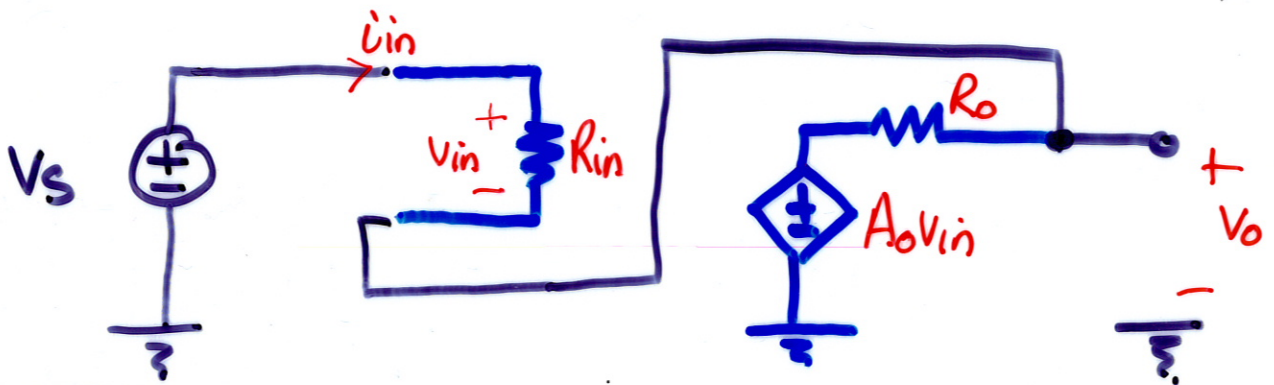

KCL at output node:

$$\frac{V_s - V_o}{R_{in}} = \frac{V_o - A_0 V_{in}}{R_o}$$

Controlling voltage:

$$V_{in} = V_s - V_o$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{1}{1 + \frac{R_{in}}{R_o + A_0 R_{in}}}$$

Typically, $R_{in} \gg R_o$

$$\Rightarrow \frac{V_o}{V_s} \approx \frac{1}{1 + \frac{1}{A_o}}$$

Typically, $A_o \gg 1$

$$\Rightarrow \frac{V_o}{V_s} \approx 1$$

This circuit often called "voltage follower"
or "buffer amplifier"

Typically,

R_{in} is of the order of many $M\Omega$


R_o 10-100 Ω

A_o 10^5

Large $R_{in} \Rightarrow$ input current is small

Large $A \Rightarrow V_{in} = V_s - V_o$ is small


Suggests an idealized op amp model.

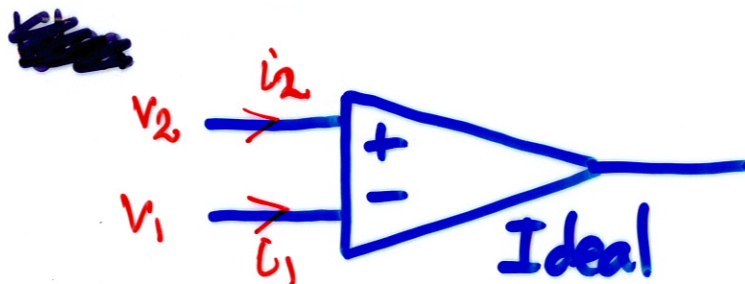

$$V_2 - V_1 = 0$$

$$i_1 = i_2 = 0$$

Try this in voltage follower circuit

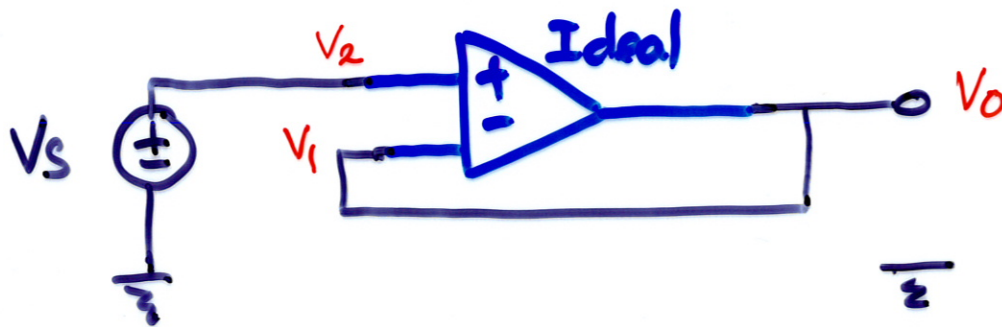

$$V_2 = V_s$$


$\Rightarrow V_1 = V_s$, ideal op amp model

$$\Rightarrow V_o = V_1$$

$$\Rightarrow V_o = V_s$$

"BUFFERING"

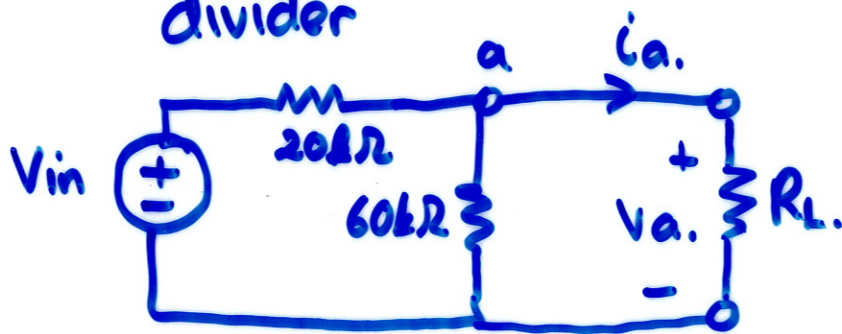- when we place a load on a circuit, it can change its performance
- Op-amps (in voltage follower form) are often used to isolate, or buffer circuits from such "loading"
- Consider the following example of a voltage divider



KCL at node A

$$\frac{V_{in} - V_a}{20k} = \frac{V_a}{60k} + \frac{V_a}{R_L}$$


$$\Rightarrow \frac{V_a}{V_{in}} = \frac{3R_L}{4R_L + 60 \times 10^3}$$

$$\text{if } R_L \gg 60 \times 10^3, \quad \frac{V_a}{V_{in}} \approx \frac{3}{4}$$

$$\text{However, if } R_L = 30 \times 10^3 \quad \frac{V_a}{V_{in}} = \frac{1}{2}$$

IN SOME CIRCUITS IT IS VERY HARD TO CHANGE R_L + the source resistors (this is why cell phones cost so much to make)

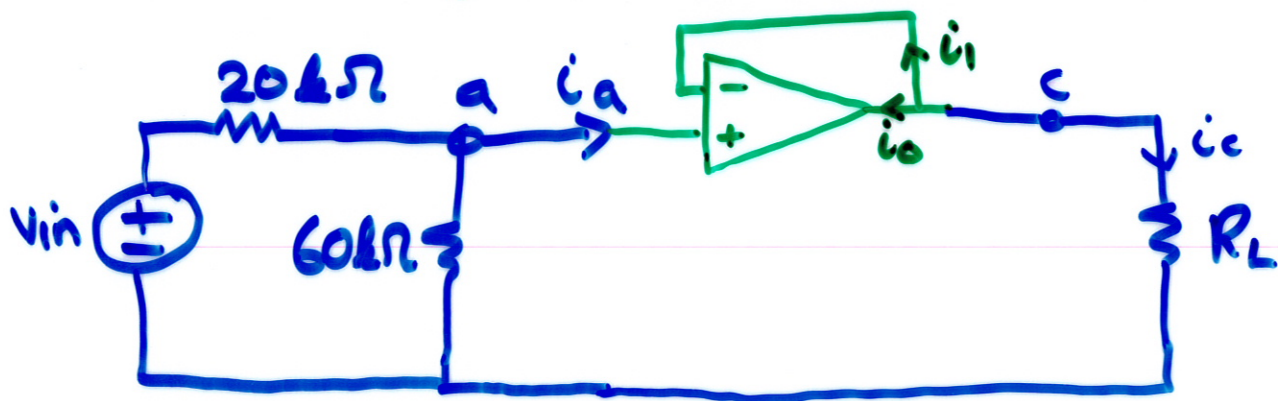To get around the loading problem, we can use a voltage follower as a "buffer"



KCL at node a.

$$\frac{V_{in} - V_a}{20k} = \frac{V_a}{60k} + i_a$$

KCL at node c

$$i_o + i_1 + \frac{V_c}{R_L} = 0.$$

Ideal op amp $\Rightarrow i_a = 0, i_1 = 0$


Ideal op amp and short ckt feedback

$$\Rightarrow V_a = V_c$$

$$\Rightarrow V_c = \frac{3}{4} V_{in}, \text{ indep of } R_L$$

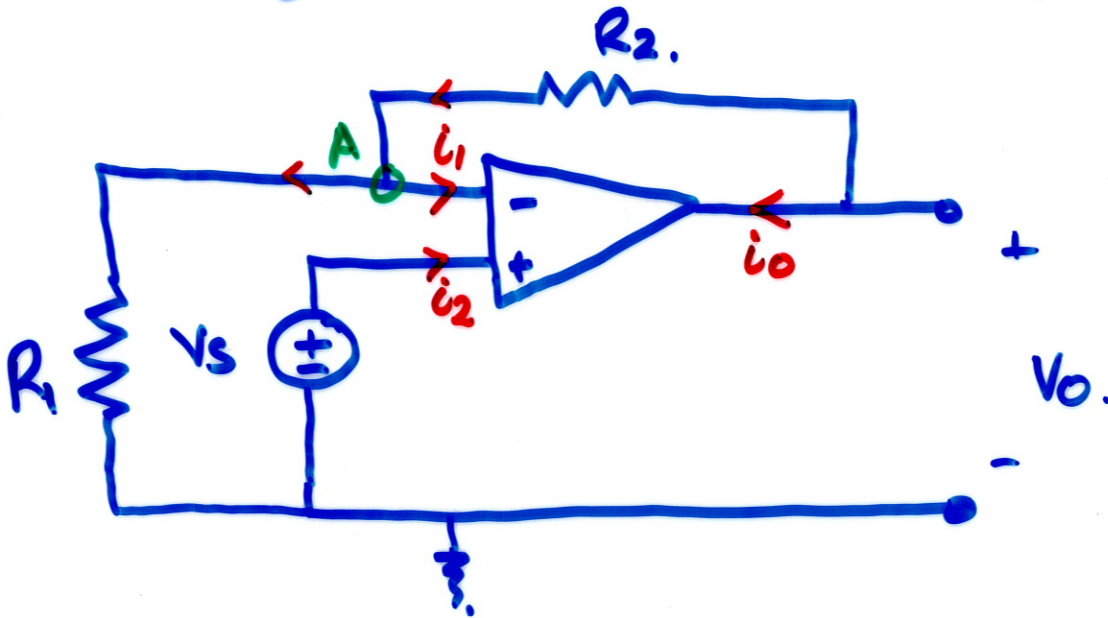EXAMPLE

Find the gain V_o/V_s for the following circuit with an ideal op-amp.



KCL at node A

current in = current out

$$\Rightarrow \frac{V_o - V_a}{R_2} = i_1 + \frac{V_a}{R_1}$$

$$\text{Ideal op-amp} \Rightarrow i_1 = 0$$

$$\text{Ideal op-amp} \Rightarrow V_a = V_s$$

$$\Rightarrow \frac{V_o}{R_2} = V_s \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$