

Dr. Mohamed Bakr, EE2C15, 2007

Note Title


10/4/2007

Lecture 12

From Section 5.3 of Textbook

Solve E5.3, E5.4, E5.5, 5.27, 5.32,
5.34, 5.37, 5.39, 5.46, 5.48, 5.5,

Thévenin's Theorem

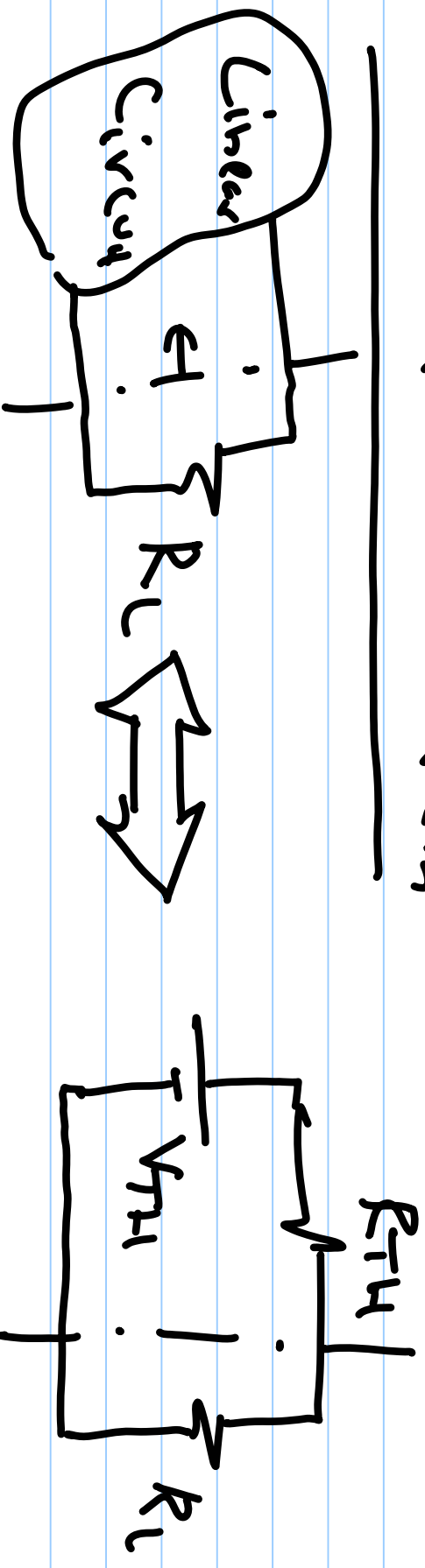


* Looking from one side of a plane,
any linear circuit can be replaced
by a voltage source in series with a
resistance

Thévenin's Theorem (Cont'd)

* Once V_{TH} and R_{TH} are determined, we can easily determine I_L and V_L for different load values

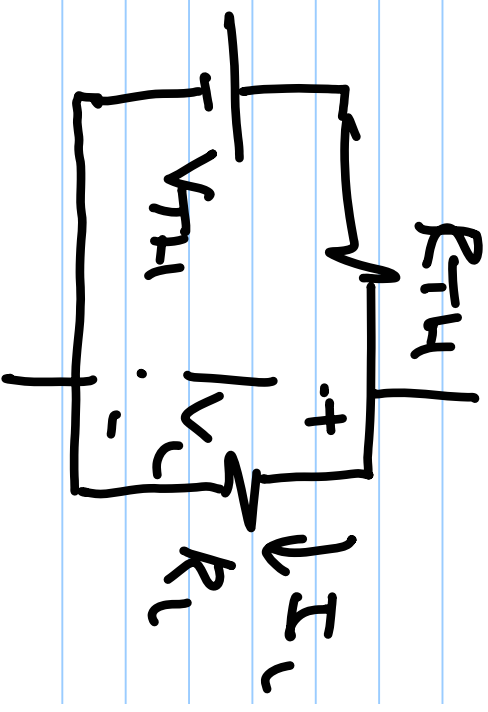
* Thévenin's theorem is a direct consequence of linearity



Determining V_{TH} and R_{TH}

1- Remove R_L


$$V_{TH} = V_{oc}$$

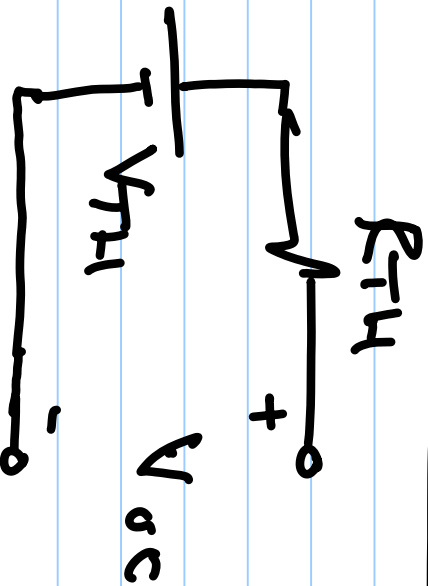


2- Short Circuit R_L

$$I_{sc} = \frac{V_{TH}}{R_{TH}}$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

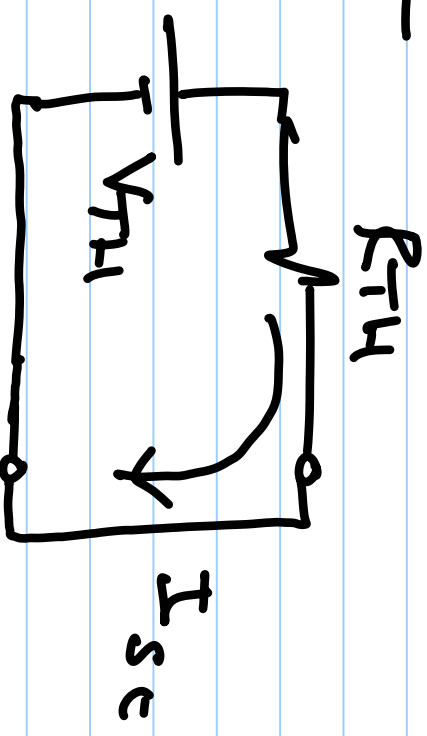


An Alternative Method

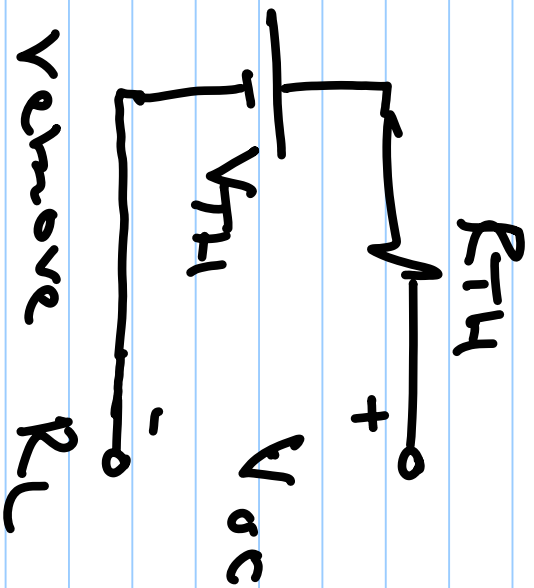

1. Remove R_L


$$V_{TH} = V_{oc}$$

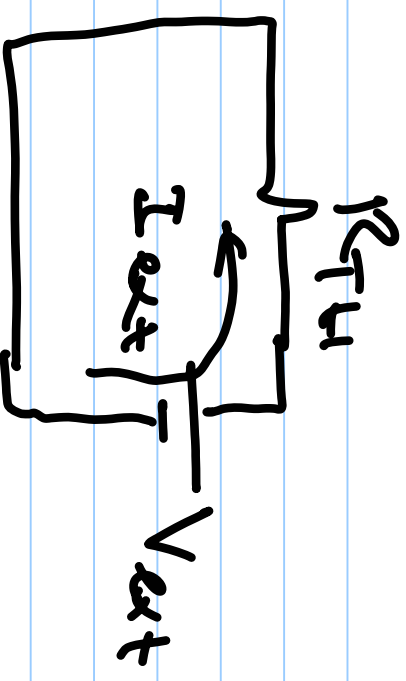

2. Make $V_{TH} = 0$ by removing all independent sources $\Rightarrow R_{TH} = \frac{V_{ext}}{I_{ext}}$


* For Circuits with no independent sources $V_{TH} = 0$

Example

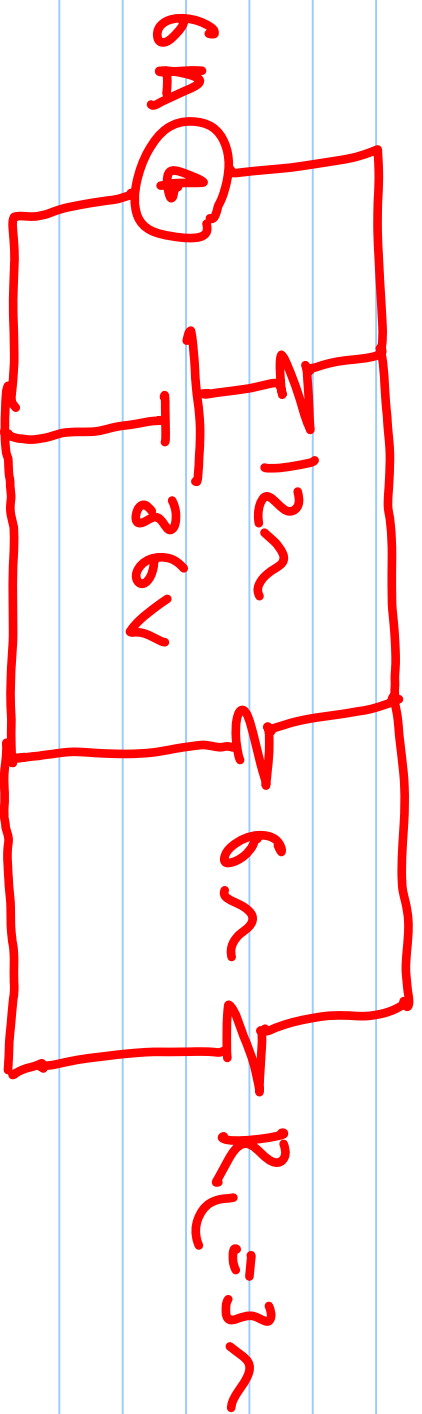


Find the current in the 3Ω resistor
Using Thévenin's theorem. What is
the current if $R_L = 10\Omega$.

Example

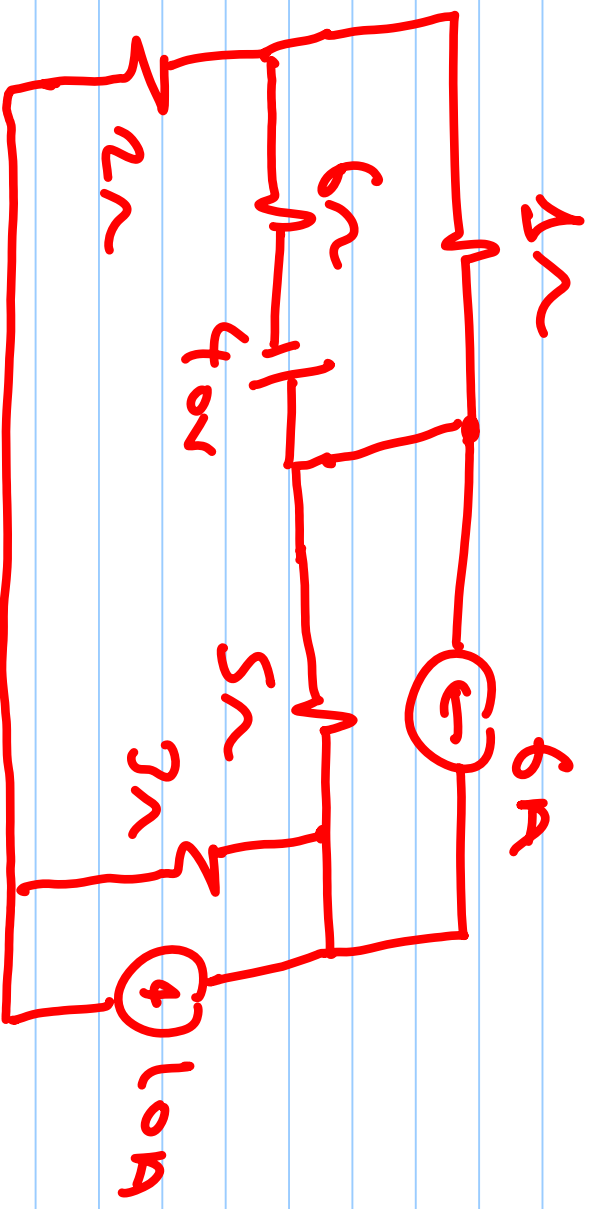

Determine the current in the 2Ω resistor using Thevenin's theorem

Example

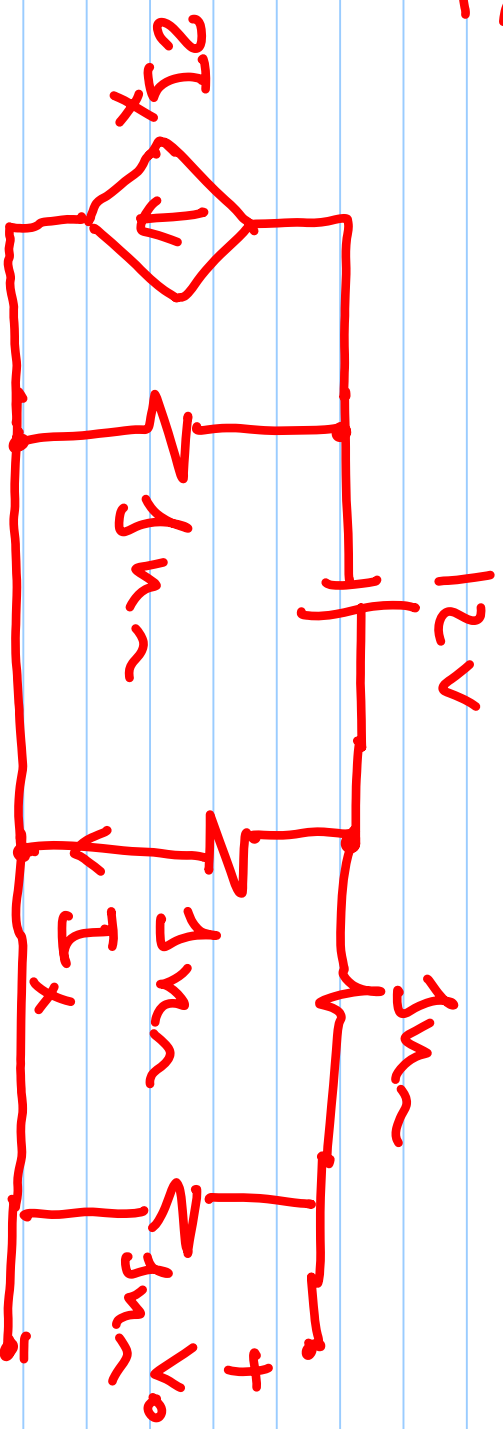

Use Thevenin's theorem to find V_o