

# Lecture 4


From Sections 2.4 - 2.6 of Textbook

Solve E2.10 - E2.16 and

2.38, 2.40, 2.41, 2.43, 2.44, 2.48,  
2.51, 2.53, 2.55, 2.61, 2.63, 2.70

# Current Divider

\* Using KCL

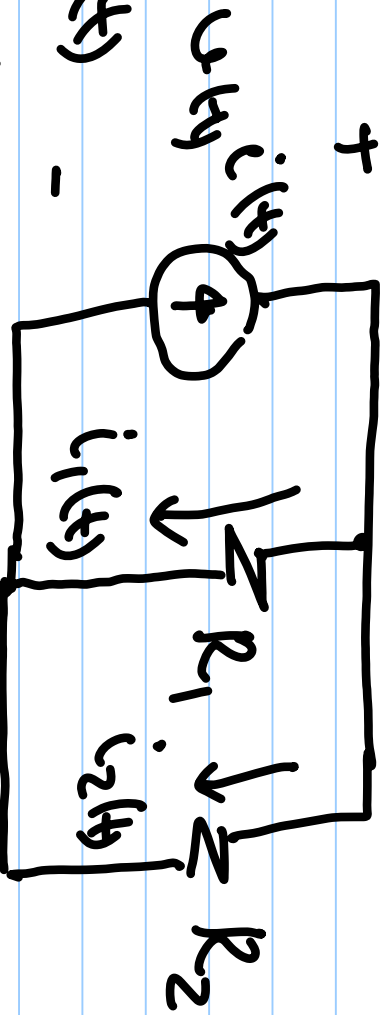

$$i(t) = i_1(t) + i_2(t)$$

$$i(t) = \frac{u(t)}{R_1} + \frac{u(t)}{R_2}$$

$$\Rightarrow i(t) = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) u(t) \Rightarrow i(t) = G_p u(t)$$

$$\Rightarrow G_p = \frac{1}{R_p} \text{ where } R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

## Current Divider (Cont'd)

$$i(t) = \left( \frac{R_1 + R_2}{R_1 R_2} \right) v(t) \Rightarrow v(t) = \frac{R_1 R_2}{R_1 + R_2} i(t)$$

$$i_1(t) = \frac{v(t)}{R_1} \Rightarrow i_1(t) = \frac{R_2}{R_1 + R_2} i(t)$$


$$i_2(t) = \frac{v(t)}{R_2} \Rightarrow i_2(t) = \frac{R_1}{R_1 + R_2} i(t)$$

The smaller resistor gets more

current!
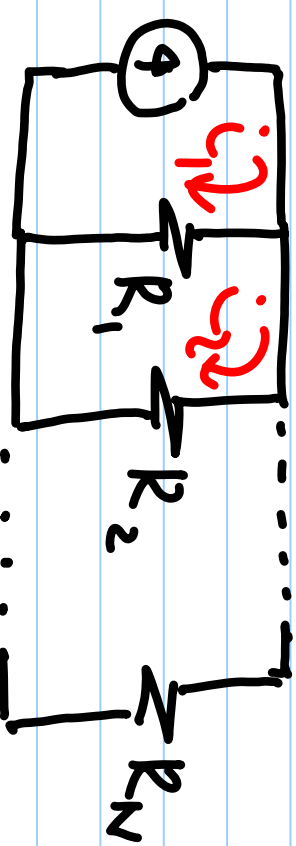
# Multiple Parallel Resistors

\* The previous result can be generalized to the case of  $N$  resistors in parallel




$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

$$i_1 = \frac{(R_2 + R_3 + \dots + R_N)}{(R_1 + R_2 + \dots + R_N)} i \quad | \quad i_k =$$


$$\frac{\sum_{k \neq i} R_k}{\sum_{k=1}^N R_k} i$$

# Example

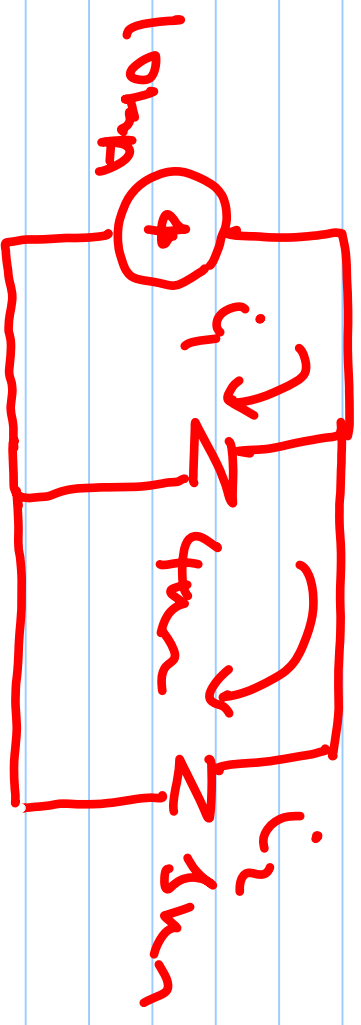

Find  $i_1(t)$  and  $i_2(t)$

## Multiple Sources

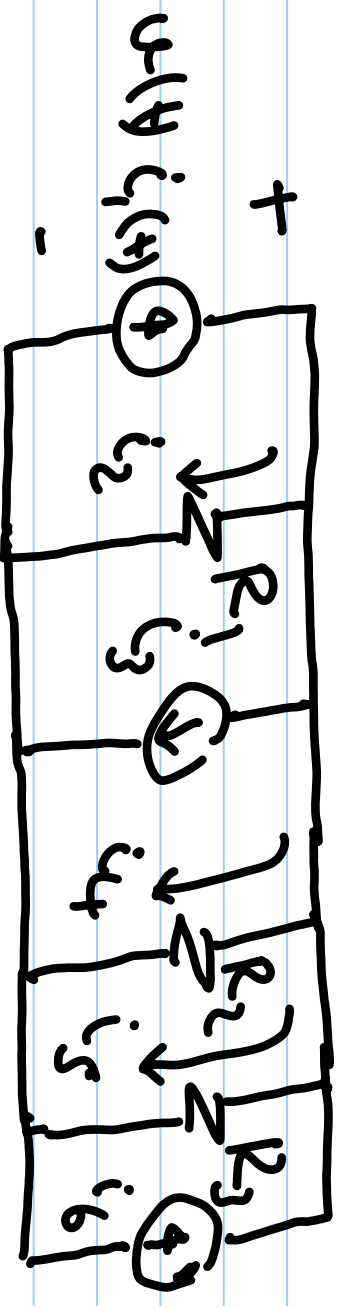

Applying KCL, we get

$$i_1 + i_6 = i_2 + i_3 + i_4 + i_5$$

$$\Rightarrow i_1 - i_3 + i_6 = i_2 + i_4 + i_5$$


$$\Rightarrow i_1 - i_3 + i_6 = u(t) \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

## Multiple Sources (cont'd)


$$\Rightarrow i_{eq} = u(t) \text{ Geq} \Rightarrow u(t) = i_{eq} R_{eq}$$

$$i_{eq} = i_1 - i_2 + i_6$$
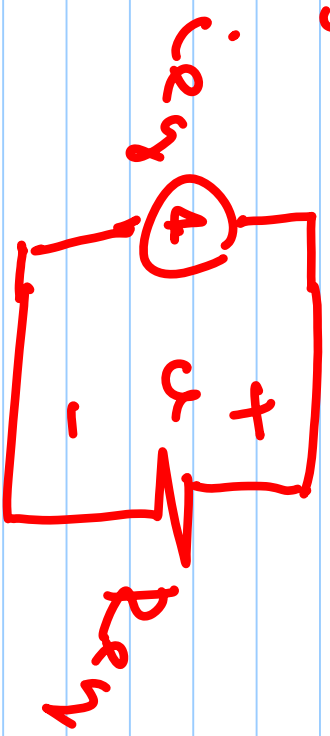
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$




# Example

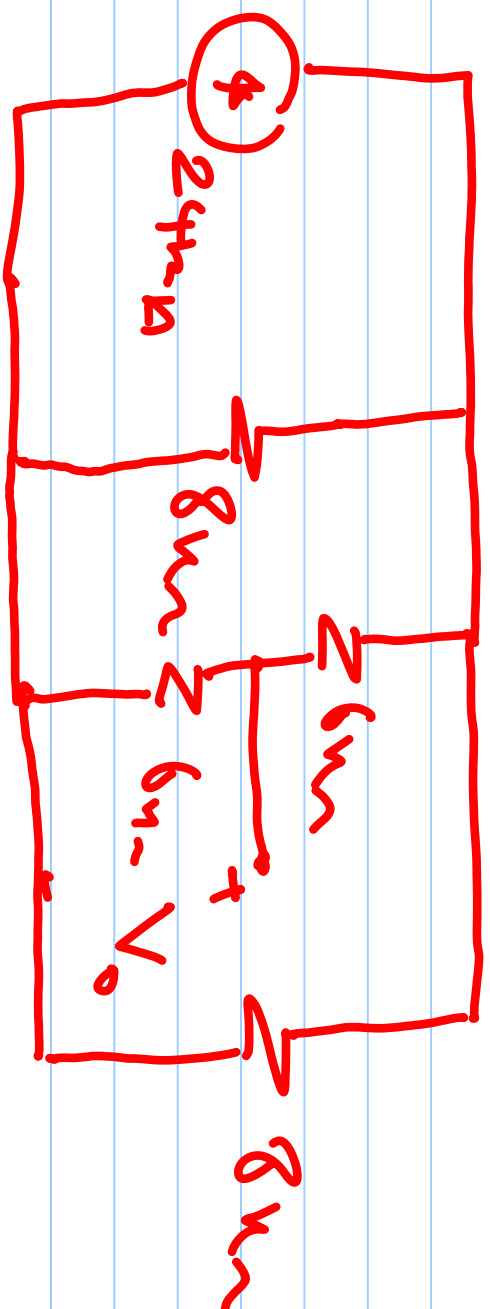

Find  $V_o$  in the shown circuit



## Example

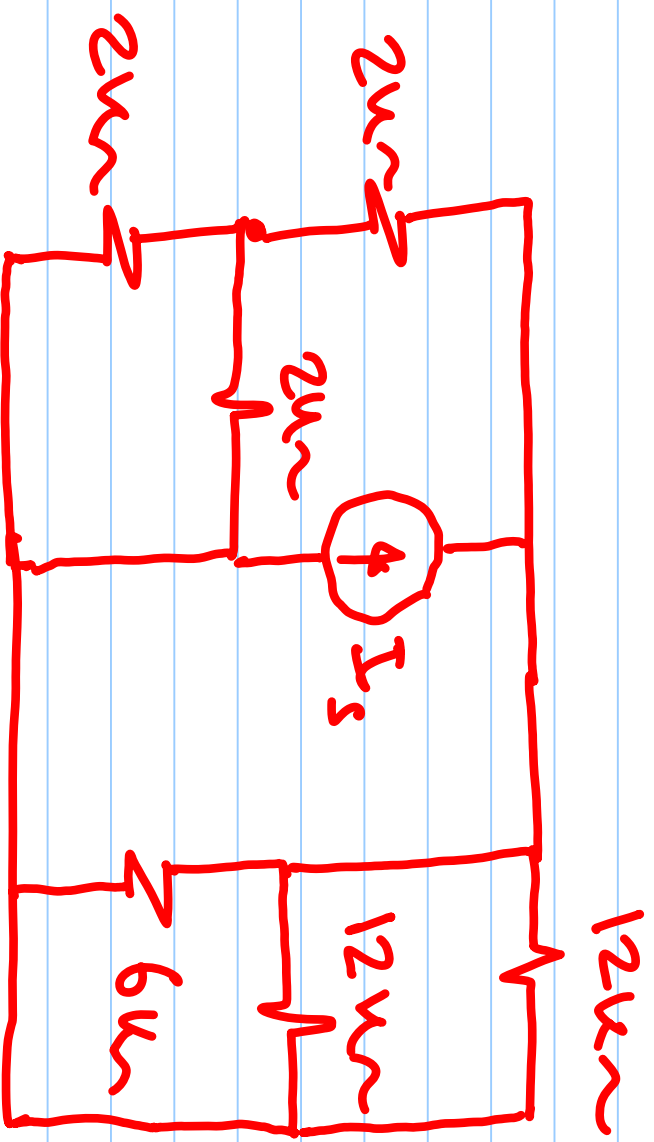


If  $P_{6\text{k}\Omega} = 56\text{mW}$ , find  $I_s$

## Series and Parallel Combinations

\* Most Circuits Contain a Combination of Series and Parallel Connections.

\* Networks are reduced to much simpler circuits



## Example

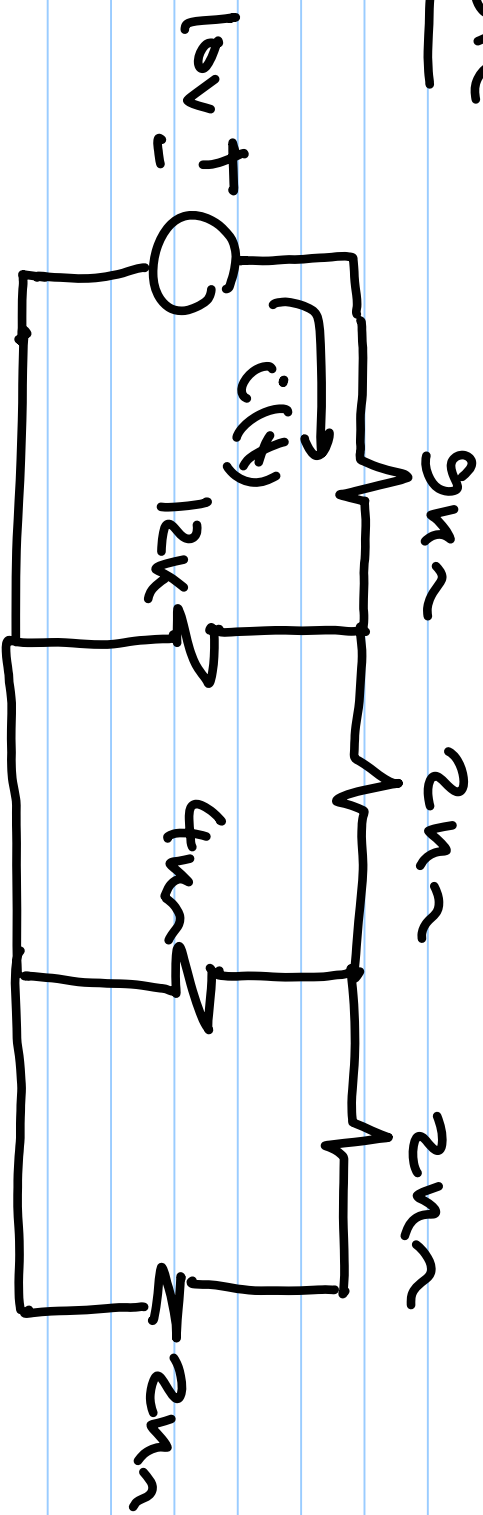


For the shown circuit find  $i(t)$ .

Sol:  $i(t) = \frac{10V}{R_{eq}}$


# Example (Cont'd)

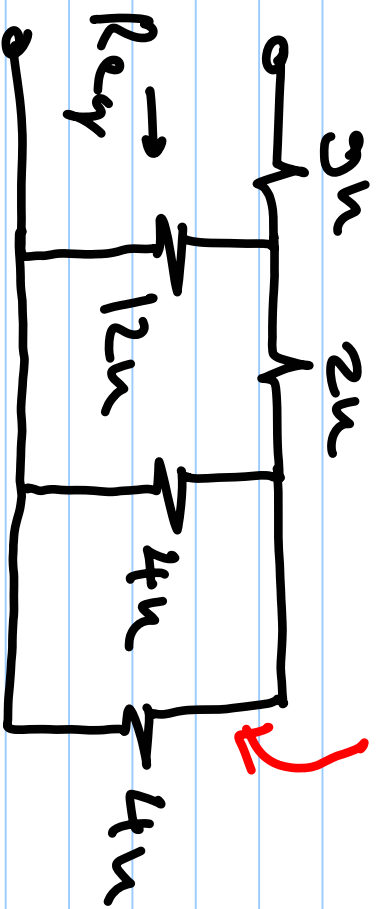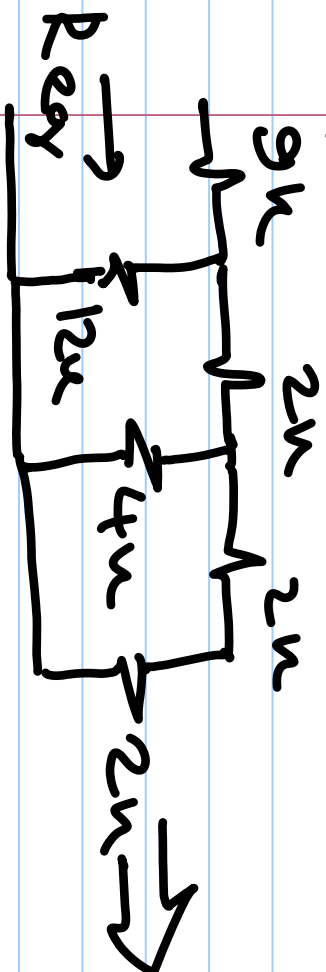

$2k + 2k$

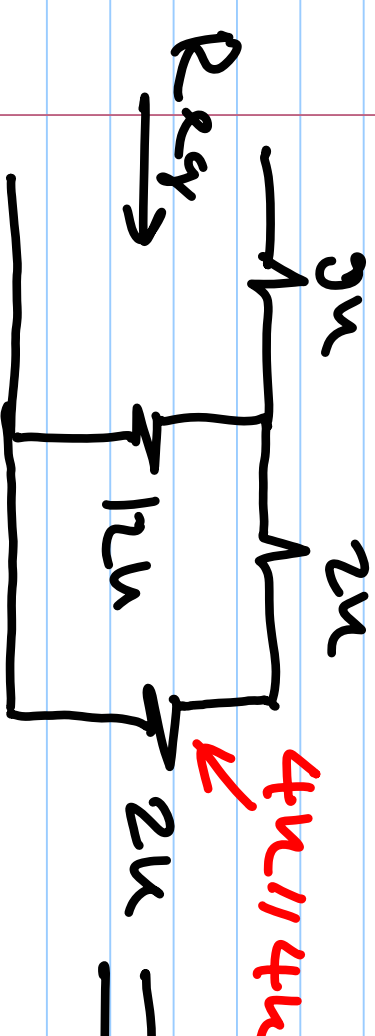


$4k || 4k$

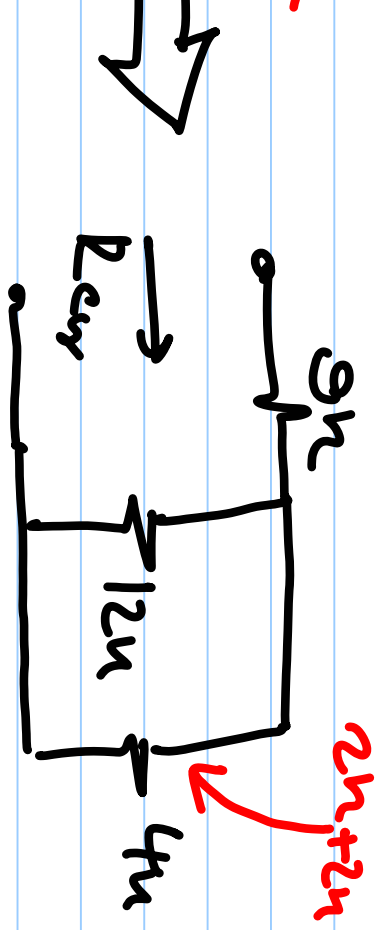

$2k + 2k$


# Example (cont'd)

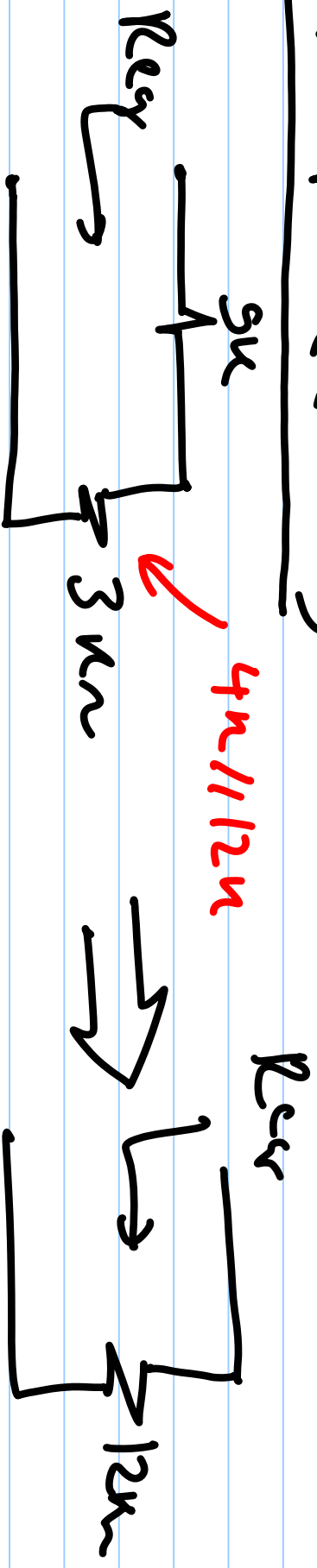

$$R_{eq} = 12\text{k}\Omega$$

$$i(t) = \frac{v(t)}{R_{eq}} = \frac{10}{12\text{k}\Omega} = 0.83\mu\text{A}$$

# Example

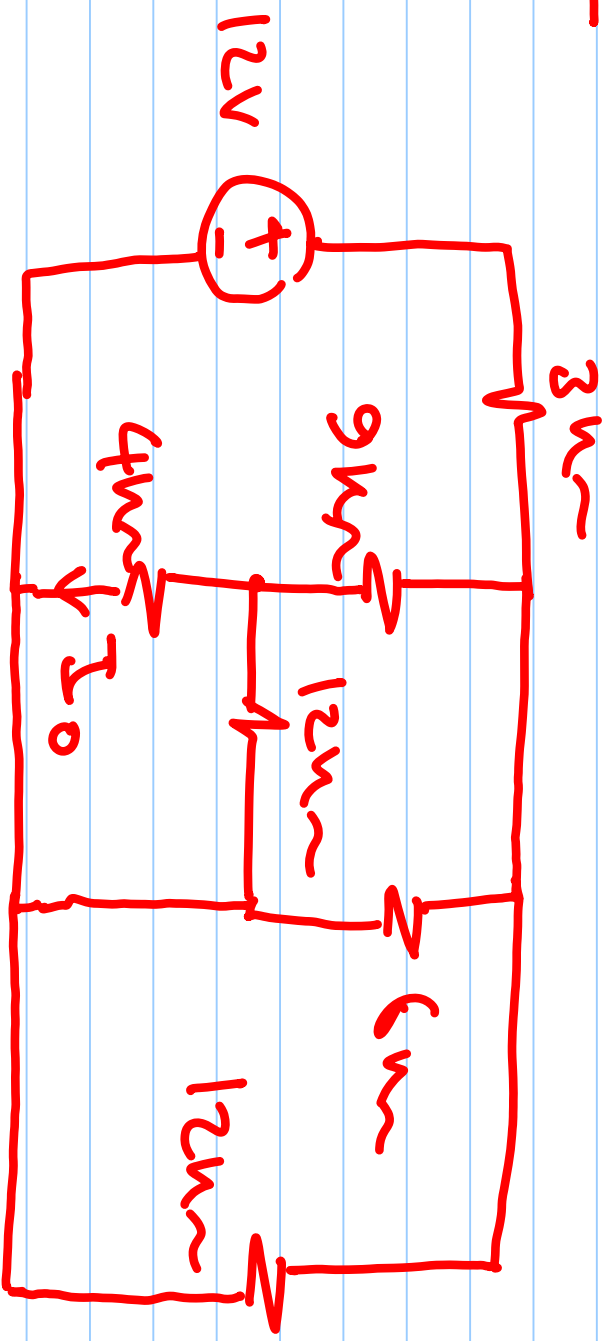

Find  $I_0$  in the shown circuit