

Dr. Mohamed Bakr, EE2C15, 2007

Note Title

9/16/2007


Lecture 6

From Section 3.1 of Textbook

Solve E3.1 - E3.4, 3.2, 3.4

Nodal Analysis

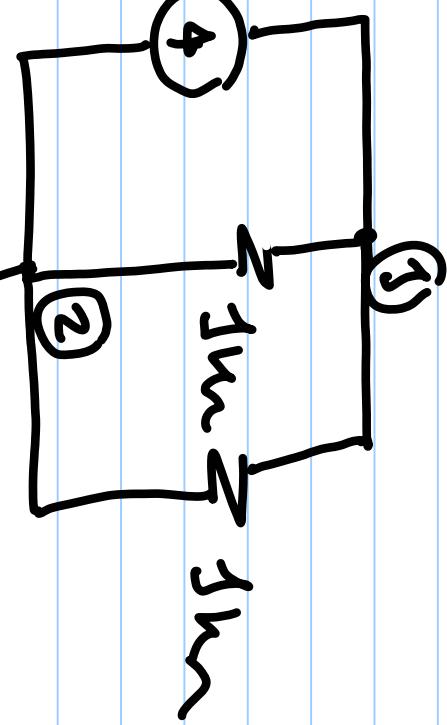
- * The shown circuit contains 2 nodes. 1A
- * The lower node is selected as the reference node (ground node)
- * The voltage of node relative to ground ($V_1 - V_2 = V_A$) is sufficient to get all currents



Nodal Analysis (Cont'd)

- * for a circuit with N nodes, we pick one node as ground. Our unknowns are the voltages of the $N-1$ other nodes relative to ground
- * KCL is written for each of these nodes to obtain $(N-1)$ equations in the $N-1$ unknowns

Example

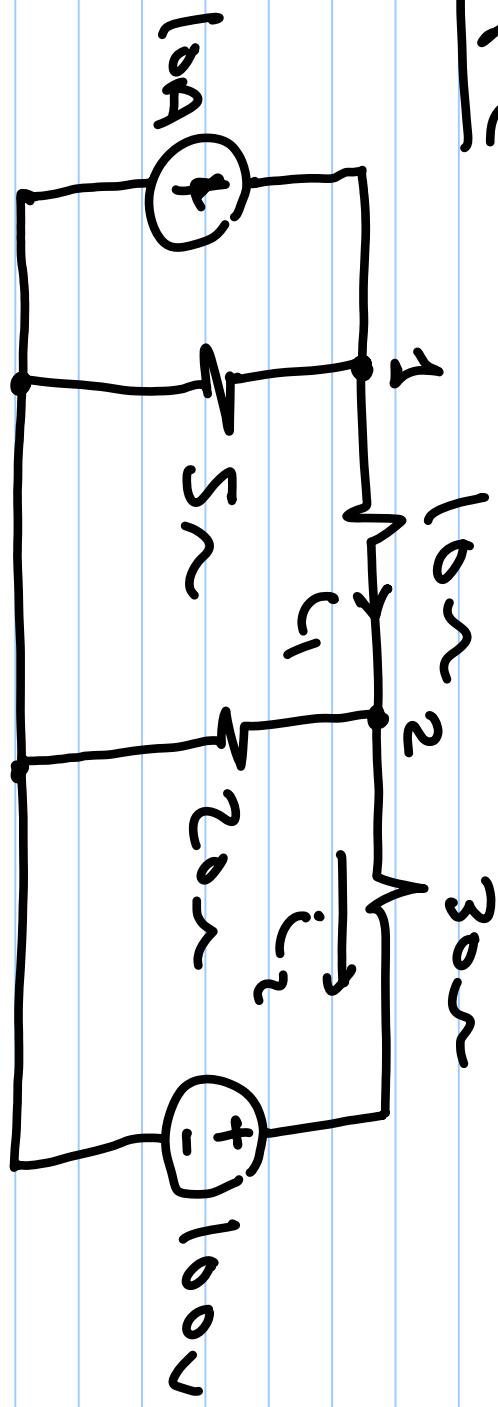


Utilize nodal analysis to solve for
the currents in all branches

Example (Cont'd)

- * This circuit contains 3 nodes.
- * The bottom node is selected as ground
- * We need 2 equations to solve for v_1 and v_2 , the nodal voltage relative to ground
- * KCL is applied to obtain these equations

Example (cont'd)

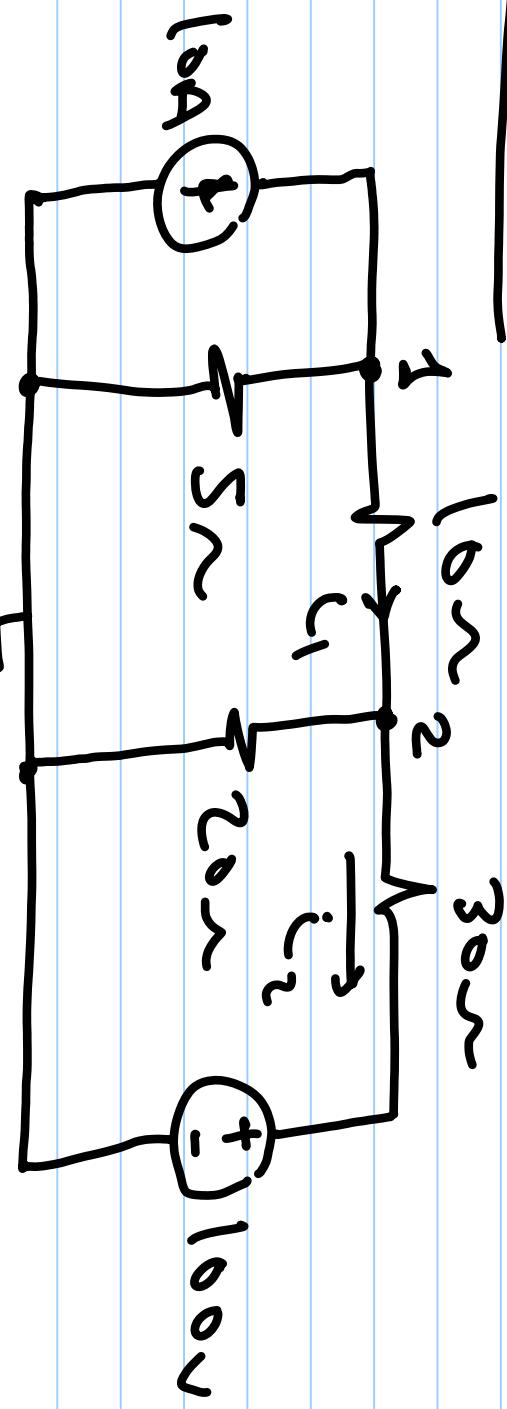

1st eq:

$$\frac{U_1}{5} + \left(\frac{G_1 - G_2}{10} \right) - 10 = 0$$
$$+ \frac{G_2}{2} + \frac{G_2 - G_3}{30} - (\frac{G_1 - G_2}{10}) = 0$$
$$= 0$$

2nd eq:

Example (Cont'd)

* arrangements, we have

$$\frac{3}{10} \underline{v}_1 - \frac{1}{10} \underline{v}_2 = 10 \quad \rightarrow \textcircled{1}$$

$$-\frac{1}{10} \underline{v}_1 + \frac{11}{60} \underline{v}_2 = \frac{10}{3} \quad \rightarrow \textcircled{2}$$

in matrix form

$$\begin{bmatrix} 3/10 & -1/10 \\ -1/10 & 11/60 \end{bmatrix} \begin{bmatrix} \underline{v}_1 \\ \underline{v}_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10/3 \end{bmatrix} \Rightarrow \bar{G}\underline{v} = \underline{I}$$

Example (Cont'd)

* Using Gaussian elimination

$$\left| \begin{array}{ccc|c} & & & 0 \\ & & & -1 \\ & & & -\frac{1}{10} \\ & & & \frac{3}{10} \\ \hline & & & 0 \\ & & & -\frac{1}{3} \\ & & & \frac{1}{3} \\ & & & 1 \\ \hline & & & 0 \end{array} \right|$$

$$Q_1 = \frac{100}{3} + \frac{400}{27} = \frac{1300}{27} Q$$
$$Q_2 = \frac{70}{3} \rightarrow Q_2 = \frac{400}{9} Q$$


Example (Cont'd)

* all currents can then be evaluated

$$\dot{i}_1 = \frac{u_1 - u_2}{10} = 0.37 \text{ A}$$

$$\dot{i}_2 = \frac{u_2 - 100}{30} = -1.85 \text{ A}$$

Example

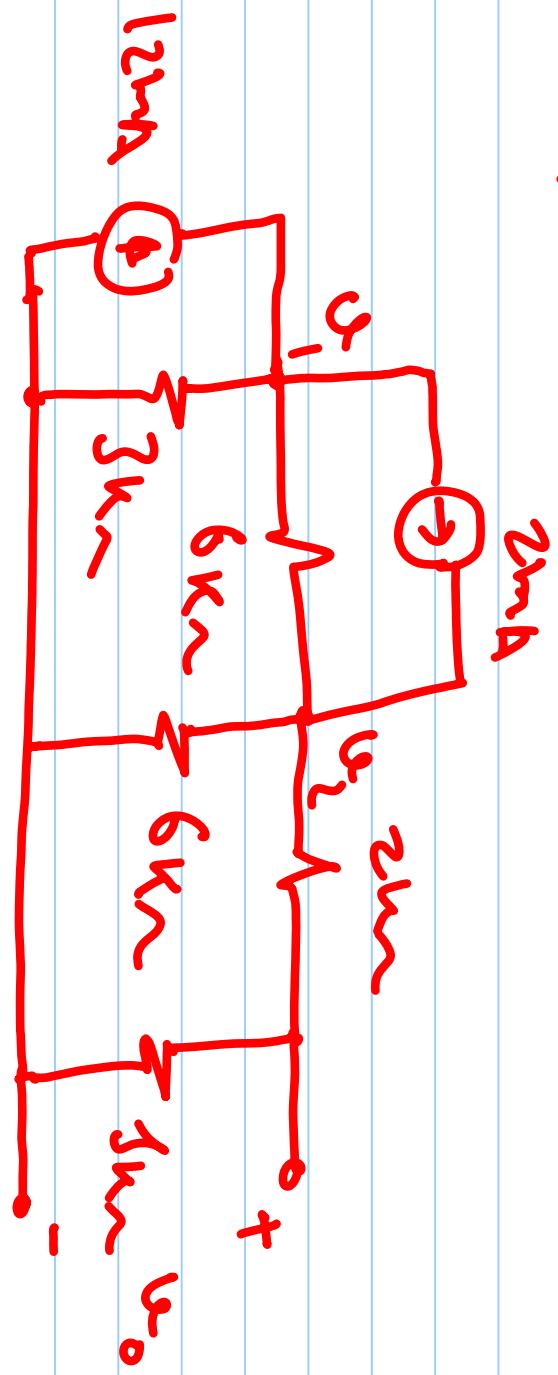

Utilize nodal analysis to solve for both
 \mathbf{Q}_1 and \mathbf{U}_o

