

# Lecture 22

From Section 8.3 and 8.4

Solve E8.3, E8.4-E8.7, 8.5, 8.6,  
8.7

## Phasor

\* phasor are time complex response function without the ejnt part

$$v(t) = A_v \cos(\omega t + \theta_v)$$



$$v(t) = \text{real}(A_v e^{j(\omega t + \theta_v)})$$



$$v(t) = \text{real}((A_v e^{j\theta_v}) e^{j\omega t})$$

## Phasors (Cont'd)

- \*  $\mathbf{v}(t) = \text{real}(\tilde{\mathbf{v}} e^{j\omega t})$
- \* the phasor  $\tilde{\mathbf{v}}$  contains all the information about amplitude and phase of the signal
- \* phasors transform differential equations to algebraic equations.

## Example

Find the phasor equivalent to  
the following signals:

$$q_1(t) = 30 \cos(120\pi t + 120^\circ)$$


$$q_2(t) = 10 \sin(60\pi t + 45^\circ)$$

$$i_1(t) = 6.1 \sin(180\pi t + 2\pi)$$

## Example


The phasor of the current through a capacitor is  $0.01 \angle -30^\circ$ . If the frequency is  $50\text{Hz}$ , find  $i(t)$ .

Example

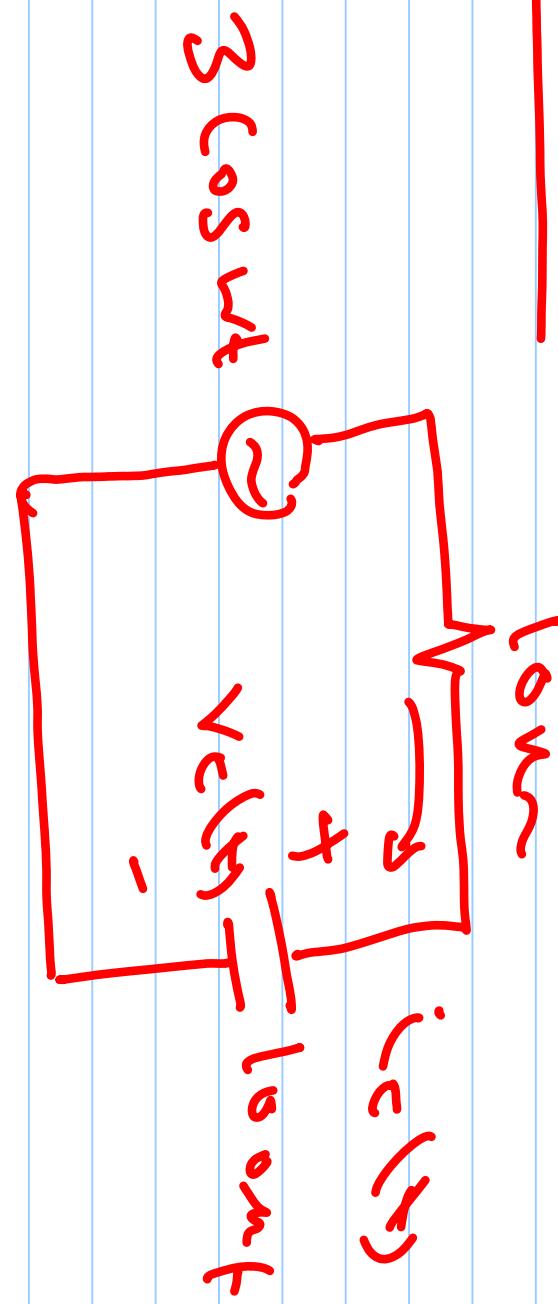

Use phasor analysis to find  
 $V_C(t)$  and  $i_C(t)$

## Example

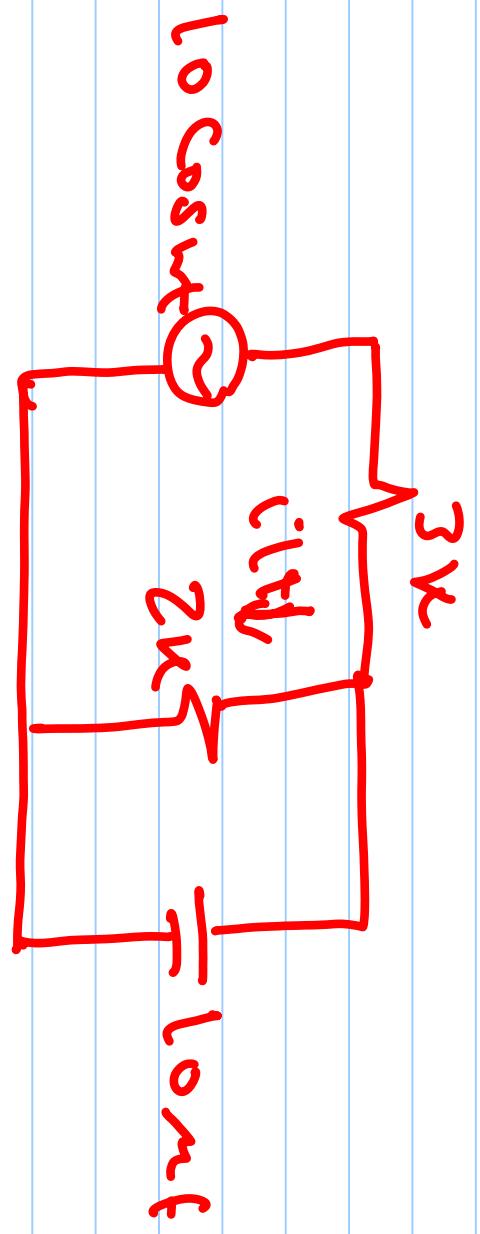

Utilize phasor analysis to find  
 $i(t)$