

Homework From Chapter 4

4.9

- $V_{GS} = 0 < V_{TN} \Rightarrow$ FET is off $\Rightarrow I_D = 0$
- $V_{GS} = 1V < V_{TN} \Rightarrow$ FET is off $\Rightarrow I_D = 0$
- $V_{GS} = 2V > V_{TN} \Rightarrow$ FET is on $V_{GS} - V_{TN} = 0.5 > V_{DS} \Rightarrow$ linear region
 $\Rightarrow I_D = \kappa_n' \frac{W}{L} (V_{GS} - V_{TN} - \frac{V_{DS}}{2}) V_{DS} = 112.5 \mu A$
- $V_{GS} = 3V > V_{TN} \Rightarrow$ FET is on $V_{GS} - V_{TN} = 1.5 > V_{DS} \Rightarrow$ linear region
 $\Rightarrow I_D = 362.5 \mu A$
- $\kappa_n = \kappa_n' \frac{W}{L} = 2.5 \text{ mA/V}^2$

4.15

a. $R_{on} = \frac{1}{\kappa_n' \frac{W}{L} (V_{GS} - V_{TN})} = 94.12 \Omega$

b. $R_{on} = 148.15 \Omega$

4.27

- a. $V_{GS} - V_{TN} = 4V < V_{DS} \Rightarrow$ saturation region
- b. $V_{GS} - V_{TN} = -1V \Rightarrow$ cutoff region
- c. $V_{GS} - V_{TN} = 1V < V_{DS} \Rightarrow$ saturation region
- d. $V_{GS} - V_{TN} = 0.5V = V_{DS} \Rightarrow$ boundary bet. linear & saturation regions
- e. $\Rightarrow V_{DS} < 0 \Rightarrow$ both source & drain are exchanged (reversed) & still we can consider the new $V_{DS} = 0.5V$, but now V_{GS} is V_{GD}
 $\Rightarrow V_{GS}' = V_{GD}' + V_{DS}' = 2.5V$
 $\Rightarrow V_{GS}' - V_{TN} = 1.5V > V_{DS}' \Rightarrow$ saturation region
- f. $V_{GS}' = V_{GD}' + V_{DS}' = 3 + 6 = 9V$
 $\Rightarrow V_{GS}' - V_{TN} = 8V > V_{DS}' \Rightarrow$ saturation region

4.35

- a. The transistor is connected such that $V_{DS} = V_{GS}$
 $\angle V_{DS} > V_{GS} - V_{TN} \Rightarrow$ The transistor is saturated

$$I_D = \frac{12 - V_{GS}}{100k} = \frac{25 \times 10^{-6}}{2} \left(\frac{10}{1}\right) (V_{GS} - 0.75)^2$$

$$\therefore 12.5 V_{GS}^2 - 17.8 V_{GS} - 4.97 = 0 \Rightarrow V_{GS} = -0.24V \text{ or } 1.66V$$

but V_{GS} can't be negative $\Rightarrow V_{GS} = 1.66V$ & $I_D = 103.4 \mu A$

b. $I_D = \frac{12 - V_{GS}}{10^5} = 12.5 \times 10^{-5} (V_{GS} - 0.75)^2 (1 + 0.025 V_{GS})$

To solve this cubic eq., we'll use trial & error & let the first trial be $V_{GS} = 1.66V$ calculated in part (a)

$$\Rightarrow V_{GS} = 1.64V \text{ & } I_D = 104 \mu A$$

c. $I_D = \frac{12 - V_{GS}}{10^5} = \frac{25 \times 10^{-6}}{2} \left(\frac{25}{1}\right) (V_{GS} - 0.75)^2$

$$\therefore 62.5 V_{GS}^2 - 91.75 V_{GS} + 11.16 = 0 \Rightarrow V_{GS} = 0.134V \text{ or } 1.334V$$

but V_{GS} can't be less than $V_{TN} \Rightarrow V_{GS} = 1.334V$ & $I_D = 107 \mu A$

4.41

a. $V_{GS} = 0V \angle V_{Dsat} = V_{GS} - V_{TN} = 2V$

Assume $V_{DS} > V_{Dsat} \Rightarrow$ transistor is saturated

$$\therefore I_{Dsat} = \frac{25 \times 10^{-6}}{2} \left(\frac{10}{1}\right) (0 + 2)^2 = 500 \mu A$$

$$\angle V_{DS} = 10V - 100k \times 500 \mu A = -40V < V_{Dsat}$$

\angle we used a wrong assumption.

So the transistor is in linear region

$$\Rightarrow I_D = \frac{10 - V_{DS}}{10^5} = 25 \times 10^{-6} \left(\frac{10}{1}\right) \left(0 + 2 - \frac{V_{DS}}{2}\right) V_{DS}$$

$$\Rightarrow V_{DS} = 0.2065V \text{ & } I_D = 97.9 \mu A \quad (V_{DS} < V_{Dsat})$$

b. Assume directly that the transistor is in linear region.

$$\frac{10 - V_{DS}}{5 \times 10^4} = 25 \times 10^{-6} \left(\frac{20}{1} \right) \left(2 - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\Rightarrow V_{DS} = 0.2065 \text{ V } (< V_{DSsat}) \text{ \& } I_D = 195.8 \mu\text{A}$$

c. In this case, both drain & source will be reversed & $V_{DS} = V_{GS}$

\therefore This is a depletion mode device (V_{TN} is -ve)

\therefore It's working in linear region ($V_{DS} < V_{GS} - V_{TN}$)

$$\frac{10 - V_{DS}}{10^5} = 25 \times 10^{-6} \left(\frac{10}{1} \right) \left(V_{DS} - (-2) - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\Rightarrow V_{DS} = 0.1876 \text{ V } \text{ \& } I_D = 98.1 \mu\text{A}$$

4.45

$$V_{TN} = V_{T0} + \gamma \left(\sqrt{V_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right) = 2.266 \text{ V}$$

$\therefore V_{GS} < V_{TN} \Rightarrow$ Transistor is off & $I_D = 0$

4.51

a. $V_{GS} - V_{TP} = -1.1 - (-0.75) = -0.35 \text{ V}$, $|V_{GS}| < |V_{GS} - V_{TP}| \Rightarrow$ linear region

$$I_D = 10 \times 10^{-6} \left(\frac{10}{1} \right) \left(-1.1 - (-0.75) - \frac{(-0.2)}{2} \right) (-0.2) = 5 \mu\text{A}$$

b. $V_{GS} - V_{TP} = -0.55 \text{ V}$, $|V_{GS}| < |V_{GS} - V_{TP}| \Rightarrow$ linear region

$$I_D = 9 \mu\text{A}$$

c. $V_{TP} = - \left[0.75 + 0.5 \left(\sqrt{1+0.6} - \sqrt{0.6} \right) \right] = -0.995 \text{ V}$


$V_{GS} = -1.1 \text{ V}$, $|V_{GS}| > |V_{GS} - V_{TP}| \Rightarrow$ saturation region

$$\therefore I_D = 0.551 \mu\text{A}$$

$V_{GS} = -1.3 \text{ V}$, $|V_{GS}| < |V_{GS} - V_{TP}| \Rightarrow$ linear region

$$\therefore I_D = 4.1 \mu\text{A}$$

4.81

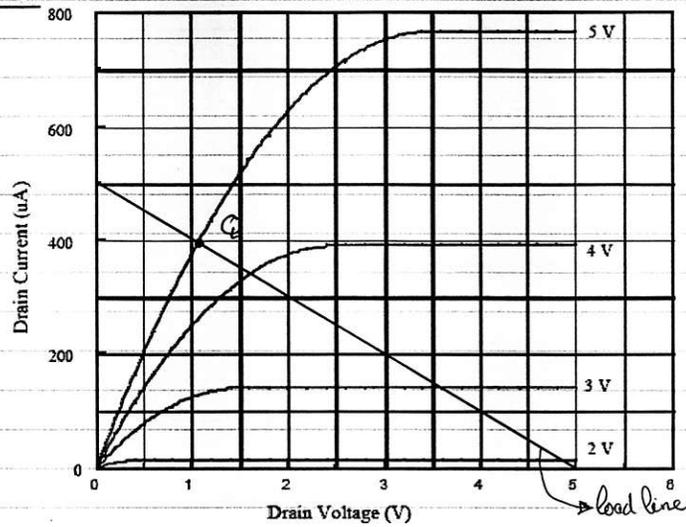

For the loadline : $V_{GS} = 0 \Rightarrow I_D = \frac{V_{DD}}{R} = 0.5 \text{ mA}$

$I_D = 0 \Rightarrow V_{GS} = V_{DD} = 5V$

Now check the intersection with $V_{GS} = 5V \Rightarrow Q \approx (390 \mu A, 1.1V)$

4.82

$V_{GS} = \frac{V_{DD}}{2} = 3V$


The loadline eq is

$V_{DD} = 10k \cdot I_D + V_{GS}$

$I_D = 0 \Rightarrow V_{GS} = 6V$

$V_{GS} = 0 \Rightarrow I_D = 0.6 \text{ mA}$

$Q \approx (140 \mu A, 4.6V)$

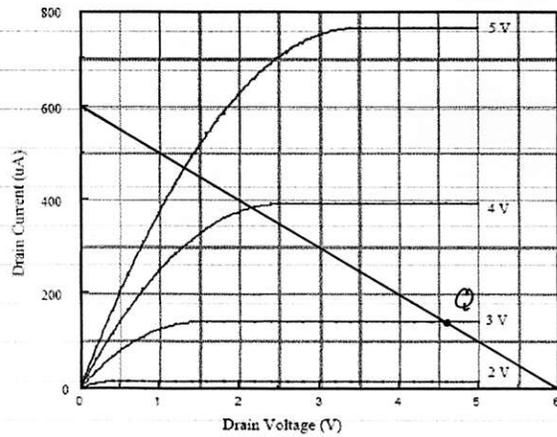

4.86

$$V_{G0} = \frac{V_{DD} R_1}{R_1 + R_2} = 3.81 \text{ V}$$

Assume saturation $3.81 \text{ V} = V_{GS} + R_3 I_D = V_{GS} + R_3 \frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{TO})^2$
 $\therefore 3.81 = V_{GS} + 47 \times 10^3 \times \left(\frac{25 \times 10^{-6}}{2}\right) \times \left(\frac{5}{1}\right) (V_{GS} - 1)^2$

Solving for V_{GS} gives $V_{GS} = 1.81 \text{ V}$ & $I_D = 42.3 \mu\text{A}$

Then from circuit analysis: $V_{DS} = 12 - (R_3 + R_4) I_D = 9 \text{ V}$

$$\therefore V_D > V_{GS} - V_{TO}$$

\therefore The saturation assumption is correct

$$\Rightarrow Q \approx (42.3 \mu\text{A}, 9 \text{ V})$$

4.102

$$a. I_D = \frac{k_n'}{2} \cdot \frac{W}{L} (V_{GS} - V_{TN})^2 = \left(\frac{25 \times 10^{-6}}{2}\right) \left(\frac{10}{1}\right) (V_{GS} - 0.75)^2$$

$$\therefore I_G = 0 \Rightarrow \text{no current in the } 10 \text{ M}\Omega \Rightarrow V_{GS} = V_{DS} = V_{DD} - 330 \text{ k}\Omega I_D$$

Solving both eq. for $V_{GS} \Rightarrow V_{GS} = 1.326 \text{ V}$ or 0.15 V ($< V_{TO}$ so refused)

$$\therefore I_D = 41.5 \mu\text{A} \quad \& \quad V_{DS} = V_{GS} = 1.326 \text{ V}$$

$$\Rightarrow Q \approx (41.5 \mu\text{A}, 1.326 \text{ V})$$

b. Repeating the same procedure $\Rightarrow Q \approx (42.1 \mu\text{A}, 1.117 \text{ V})$

4.116

a. This a PMOS & since G & D are connected \Rightarrow saturation ($V_{GS} = V_{DS}$)

$$\text{Circuit eq} \quad V_{DS} = V_{GS} = V_{DD} + I_D R = -15 + 75 \times 10^3 I_D$$

$$\text{Trans eq} \quad I_D = \frac{10^{-5}}{2} (V_{GS} - V_{TP})^2 = \frac{10^{-5}}{2} (-15 + 75000 I_D + 0.75)^2$$

$$\Rightarrow I_D = 124 \mu\text{A} \quad \& \quad V_{DS} = -5.7 \text{ V} \Rightarrow Q \approx (124 \mu\text{A}, -5.7 \text{ V})$$

b. $V_G = -15 \text{ V}$

$\therefore V_G$ is equal to largest voltage $\Rightarrow V_{GS} \gg V_{DS}$

\therefore Most probably the transistor is in the linear region

$$I_0 = \frac{V_{os} - (-15)}{75000} = 10^{-5}(-15 - (-0.75) - \frac{V_{os}}{2}) = \frac{V_{os}}{2} V_{os}$$

$$\Rightarrow V_{os} = -1.3V \text{ \& } I_0 = 182 \mu A \Rightarrow Q = (182 \mu A, -1.3V)$$

$$= V_{os} > V_{GS} - V_{TP} \Rightarrow \text{assumption was correct}$$

4.118

a. Both transistors are saturated by the way they are connected

$$\& I_{DP} = I_{DN}, \quad I_0 = -V_{GS_P} + V_{GS_N}$$

$$\frac{10 \times 10^{-6}}{2} \left(\frac{20}{1}\right) (-10 + V_{GS_N} + 0.75)^2 = \frac{25 \times 10^{-6}}{2} \left(\frac{20}{1}\right) (V_{GS_N} - 0.75)^2$$

$$\Rightarrow V_{GS_N} = 4.04V \text{ \& } V_{GS_P} = -5.96V \text{ \& } I_{DN} = I_{DP} = 2.71mA$$

$$V_0 = V_{GS_N} = 4.04V$$

b. The voltages remain the same, but the currents are scaled by 80:20

$$\Rightarrow I_{DP} = I_{DN} = 10.8mA$$

4.142 (read section 4.10.4 for current mirror circuits)

This is a normal current mirror circuit with all transistors working in saturation. But here the pinch-off effect is considered.

So for any transistor x

$$I_{ox} = \frac{(W/L)_x}{(W/L)_1} I_{ref} \frac{1 + \lambda V_{DSx}}{1 + \lambda V_{DS1}} \text{ \& } R_{ox} = \frac{1 + V_{DSx}}{I_{ox}}$$

$$V_{DS1} = V_{GS1} = V_{TN} + \sqrt{\frac{2I_{D1}}{K_n}} = 0.75 + \sqrt{\frac{2(30 \times 10^{-6})}{4(25 \times 10^{-6})}} = 1.52V$$

$$\therefore I_{O2} = \frac{10}{4} \cdot (30 \mu A) \cdot \frac{1 + 0.015(10)}{1 + 0.015(1.52)} = 84.3 \mu A, \quad R_{O2} = \frac{1}{\frac{0.015}{84.3 \mu A} + 8} = 909 k\Omega$$

$$\text{Similarly } I_{O3} = 164 \mu A, \quad R_{O3} = 455 k\Omega$$

$$I_{O4} = 346 \mu A, \quad R_{O4} = 227 k\Omega$$