

## Lecture 12 - 2EI4

- Analysis with mathematical model of diode
- Some Diode Circuits
- Zener Voltage Regulator Circuit
- Limiter/clipper circuits
- Clamping and peak detection circuits

## 2. Analysis with mathematical model of diode

$$i_D = I_s \cdot \left( e^{\frac{qv_D}{nkT}} - 1 \right) \text{ and } I_s = 10^{-13} A, n = 1 \text{ and } V_T = 0.025V.$$

$$i_D = 10^{-13} \cdot \left( e^{40v_D} - 1 \right) \text{ or } v_D = V_T \cdot \ln \left( \frac{i_D}{I_s} + 1 \right).$$

$$10V = 10^{-13} \cdot \left( e^{40v_D} - 1 \right) \cdot R + v_D \text{ or } 10V = 10^4 \cdot I_D + 0.025 \ln \left( \frac{i_D}{I_s} + 1 \right).$$


Use the Newton's method to solve for  $I_D$  or  $V_D$  (should know Newton's method from first year calculus).

$$f = 10V - \left( 10^4 \cdot 10^{-13} \cdot \left( e^{40v_D} - 1 \right) + v_D \right); \quad f' = -4 \cdot 10^{-8} \cdot e^{40v_D} - 1.$$

$$f'(V_D^0) = \frac{f(V_D^0) - 0}{V_D^0 - V_D^1} \text{ or } V_D^1 = V_D^0 - \frac{f(V_D^0)}{f'(V_D^0)}.$$

1. Make an initial guess  $V_D^0$ .
2. Evaluate  $f$  and  $f'$  for this value of  $V_D$ .
3. Calculate a new guess for  $V_D$  using  $V_D^1 = V_D^0 - \frac{f(V_D^0)}{f'(V_D^0)}$ .
4. Repeat #2 and #3 until convergence is obtained.
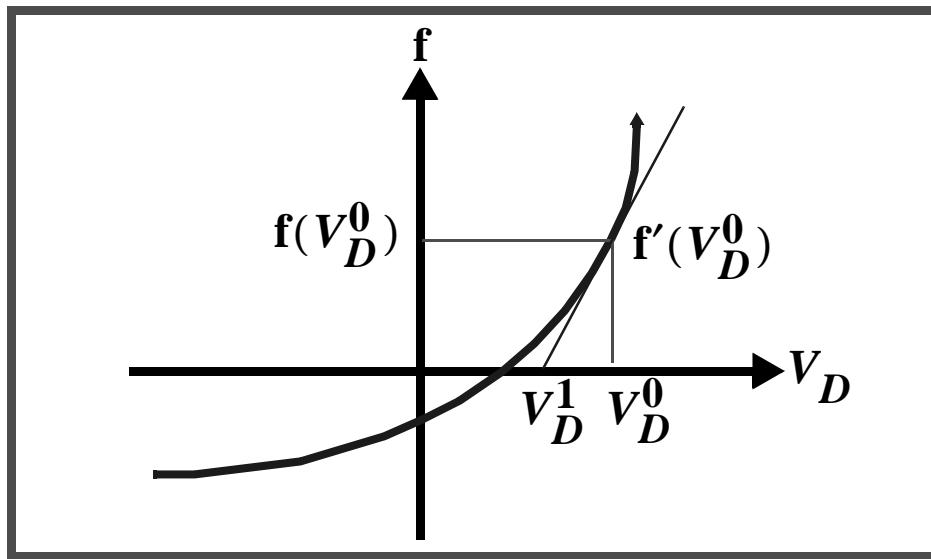
## 2. Analysis with mathematical model of diode



<i>Iteration #</i>	$V_D$	$f$	$f'$	$I_D$
0	0.8000	-7.895x10 <sup>4</sup>	-3.159x10 <sup>6</sup>	7.896x10 <sup>0</sup>
1	0.7750	-2.904x10 <sup>4</sup>	-1.162x10 <sup>6</sup>	2.905x10 <sup>0</sup>
11	0.5743	-5.989x10 <sup>-2</sup>	-3.804x10 <sup>2</sup>	9.486x10 <sup>-4</sup>
12	<b>0.5742</b>	<b>-1.876x10<sup>-4</sup></b>	<b>-3.780x10<sup>2</sup></b>	<b>9.426x10<sup>-4</sup></b>

## Example:

For the circuit shown, find the Q-points for the diodes using constant voltage drop model with  $V_{on} = 0.7$  V.

Assume  $D_1$  is on and  $D_2$  is on,

$$\therefore I_{D2} = \frac{0.7 - 0.7 - (-15)}{5k} = 3.00mA$$

$$\text{but } I_{D1} = \frac{12 - 0.7}{10k} - 3.00mA = -1.87mA$$

Therefore, assumption is wrong.


Now, assume  $D_1$  is off and  $D_2$  is on,

$$\therefore I_{D1} = 0A$$


$$I_{D2} = \frac{12 - 0.7 - (-15)}{10k + 5k} = 1.75mA$$

$$V_{D1} = 12 - 10^4 I_{D2} = -5.53V$$

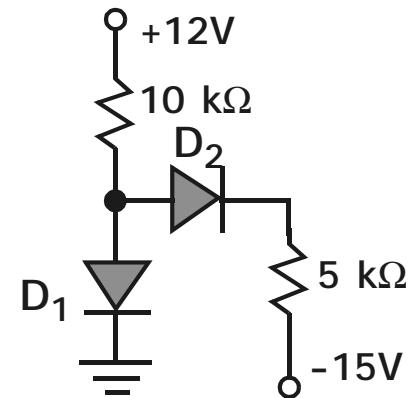Therefore,  $D_1$  is  $(0A, -5.53V)$  and  $D_2$  is  $(1.75mA, 0.7V)$ .




## Some Diode Circuits

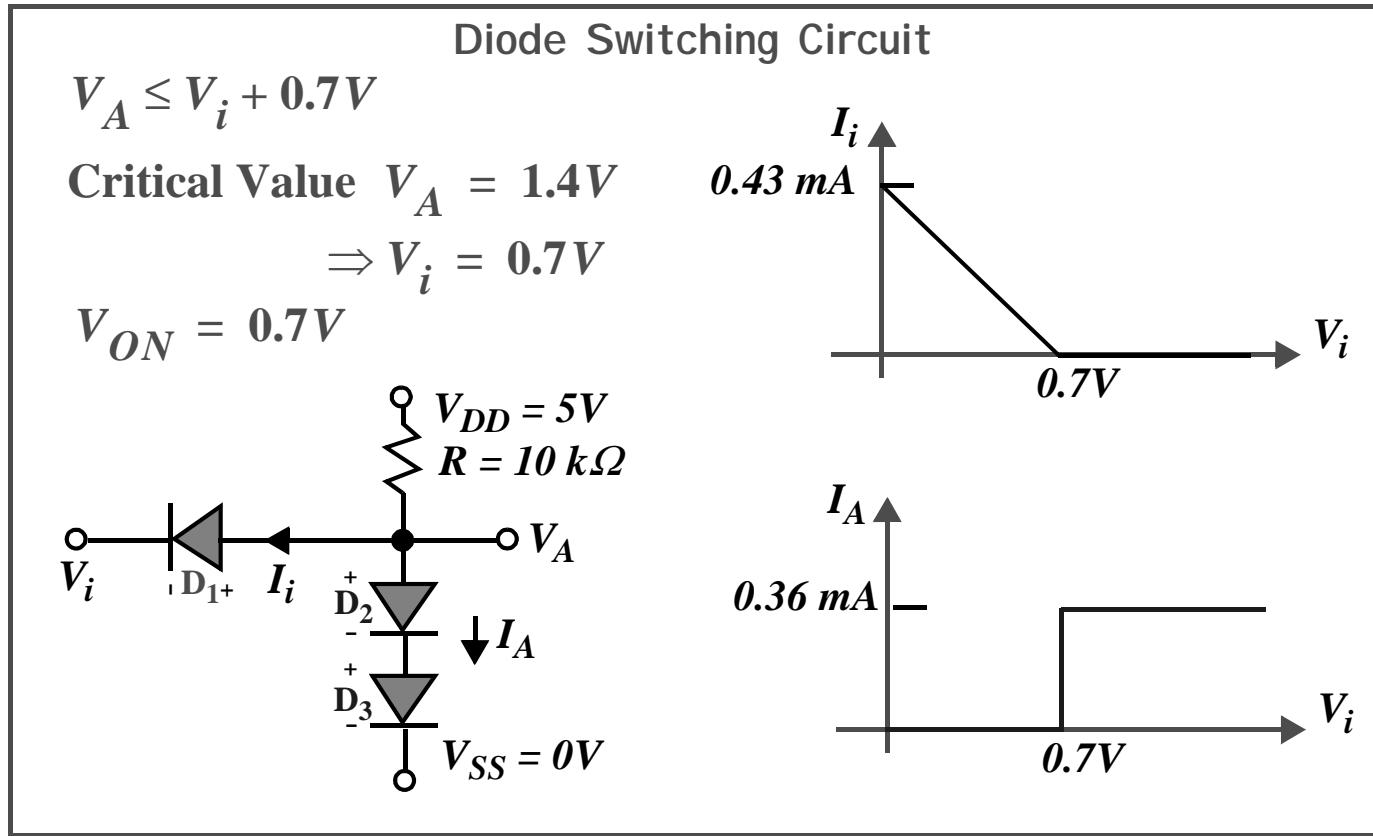


As an exercise, determine the value of  $V_A$  for the following values of input voltage  $V_i = 2V, 1V, 0V$  and  $-1V$ .

## Some Diode Circuits

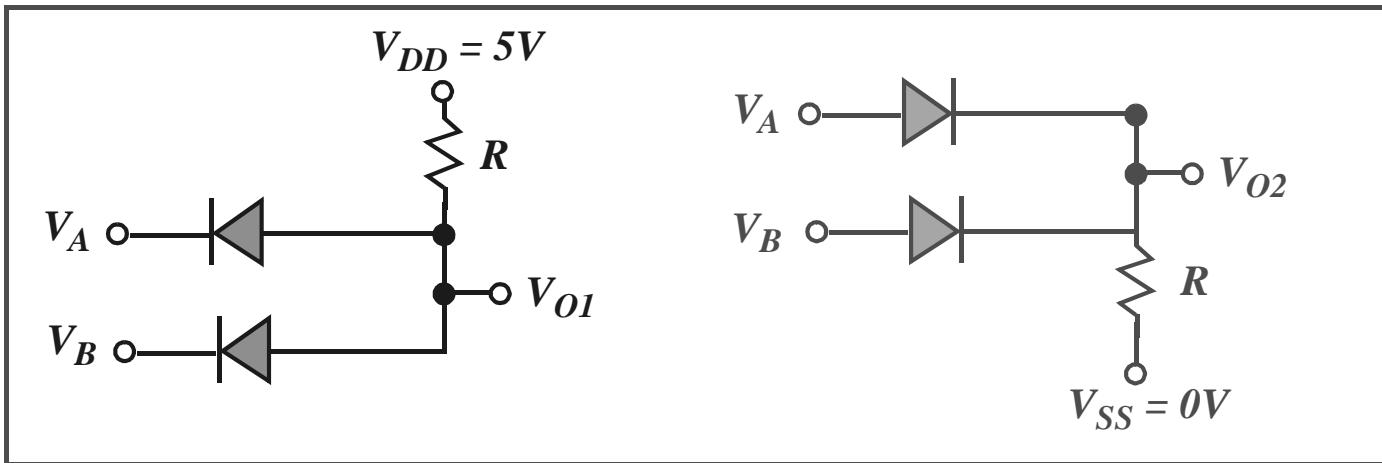

For the two circuits above, determine  $V_{O1}$  for all four combinations of  $V_A$  and  $V_B$ , of 0V and 5V, that is (0V,0V), (0V,5V), (5V,0V) and (5V,5V). How best can  $V_{O1}$  and  $V_{O2}$  be written in terms of  $V_A$  and  $V_B$ .

## Zener Voltage Regulator Circuit

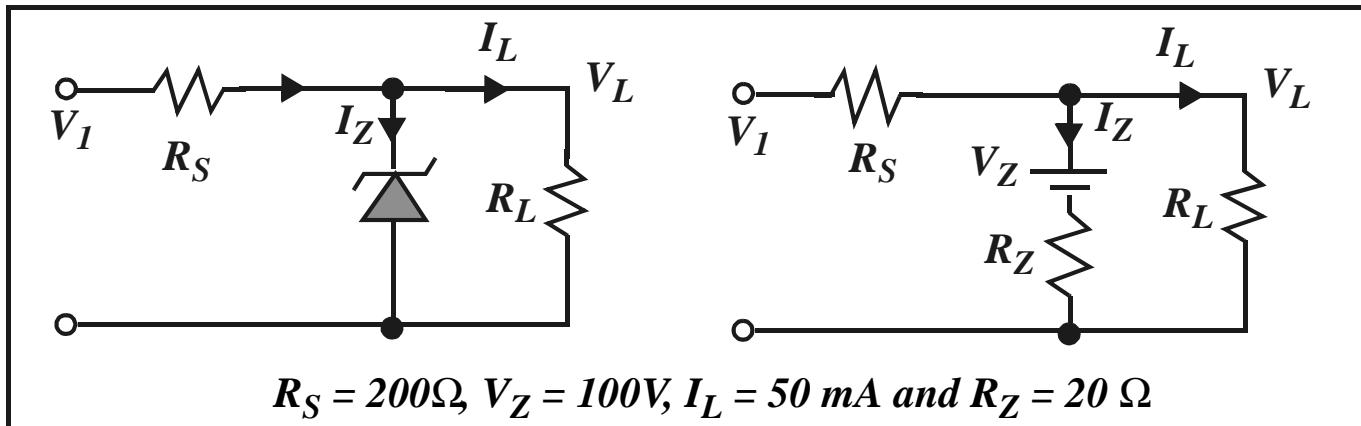

$$V_L = V_Z + I_Z \cdot R_Z = 100 + 0.01 \times 20 = 100.2V \quad . \quad I_Z = \frac{V_L - V_Z}{R_Z}$$

$$V_1 = V_L + \left( I_L + \frac{V_L - V_Z}{R_Z} \right) R_S = 100.2 + \left( 0.05 + \frac{0.2}{20} \right) 200 = 112.2V$$

$V_1$  increases by 10% to  $V_1'$ ;  $V_1' = 123.42$


$$V_1' = V_L' + \left( I_L + \frac{V_L' - V_Z}{R_Z} \right) \cdot R_S = V_L' + \left( 0.05 + \frac{V_L' - 100}{20} \right) 200$$

$$V_L' = (123.42 + 1000 - 10) / 11 = 101.22V \Rightarrow 1\% \text{ change } V_L$$
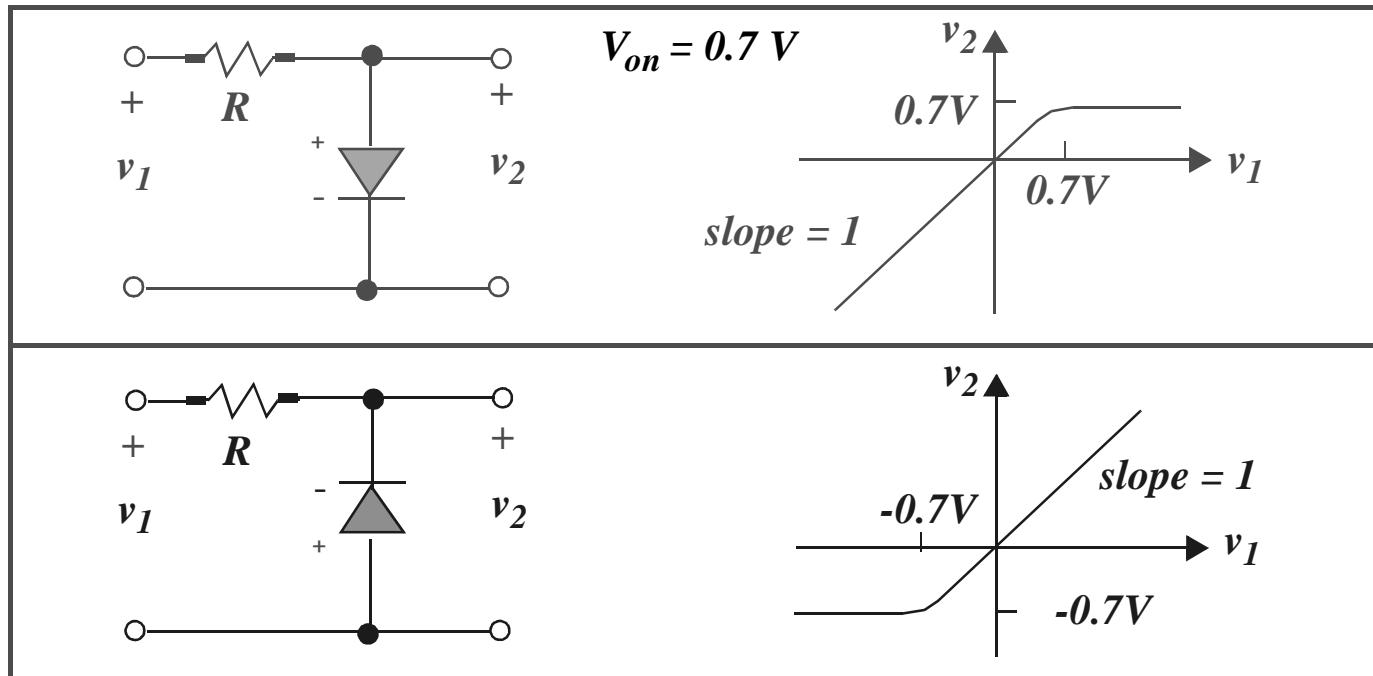
## Limiter or Clipper Circuits

Used in signal processing circuits; Limits voltage between IPs of Op-Amp.

Provides  $v_{out} \propto v_{in}$  up to a certain value(s), beyond which voltage is clipped off.




## Limiter or Clipper Circuits

Used in signal processing circuits;

Limits voltage between two inputs of Op-Amp.

Provides  $v_{out} \propto v_{in}$  up to a certain value(s), beyond which voltage is clipped

off.

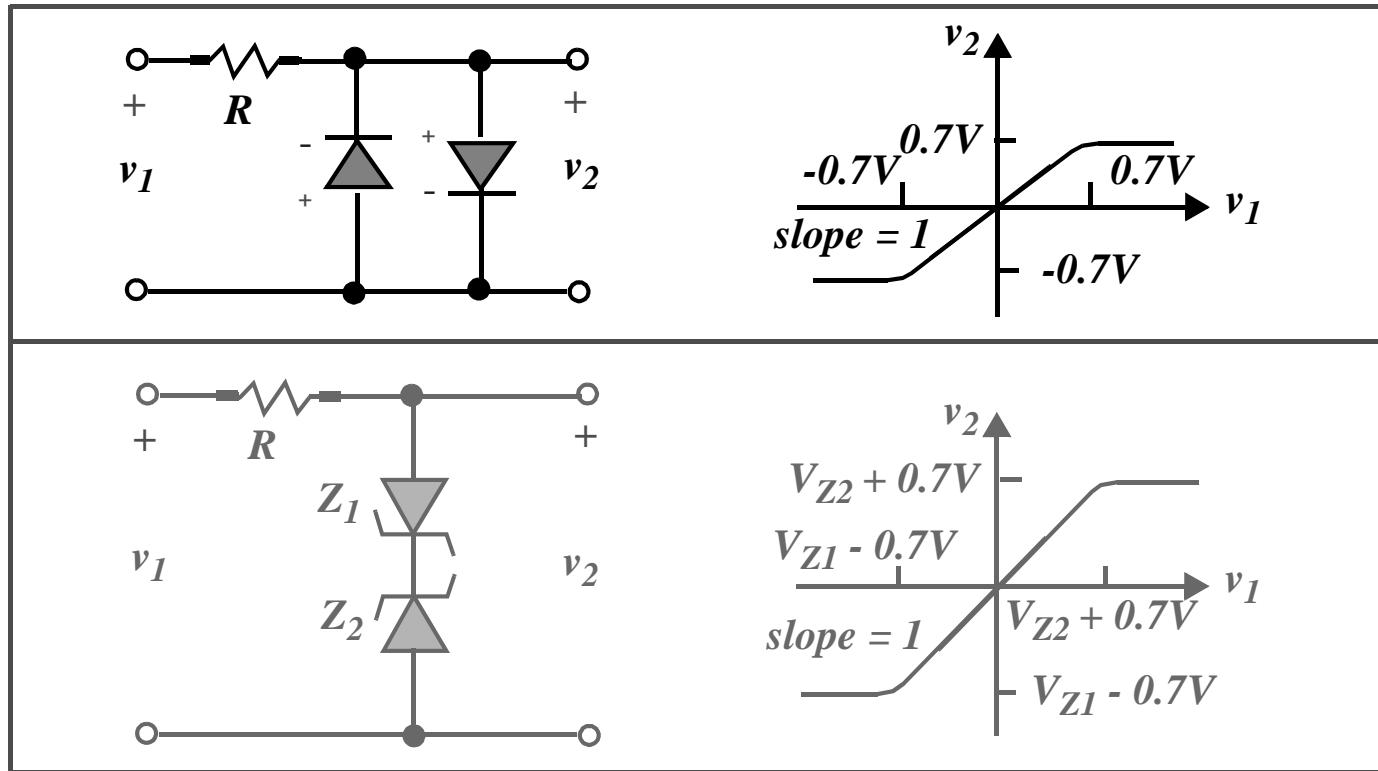


## Clamping Circuits


In TV receivers, peak values of certain signals must be held clamped to pre-determined levels

Provides  $v_{out} \propto v_{in}$  but clamps  $v_{out}$  to a certain value.

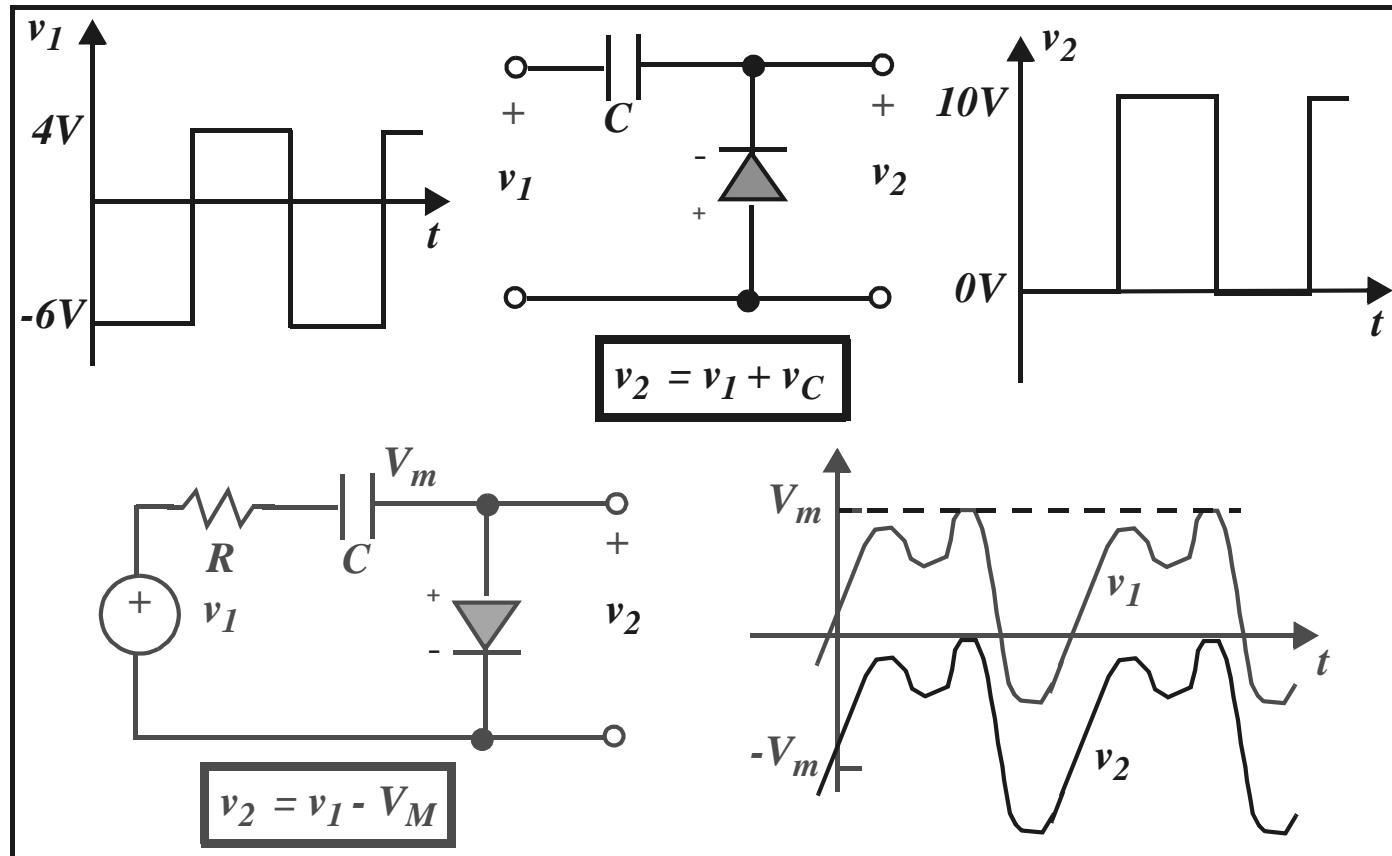In clamping, the variable component of  $v_{in}$  is transmitted and the dc value is restored.



## PSpice EXAMPLE

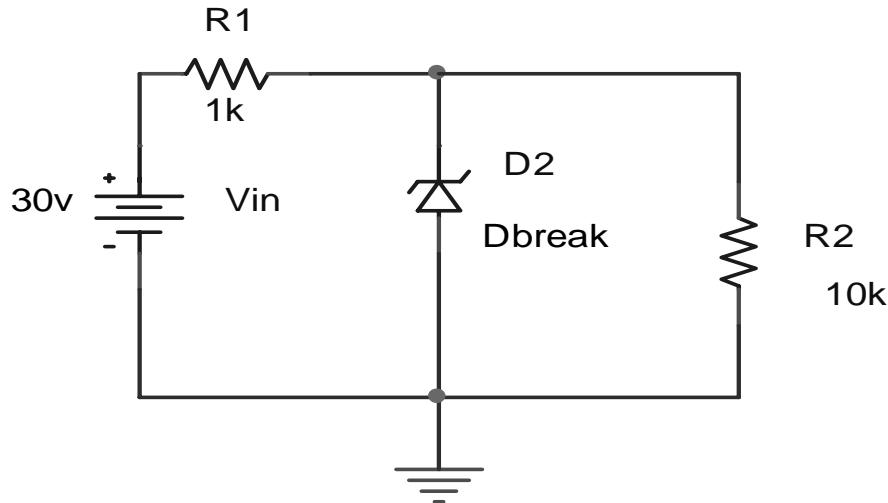

\*Libraries:

\* Local Libraries :

.LIB ".\example5.lib"

\* From [PSpICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:

.lib "nom.lib"

\*Analysis directives:

.OP

.PROBE V(\*) I(\*) W(\*) D(\*) NOISE(\*)

.INC ".\example5-SCHEMATIC1.net"

\*\*\*\* INCLUDING example5-SCHEMATIC1.net \*\*\*\*

\* source EXAMPLE5

R\_R1 N00125 N00047 1k

D\_D2 0 N00047 Dbreak

## PSpice EXAMPLE (Cont'd)

V\_Vin N00125 0 30v

R\_R2 0 N00047 10k

\*\*\*\* RESUMING example5-SCHEMATIC1-Example5Profile.sim.cir \*\*\*\*

.END

\*\*\*\* Diode MODEL PARAMETERS

Dbreak

IS 10.000000E-15

BV 20

IBV 10.000000E-09

CJO 100.000000E-15

\*\*\*\* SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
------	---------	------	---------	------	---------	------	---------

(N00047)	20.3500	(N00125)	30.0000				
----------	---------	----------	---------	--	--	--	--